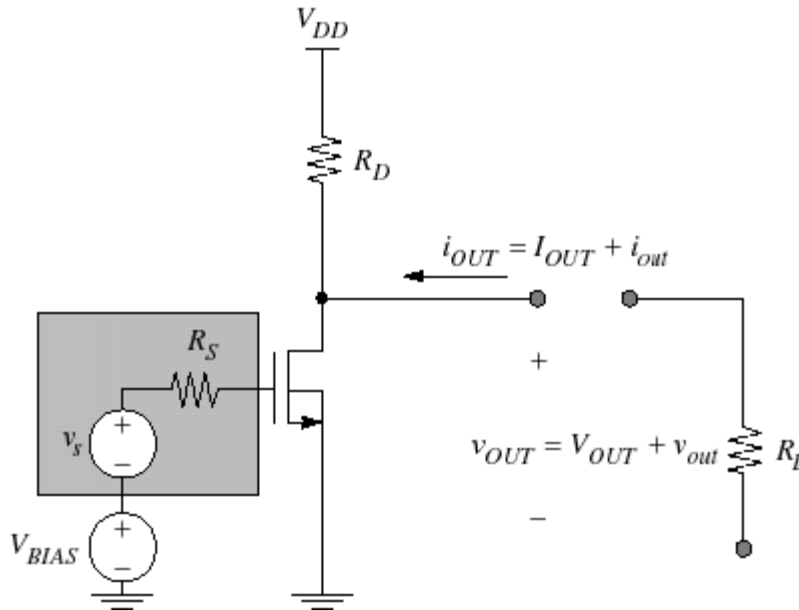


Common-Source Amplifier

- * “Common” means “grounded” or more generally, “connected to a DC supply”



What is going on with the load resistor R_L ?

DC level of the output voltage is NOT zero ... but


A “typical load” does not draw much if any DC current ... because it is non-linear and the load resistor is the load’s small-signal model!

What is a “typical load”?

DC Bias Point of the Common-Source Amplifier

For biasing, we

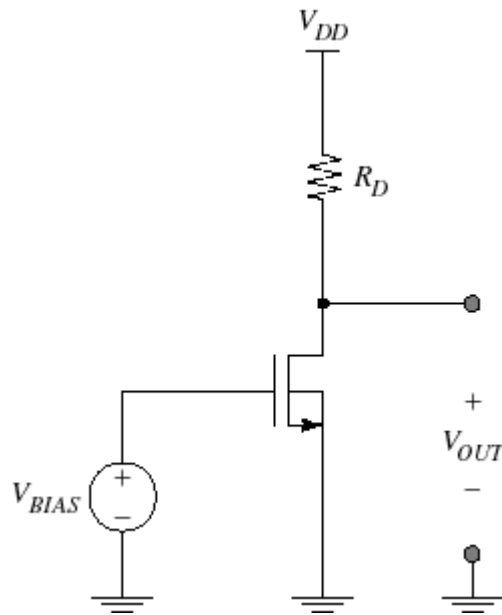1. ignore the small-signal source vs and its small-signal resistance: $R_S \rightarrow 0 \Omega$
2. ignore the load resistor (since it's a small-signal resistance, too): $R_L \rightarrow \text{inf. } \Omega$





Where to set V_{OUT} ?

Graphical “Load-Line” Analysis

The current through R_D must equal the drain current.


$$I_D = \frac{V_{DD} - V_{OUT}}{R_D} = I_{R_D}$$

What does this equation mean?

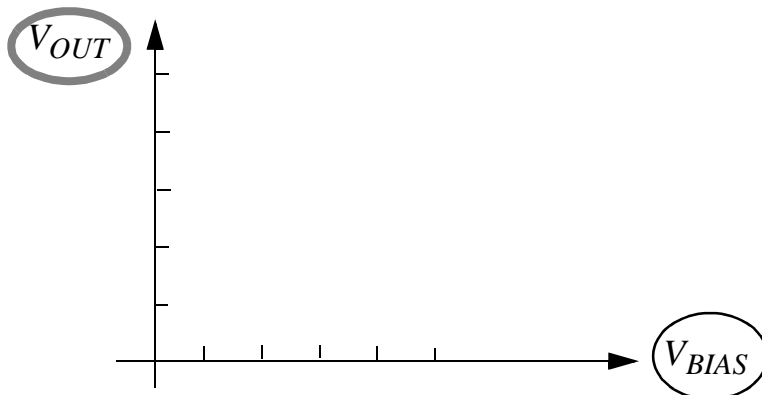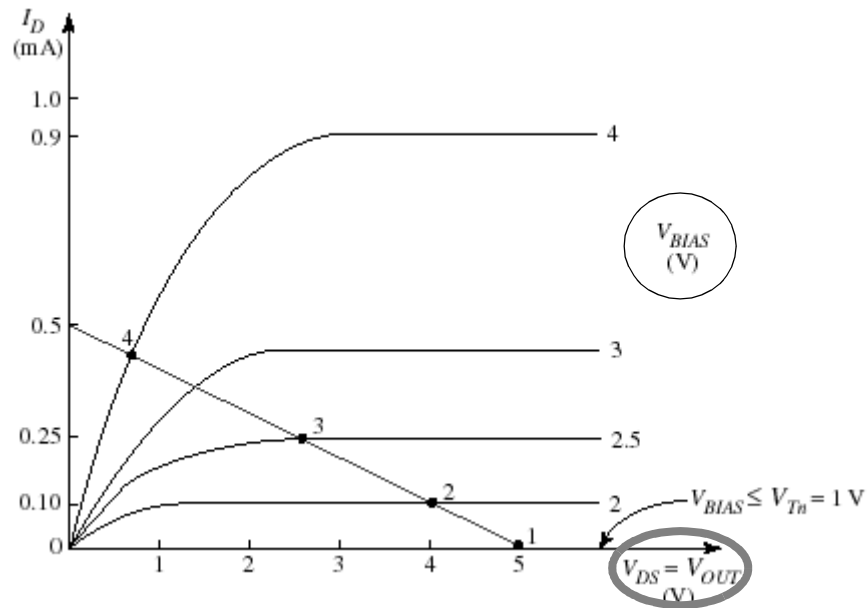

Small-Signal Model of CS Amplifier

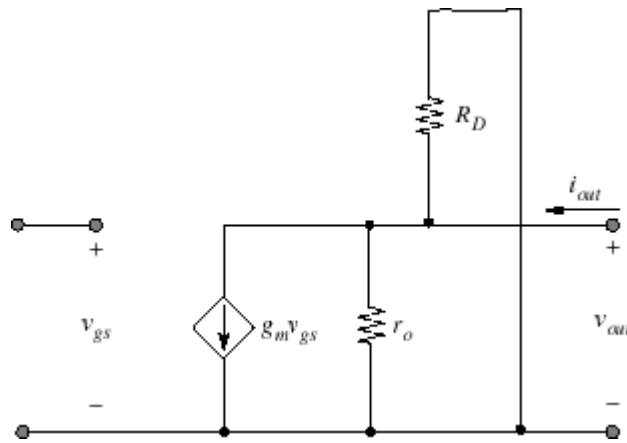- * Substitute parameters at operating point selected so that $V_{OUT} \approx V_{DD}/2$



- * Find two-port parameters of this amplifier:
“natural” to use the transconductance form


$$R_{in} =$$

$$R_{out} =$$

$$G_m =$$

Two-Port Model of Common-Source Amplifier

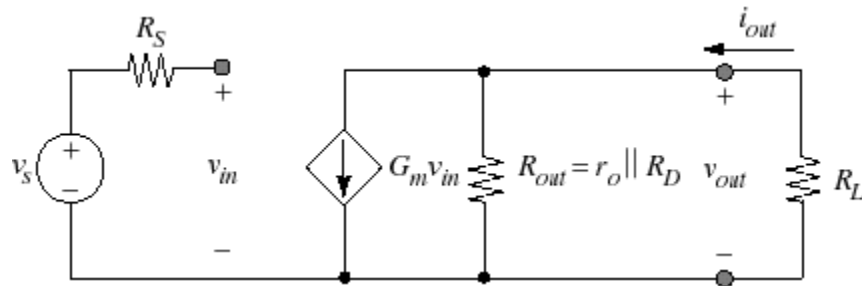- * Attach the source and load to find output current as a function of the source voltage




Infinite input resistance is ideal for a voltage input

Output resistance increases with R_D increasing, but DC drain current I_D will decrease and g_m will decrease with $I_D^{1/2}$

Current-Source Supplies

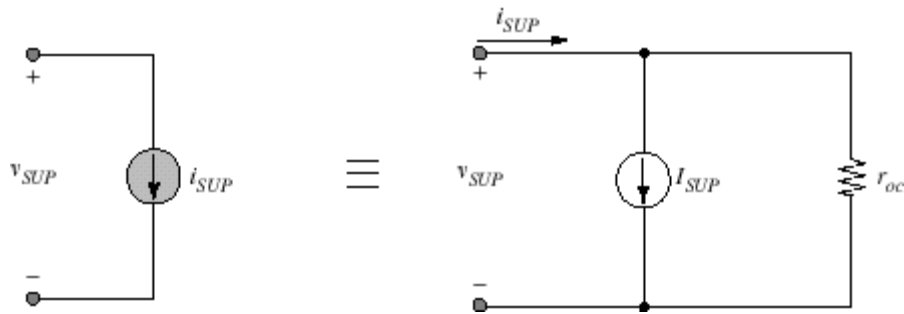- * A current source to supply current, rather than a resistor, allows a high DC current for the device with a large incremental (small-signal) resistance




The plot of i_{SUP} vs. v_{SUP} is: (note that v_{SUP} must be positive)




Common-Source with Current Source Supply

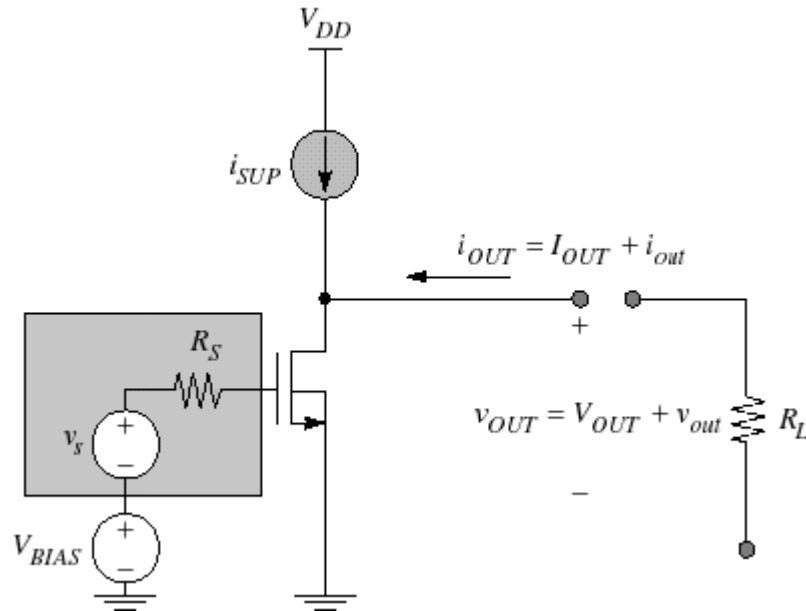
- * R_D is replaced with idealized current source with internal resistance



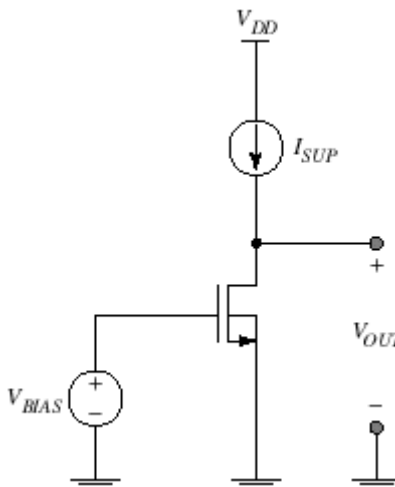
- * For DC bias analysis, the small-signal source (with R_S) and the load resistor R_L are eliminated, along with the internal resistance r_{oc} of the current source



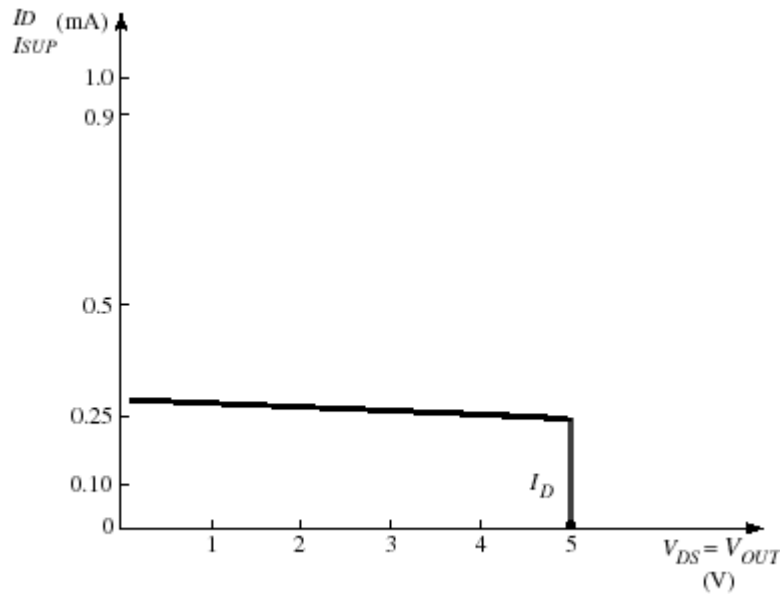Graphical Analysis of CS Amplifier with Current-Source Supply




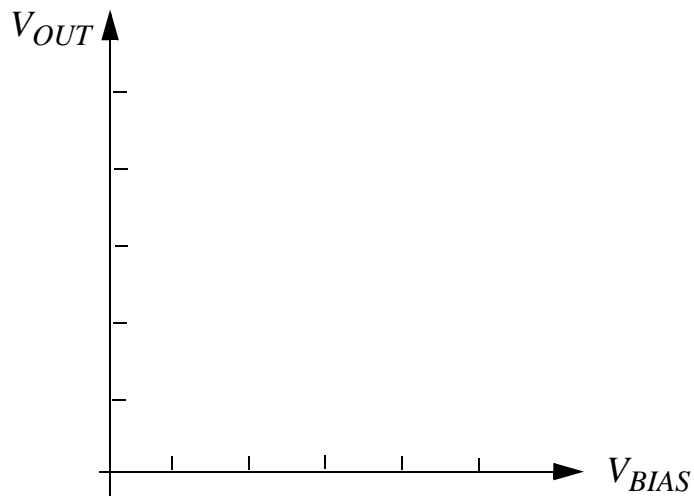The region of input bias voltage V_{BIAS} for which the current source and the MOSFET are in their constant-current regions is *extremely* small



Common-Source/Current-Source Supply Models

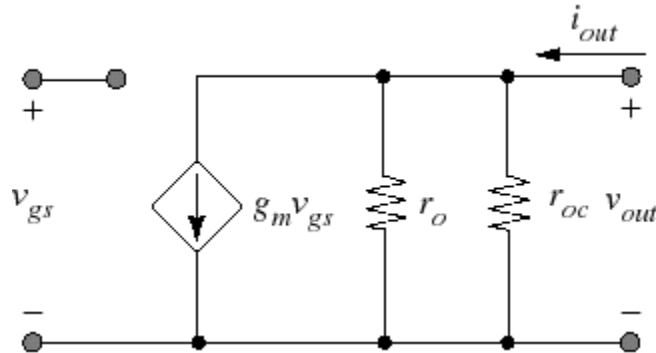
- * The small-signal model is identical to the resistor supply, except that the current source's internal resistance r_{oc} replaces R_D



Tradeoffs are different from case of resistor load since I_D is now decoupled from the small-signal current supply resistance r_{oc}

p-Channel Common-Source Amplifier

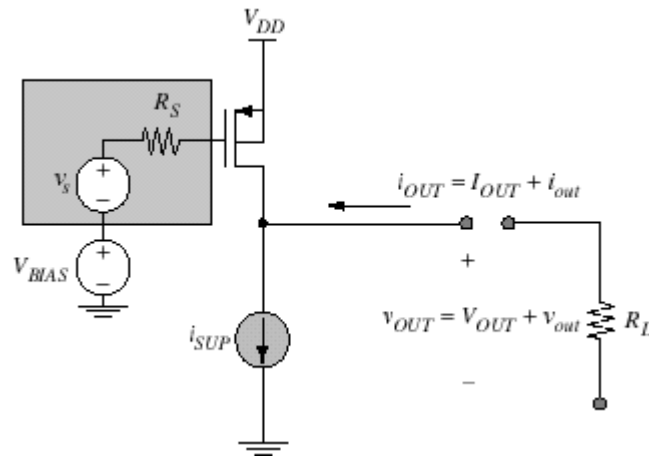- * Source of p-channel is tied to positive supply; current supply sinks I_{SUP} to ground or to lower supply




- * DC bias:

Eliminate small-signal sources; control voltage is $V_{SG} = V_{DD} - V_{BIAS}$

p-Channel CS Small-Signal Model

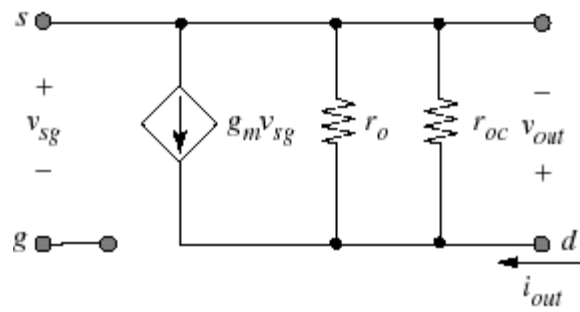- * p-channel MOSFET small-signal model has the source at the top



Transform this into a circuit with v_{gs} as the control voltage