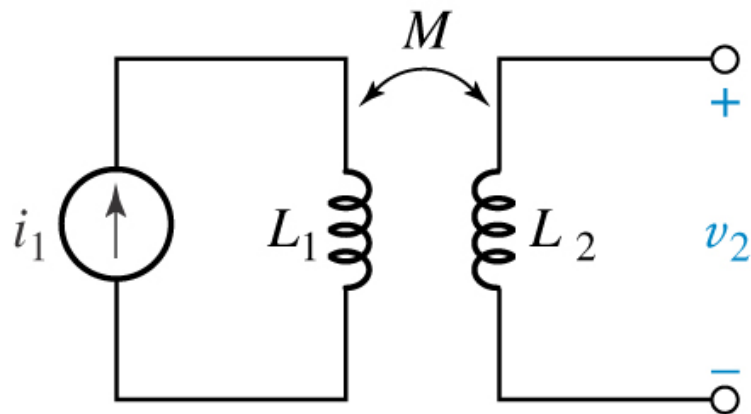



Magnetically-Coupled Circuits

Magnetically-Coupled Circuits



(a)

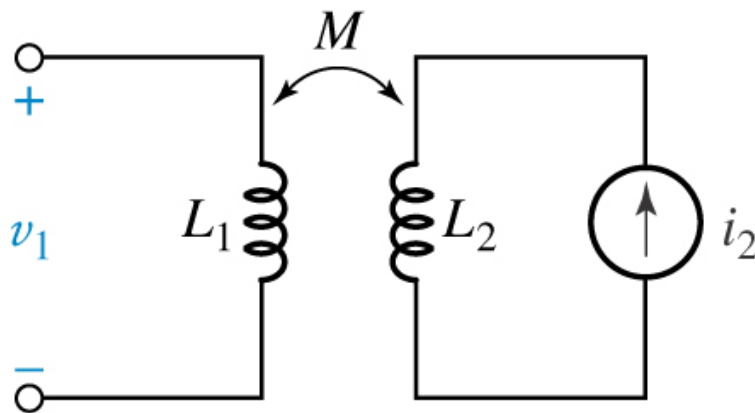
(a) A current i_1 at L_1 produces an open-circuit voltage v_2 at L_2 .




(b)

(b) A current i_2 at L_2 produces an open-circuit voltage v_1 at L_1 .


Magnetically-Coupled Circuits

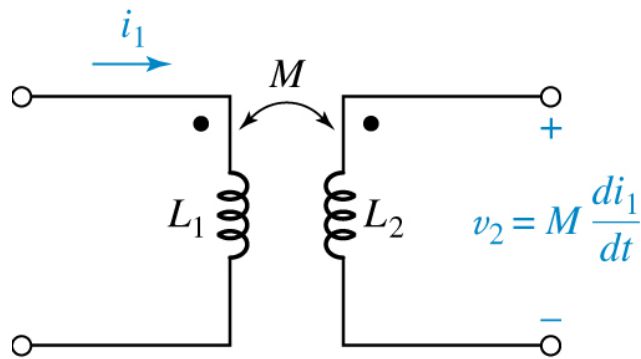


(a)

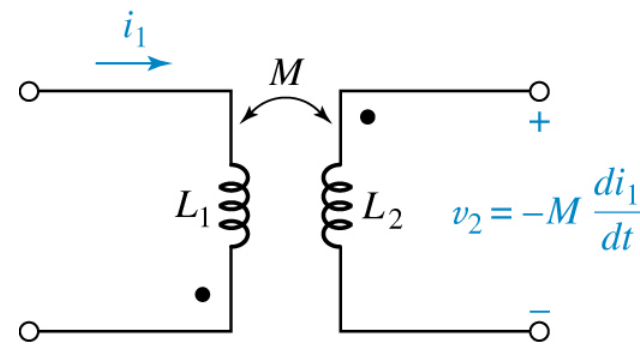

(c)

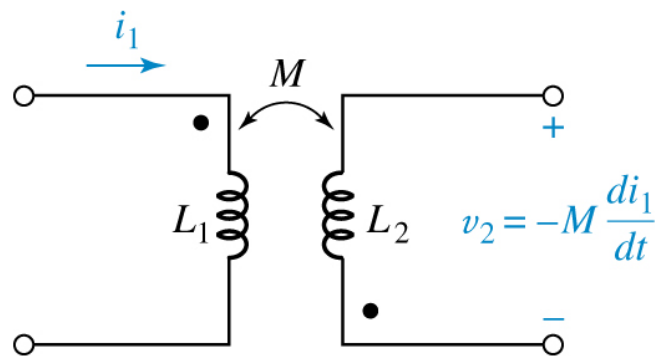

(b)


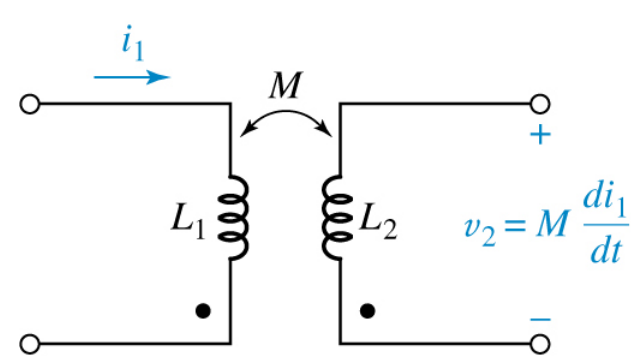


(d)


Current entering the dotted terminal of one coil produces a voltage that is sensed positively at the dotted terminal of the second coil. Current entering the undotted terminal of one coil produces a voltage that is sensed positively at the undotted terminal of the second coil.

Magnetically-Coupled Circuits

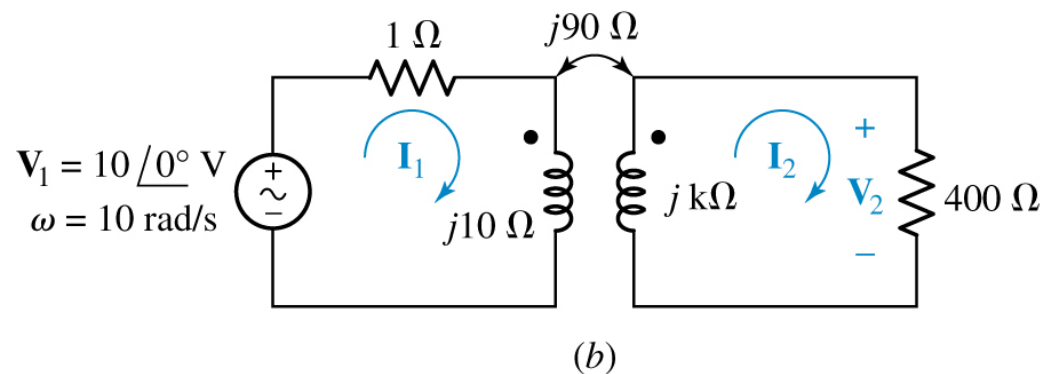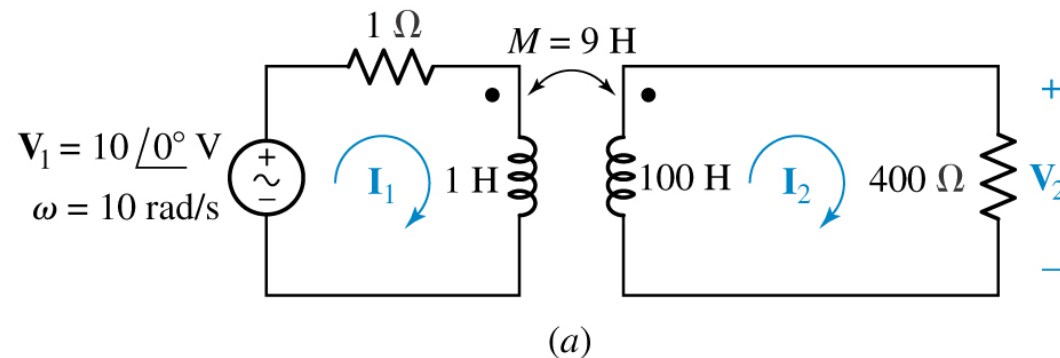
(a) A circuit containing mutual inductance in which the voltage ratio $\mathbf{V}_2/\mathbf{V}_1$ is desired. (b) Self and mutual inductances are replaced by the corresponding impedances.



Magnetically-Coupled Circuits

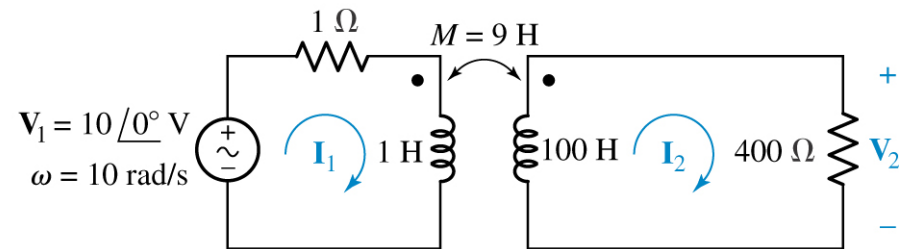

(a)

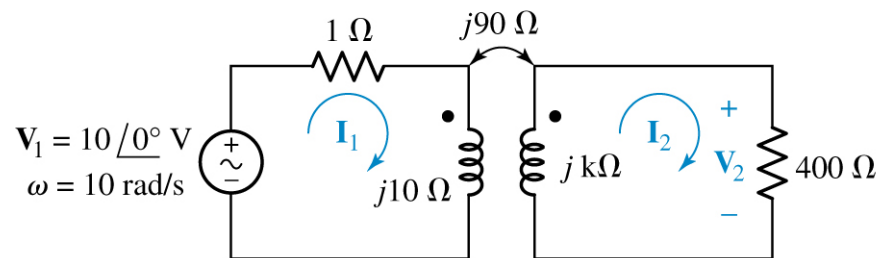


(b)

$$\begin{cases} -10 + I_1 + j10I_1 - j90I_2 = 0 \\ j1000I_2 - j90I_1 + 400I_2 = 0 \end{cases} \Rightarrow \begin{cases} I_1 = 2.063\angle -38.5^\circ \\ I_2 = 0.172\angle -16.7^\circ \end{cases}$$

$V_2 = 400I_2 = 68.8\text{ V} > V_1 \Rightarrow$ Voltage gain is possible with a transformer, but not actual power gain. Current gain is also possible.

Magnetically-Coupled Circuits

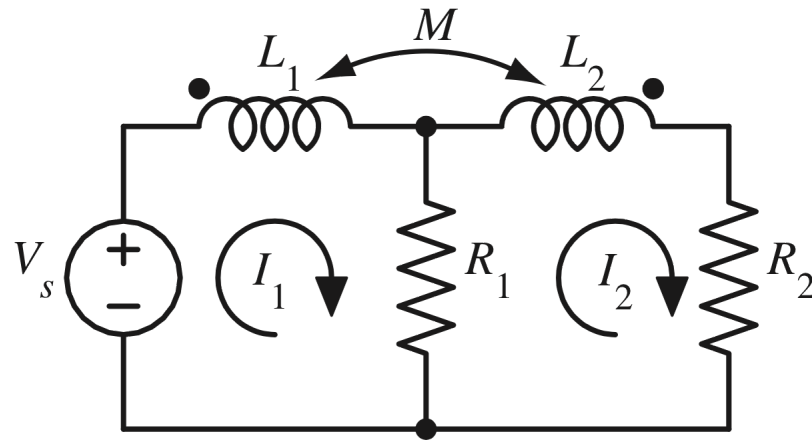


$$v_s(t) = 2 \cos(100\pi t) \text{ V} , R_1 = 3\Omega , R_2 = 8\Omega$$

$$L_1 = 50\text{mH} , L_2 = 100\text{mH} , M = 60\text{mH}$$

$$-2 + j100\pi(0.05)I_1 - j100\pi(0.06)I_2 + 3(I_1 - I_2) = 0$$

$$3(I_2 - I_1) + j100\pi(0.1)I_2 - j100\pi(0.06)I_1 + 8I_2 = 0$$

Magnetically-Coupled Circuits

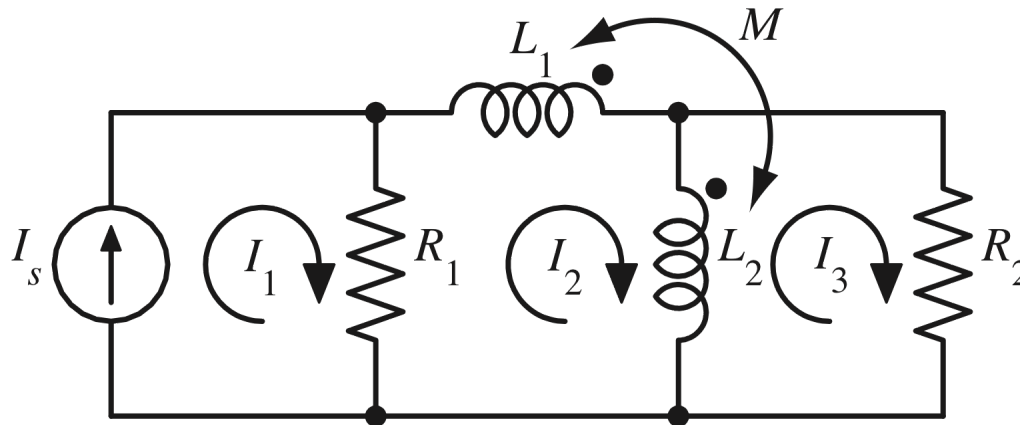

$$i_s(t) = 5 \cos(120\pi t) \text{ A} , R_1 = 50\Omega , R_2 = 100\Omega$$


$$L_1 = 1\text{H} , L_2 = 3\text{H} , M = 1.5\text{mH}$$

$$50(I_2 - I_1) + j120\pi(1)I_2 - j120\pi(1.5)(I_2 - I_3) \\ + j120\pi(3)(I_2 - I_3) - j120\pi(1.5)I_2 = 0$$


$$j120\pi(3)(I_3 - I_2) + j120\pi(1.5)I_2 + 100I_3 = 0$$

$$I_1 = 5$$

Transformer T Equivalent

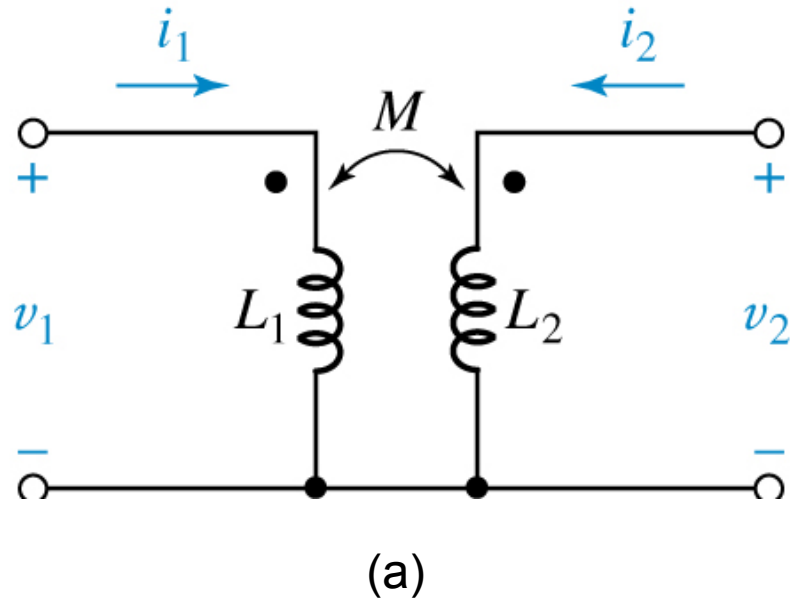

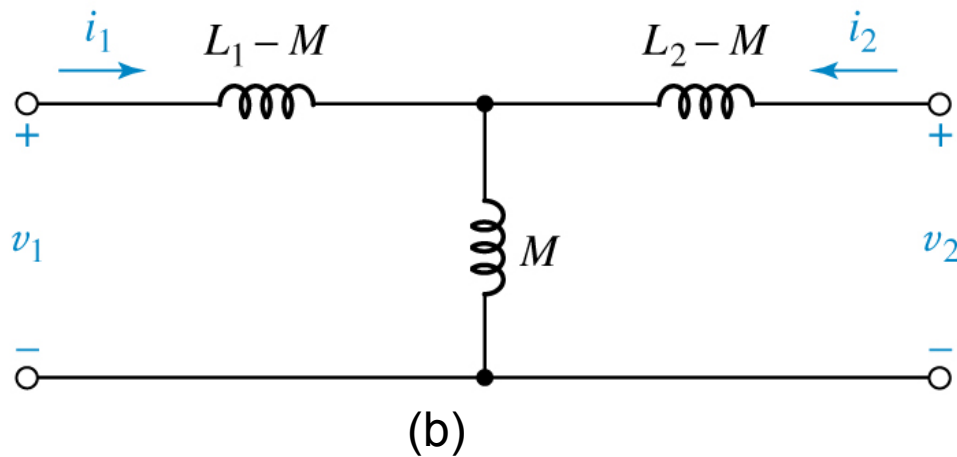(a) A given transformer which is to be replaced by an equivalent network.




(b) The T equivalent.

$$M \leq \sqrt{L_1 L_2}$$

The coupling

coefficient k is $\frac{M}{\sqrt{L_1 L_2}}$


The Ideal Transformer

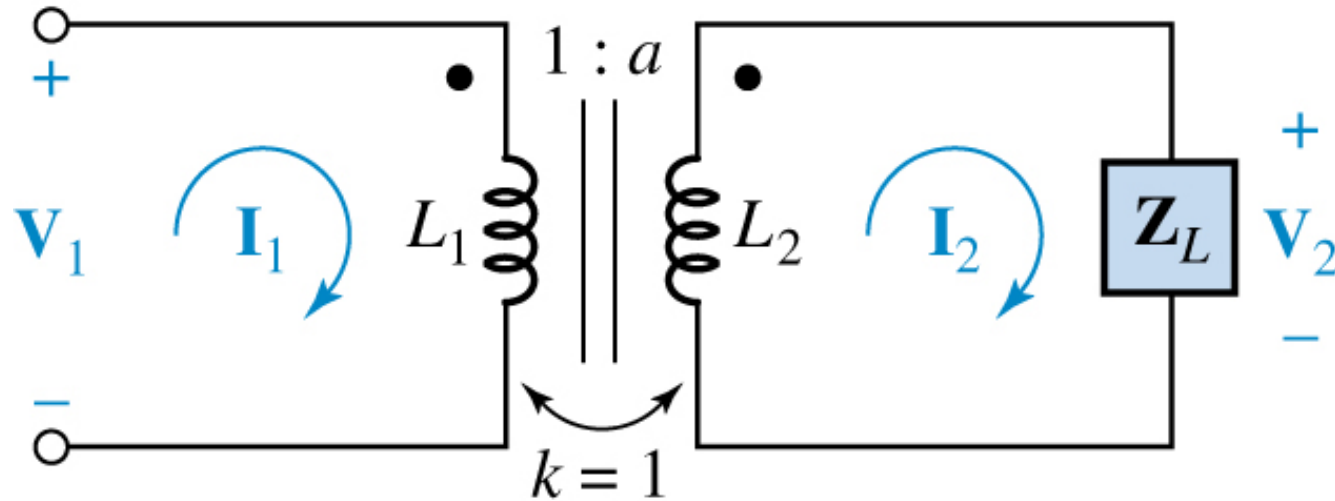

An ideal transformer is connected to a general load impedance.

The ideal transformer is a transformer with unity coupling coefficient k and with L_1 and L_2 very large (approaching infinity).

The Ideal Transformer

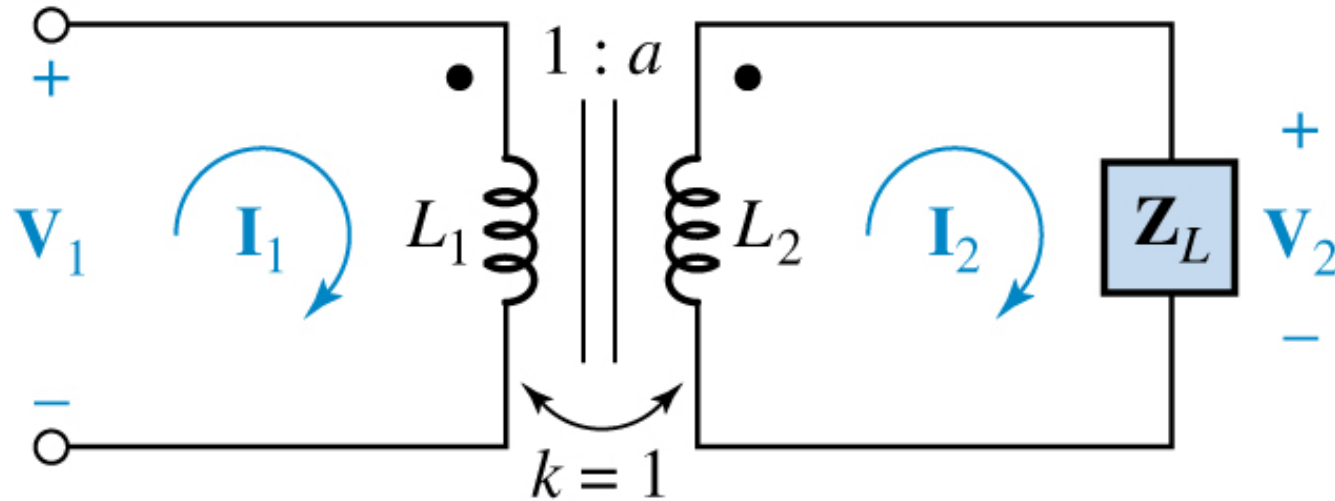


An ideal transformer is connected to a general load impedance.

$$a = \frac{N_2}{N_1} , \quad V_2 = aV_1 , \quad I_1 = aI_2 , \quad \frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} = a^2$$

$Z_{in} = \frac{Z_L}{a^2}$, where N_1 and N_2 are the numbers of turns in L_1 and L_2 .

The Ideal Transformer

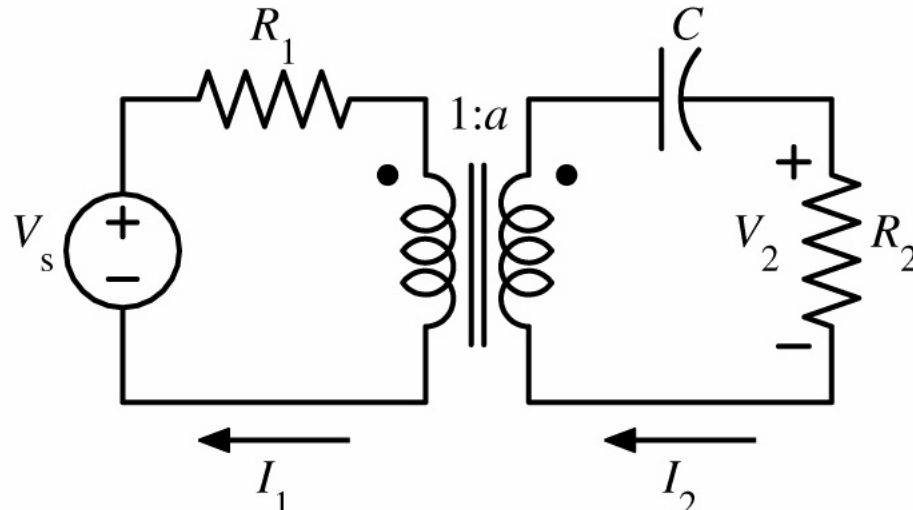

$$V_s = 120 \angle 0^\circ, \quad R_1 = 50 \Omega, \quad C = 3 \mu\text{F}, \quad R_2 = 200 \Omega, \quad a = 5$$

$$f = 60 \text{ Hz} \Rightarrow \omega = 377 \text{ rad/s}$$

$$-120 + I_1 \left(50 + Z_L / 5^2 \right) = 0$$

$$\text{where } Z_L = \frac{1}{j377 \times 3 \times 10^{-6}} + 200 = 906.5 \angle -77.25^\circ$$

$$I_1 = 1.7655 \angle 31.374^\circ, \quad I_2 = I_1 / 5 = 0.3533 \angle 31.374^\circ$$

$$V_2 = R_2 I_2 = 70.66 \angle 31.374^\circ$$