

**Department of Electrical Engineering**  
**Final Assignment**  
**Date: 24/06/2020**

**Course Details**

**Course Title:** Linear Circuits Analysis      **Module:** 3  
**Instructor:** \_\_\_\_\_      **Total Marks:** 50

**Student Details**

**Name:** \_\_\_\_\_      **Student ID:** \_\_\_\_\_

**INSTRUCTIONS:**


1. The solution must be uploaded before the end of deadline mentioned on the Online Portal of subject.

**Question 1**

**(15)**

Find the Value of  $i_x$  for the circuit using

- i. Nodal Analysis
- ii. Mesh Analysis
- iii. Superposition Theorem
- iv. Compare the number of steps and degree of easiness of all the three methods with each other

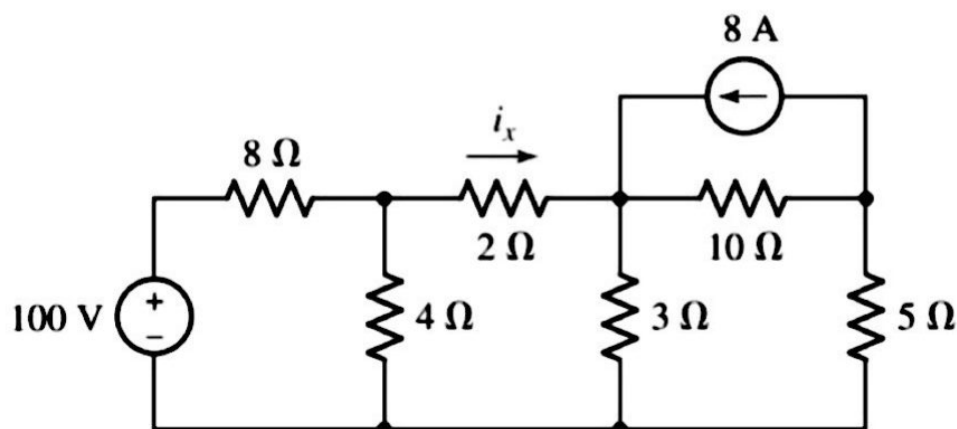


**Question 2**

**(20)**

Consider the 200 ohms resistor in figure as load resistor and develop


- i. Thevenin equivalent circuit
- ii. Norton equivalent circuit.
- iii. Find out what value of Thevenin resistance should be used to deliver maximum power to the load

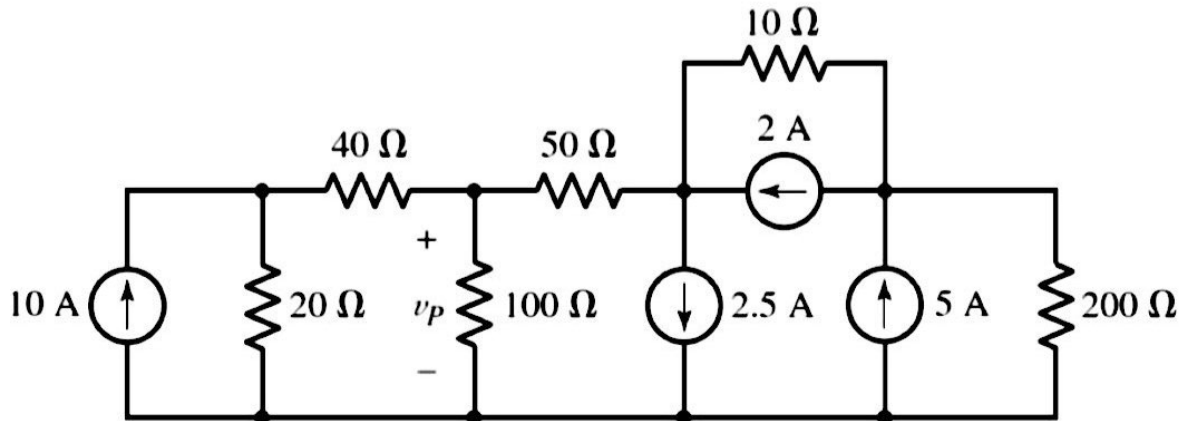

**Question 3**

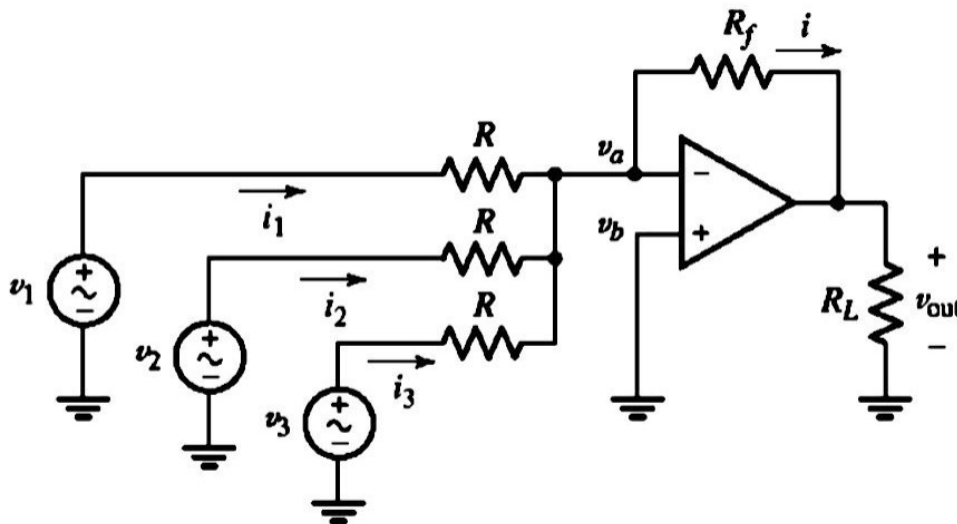**(15)**

Obtain an expression for  $V_{out}$  in terms of  $v_1$ ,  $v_2$ , and  $v_3$  for the op amp circuit in figure, also known as a summing amplifier.



Name : Adnan Khan

ID No: 16208

Dep. : B E Electrical

Semester : 2nd

Iqra National University.

Question 1:-

Find the value of  $i$  for the circuit using.


i) Nodal analysis

ii) Mesh analysis

iii) Superposition theorem

iv) Compare the number of steps and degree of easiness of all the three methods with each other.

Solution: i)

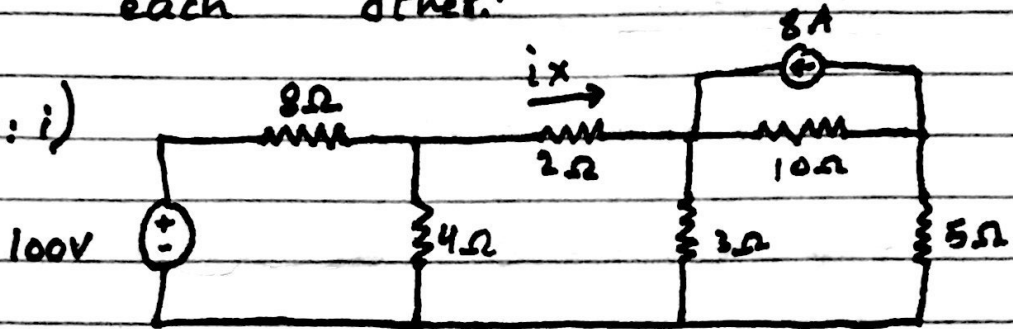

⇒ Nodal analysis

Apply KCL on Node 1

$$V_1 \frac{-100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 = 100 + \frac{2V_1}{4} + \frac{4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (i)}$$

Apply KCL on Node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_2}{18} = 8$$

$$\frac{30V_2 - 30V_1 + 20V_2 + 8V_2 - 3V_2}{60} = 8$$

②

$$-30V_1 + 53V_2 - 3V_2 = 480 \quad \text{--- (2)}$$

Apply KCL on node 2

$$\frac{V_2 - V_2}{10} + \frac{V_2}{5} = -8$$

$$\frac{V_2 - V_2 + 2V_2}{10} = -8$$

$$V_2 - V_2 + 2V_2 = -80$$

$$-V_2 + 3V_2 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Taking eq (2)

$$-V_2 + 3V_2 = -80$$

$$V_2 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting eq (a) and (b) in (2)

$$-30(0.5V_2 + 14.28) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.1V_2 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_1 = 828.39$$

(7)

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.91$$

putting  $V_2$  in eq (a)


$$V_2 = \frac{4(20.91) + 100}{7}$$

$$V_2 = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.91}{2}$$

$$i_x = 2.79 \text{ A}$$

Solution ii)

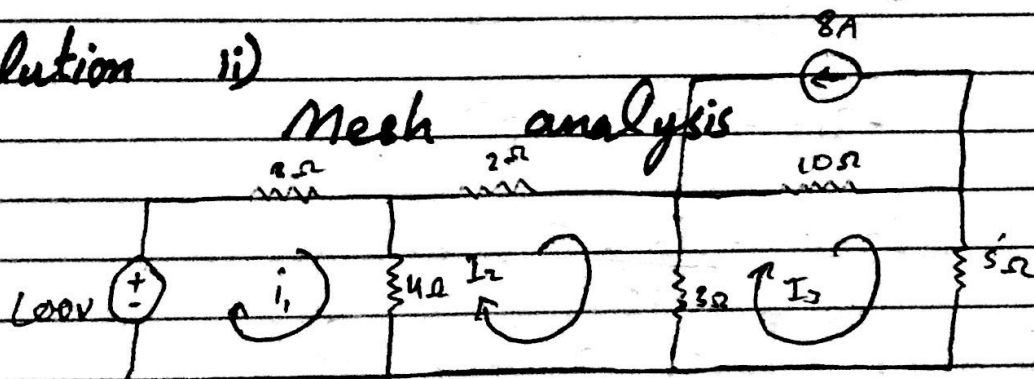

Apply KVL on loop 1

$$8i_1 + 4(i_2 - i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Apply KVL on loop 2

$$2i_2 + 4(i_1 - i_2) + 3(i_2 - i_2) = 0$$

(4)

$$2i_2 + 4i_2 - 4i_2 + 8i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on Loop (3)

$$3(i_2 - i_3) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_2 + 8i_3 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (2)}$$

Taking eq (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (b)}$$

putting eq (a) and (b) in eq (2)

$$-4(0.33i_2 - 8.32) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

$$-1.32i_2 + 9i_2 - 0.48i_2 + 33.32 - 13.32 = 0$$

$$7.2i_2 + 120 = 0$$

$$7.2i_2 = -120$$

$$i_2 = \frac{-120}{7.2}$$

②


$$I_2 = I_x$$

$$I_2 = 2.79 A$$

$$\boxed{I_x = 2.79 A}$$

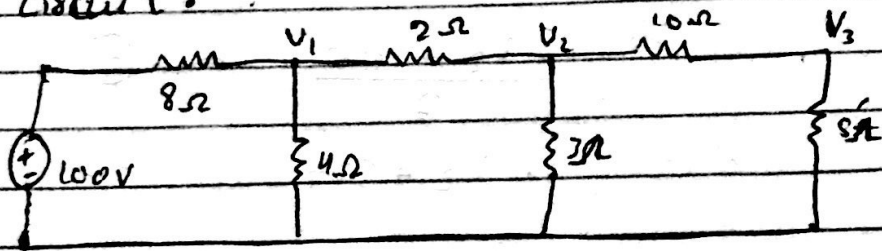iii) Superposition theorem :

First we remove the current source and then making it an open circuit. Re drawing the circuit.



Apply KCL on node 1

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$\frac{V_1 - 100 + 4V_1 - 4V_1 + 2V_2}{8} = 0$$

$$7V_1 - 4V_2 + 100 = 0 \quad \text{--- (1)}$$

Apply KCL on node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 + 57V_2 - 3V_3 = 0$$

Apply KCL on node 3



(5)

$$\frac{V_2 - V_2}{10} + \frac{V_2}{5} = 0$$

$$\frac{V_3 - V_2 + V_2}{10} = 0$$

$$= V_2 + 2V_2 = 0 \quad \sim (2)$$

Now taking eq (1) and (2)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \sim (a)$$

$$\text{Now } -V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3} V_2 \quad \sim (b)$$

Putting in eq (a)

$$-30(0.5 + V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 48.4 - 4V_2 + 0.60V_2 = 0$$

$$V_2 = -20.95$$

Putting in eq (a)

$$V_1 = 2.81$$

$$i_x = \frac{2.81 + 20.95}{2}$$

$$i_x = 11.63$$

v) Compare the number of steps and degree of easiness of all the three methods with each other.

iv) Sol:- The number of steps in nodal and mesh analysis are almost equal but in superposition the number of steps are almost of mesh and nodal analysis.

### Degree of easiness

As according to opinion mesh analysis is easier than the nodal analysis and superposition analysis.

Q2

Soln: Consider the  $200\ \Omega$  resistor in the figure and load resistor. Develop

Thevenin equivalent circuit  
Norton equivalent circuit

i) Find out what value of thevenin resistance should be used to deliver maximum power to the load.

Thevenin's and Norton's Equivalent Circuit Tutorial;

Thevenin's theorem states that we can replace entire network by an equivalent circuit that contains only an independent voltage source in series with an resistor such that the current-voltage relationship at the load is unchanged.

Norton's theorem is identical to Thevenin's theorem except that the equivalent circuit is a independent current source in parallel with an impedance (resistor).

Therefore, the Norton equivalent

(12)

Circuit is a source transforming of the Thevenin's equivalent circuit

if the circuit contains / you should do

a) Resistor and independent source

1) Connect an open circuit b/w (a) and (b)  
2) Find the voltage across the open circuit which is  $V_{oc}$ .  $V_{oc} = V_{th}$

3) Deactivate the independent source  
voltage source  $\rightarrow$  open circuit  
current source  $\rightarrow$  short circuit

4) Find  $R_{th}$  by circuit resistance reduction.

b) Resistors and dependent sources or independent sources:

1) Connect an open circuit b/w a and b

2) Find the voltage across the open circuit which is  $V_{oc}$ .  $V_{oc} = V_{th}$

\* if there are both dependent and independent sources.

3) Connect a short circuit b/w (a) and (b)

(13)

4) Determine the current between (a) and (b)

5)  $R_{th} = V_{oc} / I_{ab}$


if there are only dependent sources

6) Connect 1 ampere current source flowing from terminal b to a.  $i_t = 1 \text{ [A]}$

7) Then  $R_{th} = V_{oc} / I_t = V_{oc} / 1$

Q3

Solution:-

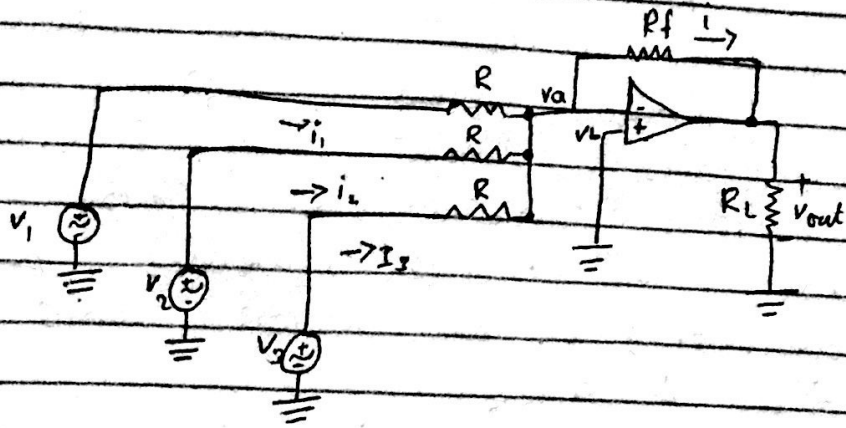

The goal is to obtain an expression for \$v\_{out}\$ (which appears across a load resistor \$R\_L\$) in terms of the input \$v\_1, v\_2\$ and \$v\_3\$.

No current can flow into the inverting input terminal.

$$i = i_1 + i_2 + i_3$$

Therefore we can write the following equation at the node labeled as

$$0 = \frac{v_a - v_{out}}{R} + \frac{v_a - v_1}{R} + \frac{v_a - v_2}{R} + \frac{v_a - v_3}{R}$$

The equation contains both \$v\_{out}\$ and the input voltage but unfortunately it also contains the node voltage \$v\_a\$. To remove this unknown quantity from our expression we need to write an additional equation that relates \$v\_a\$ to \$v\_{out}\$.

(15)

The input voltages  $R_f$  and  
for  $R$  At this point we  
remember that we have next  
yet used ideal op amp rule  
2. and that we will  
almost certainly require the  
use of both rules when  
analyzing an op amp circuit  
thus since

$v_a = v_b = 0$  we can  
write the equation as following.

$$0 = \frac{v_{out}}{R_f} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

Now Rearrange - we obtain  
the following expression for  $v_{out}$

$$v_{out} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

In the special case where  
 $V_2 = V_3 = 0$  we see that  
our result agrees with eq-3  
which was derived for  
essentially the same circuit.