

Department of Electrical Engineering

Assignment

Date: 23/06/2020

Course Details

Course Title: Instrumentation and Measurement

Module: 6th (BE)

Instructor: Engr Waleed Jan

Total Marks: 50

Student Details

Name: Idress Iqbal

Student ID: 13171

Note: Draw neat diagrams where necessary. Assume missing details if required.

Q1.		A student has connected two voltmeters in series and have applied 500V across them. Both voltmeters have the same range of 0-300V. What will be their readings if their internal resistances are 25k Ω and 15 k Ω respectively?	Marks 10
			CLO 2
Q2.		A dynamometer type wattmeter has two current coils each having a resistance of 0.5 Ω . Both of the coils are connected in parallel. The wattmeter voltage coil is connected to the supply side. The wattmeter shows a reading of 200W while the reading on the ammeter is 4A which is connected in series with the current coil of the wattmeter. Calculate the following parameters: a) Power dissipated in the wattmeter b) True load power c) Percentage error due to the connection of wattmeter	Marks 10
			CLO 2
Q3.	(a)	What is the difference between Kelvin's bridge and Wheatstone Bridge? Explain briefly.	Marks 05
			CLO 3
	(b)	Explain how the potential on the upper (top) node in a DC bridge is equal to the potential on the lower (bottom) node?	Marks 05
			CLO 3

Q4.	(a)	Why the energy meters designed for DC circuits cannot be used for AC circuits?	Marks 05
			CLO 03
	(b)	What will happen if the phase difference between two alternating fluxes in an induction type energy meter is zero degrees?	Marks 05
			CLO 03
Q5.	(c)	Why the series magnet is wound with a wire of few turns as compared to shunt magnet in an induction type energy meter?	Marks 05
			CLO 03
	(d)	What is the significance of meter constant in an energy meter?	Marks 05
			CLO 03

(1)

Name Idrees Iqbal (ID) (13171) Semester 8th

Q No 1:

Ans)

Given data

Two Voltmeter Range = 0-300V

$$R_1 = 25 \text{ k}\Omega$$

$$R_2 = 15 \text{ k}\Omega$$

$$\text{Total Voltage } V_1 = 500 \text{ V}$$


Required:

Voltage Reading in 1st

$$\text{Voltmeter} = V_1 = ?$$

Voltage Reading in 2nd Voltmeter $V_2 = ?$

Diagram

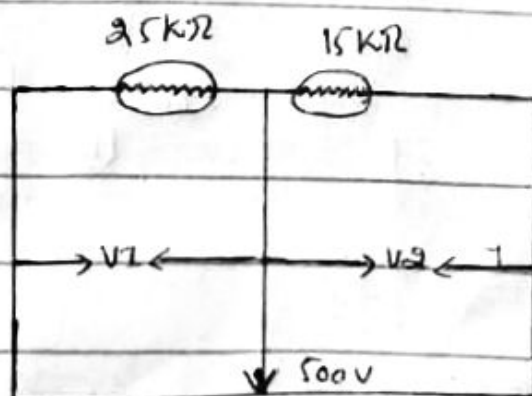

(2)

Solution.

Here we use Voltage divider
Rule the reading of the two
Vollmeters are.

$$V_1 = \frac{25 \text{ K}\Omega}{25 \text{ K}\Omega + 15 \text{ K}\Omega} \times 500 \text{ V}$$

$$V_1 = 312.5 \text{ V}$$

$$V_2 = \frac{15 \text{ K}\Omega}{25 \text{ K}\Omega + 25 \text{ K}\Omega} \times 500 \text{ V}$$

$$V_2 = 187.5 \text{ V}$$

(3)

Ques :

Ans)

Given data:

$$R_1 = 0.5 \Omega$$

$$R_2 = 0.5 \Omega$$

$$\text{Power } P = 200 \text{ W}$$

$$I = 4 \text{ A}$$


Required:

(a) power dissipated in the
Watt meter = ?

(b) True load power = ?

(c) percentage error due to
the connection of Wattmeter = ?

Diagram:

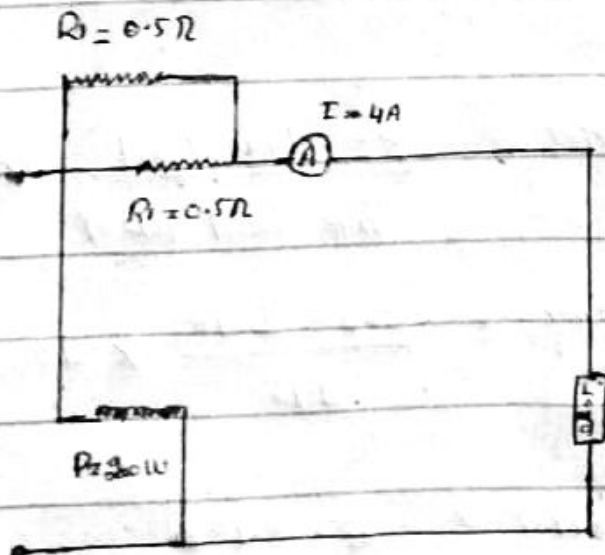

(4)

Solution.

Resistance of Current coils

$$R_c = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_c = \frac{0.5 \times 0.5}{0.5 + 0.5}$$

$$R_c = \frac{0.25}{1} = 0.25 \Omega$$

(a) Power dissipated in wattmeter = $I^2 R_c$

$$I^2 R_c = (4)^2 \times 0.25$$

$$I^2 R_c = 16 \times 0.25$$

$$I^2 R_c = 4 \text{ W}$$

(b) True Load Power = $200 - 4$

$$= 196 \text{ W}$$

(c) % error = $\frac{P - \text{True load}}{\text{True load}} \times 100$

$$\% \text{ error} = \frac{200 - 196}{196} \times 100$$

$$\% \text{ error} = 2.0408$$

(5)

Q No 3 part (v)

Ans)

Differences between Ke~~l~~vin's bridge
and Wheatstone bridge
Wheatstone bridges

* ~~The~~ The Wheatstone bridge is used to measure an unknown electrical resistance.


* The Wheatstone bridge is the combination of 4 resistance forming a bridge.

* The four resistance in the circuit are referred to as arms of bridge.

* The unknown resistance is connected with two known resistor and a galvanometer.

* To find the value of unknown resistor, the deflection of galvanometer is made zero by adjusting the variable resistor.

(6)

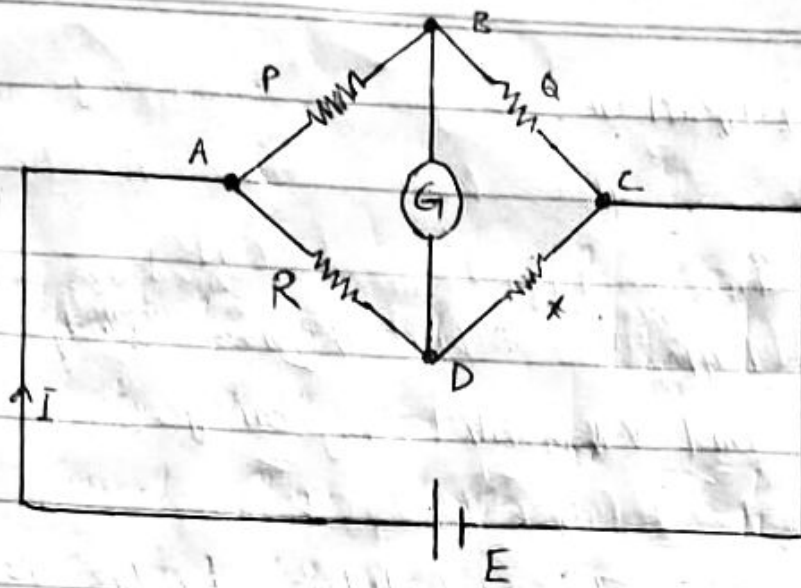

Where P & Q are known resistance
 R is a variable resistor
 X is unknown resistor
 E is dc power supply.

Kelvin bridge:

* This bridge is modification of Wheatstone bridge and is used to measure low resistance very accurately.

* When we are implementing Wheatstone bridge in the laboratory, we connect all the resistances through connection wires.

(7)


* Hence, these connecting wires also have some resistance and in order to measure it we will use Kelvin's bridge.

* In Kelvin bridge, we have a connecting wire between point m & n having a resistance x .

* The galvanometer can connect both to point m & n .

where G is connected to $M \rightarrow S + x$

$$\Rightarrow R = \frac{P}{Q} (S+x)$$

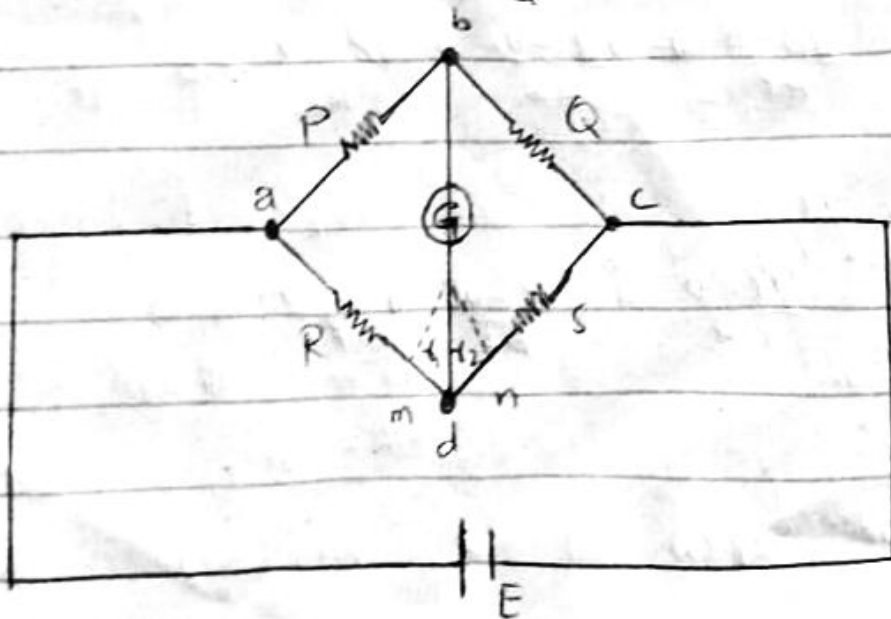


(8)

Q No. 3 Part b

Ans)

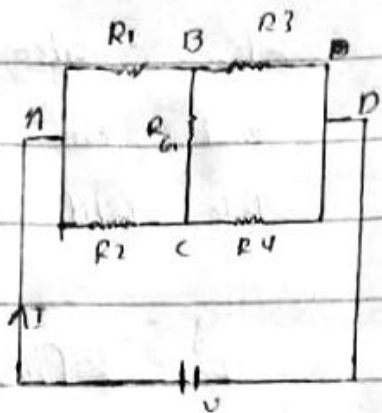If bridge is not balanced then some current flows through G and let resistance offered be R_g .



$$\text{Total Current} = I$$

$$\text{Total Voltage} = V$$

Then

$$R_{op} = \frac{V}{I} = \frac{V}{\frac{V_B}{R_3} + \frac{V_C}{R_4}}$$

Applying KCL eqⁿ for V_B & V_C

For V_B

$$\frac{V_B - 0}{R_3} + \frac{V_B - V_C}{R_g} + \frac{V_B - V}{R_1} = 0 \quad \text{--- eq(1)}$$

For V_C

$$\frac{V_C - 0}{R_4} + \frac{V_C - V_B}{R_g} + \frac{V_C - V}{R_2} = 0 \quad \text{--- eq(2)}$$

Solve eq(1) and (2) we get

$$\frac{V_B}{R_3} = \frac{V_C}{R_4}$$

(9)

Q No 4 Part a

Ans)

No PL is because AC Energy meter works due to the involvement of two alternating magnetic field produced by AC quantities (Voltage and Current respectively) that interacts with an aluminium disk causing eddy current to ~~induce~~ induced in the disk due to this eddy current and pre-existing magnetic field disks experience a force which causes it to rotate and increment the reading in proportion to the amount of energy consumed (in units or kWh both are same). In DC such induction effect and eddy current are not produced so the same energy meter cannot measure the energy consumed by any DC circuit until unless you convert the DC to AC then put it through, the energy meter and again convert it to DC and the supply to the DC load.

(10)

Q No 4 part b)

Ans)

It should be noted that when $\phi = 0^\circ$ (i.e. two fluxes are in phase) then deflecting torque is zero or no torque can be produced.

Torque will be maximum when $\phi = 90^\circ$

Q No 5 part a

Ans)

Series magnet

This series magnet consist a number of U-shaped lamination assemble together to form a core. A thick wire of few turns is wound on both legs of the U-shaped laminated core. The wound coil is known as current coil and is connected in series with the load so that it carries the load. The series magnet is placed underside the aluminium disc and produces magnet field proportional to and in phase with current.

Shunt magnet

The shunt magnet consist of a number of M-shaped laminations assembled together to form a core. A fine wire of large turns is wound on the central

(19)

Limb of this magnet. The wound coil is known as pressure coil is connected across the load. So that the carried current proportional to supply voltage. The shunt magnet is

In order to obtain deflecting torque current in the pressure coil must lag behind the supply voltage by 90° .

This copper ring as a short circuited transformer secondary. As its inductance is high as compared with its resistance the current circulating in the ring will lag by nearly 90° behind the voltage producing it.

————— * ————— * ————— * —————

Q No 5 part b

Ans) Energy meter constant is the amount of kWh used in its low voltage circuit for each revolution of the induction disc.

Calculation.

typical industrial 3-phase energy

(13)

Meter which is fed by a suitable current transformer (CT) and potential transformer (PT)

To calculate the MIC if it is given that No. of Revolutions per kWh then MIC is inverse of

this no. for example let's say

for a certain energy meter. No of Rev./kWh is given as

400, then $MIC = 1/400$. If the

No. of Rev. per kWh is given as

a very small no. like 0.06 or 0.16

etc. then it refers to kWh value

in primary circuit. This is kWh

value passes in H₀ circuit for

giving amount of Rev. To calculate

MIC in such cases, invert

such no. & then divide by

CT & PT ratio.