

## Course Details

Course Title

EDC

Module

3rd

Instructor

Dr - Shahryar

## Student Details

Name

Faiz ur Rehman

ID

141623

Sign

Faiz ur Rehman

Q1

### Part (A)

What types of circuit is this?  
this type of circuit is center tapped full wave rectifier

### Part (B)


What is the total peak secondary voltage?

$$V_p(\text{sec}) = n V_p(\text{Pri}) = 0.25(50) = 12.5\text{V}$$

$$V_p(\text{sec}) = 12.5\text{V}$$
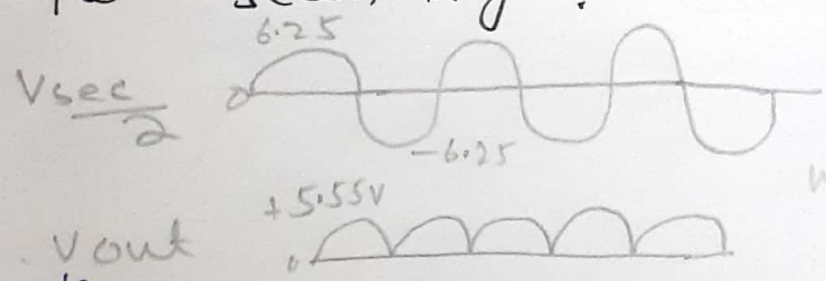
### Part (C)

Find the voltage across each half of the secondary?



6.25 Peak to Peak voltage the output voltage has peak value  $6.25 - 0.7$  which is diode drop.

### Part (d)

What is the peak current through each diode?

$$I_F = \frac{\frac{V_p(\text{sec}) - 0.7}{2}}{R_L} = \frac{5.55\text{V}}{10\text{K}\Omega}$$

0.555mA

p.

Q<sub>1</sub>

Part (E)

What minimum PIV rating must the diode have?

PIV Rating must diode have

$$\begin{aligned} \text{PIV} &= 2V_P(\text{out}) + 0.7 \\ &= 2(5.55\text{V}) + 0.7 \\ &= 11.8\text{V} \end{aligned}$$

Q<sub>2</sub> Determine the ripple factor for the filtered  $\dots\dots$  indicated in figure 2?

The transformer turns ratio  $n=0.5$

The peak primary voltage

$$\begin{aligned}V_p(\text{Pri}) &= 1.414 V_{\text{rms}} \\ &= 1.414(120) \\ &= 170 \text{ V}\end{aligned}$$

The peak secondary voltage is

$$\begin{aligned}V_p(\text{sec}) &= n V_p(\text{Pri}) \\ &= 0.5(170) = 85 \text{ V}\end{aligned}$$

Unfiltered peak full-wave rectified voltage is

$$\begin{aligned}V_p(\text{rect}) &= V_p(\text{sec}) - 1.4 \\ &= 85 - 1.4 \\ &= 83.6 \text{ V}\end{aligned}$$

Frequency of a full-wave rectified voltage is 120 Hz. The approximate peak to peak ripple voltage at the output is

$$V_r(\text{PP}) = \left( \frac{1}{f R_L C} \right) V_p(\text{sec})$$

$$= \left( \frac{1}{(120 \text{ Hz})(3300 \Omega)(100 \times 10^{-6} \text{ F})} \right) \cdot 83.6 \text{ V}$$

$$V_r(\text{PP}) = 2.111 \text{ V}$$

Approximate dc value of the output voltage is determine as follow

$$V_{DC} = \left( 1 - \frac{1}{2fR_L C} \right) V_p(\text{rect})$$

$$V_{DC} = \left( 1 - \frac{1}{(240)(3300)(100 \times 10^{-6})} \right) (83.6)$$

$$V_{DC} = \left( 1 - \frac{1}{79.2} \right) 83.6$$

$$V_{DC} = (1 - 0.0126) 83.6$$

$$= (0.9874) 83.6$$



$$V_{DC} = 82.5$$

Resulting ripple factor is




$$V_r(\text{PP}) = \frac{2.111}{82.5}$$

$$= 0.025$$

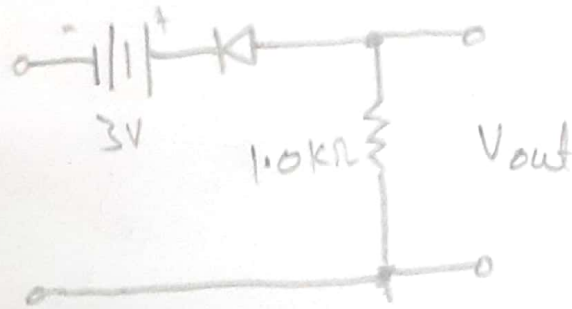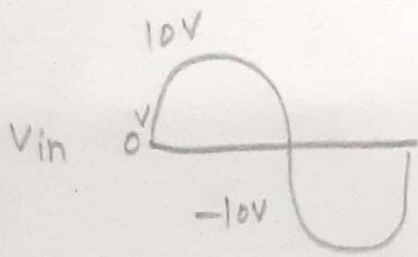Q<sub>3</sub> Determine the output waveform for the circuit given in Figure 3



output waveform of clipper circuit

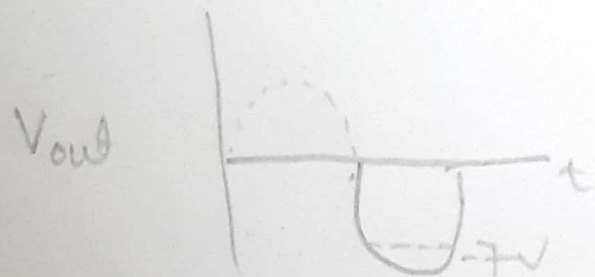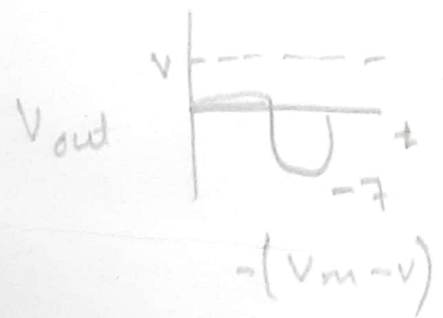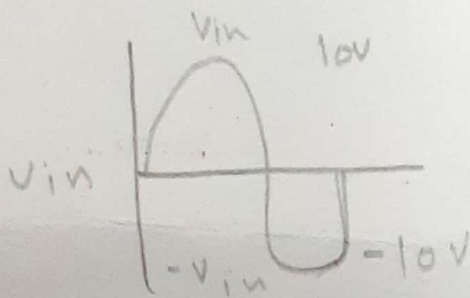

Q4

Assume the RC time constant is much greater than period of input.

So if we


( $5T_{\text{discharge}} > 50T/2$ ) Thus we obtain condition for the clamping operation

$$T_{\text{discharge}} \geq 5T$$

So


$$V_o = V_i - V + V_p(0V) \quad \therefore T \text{ is the}$$

period of input signal  $V_i$

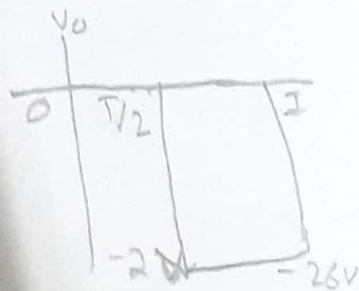

Q.5 (a) Part .

# Power Supply Filter.

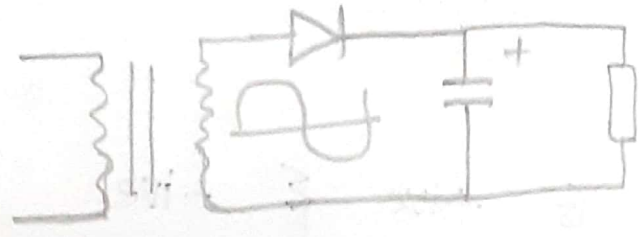

Act as filter


Reducing Ripples  
 Capacitor charging & discharging

(b) Part.
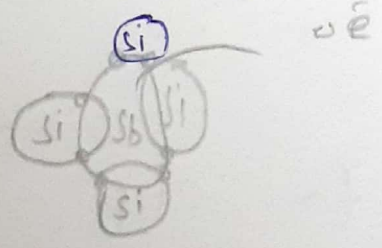
## N-TYPE

When a small amount of Pentavalent impurity added to a pure silicon crystal. It is N-type semiconductor.


The addition of Pentavalent impurity produce a large no. of free electron in the host crystal.


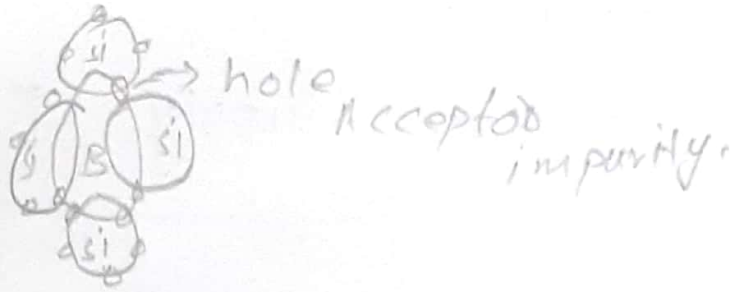
## P-TYPE

Extrinsic semiconductor formed when a trivalent impurity added to a pure semiconductor a small amount & as a result a large numbers of holes create








Part (c)

Diode limiter  $\&$  +ive  $\&$  -ive




Diode Limiter A type of circuit which is designed to clip a part of signal or A.C signal to desired wave-form.

Positive Diode limiter.

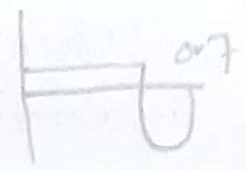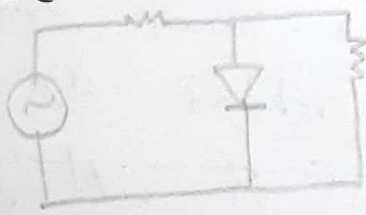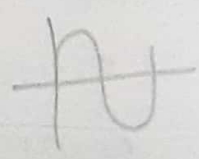

Used to clip +ive half cycle of sinusoidal wave

Negative Diode Limiter

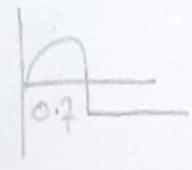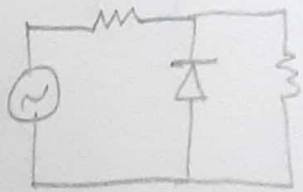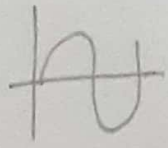


Used to clip -ive half cycle to clip to desired level.

Q5 Part (D)

Capacitor Effectively act as a battery in clamping circuit.

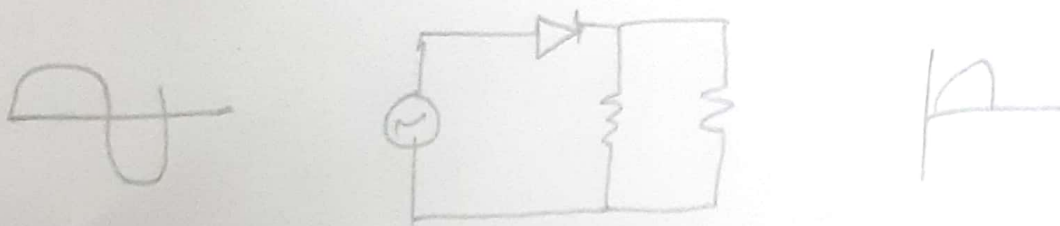Part (E)


output frequency of half wave rectifier is equal as input this means as input complete one cycle at output also complete one cycle.



$$f_{in} = f_{out}$$



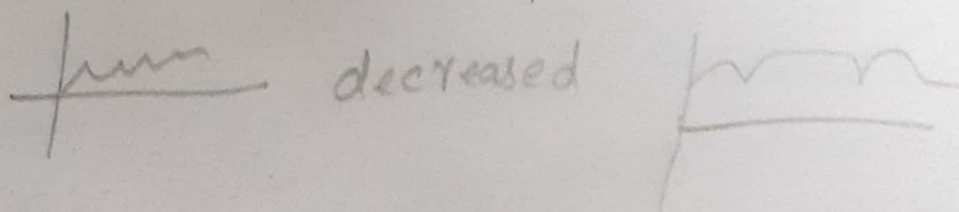
(f) Part

The load resistance to filtered power supply decrease the charging and discharging time of capacitor also increase. so takes longer time to charge & discharge.


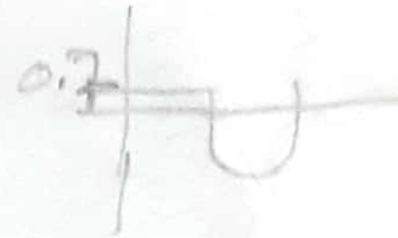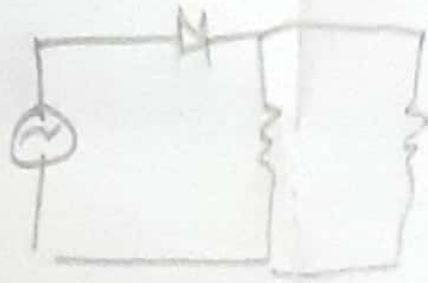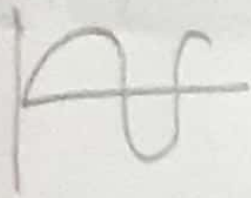
## Part (9)

It is a circuit which is used to clip a sinusoidal wave from at a desired level.



used as a voltage regulator to keep the voltage at a desired level.