

Name Hital Khan

UID → 6966

Program B.Tech Elect


Subject/paper : Network Analysis 01

Submitted to Eng. Aamir Aman

Question 01 Part (A).


Q1
for the bridge network in the figure below.

Find R_{ab} and I .

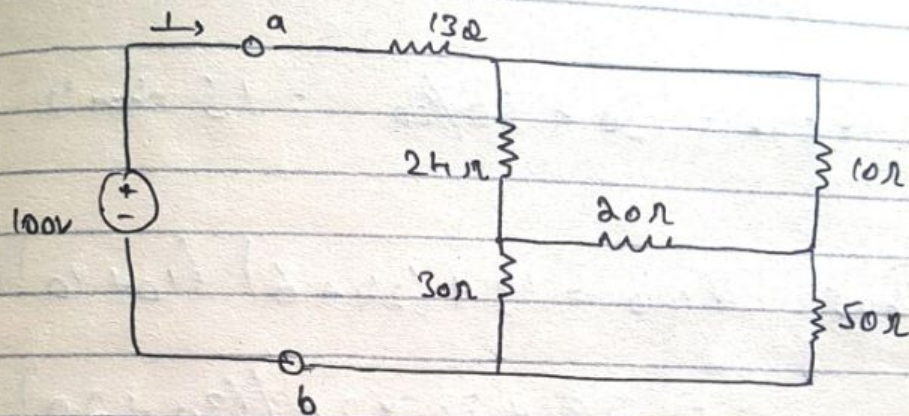

Solution

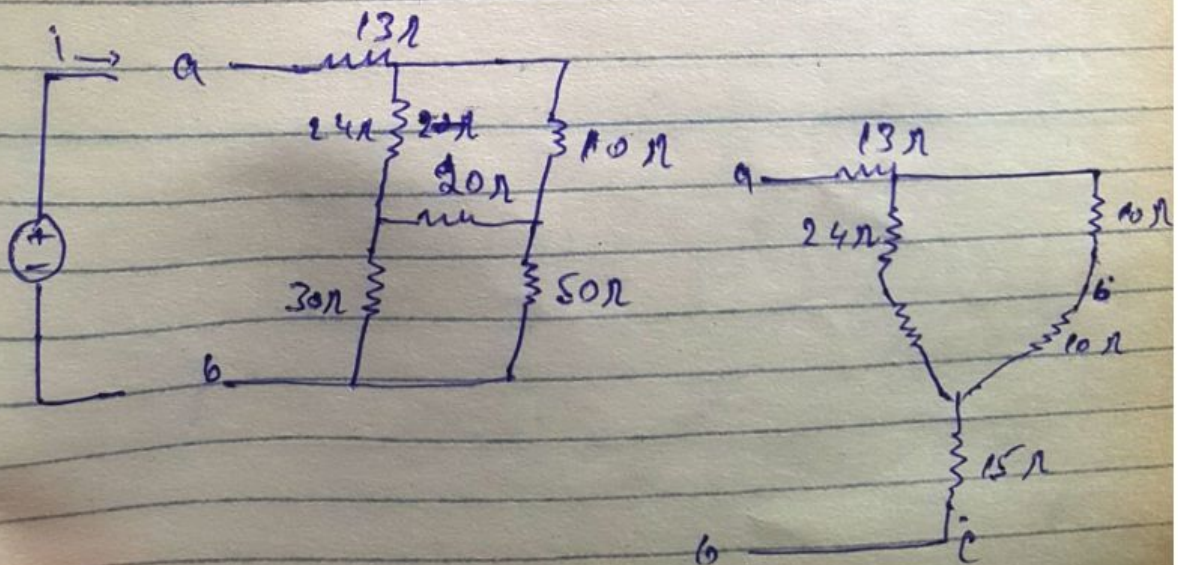first find the equivalent resistance, R . we convert the delta sub-networking to a wye connected form.



$$\begin{aligned} * R_{\text{in}} &= 20 \times 30 / [20 + 30 + 50] \\ &= 60 \text{ ohms} \end{aligned}$$

$$* R_{\text{bin}} = 20 \times 50 / 100 = 10 \text{ ohms}$$

$$R_{\text{cin}} = 30 \times 50 / 100 = 15 \text{ ohms}$$


$$\begin{aligned} \text{Thus } R_{\text{ab}} &= 13 + (24 + 6) / (10 + 10) + 15 \\ &= 28 + 30 \times 20 / (30 + 20) \\ &= 40 \text{ ohms} \end{aligned}$$

$$I = 100 / R_{\text{ab}} = 100 / 40 = \underline{2.5 \text{ amp.}}$$



}

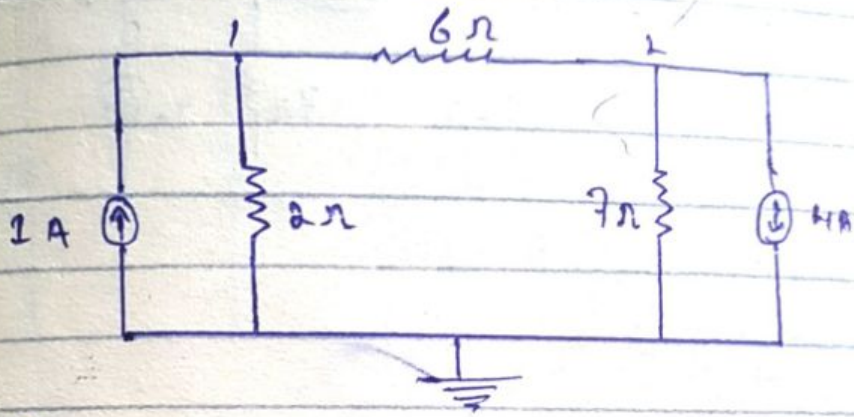
Question = 2 Part (B)

Obtain the node voltages in the circuit given below.



Solution →

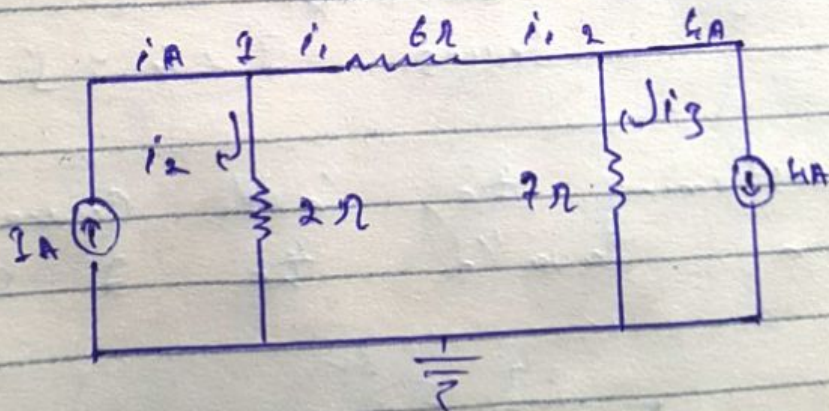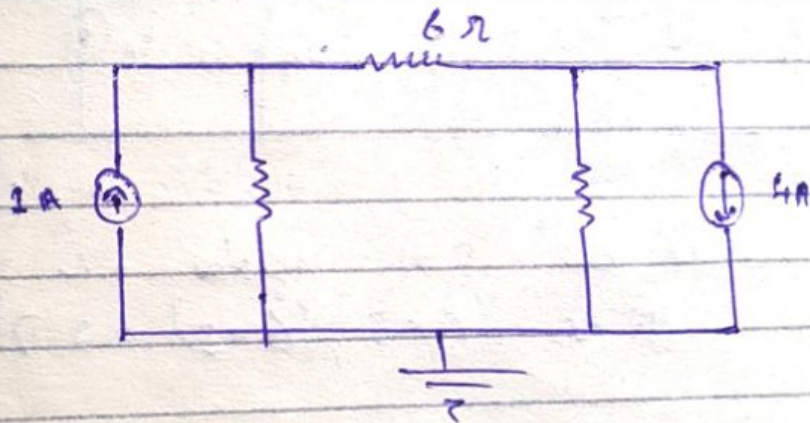

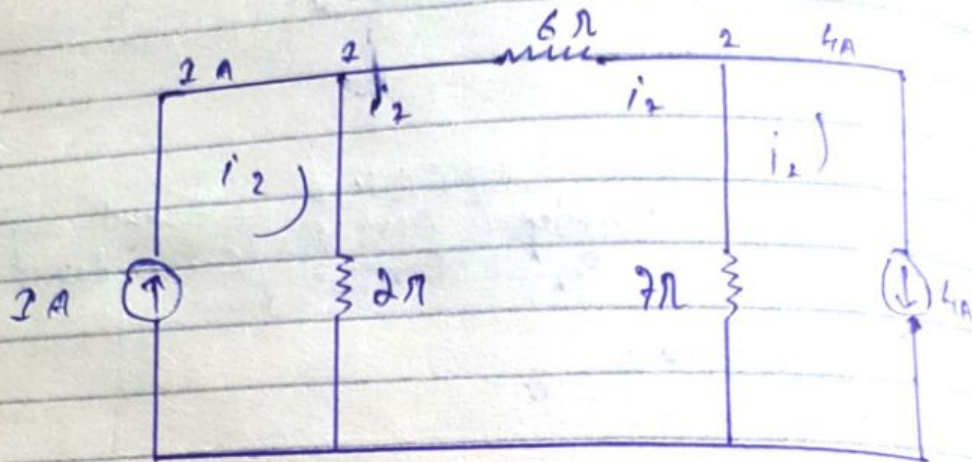

at node 1,

$$1 = i_1 + i_2 \rightarrow 2 = \frac{V_1 - V_2}{6} + \frac{V_1 - 0}{2}$$

$$\text{or } 6 = 4V_1 - V_2 \quad (1)$$

Node 2

$$i_2 = 4 + i_3 \rightarrow \frac{V_1 - V_2}{6} = 4 + \frac{V_2 - 0}{7}$$

$$\text{or } 168 = 7V_1 - 13V_2 \quad (2)$$

$$V_1 = 2V, \quad V_2 = -14V$$


Question: 02 Part (A)

Answers

Supernode

is a theoretical construct that can be used to solve a circuit. This is done by viewing a voltage source on a wire as a point source voltage in relation to other point voltages located at various nodes in the circuit relative to a ground node assigned a zero or negative charge.


A supernode is often used where a voltage source are in a weird place e.g. where the V_A source, without using a supernode, it would be difficult to do nodal analysis bcs you have no way of knowing what current is coming from V_A .

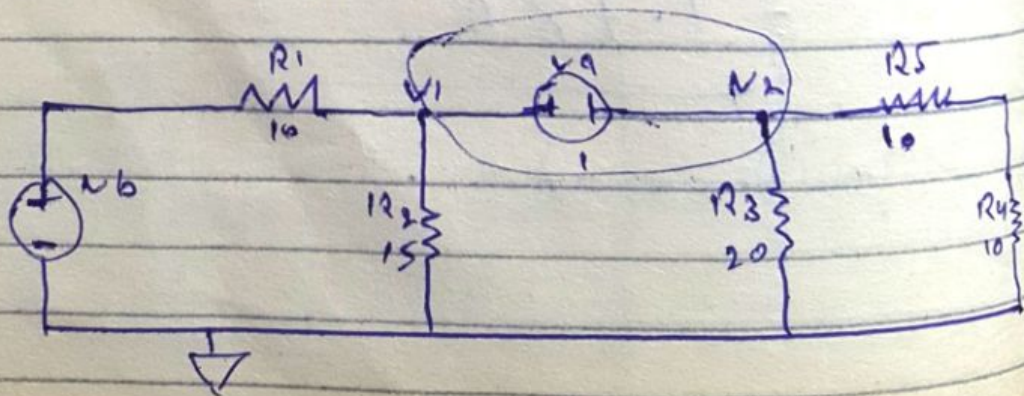


Pages 05
 Question = 02 Part (B)

6966

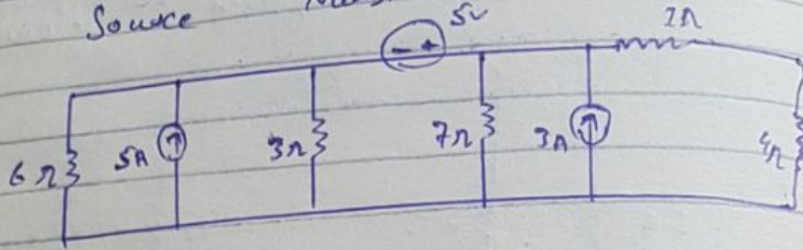Q1
 Find i_o in the circuit Show below
 Source transform \rightarrow




Solution

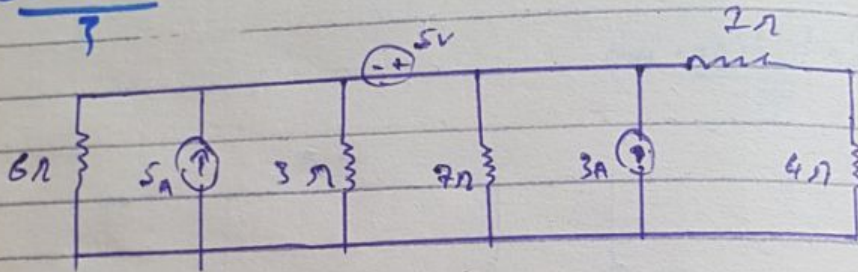

6Ω and 3Ω resistor in parallel
 gives $(6 \times 3) / (6 + 3) = 2\Omega$


Adding the 2Ω & 4Ω resistors
 in series $2 + 4 = 5\Omega$

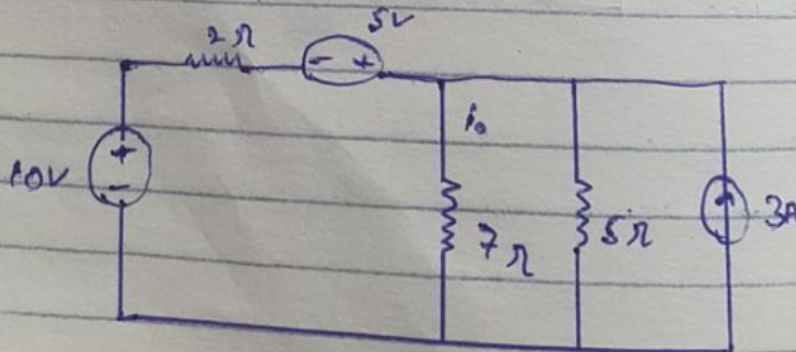Transforming the left current source
 in parallel the 2Ω resistor.




Adding the 10-v & 5-v voltage source
a 15-v voltage source

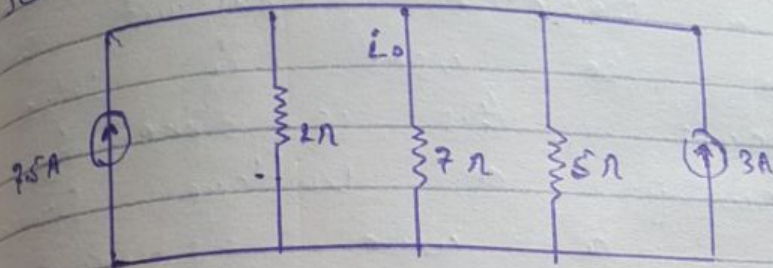below
Transforming the 15-v voltage source
series with the 2- Ω resistor.



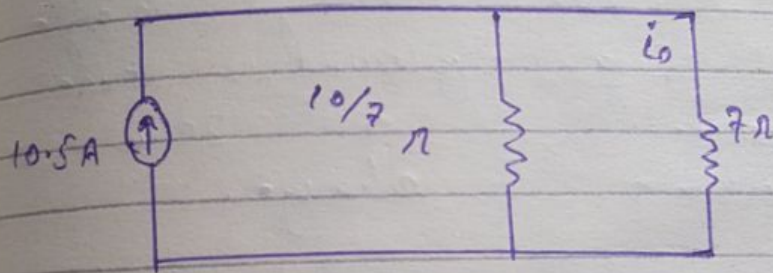Two 10A current source 2- Ω
and the 5- Ω resistor load 1k.



1k Device

$$I_o = \frac{\frac{10}{7}}{\frac{10}{7} + 7} (10.5) = 1.78A$$

$$= 1.78A$$


}

Page = 07

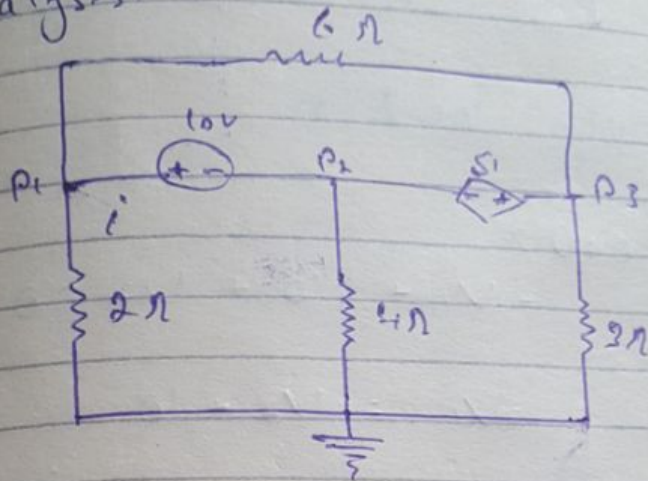
Question = 03.

6966
Part (A)

find V_1 , V_2 and V_3 in the circuit given using nodal analysis.



Solution

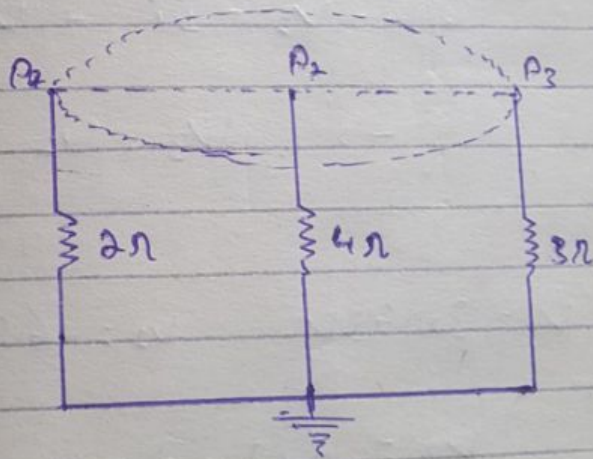


Applying KCL

$$\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$6V_1 + 3V_2 + 4V_3 = 0$$

Page: 08

~~110~~ 66 6966

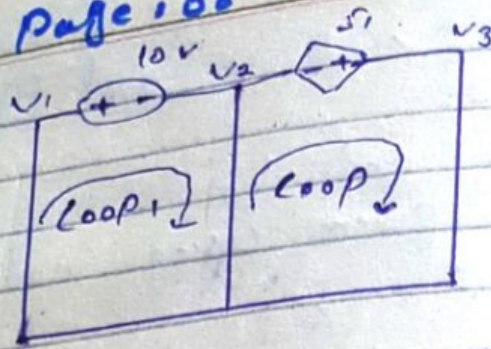

Apply KVL \Rightarrow

Loop 1

$$-V_1 + 10 + V_2 = 0$$

$$V_1 = V_2 + 10 \quad (1)$$

Loop 2

$$-V_2 - S_i + V_3 = 0$$

$$\rightarrow V_3 = V_2 + S_i \quad (2)$$


$$V_1 = 32043V. \quad V_2 = -6.956V.$$

$$V_3 = 652.2mV.$$

Q3: (B)

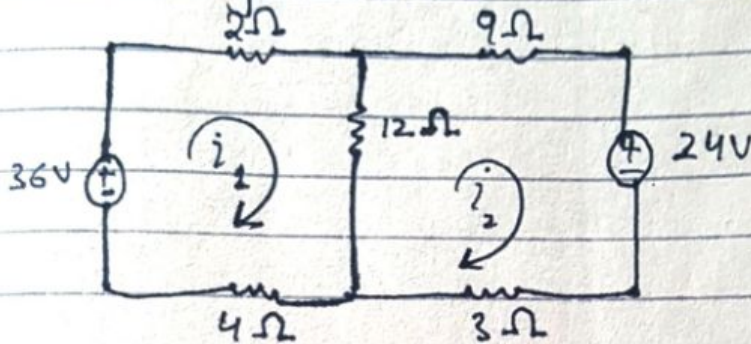Question = 03 Part (B)

Calculate the mesh currents i_1 and i_2 of the circuit given below.



Solution:

Applying KVL

$$-36 + 18i_1 - 12i_2 = 0$$

$$\text{Mesh 1} \rightarrow 3i_1 - 2i_2 = 6 \quad (1)$$

$$24 + 24i_2 - 12i_1 = 0$$

$$\text{Mesh 2} \rightarrow -3i_1 + 6i_2 = -6 \quad (2)$$

From (1) and (2) we get


$$i_1 = \boxed{2A}$$

$$i_2 = \boxed{0A}$$

Q4 (A)

Question = 04 (Part (A))


Use the superposition theorem to find v_o in the circuit shown below.

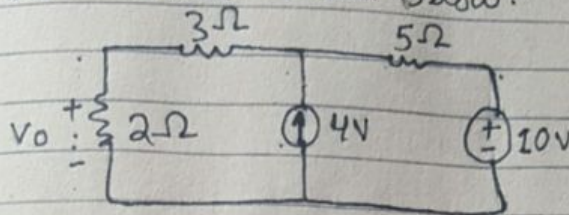Solution:

$$\text{Let } v_o = v_1 + v_2$$

Where v_1 and v_2 are contributions to the 10V and 4A respectively.

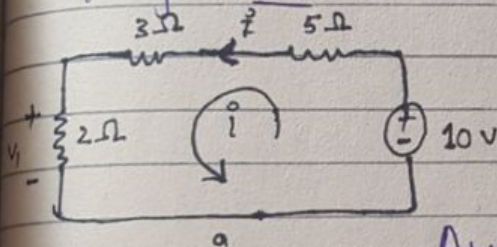To get v_1 , consider the circuit in Fig:




Apply Ohm's law

$$(2 + 3 + 5)i = 10$$

$$\rightarrow i = 10 / (10) = 1A$$

$$v_1 = 2i = 2V$$

To get v_2 consider the circuit:

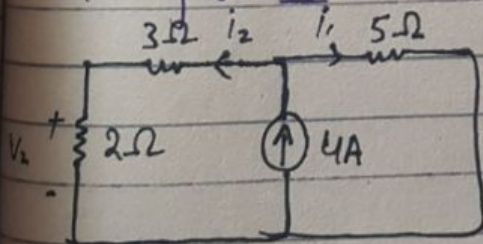

$$i_1 = i_2 = 2A, v_2 = 2i_2 = 4V$$

Thus,

$$v = v_1 + v_2$$

$$v = 2 + 4$$

$$v = \underline{6V}$$

Q4(B): Question (4) part (B)

What is Thevenin's Theorem:?

THEVENIN'S THEOREM:

Thevenin's theorem states that "any complicated network across its load terminals can be substituted by a voltage source with one resistance in series."

This theorem helps in the study of the variation of current in a particular branch when the resistance of the branch is varied while the remaining network remains the same.

For example:

In Designing electrical and electronic circuit-

* This theorem was derived by Leon Charles Thevenin in 1833,

* Thevenin's theorem is widely used when it's not possible to simplify a circuit using Kirchoff's law, Ohm's law etc.

Theorem also states that


"Any linear circuit with any number of voltage source and resistors can be replaced with a single voltage source in series with a resistance connected across a load".

Page: 12

661 6966

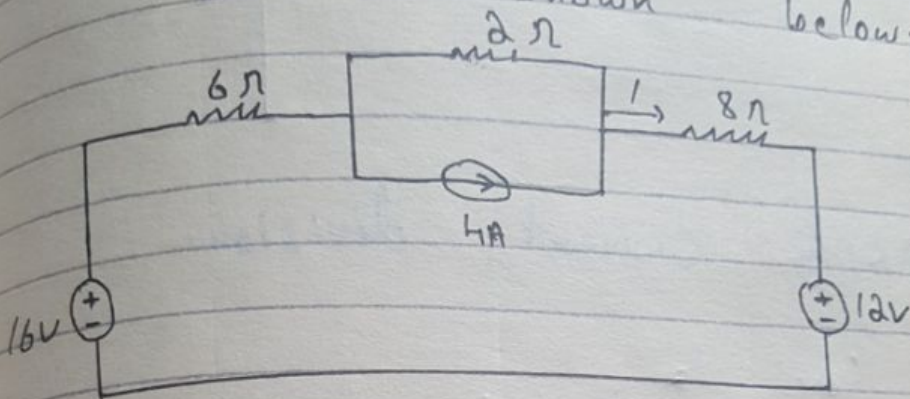Question = 05


Use the Superposition
Principle to find I in the
Circuit shown below.



Solution:


$$I = I_1 + I_2 + I_3$$

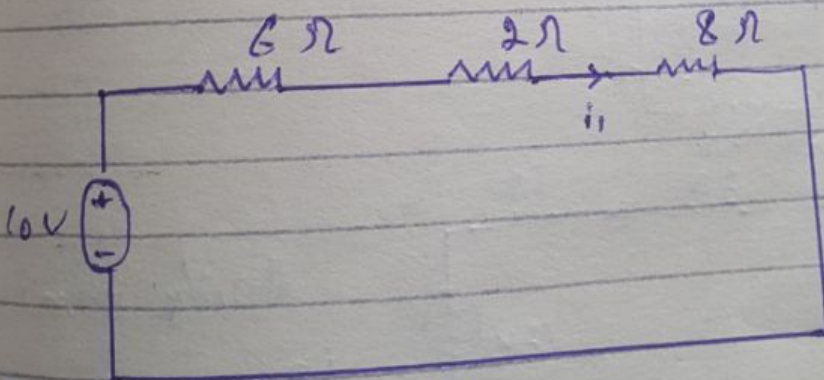where I_1 , I_2 and I_3 are contribution
due to 16V, 4A, 12V source
respectively.



Apply OHM'S LAW.

$$I_1 = \frac{16}{6 + 2 + 8} = 1A$$


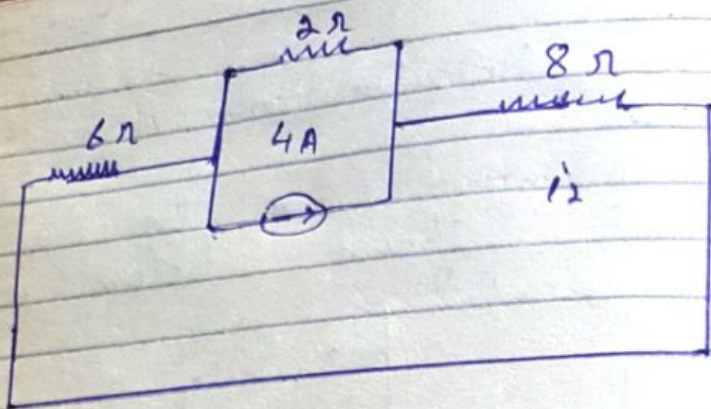


Apply Current division

For i_2

By Current division

$$i_2 = \frac{2}{2 + 14} (4) = 0.5$$

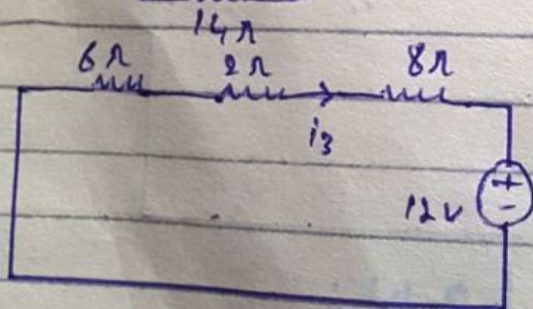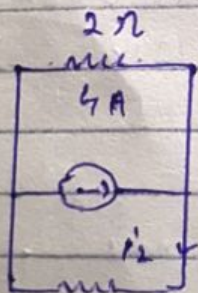

Apply Ohm's Law

$$i_3 = \frac{12}{16}$$

$$i_3 = \frac{12}{16} = 0.75 \text{ A}$$

thus $i = i_1 + i_2 + i_3$
 $= 1 + 0.5 - 0.75$
 $= 750 \text{ mA}$