

Digital Logic Design


Assignment 6
Sir. Muhammad Amin




HASSAN MEHDI

15453
Csc-201


Q1

 


Q2

 


Q3

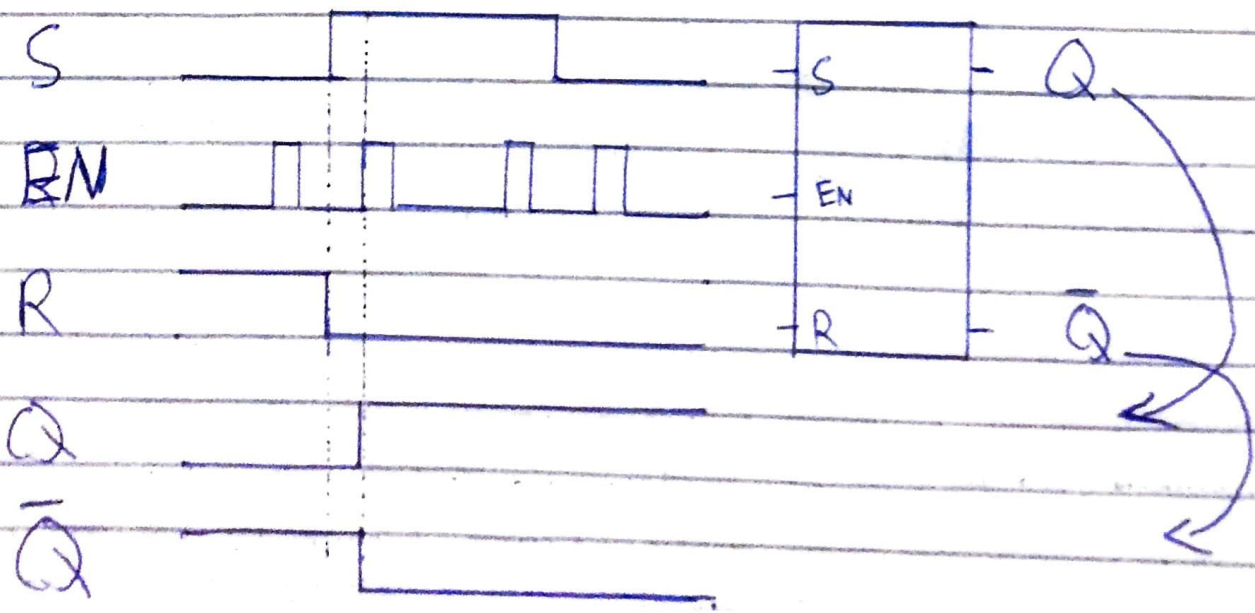

Q4

 

Q5

 


The main difference between (a) and (b) edge triggered JK-Flip-Flops is that


The flip flop (a) triggers on the - Negative edge of the clock pulse, while

The flip flop (b) triggers on the + Positive edge of the clock pulse.


(b)

 


Q7:

 


Q8:

 


Q9:

 


Q10:

 


Q11:

 

Q12

 

Q14

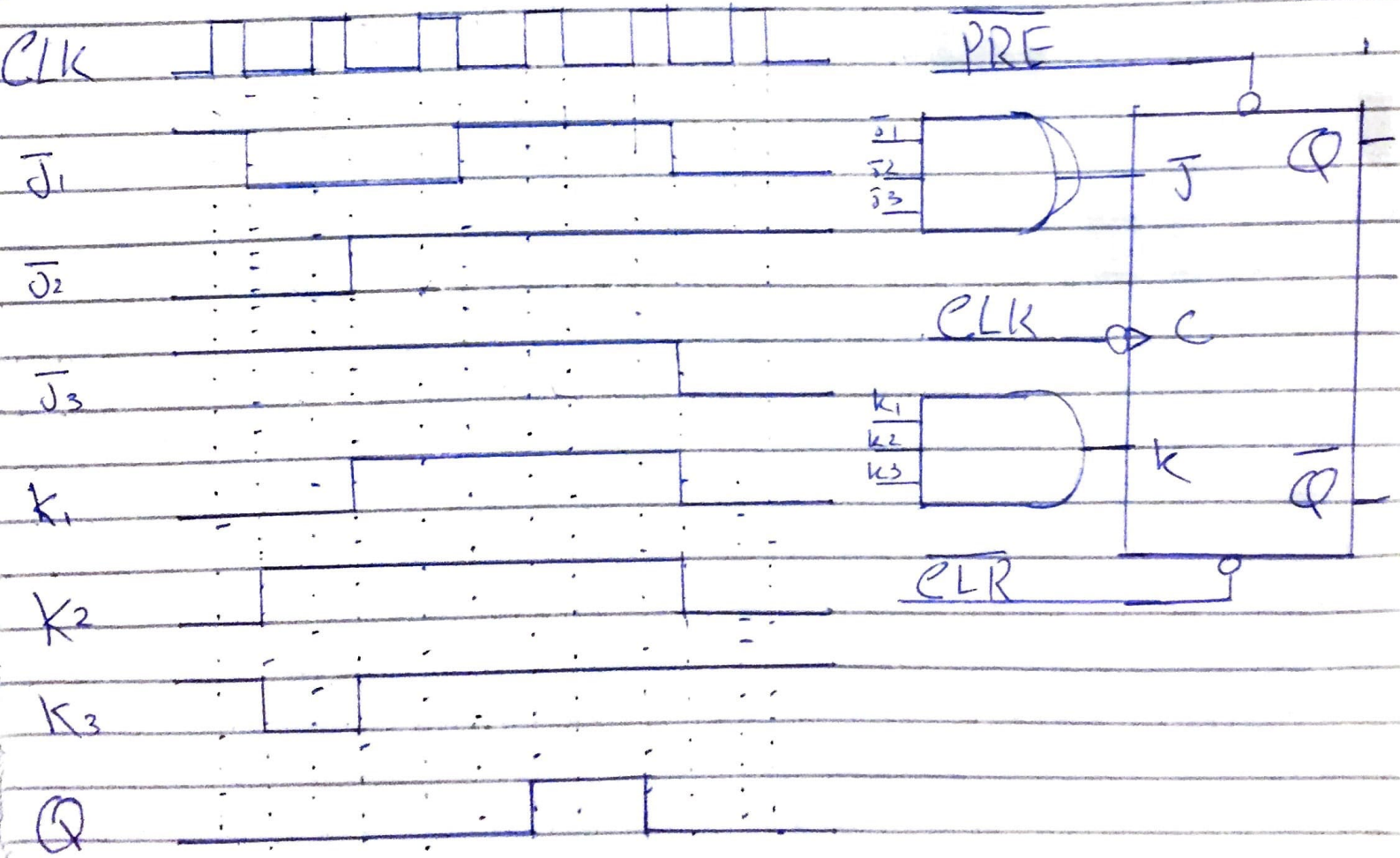

Q#13

$$\bar{d}_1 = 1010011$$

$$\bar{d}_2 = 0111010$$

$$\bar{d}_3 = 1111000$$

$$\bar{d} = 0010000$$

$$k_1 = 0001110$$

$$k_2 = 1101100$$

$$k_3 = 1010101$$

$$k = 0000100$$

$$\bar{d} = 0010000$$

$$k = 0000100$$

$$Q = 0011000$$

Q15

CLK

\bar{J}_1

\bar{J}_2

\bar{J}_3

K_1


K_2



K_3

PRE


CLR

Q

 

 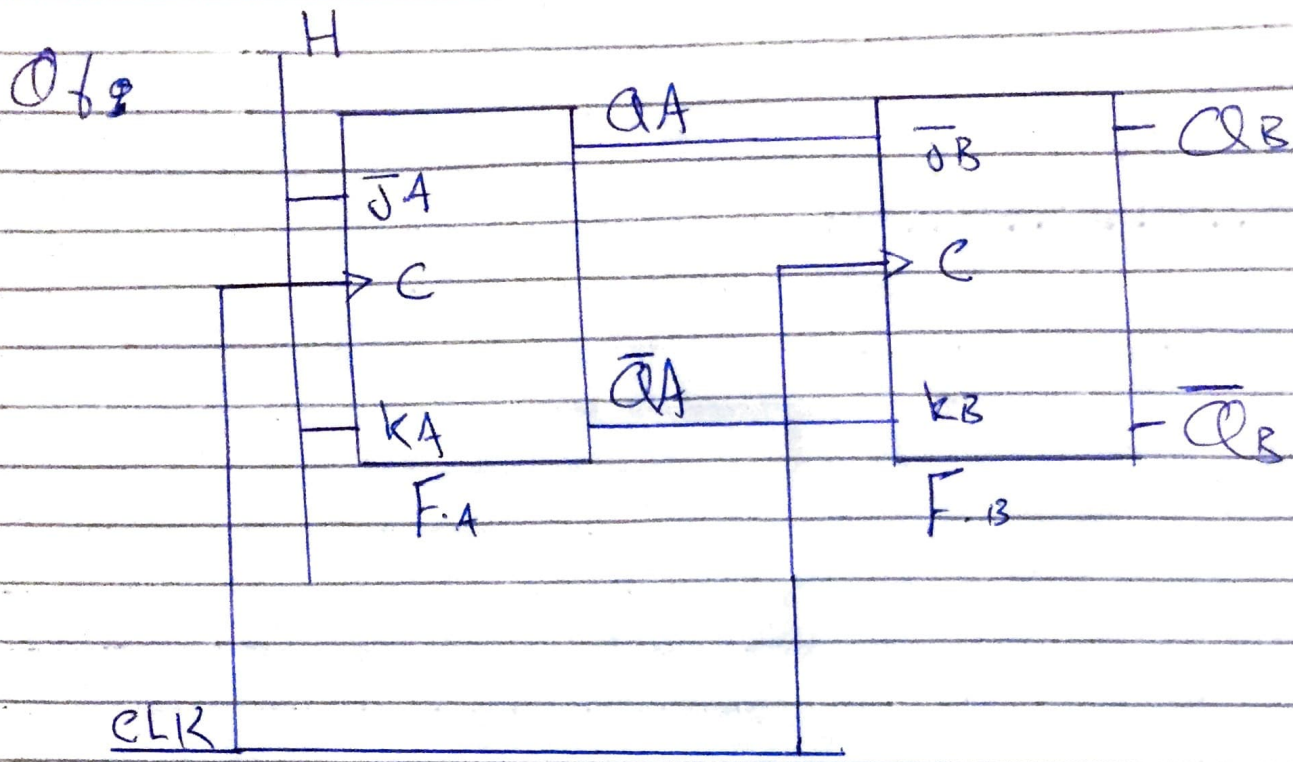


Q17:

 

The device performs the
Divide-by-two function

Q18:

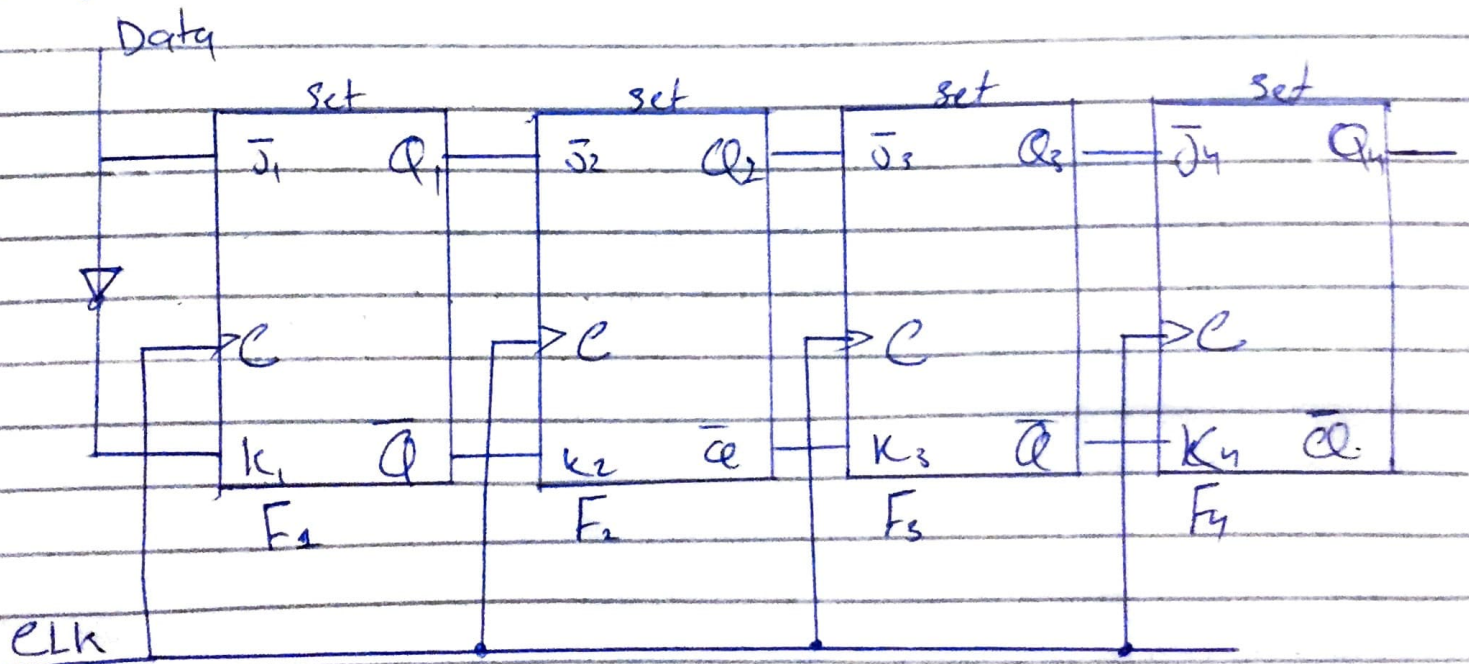


Q19:

$$Q_A = f/2$$

$$Q_B = f/4$$

$$Q_C = f/8$$

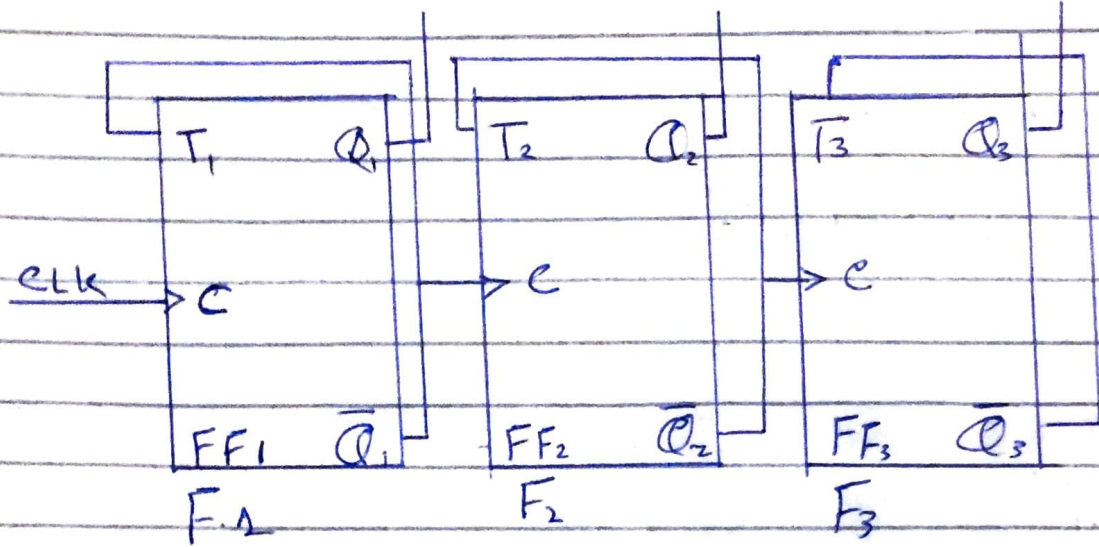

Here if the input frequency is 8 kHz then at given nodes frequency will be as follows

$$Q_A = f/2 = 4 \text{ kHz}$$

$$Q_B = f/4 = 2 \text{ kHz}$$

$$Q_C = f/8 = 1 \text{ kHz}$$