

(1)

Name: Awcus Cahafar
ID #: 15269
Dep: BScs
Subject: Basic Electronics
Teacher: Sir Khatid. Hameed.

(Q NO: 1)

(A) Explain JFET works including the Pinch off and Source cutoff voltage?


Ans:

The working of JFET can be explained as follows.

Case I

When a voltage V_{DS} is applied between the Drain and Source terminals and the gate voltage is zero as shown in the following figure. The two p-n junctions at the sides of the BAR establish depletion layers.

(2)

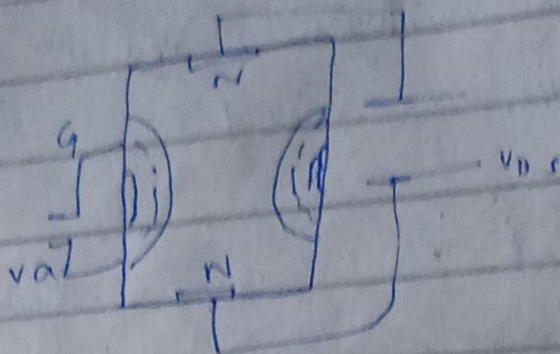

And the cut off voltage is voltage at which a battery is considered fully discharged could cause harm and the pinch off voltage is the drain to source voltage after which the drain source current becomes almost constant and JFET enter into saturation region. and is defined only when gate to source is zero.

Compare the JFET and bipolar junction transistor. Also explain the advantage and disadvantage of each.
ans. The comparison of the JFET and bipolar junction transistor. Also explain the advantage and disadvantage of.
in reverse biased the gate current is particularly zero.

(3)

And the base current of the BJT is always some value greater than zero.

Advantage of JFET.

- i) The JFET has high input impedance.
- ii) JFET are protected to radiation.
- iii) The JFET is a low power consumption device.

Disadvantage.

- i) The main disadvantage of JFET is relatively low gain bandwidth product.
- ii) The performance of JFET go down as frequency increases due to feedback by internal capacitance.

Advantage of BJT:

- 1) It has a large gain bandwidth.
- 2) It shows better performance at high frequency.
- 3) It has a better voltage gain.

Disadvantage


- i) The BJT is more an effect of radiation.
- ii) It more noise produced.
- iii) It has a low thermal stability.

Q. NO. 2.

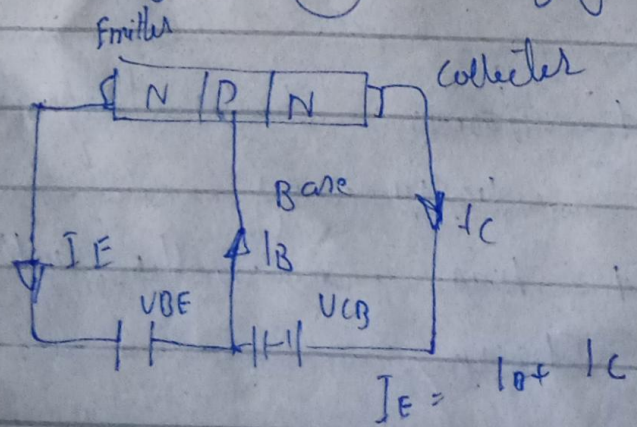a) Draw a npn transistor showing the p region and the bias transistor properly and explain how it works.

Bipolar transistor or BJT comes in to basic forms. And NPN negative - positive Negative and PNP (Positive Negative


The most commonly used transistor is NPN. A bipolar NPN transistor configuration drawn following configuration.



(6).

A graph of the collector characteristics versus V_{CE} is shown in following

fig.

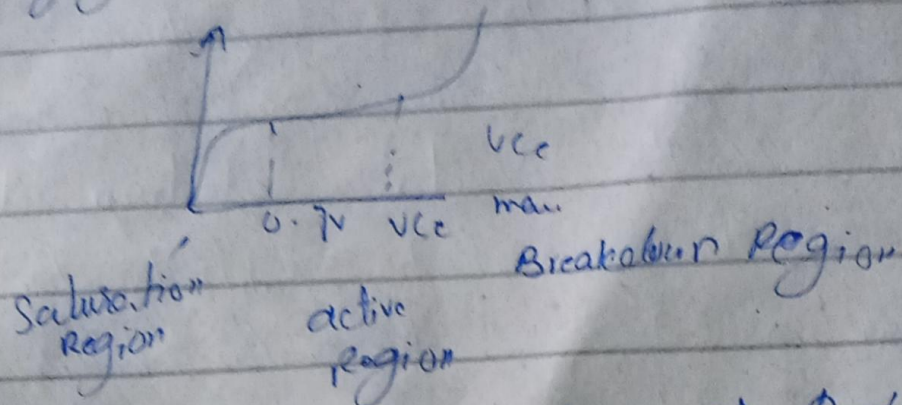

Suppose V_{BE} and V_{CE} are positive a current $i_B = 0$ and $V_{CE} = 0V$ then both BE and BC junction are forward biased. The saturation region corresponds to the case where both junctions are forward biased.


if V_{CE} increases too much the transistor goes into the breakdown region. This should be avoided.

The following fig. shows collector curves for different I_{B} values of base current when $I_E = 0$.

The transistor is in its cutoff region and only a small leakage.

(7)

Current flows as I_c

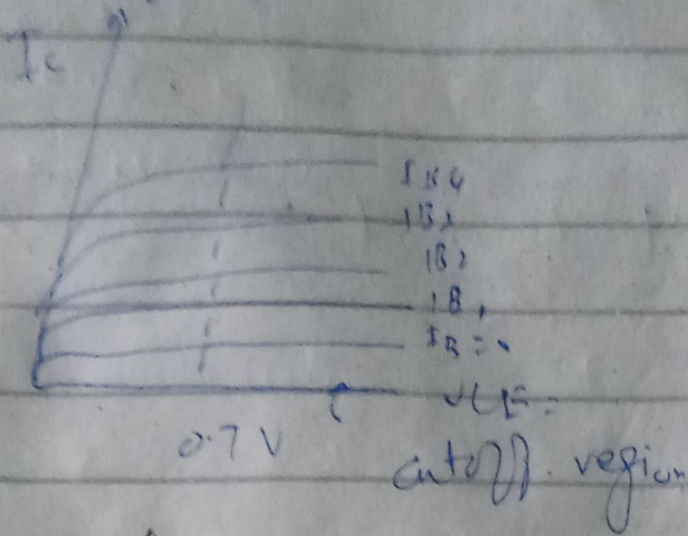


Q: NO: 1

b)

Draw the drain curves and the transconductance curve for a JFET?


Ans. The following are the drain curves and the transconductance curve of

a JFET

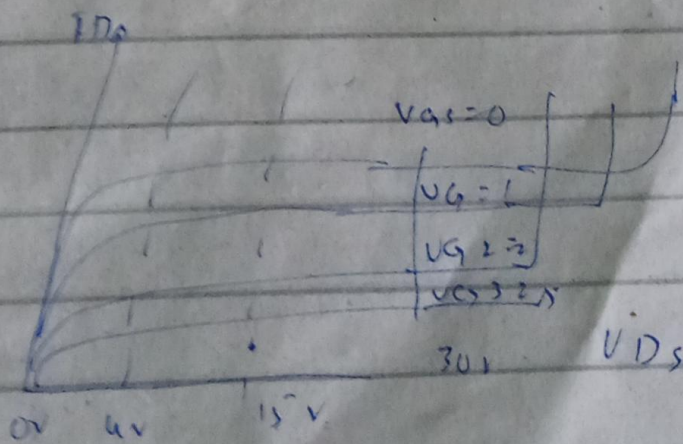

(a) (Drain Curves)

8

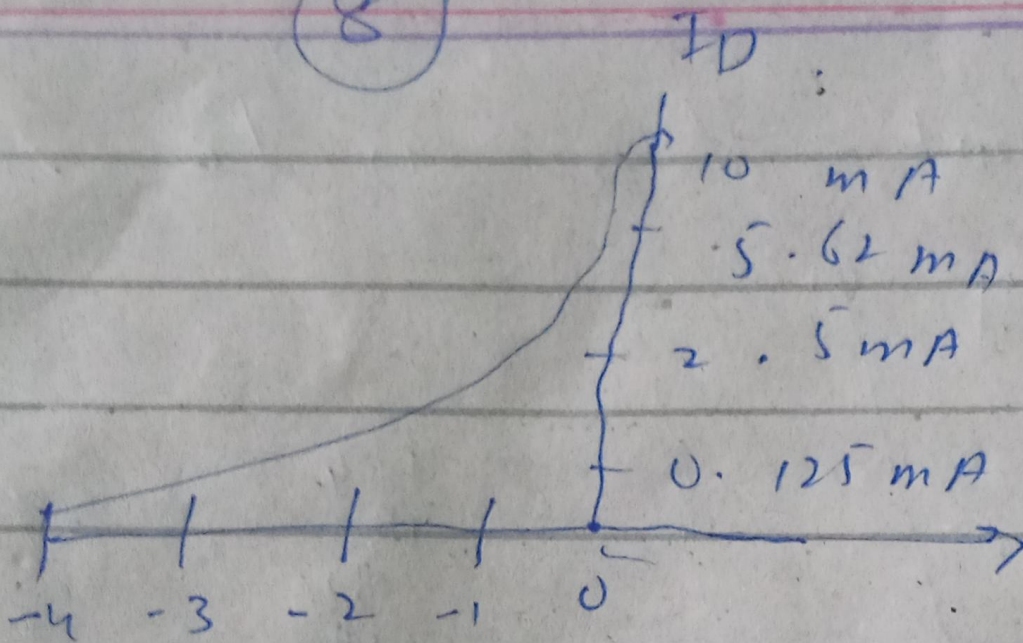

1b)

Trans conductance Curve

