

Name → Hamza

ID → 13042

SUBJECT → Power Electronics

Semester → 8th

Submitted TO → Sir Shayan Tariq

D/p → Electrical.

1

QNO 1:-

Uncontrolled Half wave Rectifiers-

(1) The rectifier element connected to the line at the highest +ve instantaneous voltage can only conduct and pulsates b/w V_{max} and $0.5V_{max}$.

(2) It is called 3- ϕ 3 pulse rectifier as the opp is repeated thrice in every cycle of V_s .

(3) The ripple frequency (F_r) of the opp voltage is " $F_r = nF_s$ " $n = \text{no of diodes}$, $F_s = \text{AC supplies Freq}$

(4) The ON diode connects its most +ve source terminal to the other two diode cathodes keeping the other diodes off.

(5) The sudden switchover from one diode to another is called commutation.

(6) Each diode conducts for 120° intervals.

(2)

Full Wave Bridge Rectifier:-

① On the positive half cycle of transformer secondary supply voltages diode D_1 and D_2 conduct supply this voltage to the load.

② On the negative half cycle of supply voltages, diodes D_3 and D_4 conduct supplying this voltage to the load.

③ It can be seen from the waveforms that the peak inverse voltage of the diode is only V_m .

④ The average output voltage is the same as that for the centre tapped transformer full wave rectifier.

⑤ Peak repetitive current diode = V_m/R

⑥ A.V. output voltage $V_o = \frac{2V_m}{\pi}$, ~~RMS~~

RMS output voltage = $\frac{V_o}{\sqrt{2}}$

3)

(2) Uncontrolled Rectifier:-

(i) Higher o/p voltage for given i/p voltages.

(ii) Lower amplitude ripples i-e output voltage is smoother.

(iii) Higher frequency ripples simplifying filtering.

(iv) Higher overall efficiency.

Control Rectifiers:-

(i) Unlike diode, an SCR does not become conducting immediately after its voltage has become positive.

(ii) It requires triggering by means of pulse at gate.

(iii) So it is possible to make the thyristor conduct at any point on the half wave which applies positive voltage to its node.

(4)

Q2:

Given data:

$$V_m = 42 \text{ v}$$

$$R = 13 \Omega$$

Required

	Half wave	Full wave Bridge
(i)	V_{dc}	(i) V_{dc}
(ii)	I_{dc}	(ii) I_{dc}
(iii)	I_{rms}	(ii) I_{rms}
(iv)	V_{rms}	(iv) V_{rms}

Solution:-

We know that,

V_{dc} for half wave is

$$V_{dc} = \frac{V_m}{\pi}$$

$$V_{dc} = \frac{42}{3.14}$$

$$V_{dc} = 13.37 \text{ v}$$

(ii) $I_{dc} = \frac{V_m}{\pi R}$

$I_{dc} = \frac{42}{3.14 \times 13}$

$I_{dc} = \frac{42}{40.82}$

$I_{dc} = 1.02 \text{ Amp}$

(iii) $I_{rms} = \frac{V_m}{2R}$

$I_{rms} = \frac{42}{2 \times 13} = \frac{4}{26}$

$I_{rms} = 0.153 \text{ A}$

(iv) $V_{rms} = \frac{V_m}{2}$

$V_{rms} = \frac{42}{2}$

$V_{rms} = 21 \text{ v}$

→ Now for Full wave bridge

(i) $V_{dc} = \frac{2V_m}{\pi}$

$V_{dc} = \frac{2(42)}{3.14} = 26.75$

$V_{dc} = 26.75 \text{ v}$

(6)

(ii) $I_{dc} = V_m/R$
 $I_{dc} = 42/13$

$$I_{dc} = 3.23 \text{ A}$$

(iii) $I_{rms} = I_{dc}/2$

$$I_{rms} = 3.23/2$$

$$I_{rms} = 1.615 \text{ A}$$

(iv) $V_{rms} = \sqrt{2} V_s$

$$V_{rms} = \sqrt{2} V_{dc}$$

$$V_{rms} = 1.41 \times 26.75$$

$$V_{rms} = 37.7175 \text{ V}$$

Full wave rectifier is better than half wave because it allows both positive and negative cycle. But in half wave it block negative and just allow the positive to move.

(7)

Q3

Answer

Buck chopper Application

when Switch is opens-

when switch is open the

inductor stores energy in the

form of a magnetic field. If the

switch is opened while the current

is still changing, then there will

always be a voltage drop across the

inductor, so the net voltage at

the load will always be

less than the input voltage source.

(8)

When switch is closed:-

When the switch is ~~not~~ closed

The current will begin to increase

and the inductor will produce an

opposing voltage across its terminals

in response to the changing current.

This voltage drop counteracts the

voltage of the source and therefore

reduces the net voltage across the

load.

Working of buck chopper :-

The buck converter circuit consists of

the switching transistor, together with

(9)

the flywheel circuit (DI, L1 and C1)

while the transistor is on current

is flowing through the load via

the inductor L1. The action of any

inductor opposes changes in current

flow and also acts as a store of

energy.

Numerical:-

Given data:

$$V_{in} = 50V$$

$$D = 42\%$$

$$R = 13$$

$$F = 20KHZ$$

Required

V_{out} , I_{out} , I_{in} , inductor = ?

(10)

(i) $V_{out} = ?$

We know that:

$$V_o = d(V_i)$$
$$= (0.42 \times 50)$$

$$V_o = 21 \text{ V}$$

(ii) $I_{out} = ?$

$$I_{out} = V_o / R$$

$$I_{out} = 21 / 13$$

$$I_{out} = 1.615 \text{ A}$$

(iii) $I_{in} = ?$

$$I_{in} = V_i / R$$

$$I_{in} = 50 / 13$$

$$I_{in} = 3.84 \text{ A}$$

(iv) Inductor (L) = ?

$$L = \frac{T_{off}}{2} \times R \rightarrow (A)$$

So we have

$$V_o = dV_i$$

$$d = V_o / V_i$$

$$d = 21 / 50$$

$$d = 0.42$$

(11)

now

$$\frac{T_{ON}}{T} = 0.42 \rightarrow (B)$$

$$T_{ON} = 0.42 \times T$$

Note: $T = \frac{1}{F}$

$$T_{ON} = 0.42 \times \frac{1}{F}$$

$$T_{ON} = \frac{0.42}{F}$$

$$T_{ON} = \frac{0.42}{20,000}$$

$$T_{ON} = 0.00021 \text{ s}$$

put in (B) we get,

$$\frac{T_{ON}}{T} = 0.42$$

$$T = \frac{0.00021}{0.42}$$

$$T = 0.0005 \text{ s}$$

now $T = T_{ON} + T_{OFF}$

$$T_{OFF} = T - T_{ON}$$

$$= 0.0005 - 0.00021$$

$$T_{OFF} = 0.00029 \text{ s}$$

(12)

now put this in eq (A)

we get

$$L = \frac{0.00029}{2} \times 13$$

$$L = 0.001885 \text{ H}$$

OR

$$\boxed{L = 18.85 \text{ MH}} \text{ Ans}$$


Q4:

Answer.

Working Principle:-

The main working principle of boost converter is that the inductor in the input circuit resists sudden variations in input current.

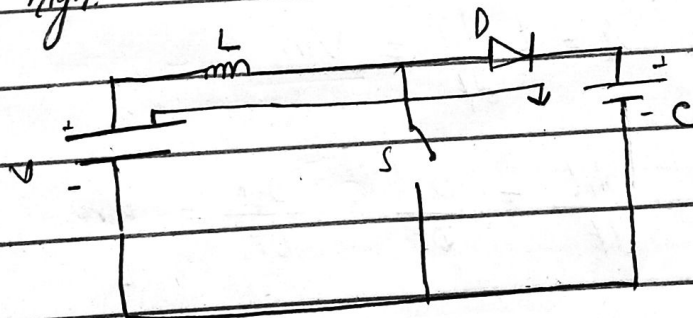When switch is off the inductor stores energy in the form of magnetic energy E , discharges it when switch is closed. The capacitor in the output circuit is assumed large enough that the time constant of RC circuit in the output stage is high.



The output capacitor is charged to the input voltage + one diode drop.

(14)

When SW is ON. our signal source goes high, turning on MOSFET. All the current is directed through to the MOSFET through the inductor. The output capacitor stays charged since it can't discharge through the now back-biased diode. is ON for a time T_{ON} & is OFF for time T_{OFF} . we define the time period, T as $T = T_{ON} + T_{OFF}$ & the switching frequency $f_{switch} = 1/T$

now define another term duty cycle $D = T_{ON}/T$

Boost converter in steady state equation for this made using KVL.

$$V_{in} = V_L$$
$$V_L = L \frac{di_L}{dt} = V_{in}$$

$$\frac{di_L}{dt} = \frac{di_L}{dt} = \frac{di_L}{DT} = \frac{V_{in}}{L}$$

Since the switch is closed for a time $T_{ON} = DT$ we can say that $DT = DT$.

$$(di_L) = \left(\frac{V_{in}}{L} \right) DT$$

Numerical part:-

Given data:-

$$V_{in} = 50 \text{ V}$$

$$D = 42\% = 0.42$$

$$R = 13$$

$$F = 20 \text{ KHZ}$$

Required

V_{out} , I_{out} , I_{in} , inductor = ?

Solution:-

As we know that,

$$(i) \quad V_{out} = \frac{V_s}{1-D}$$

$$V_{out} = \frac{50}{1-0.42}$$

$$V_{out} = 86.20 \text{ V}$$

$$(ii) \quad I_{out} = ?$$

$$I_{out} = \frac{V_{out}}{R} = \frac{86.20}{13}$$

16

$$I_{out} = 6.630A$$

$$(iii) \quad I_{in} = \frac{I_{out}}{1-D} =$$

$$I_{in} = \frac{6.630}{1-0.42}$$

$$I_{in} = 11.43A$$

(17)

Q5:-

Definition:

Buck Boost Converter:

The buck boost converter is a type of DC-DC that has output voltage magnitude that is either greater than or less than input voltage magnitude it is equal to bly back converter using a single inductor instead of a transformer.

Principles and working of Buck

Boost converter:

The main working principle of buck boost converter is that the inductor in the input circuit result sudden variations in input current.

When switch is ON the inductor store energy in the form of

(18)

magnitude energy and discharged it when sw is closed the capacitor in the output circuit is assumed large is enough that the time constant of RC circuit in the output stage is high the large time constant compare to switching period ensure a constant output voltage $V_o(t) = V_o$ (constant).

Numerical:-

$$V_{in} = 50 \text{ V}$$

$$V_{out} = 42\% = 0.42$$

$$R = 13 \Omega$$

$$f = 20 \text{ KHz}$$

Find (i) Duty cycle, I_{out} , V_{in} , inductor = ?

Solution,

We can't find the duty cycle because the time is not given so the duty cycle is zero.

19

(ii) $I_{out} = V_{out}/R$

$$I_{out} = \frac{0.42}{13}$$

$$I_{out} = 0.032 \text{ A}$$

(iii)

$$V_{in} = 50 \text{ V}$$

(iv)

Inductor (L)?

we also can't find inductor because the time is not given.