

Department of Electrical Engineering
Assignment

Date: 20/04/2020

Course Details

Course Title:

Power System Analysis

Module:

6th

Instructor:

Engg. Anand Anand

Total Marks:

30

Student Details

Name:

Sifatullah


Student ID:

~~149~~
14200

Sifatullah ID 14200


1

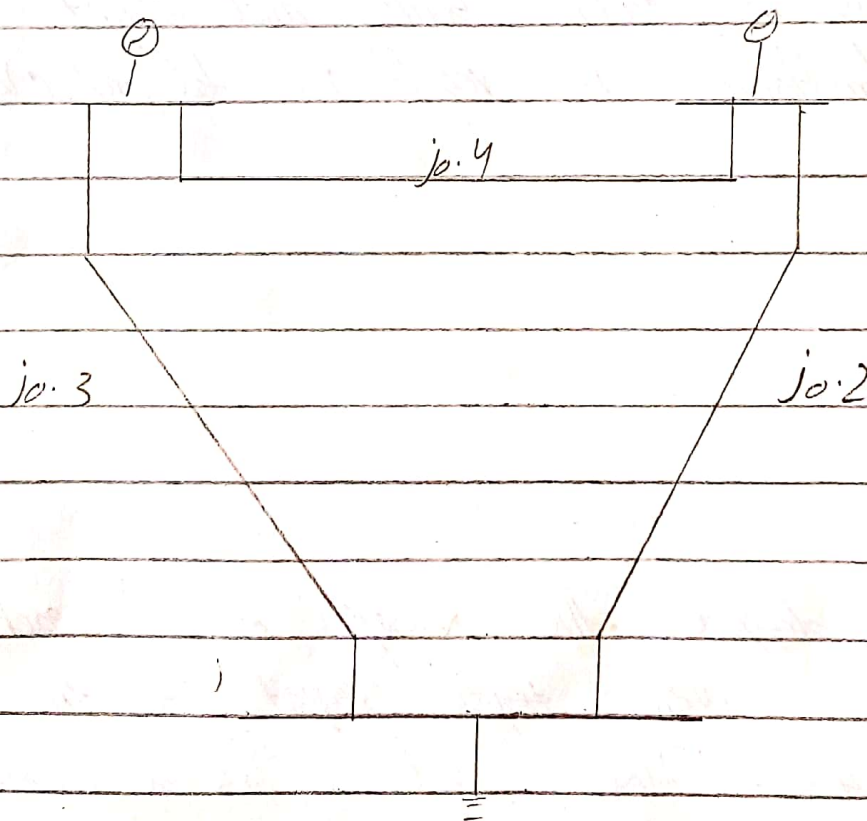Q3a For the simple line diagram shown below. Generator are connected to high tension buses 1 and 2 and supply to load connected at bus 3. Find the reactance diagram, the convert into equivalent current source and shunt admittance. Then find the admittance matrix and find the total current.




Ans. For all analysis all machines and any one bus are treated as a single machine and represented by a single emf and series resistance.

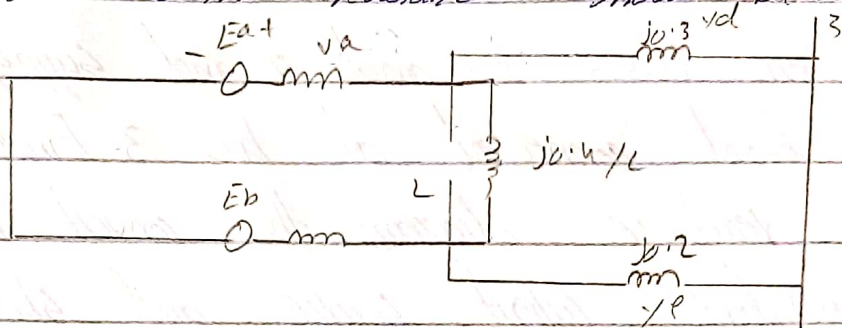The reactance diagram will be as follows with reactance show below.



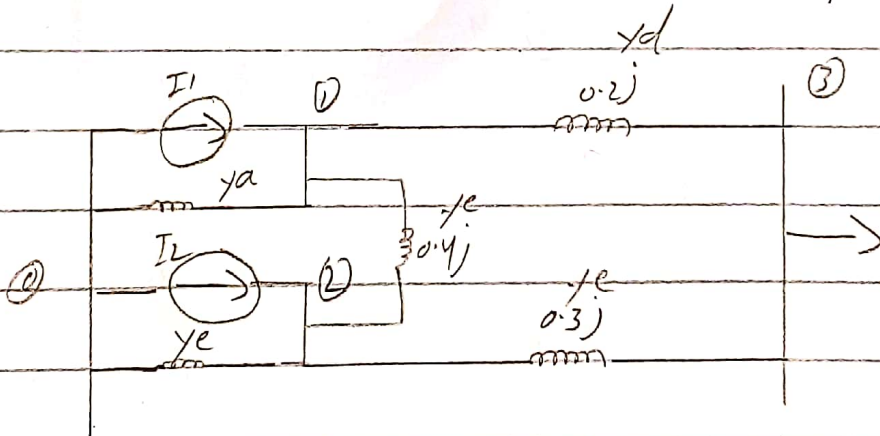If the ckt is redrawn with emf and impedance in series replaced by equivalent current source and shunt admittance. The result is following ckt.



To designate the voltage of each buses with respect to the neutral. Take node 0 as a reference.

Apply Kcl node 1

$$I_1 = v_1 y_a + (v_1 - v_2) y_b + (v_1 - v_3) y_d$$

$$I_2 = v_1 (y_a + y_c + y_d) - v_2 y_c - v_3 y_e \quad (1)$$

Similarly at node 2

$$I_2 = v_2 (y_b + y_c + y_e) - v_1 y_c - v_3 y_e \quad (2)$$

node 3

$$\textcircled{1} \rightarrow 3 = v_3 (y_d + y_e) - v_1 y_d - v_2 y_e \textcircled{3}$$

The standard form the the undrunk.

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \textcircled{5}$$

$\textcircled{5}$ is denoted as y_{bus} and called the bus admittance matrix.

The admittance y_i are called self admittance at the node and each equal the sum of all the admittances term on the node. They other admittance are called mutual admittance.

$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \end{bmatrix} = \begin{bmatrix} y_a + y_c - y_d - y_c & -y_d & -y_c \\ -y_c & y_b + y_e + y_e & -y_e \\ -y_d & -y_e & y_d + y_e \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$I_T = I_1 + I_2$$


$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \end{bmatrix} = \begin{bmatrix} y_a + 0 \cdot y_j - 0 \cdot y_j & -0 \cdot 2j \\ 0 \cdot y_j & -y_b + 0 \cdot y_j & -0 \cdot 3j \\ -0 \cdot 2j & -0 \cdot 3j & 0 \cdot 5j \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Sifatullah


ID 142010

4

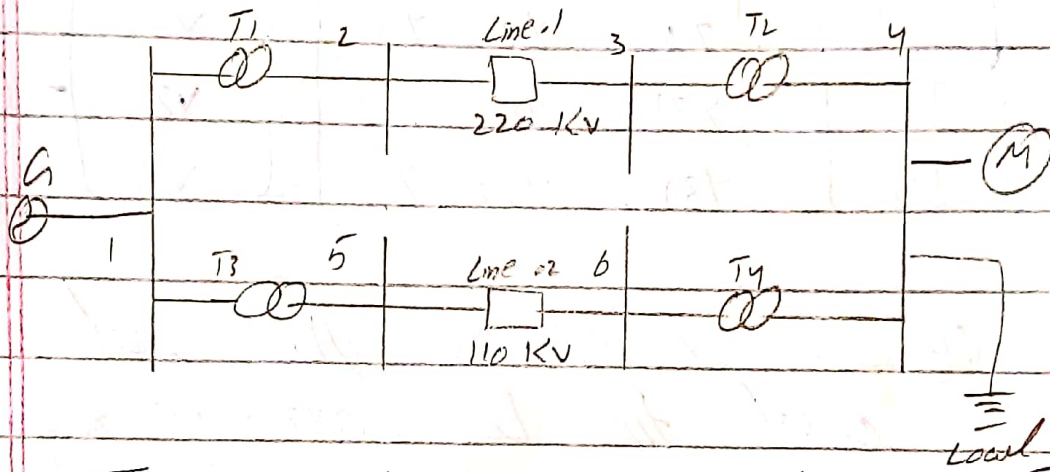Q2a) Single line diagram of 3 ϕ power system is shown in the below figure. Draw an impedance and reactance diagram in p.u.





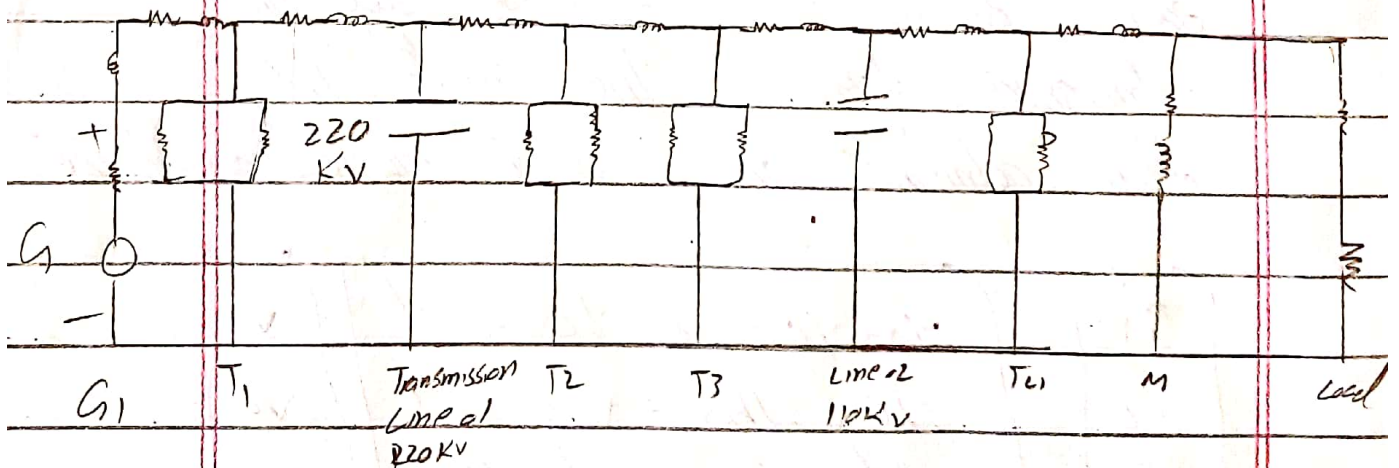Ans The impedance diagram of above system can be drawn as



The resistance is often omitted when making fault calculation because the inductive reactance of a system is much larger than its resistance.

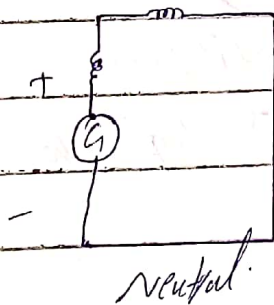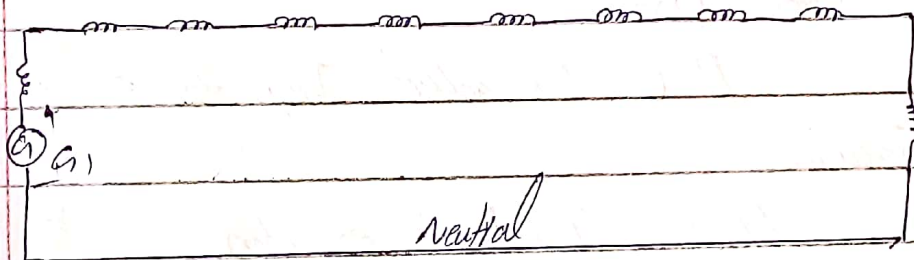If we decide to simplify our calculation of fault current by omitting all static load all resistance and capacitance of transmission line. The end use diagram reduces to the resistance diagram. Two simplification apply the fault calculation only.



Q1

Q1(b) Find the per unit equivalent impedance of an 11/132 kV transformer having 10Ω 1440Ω , the equivalent impedance. The primary and secondary current are 909 Amp and 75.75 amps respectively.

Ans Solution: Given data Quantities:

$$V_P = 11 \text{ KV}$$

$$V_S = 132 \text{ KV}$$

$$I_P = 909 \text{ Amp}$$

$$I_S = 75.75 \text{ Amp}, Z_1, Z_2, Z = 25$$

$$\text{impedance} = 10\% \rightarrow 1440 \Omega$$

Required Data:

P.U Equivalent Impedance = ?

Solution:

From Transformer equation

$$V_P / V_S = I_S / I_P = N_P / N_S = K \text{ or}$$

$$Z_1 \cdot P.U = \frac{Z_1}{Z_2} = \frac{Z_1}{V_P / I_P}$$

$$Z_1 \cdot P.U = Z_1 + \frac{I_P / V_P}{11000} = 0.826$$

$$Z_2 \cdot P.U = Z_2 + I_P / V_S$$

$$Z_2 \cdot P.U = 1440 \times \frac{75.75}{13200} = 0.82$$

Hence P.U equivalent Impedance of T/F is same referred to primary or secondary.

$$\boxed{Z_1 \cdot P.U = Z_2 \cdot P.U}$$

✗ ✗ ✗ ✗