

Department of Electrical Engineering

Assignment

Date: 13/04/2020

Course Details

Course Title: Electrical Network Analysis
 Instructor: Dr. Shehryar Shafique



Module: 4th
 Total: 30
 Marks:


Student Details

Name: Adnan Shahzada

Student ID: 14780

Student Signature: Adnan Shahzadaq

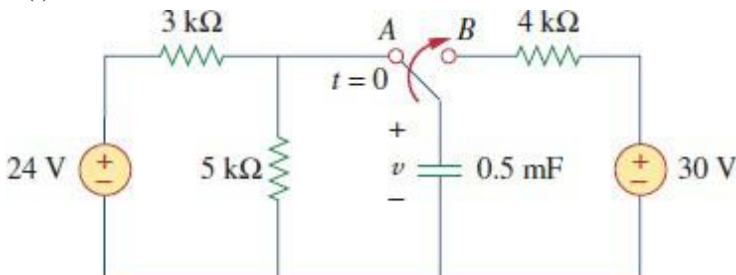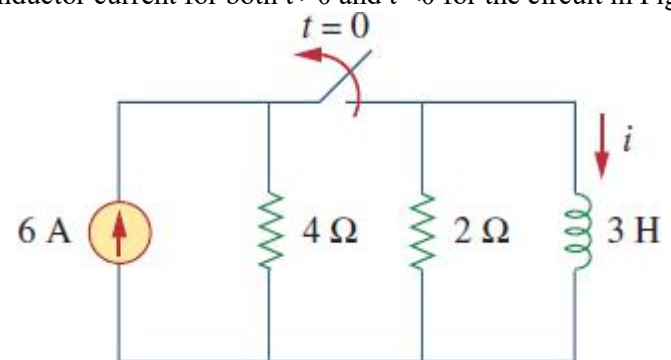
Q1.	<p>The switch in Fig. 1 has been in position <i>A</i> for a long time. At $t = 0$ the switch moves to <i>B</i>. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 2\text{s}$ and 8s.</p> <div style="text-align: center;">  <p>Figure 1</p> </div>	Marks 06 CLO 01
Q2.	<p>Determine the inductor current for both $t > 0$ and $t < 0$ for the circuit in Fig. 2.</p> <div style="text-align: center;">  <p>Figure 2</p> </div>	Marks 06 CLO 01
Q3.	<p>A series RLC circuit is described by</p> $\text{---} + \text{---} + \text{---} =$ <p>Find the response when $L = 0.5\text{ H}$, $R = 4\ \Omega$ and $C = 0.2\text{ F}$. Let $i(0) = 1$, $di(0)/dt = 0$</p>	Marks 06 CLO 01

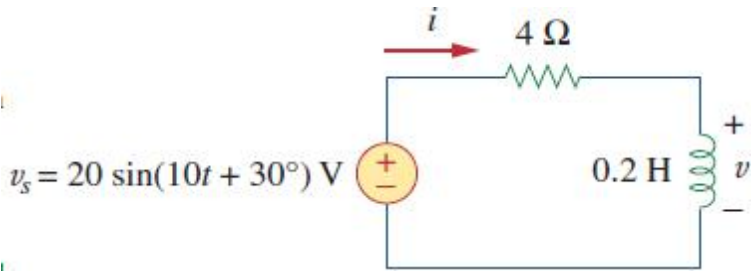Q4.	A series RLC circuit has $R = 100\Omega$, $L = 240\text{ H}$ and $C = 10\text{mF}$. If the input voltage is $v(t) = 10\cos 2t$, find the current flowing through the circuit.	Marks 06 CLO 03
Q5.	<p>Find $v(t)$ and $i(t)$ in the circuit shown in figure 3.</p>  <p style="text-align: center;">Figure 3</p>	Marks 06 CLO 03

(1) (2)

Q1 :- The switch in Fig. 2 has been in position A for a long time. At $t = 0$ the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 2s$ and $8s$.

Ans :-

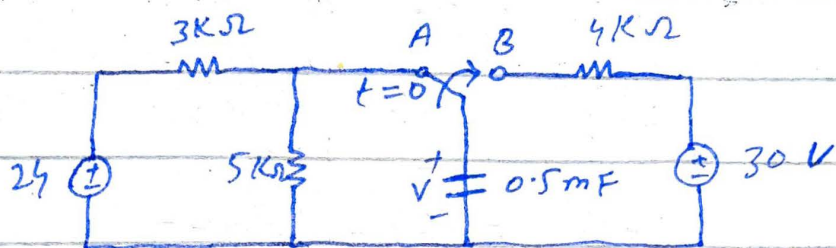

Sol \rightarrow

$$v(0) = \frac{5}{5+3} (24) = 15V$$

using the fact the capacitor voltage cannot change instantaneously

$$v(0) = v(0^-) = v(0^+) = 15V$$

For $t > 0$ the switch is in position B. The Thevenin resistance connected to the capacitor is $R_{Th} = 4k\Omega$ and time constant is

$$\tau = R_{Th} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2s$$

Since the capacitor acts like an open circuit to DC at steady state

$$v(\infty) = 30V \quad \text{Thus}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$= 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-t/2})$$

At $t = 2s$ $-0.5(2)$

$$v(2) = 30 - 15e$$

$$v(2) = 30 - 15e^{-2}$$

$$v(2) = 30 - 15(0.3678)$$

$$v(2) = 30 - 5.517$$

$$\boxed{v(2) = 24.483}$$

At $t = 8s$

$$v(8) = 30 - 15e^{-0.5(8)}$$


$$v(8) = 30 - 15e^{-4}$$

$$v(8) = 30 - 15(0.0183)$$

$$v(8) = 30 - 0.2745$$

$$\boxed{v(8) = 29.7255}$$

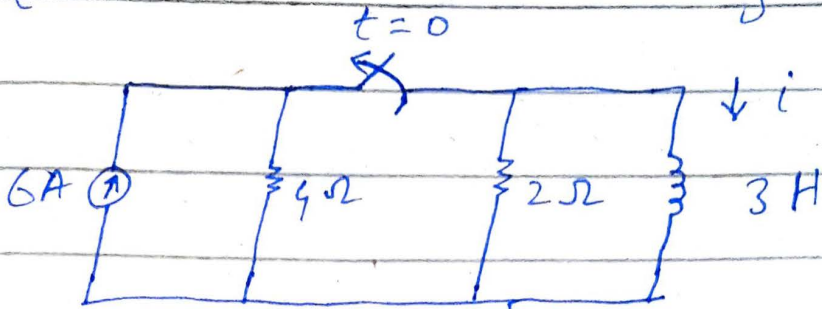Q2:- Determine the inductor current for both $t > 0$ and $t < 0$ for the circuit in fig. 2



Sol

For $t < 0$

The switch is closed and inductor acts as short circuit therefore inductor current is

$$i = 6A$$

For $t > 0$

The switch is open and time constant $\tau = L/R$

$$\tau = \frac{3}{2}$$

Now the inductor current

$$i(t) = 6e^{-t/\tau}$$

$$i(t) = 6e^{-t/3/2}$$

$$i(t) = 6e^{-2t/3} \text{ A}$$

(4)

Q3 :- A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 20$$

Find response when

$$L = 0.5 \text{ H}, R = 4 \Omega \quad \& \quad C = 0.2 \text{ F}$$

$$\text{Let } i(0) = 2, \quad \frac{di(0)}{dt} = 0$$

Sol

Given data

$$L = 0.5 \text{ H}$$

$$R = 4 \Omega$$

$$C = 0.2 \text{ F}$$

$$i(0) = 2 \text{ A}$$

$$\frac{di(0)}{dt} = 0$$

voltage of the given RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 20$$

Divided by L

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{20}{L}$$

(5)

For R.H.S of the equation
multiply by $\frac{C}{L}$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{I_0 C}{LC}$$

$C = 0.2 F$, thus

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{2}{LC}$$

substitute,

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10 i = 20 \dots (1)$$

general equation of a RLC circuit
is given by

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_0}{LC} \dots (2)$$

compare (1) & (2)

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \rightarrow (4)$$

$$\frac{I_0}{LC} = 20 \rightarrow (5)$$

From eq 3 α is given by

(6)

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/s} \rightarrow (6)$$

$$\omega_0 = \sqrt{\frac{2}{LC}}$$

From eq (4)

$$\omega_0 = \sqrt{20} \text{ rad/s} \rightarrow 7$$

\therefore The circuit is over damped

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 + \sqrt{4^2 - \sqrt{20}^2}$$

$$= -4 + \sqrt{6} \text{ rad/s}$$

And

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 - \sqrt{4^2 - \sqrt{20}^2}$$

$$= -4 - \sqrt{6} \text{ rad/s}$$

From eq 5 the steady state current is given by

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2 = 2A \rightarrow 8$$

(7)

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \text{---} 29$$

 $t = 0,$

$$i(0) = 1s + A_1 + A_2$$

$$2 = 2 + A_1 + A_2$$

Thus

$$A_1 + A_2 = -2 \quad \longrightarrow \quad 20$$

From eq (9) find $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

 $t = 0,$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

→ substitute the value

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0 \quad \longrightarrow (21)$$

solve (20) & (21) simultaneously

$$A_1 = -1.326$$

$$A_2 = 0.326$$


substitute in 9

$$i(t) = 2 - 1.326 e^{(-4 + \sqrt{6})t} + 0.326 e^{(-4 - \sqrt{6})t} \quad A$$

$$i(t) = 2 - 1.326 e^{(-4 + \sqrt{6})t} + 0.326 e^{(-4 - \sqrt{6})t} \quad A$$

Q4:- A series RLC circuit has $R = 100 \Omega$, $L = 240 \text{ mH}$ & $C = 20 \text{ mF}$. If the input voltage is $v(t) = 20 \cos 2t$, find the current flowing through the circuit.

circuit diagram :-

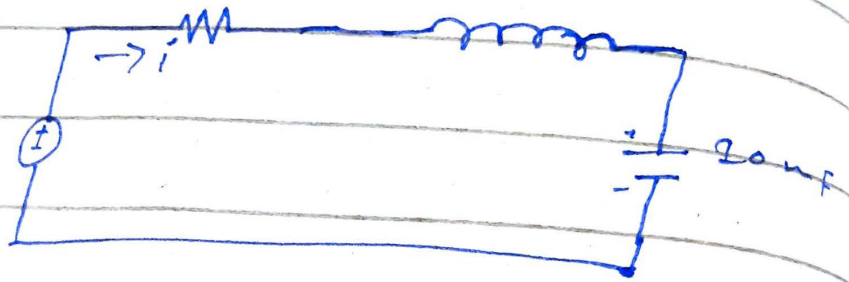

Input voltage is ~~$v(t) = 20 \cos 2t$~~ $v(t) = 20 \cos 2t \text{ v}$

Here

Amplitude = $v_m = 20 \text{ v}$

Angular frequency, $\omega = 2 \text{ rad/s}$

Phase angle, $\phi = 0^\circ$

So phase for the voltage $v(t)$

$v(t) = 20 \angle 0^\circ \text{ v}$

(10) (9)
Now for inductive reactance

$$X_L = \omega L$$

$$\text{So } \omega = 2 \text{ rad/s}, L = 240 \text{ H}$$

$$X_L = (2)(240) \\ = 480 \Omega$$

Now for capacitive reactance

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2 \text{ rad/s}, C = 10 \text{ mF}$$

$$\frac{1}{2(10 \times 10^{-3})}$$

$$\frac{1}{2 \times 10^2}$$

$$\frac{1 \times 10^2}{2}$$

$$\frac{100}{2}$$

$$X_C = 50 \Omega$$

Now for Impedance

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, X_L = 480 \Omega, X_C = 50 \Omega$$

$$Z = (100 + 480 - 50) \Omega$$

$$(900 + j430) \Omega$$

Represent Z in phase form

$$Z = (100 + j430) \Omega$$

$$= \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left(\frac{430}{100} \right)$$

$$\sqrt{20000 + 184900} \angle \tan^{-1} (4.3)$$

$$= 441.47 \angle 76.90^\circ \Omega$$

for current flowing

$$i = \frac{v(t)}{Z}$$

(21) (1)

$$v(t) = \frac{20 \angle 0^\circ \text{ V}}{441.47 \angle 76.9^\circ \Omega}$$

$$\frac{20}{441.47} \angle [0 - 76.9] \text{ A}$$


$$= 22.6 \times 10^{-3} \angle -76.9^\circ \text{ A}$$

general expression for (i)

$$i = 22.6 \cos(2t - 76.9^\circ) \text{ mA}$$

~~~~~ \* ~~~~~ \* ~~~~~ \*

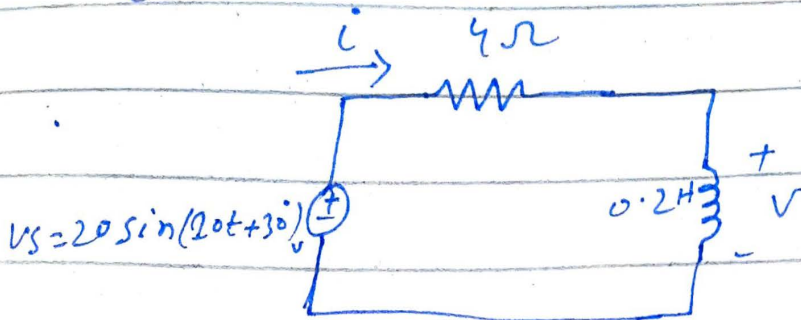Q8:- ~~Find~~ Find  $v(t)$  and  $i(t)$  in the circuit shown in figure 3



Sol

From the voltage source

$$(v_s) = 20 \sin(20t + 30^\circ) \text{ V}$$

$$v_s = 20 \cos(20t + 30^\circ - 90^\circ) \text{ V}$$

$$v_s = 20 \cos(20t - 60^\circ) \text{ V}$$

$$v_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 20 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 20 \times 0.2$$

$$0.2 \text{ H} = j2 \Omega$$

Given circuit can be represented as

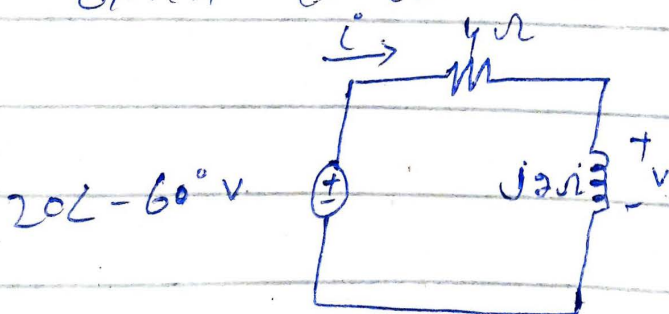

From the circuit diagram

$$Z = 4 + j2 \Omega$$

Hence, the current is,

$$I = \frac{20 \angle -60^\circ}{4 + j2}$$

$$I = \frac{20 \angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$

$$I = \frac{20 \angle -60^\circ}{4.472 \angle 26.57^\circ}$$

$$I = 4.472 \angle -86.57^\circ$$

convert into time domain

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

from the circuit voltage across the inductor is,

$$V = j\omega \times i$$

$$V = j\omega \times (4.472 \angle -86.57^\circ)$$

convert polar form to rectangular form we get

$$V = j\omega \times (0.267 \angle 56^\circ - j4.464)$$

$$V = 8.928 + j0.53512$$

from rectangular to polar form

$$\Rightarrow V = \left( \sqrt{(8.928)^2 + (0.53512)^2} \right) \angle \tan^{-1} \left( \frac{0.53512}{8.928} \right)$$

Now into time domain



$$v(t) = 8.944 \cos(20t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(20t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(20t + 93.4^\circ) \quad v$$

Thank you