

Course Details

Course Title :- ENA

Instructor Name :- Sir Shahrayer

Student Details.

Name :- Naveed Alam


Modul :- 4th Semester.

Student ID :- 14965

Q1 For the circuit in Fig 1

$$i_f \quad v = 10e^{-4t} \quad \& \quad 0.2e^{-4t} \quad t > 0$$

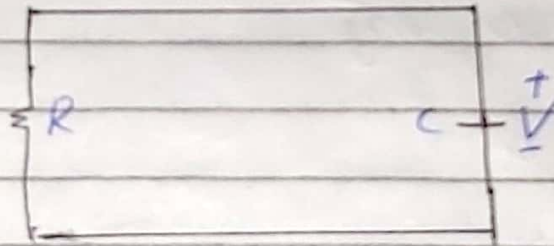(a) Find R & C (b) ... (c) ... (d) ...
50% of the initial energy.



STEP 1

$$(A) \quad T = RC = \frac{1}{4}$$

$$\Rightarrow -1 = C \frac{dv}{dt}$$

$$\Rightarrow -0.2e^{-4t} = C(10)(-4)e^{-4t}$$

$$\Rightarrow C = 5 \text{ mF}$$

$$R = \frac{1}{4C} = 50 \Omega$$

STEP 2

$$(b) \quad T = RC = \frac{1}{4} = 0.250$$

STEP 3

$$(C) \quad W_c (0) = \frac{1}{2} C V^2$$

$$\Rightarrow \frac{1}{2} (5 \times 10^{-3}) (100)$$

$$\Rightarrow 250 \text{ mJ}$$

STEP 4

$$(D) \quad W_p = \frac{1}{2} \times \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{1}{2} C V_0^2 (1 - e^{-2t_0}) = \frac{1}{2}$$

OR


$$e^{8t_0} = 2$$

$$\textcircled{E} T_0 = \frac{1}{8} (n C_2)$$

$$\Rightarrow 86.6 \text{ mJ}$$

Q2 A 120-v dc generator energize a motor whose coil

circuit breaker

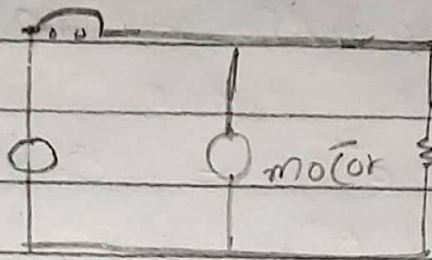

Qee the inductor current for $t < 0$

$$i(0) = \frac{120}{100} = \frac{12}{10}$$

$$\Rightarrow \frac{6}{5} = 1.2 \text{ A}$$

For $t > 0$ we have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100 + 400}$$

$$\Rightarrow \frac{50}{500} \Rightarrow \frac{5}{50}$$

$$\Rightarrow \frac{L}{10} = 0.1$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 1.2 e^{-10t}$$

AC $t = 100 \text{ ms} = 0.1 \text{ s}$

$$i(0.1) = 1.2 e^{-1} = 0.441 \text{ A}$$

Which is the same as the current through the resistor

(B) $\tau = 10 \text{ ms} = 60 \mu\text{s}$

An integrator

$$\tau_c = 0.1 \text{ s} = 6 \mu\text{s}$$

$$\tau_{\text{max}} = 6 \mu\text{s}$$

$$\Rightarrow \omega = 15$$

$$\Rightarrow \frac{R}{\omega L} = 15 \rightarrow (d)$$

$$200 = \omega^2 L \Rightarrow L = 200 \rightarrow (d)$$

STEP 3

$$i(t) = C \frac{dv(t)}{dt} = C [200e^{-20t} - 300e^{-30t}]$$

$$(A_1 e^{s_1 t} + A_2 e^{s_2 t}) \times 10^{-3} \text{ A} = C [200e^{-20t} - 300e^{-30t}]$$

OR

$$[s_1 = s_1', \quad s_2 = s_2']$$

$$\Rightarrow 200C A_1' = 40 \times 10^{-3}$$

$$\Rightarrow C = 200 \times 10^{-6} \text{ F} \Rightarrow C = 200 \mu\text{F}$$

Using Eqn (c) & (d)

$$L = \frac{1}{200 \text{ R}} \text{ F} = \frac{1}{200 \times 200 \times 10^{-6}} \Rightarrow L = 25 \text{ H}$$

$$\text{R} = 50 \Omega = 30 \times 25 = 750 \Omega$$

Q3 The Response of RLC Series RLC Circuit Determine The value of R, L, C

Series RLC circuit
 $V_2(t) = 30 - 10e^{-20t} + 30e^{-10t}$ V

$$V(t) = V_2 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha 700]$$

$$40 e^{-20t} - 60 e^{-30t} \text{ mA}$$

$$\Rightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha 700]$$

Comparing these equ. we get

$$V_s = 30$$

$$A_1 = -10, \quad A_2 = 30$$

$$s_1 = -20, \quad s_2 = -10 \rightarrow (a)$$

$$A_1 = 40, \quad A_2 = -60,$$

$$s_1 = -20, \quad s_2 = -10 \rightarrow (b)$$

STEP 2

Now Eqn (a) & (b)

$$s_1 = -\alpha + \sqrt{\alpha^2 + \omega^2} \quad \text{And } s_2 = -\alpha - \sqrt{\alpha^2 + \omega^2}$$

$$s_1 + s_2 = -2\alpha \quad \& \quad s_1 s_2 = \omega^2$$

$$\left[\text{where } \alpha = \frac{R}{2L} ; \omega = \frac{1}{\sqrt{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$V_2 = V_1 + (2)(2V_0) = V_1 + 4V_0$$

$$V_2 = \frac{-24}{11 + j4} \cdot (2 - j4 + 4) = (-24) \frac{(6 - j4)}{11 + j4}$$

$$S = V_2 I = V_2 (2V_0)$$


$$S = \frac{(-24)(6 - j4)}{11 + j4} = \frac{-48}{11 + j4} = \frac{(11\sqrt{2})(6 - j4)}{137}$$

$$S = (50.45 - j33.64) \text{ VA}$$

$$V(0) = 20 \text{ V or } A = -20$$


$$V(t) = 20 \left(1 - e^{-\frac{34}{25}t} \right) \text{ V}$$

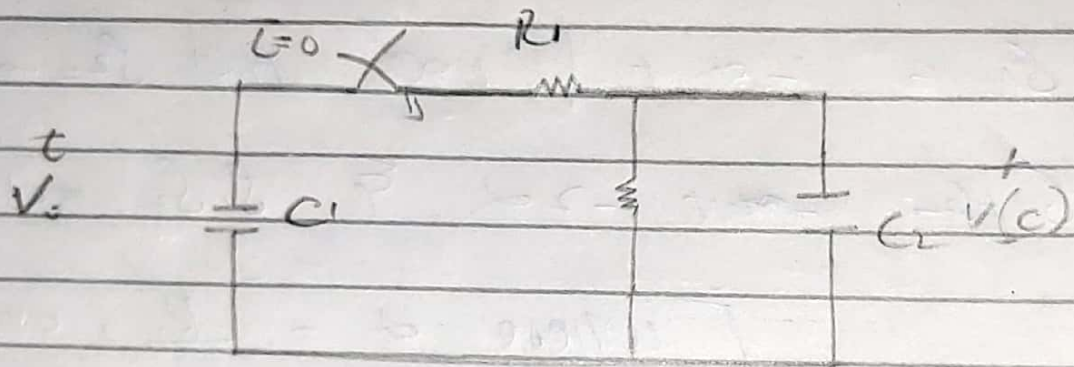Q4 The circuit in fig. 3 is the electrical analog of body junction



For $t = 0 \rightarrow V(c) = 0$

For $t > 0$ the circuit is shown below

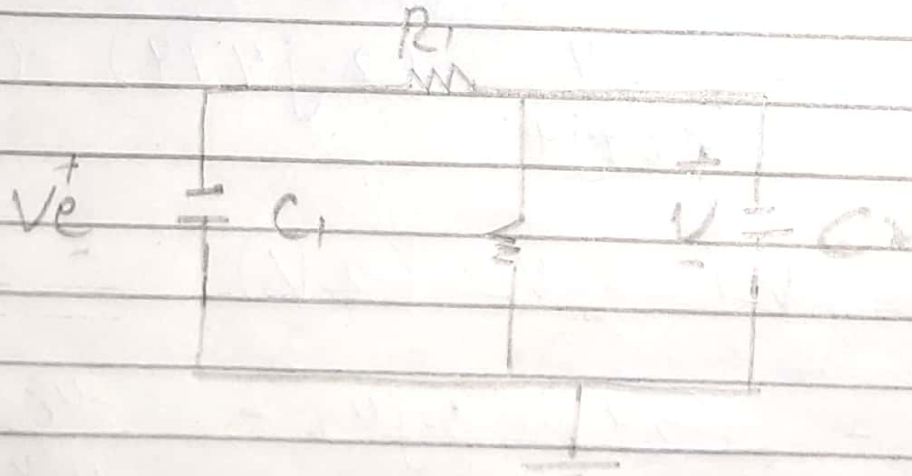

$$V_0 - V_R = (V/R_2) + C_2 \frac{dv}{dt}$$

$$V_0 = V(1 + R_1/R_2) + R_1 C_2 \frac{dv}{dt}$$

$$60 = (1 + 5/2.5) + (5 \times 10^6 \times 5 \times 10^{-6}) \frac{dv}{dt}$$

$$60 = 3V + 25 \frac{dv}{dt}$$

$$V(t) = V_3 + [A e^{-3t/25}]$$


where

$$3V_3 = 60 \text{ yields } V_3 = 20$$

$$V(0) = 0 = 20 + A = -20$$

$$V(t) = 20(1 - e^{-3t/25}) \text{ V.}$$

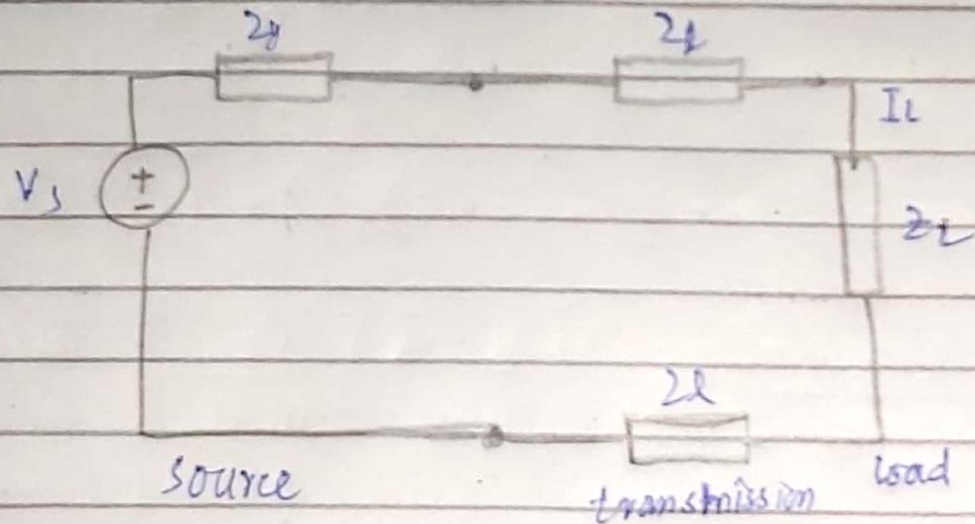Q5r A power transmission system is modeled as shown... Find the load current -



$$Z = z_a + 2z + z_c$$


$$Z = (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$Z = 25 + j20$$

$$I_L = \frac{V_s}{Z} = \frac{125 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = 3.592 \angle -38.66^\circ \text{ A}$$

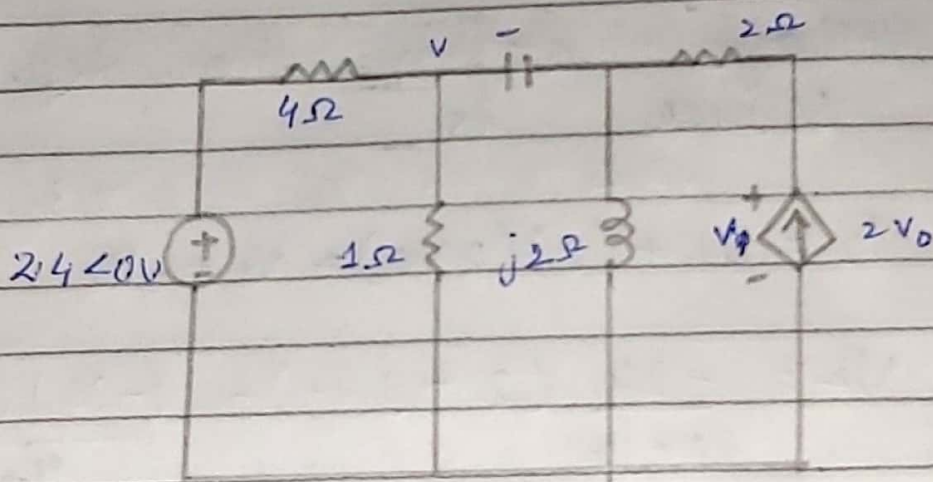Q6 :- For the current in Fig. 5 - Find the ave.....?



Consider the circuit as shown

→ At node ②

$$\frac{24 - V_0}{4} = \frac{V_0}{1} + \frac{V_0 - V_1}{-j}$$

$$24 = (5 + j4)V_0 - j4V_1 \rightarrow (1)$$

→ At node 1

$$\frac{V_0 - V_1}{-j} + 2V_0 = \frac{V_1}{j2}$$

$$V_1 = (2 - j4)V_0 \rightarrow (2)$$

substituting (2) into (1)

$$24 = (5 + j4 - j8 - 16)V_0$$

$$V_0 = \frac{-24}{11+j4} ; V_1 = \frac{(-24)(2-j4)}{11+j4}$$

Voltage across the dependent source is

$$V_2 = V_1 + (2)(2V_0) = V_1 + 4V_0$$

$$V_2 = \frac{-24}{11+j4} (2-j4) = \frac{(-24)(6-j4)}{11+j4}$$

$$S = \frac{1}{2} V_2 I = \frac{1}{2} V_2 (2V_0)$$

$$S = \frac{(-24)(6-j4)}{11+j4} \cdot \frac{-24}{11-j4}$$

$$S = \left(\frac{576}{137} \right) (6-j4)$$

$$S = 25.23 - j16.82 \text{ VA}$$

Q 7:- A balanced Y-load to a 60Hz three phase — phase draw 5kW.

(a) Determine the load impedance

(b) Find I_a , I_b & I_c .

→ (a)

$$|V_{ab}| = \sqrt{3}V_p = 240 \rightarrow V_p = \frac{240}{\sqrt{3}} = 138.56$$

$$V = V_p \angle -30^\circ$$

$$P_f = 0.5 = \cos\theta \rightarrow \theta = 60^\circ$$

$$P = S \cos\theta \rightarrow S = \frac{P}{\cos\theta} = \frac{5}{0.5} = 10 \text{ kVA}$$

$$Q = S \sin\theta = 10 \sin 60 = 8.66$$

$$S_p = 5 + j8.66 \text{ kVA}$$

But

$$S_p = \frac{V_p^2}{Z_p} \rightarrow Z_p = \frac{V_p^2}{S_p} = \frac{138.56^2}{(5 + j8.66) \times 10^3}$$

$$Z_p = 0.96 - j1.663$$

$$Z_p = 0.96 + j1.6637 \Omega$$

$$\textcircled{b.} \rightarrow \bar{I}_a = \frac{V}{Z_Y} = \frac{138.56 \angle -30^\circ}{0.96 + j1.6627} = 72.17 \angle -90^\circ \text{ A}$$

$$\bar{I}_b = \bar{I}_a \angle -120 = ~~72.17~~ 72.17 \angle -210^\circ \text{ A}$$

$$\bar{I}_c = \bar{I}_a \angle +120 = 72.17 \angle 30^\circ \text{ A}.$$