

Department of Electrical Engineering
Assignment

COURSE Title: Electrical Network Analysis

Name: Hazrat Bibal


ID: 14622

Q1:- For the circuit in Fig (1)

if $v = 10e^{-4t}$ & $i = 0.2e^{-4t}$ $t > 0$

a) Find R & C, b) ... , c) ... , d) ... ,

50% of the initial energy.

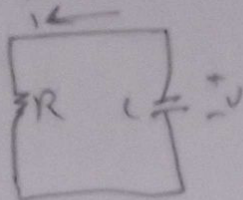

step 1

a)

$$\tau = RC = \frac{1}{4}$$

$$\Rightarrow -1 = C \frac{dv}{dt}$$

$$\Rightarrow -0.2e^{-4t} = C(10)(-4)e^{-4t}$$

$$C = 5 \mu F$$

$$R = \frac{1}{4C} = 50 \Omega$$

step 2:

$$b) \tau = RC = \frac{1}{4} = 0.250$$

step 3:

$$c) W(0) = \frac{1}{2} C v^2$$

$$\Rightarrow \frac{1}{2} (5 \times 10^{-6}) (100)$$

$$\Rightarrow 250 \mu J$$

step u

d)

$$w_R = \frac{1}{2} \times \frac{1}{2} C U_0^2$$

$$\Rightarrow \frac{1}{2} C U_0^2 (1 - e^{-2t_0})$$

$$0.5 = 1 - e^{-2t} \Rightarrow e^{-2t} = \frac{1}{2}$$

OR


$$e^{2t_0} = 2$$

$$t_0 = \frac{1}{2} \ln(2)$$

$$\Rightarrow 86.6 \text{ ms}$$

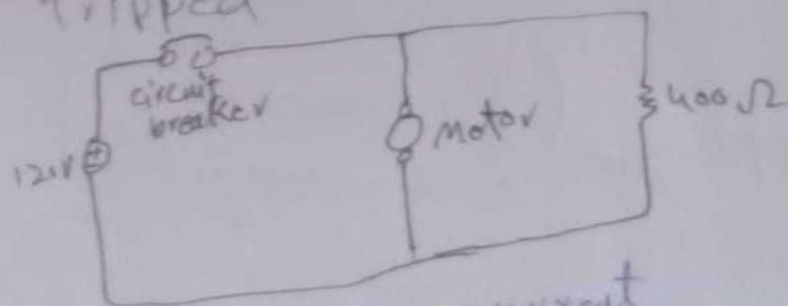Q3:-

A 12-V DC generator energize a motor whose coil the breaker is tripped



Let the inductor current

$$\text{For } t < 0 \quad i(0) = \frac{12 \text{ V}}{100} = \frac{12}{10}$$

$$\Rightarrow 0.15 = 1.2 \text{ A}$$

For $t > 0$ we have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100 \times 400} \Rightarrow \frac{50}{50000} = 0.1$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

$$i(t) = 1.2e^{-10t}$$

$$\text{At } t = 100 \text{ ms} = 0.1 \text{ s}$$

$$i(0.1) = 1.2e^{-1} = 0.441 \text{ A}$$

Q3: The response of RLC series RLC circuit the value of determine the value of R, L, C

Series RLC circuit

$$v(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$v(t) = v_0 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [s_1 \neq s_2]$$

Comparing these eq. ... we get

$$v_0 = 30$$

$$A_1 = -10 ; \quad A_2 = 30 ;$$

$$s_1 = -20 ; \quad s_2 = -10 \quad \text{--- (a)}$$

$$A_1 = 40 ; \quad A_2 = -60$$

$$s_1' = -20 ; \quad s_2' = -10 \quad \text{--- (b)}$$

Step 2 Here eq a & b

$$s_1 = -\alpha + \sqrt{\alpha^2 + \omega_0^2} \quad \text{And} \quad s_2 = -\alpha - \sqrt{\alpha^2 + \omega_0^2}$$

$$s_1 + s_2 = -2\alpha \quad \& \quad s_1 s_2 = \alpha^2$$

$$\left[\text{where } \alpha = \frac{R}{2L}; \quad \alpha_0 = \sqrt{\frac{1}{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$\Rightarrow \alpha = 15$$

$$\Rightarrow \frac{R}{2L} = 15 \quad \text{--- (d)}$$

$$200 = \alpha^2, \Rightarrow \frac{1}{LC} = 200 \quad \text{--- (d')}$$

Step 3

$$i(t) = \left(\frac{dv(t)}{dt} \right) = \left[200e^{-20t} - 300e^{-30t} \right]$$

$$\left(A_1' e^{s_1 t} + A_2' e^{s_2 t} \right) \times 10^{-3} \text{ A} = \left\{ \left[200e^{-20t} - 300e^{-30t} \right] u \right\}$$

or

$$\left[s_1 = s_1', \quad s_2 = s_2' \right]$$

$$\Rightarrow 200 \times 10^{-3} = A_1' = 40 \times 10^{-3}$$


$$\Rightarrow C = 200 \times 10^{-6} \text{ F} \Rightarrow C = 200 \mu\text{F}$$

using eq 4 c & d

$$L = \frac{1}{200 \times 200 \times 10^6} \Rightarrow L = 25 \text{ nH}$$


$$\& \quad R = 30L = 30 \times 25 \text{ nH} = 750 \text{ nH}$$

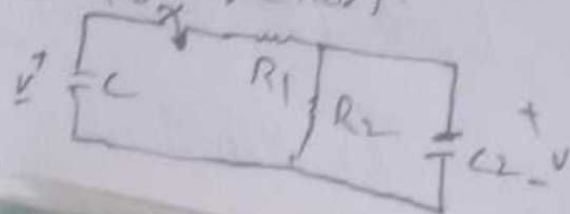Q4:- The circuit in Fig 3 is the electrical analog to body to function.



For $t=0$, $v(0) = 0$

For $t > 0$ the circuit is shown below

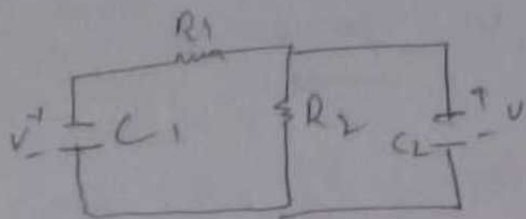

$$v_0 - v/R_1 = (v/R_2) + C_2 \frac{dv}{dt}$$

$$v_0 = v \left(1 + \frac{R_1}{R_2}\right) + R_2 C_2 \frac{dv}{dt}$$

$$60 = \left(1 + \frac{5}{2 \cdot 5}\right) + (5 \times 10^{-6} \times 5 \times 10^6) \frac{dv}{dt}$$

$$60 = 3v + 25 \frac{dv}{dt}$$

$$v(t) = v_s + \left[A e^{-3t/25} \right]$$

where

$$3v_s = 60 \text{ yields } v_s = 20$$

Q5: A power transmission system is modeled as shown. ... Find the load current I_L

$$Z = Z_0 + 2Z + Z_0$$


$$Z = (1 + j0.8 + 25 \cdot 2) + j(0.5 + 0.6 + 13.9)$$

$$Z = 25 + j20$$


$$I = \frac{V_s}{Z}$$

$$\frac{115 \angle 0}{32.02 \angle 38.66^\circ}$$
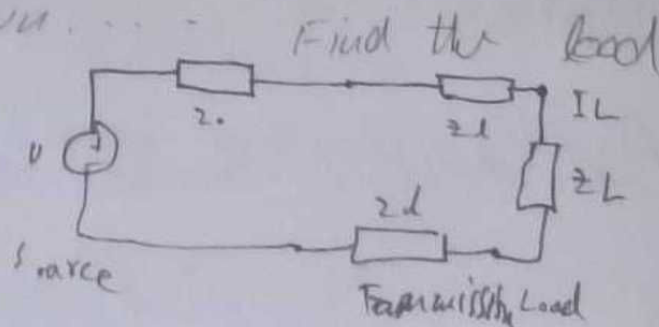
$$I_L = 3.59 \angle -38.66^\circ \text{ A}$$



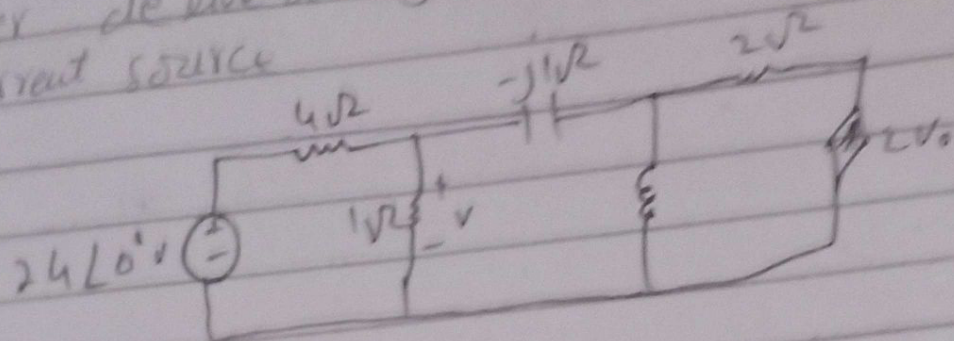- For the circuit in Fig 5
 Find the average, reactive and complex
 power delivered by the dependent
 current source



At node 1,

$$\frac{24 - v_0}{4} = \frac{v_0}{1} + \frac{v_0 - v_1}{-j}$$

$$24 = (5 + j4)v_0 - j4v_1 \quad (1)$$

At node 2,

$$\frac{v_0 - v_1}{-j} + 2v_0 = \frac{v_1}{j2}$$

$$v_1 = (2 - j4)v_0 \quad (2)$$

Substituting 2 into (1)

$$24 = (5 + j4 - j8 - 16)v_0$$

$$v_0 = \frac{-24}{11 + j4} \quad \Rightarrow \quad v_1 = \frac{(-24)(2 - j4)}{11 + j4}$$

The voltage across the dependent source

$$v_2 = v_1 (2) (2v_0) = v_1 + 4v_0$$

$$v_2 = \frac{-24}{11 + j4} - (2 - j4 + 4) = \frac{(-24)(6 - j4)}{11 + j4}$$

$$S = U_3 \bar{I} = U_2 (2 U_0')$$

$$S = \frac{(-24)(6-j4)}{11+j4}$$

$$= \frac{-48 - \left(\frac{118^2}{137}\right)(6-j4)}$$

$$S = (50.45 - j33.64) \text{ VA}$$