

Name — Salman Farooq

ID No — 15 276

Subject — power Transmission

Instructor Name — Eng Amir Aman

Q: A single phase line has two parallel conductors 2 meters apart. The diameter of each conductor is 1.2 cm. Calculate the loop inductance per km of the line.

Sol

Given data:

Spacing of conductor $d = 2 \text{ m} = 200 \text{ cm}$

Radius of conductor, $r = 1.2/2 = 0.6 \text{ cm}$

Loop inductance Per meter length of the

$$\text{Line} = 10^{-7} (1 + 4 \log_e d/r) \text{ H}$$

$$= 10^{-7} (1 + 4 \log_e 200/0.6) \text{ H}$$

$$= 24.23 \times 10^{-7} \text{ H}$$

\Rightarrow Loop inductance per km of the

\Rightarrow Line = $24.23 \times 10^{-7} \times 1000 \text{ H}$

\Rightarrow = $24.23 \times 10^{-7} \text{ H}$

\Rightarrow = 2.423 mH

Question No 2

Sol

Given data:

Spacing of Conductor = $d = 3 \text{ m} = 300 \text{ cm}$

Radius of Conductor, $r = 1 \text{ cm}$

Loop inductance = $10^{-7} (\mu_r + 4 \log_e d/r) \text{ H/m}$

(i) with Copper conductors, $\mu_r = 1$

$$\therefore \text{Loop inductance/m} = 10^{-7} (1 + 4 \log_e d/r) \text{ H}$$

$$\Rightarrow 10^{-7} (1 + 4 \log_e 300/1) \text{ H} = 23.8 = 10^{-7} \text{ H}$$

$$\Rightarrow \text{Loop inductance/Km} = 23.8 \times 10^{-7} \times 1000$$

$$\Rightarrow = 2.38 \times 10^{-3} \text{ H}$$

$$\Rightarrow = 2.38 \text{ mH}$$

(ii) with Steel conductor $\mu_r = 100$

$$\therefore \text{Loop inductance/m} = 10^{-7} (100 + 4 \log_e 300/1) \text{ H}$$

$$\Rightarrow = 122.8 \times 10^{-7} \text{ H}$$

$$\Rightarrow \text{Loop inductance / Km}$$

$$= 122.8 \times 10^{-7} \times 1000 = 12.28 \times 10^{-3} \text{ H}$$

$$\Rightarrow = 12.28 \text{ mH}$$

Ferranti effect :

The effect in which the voltage at the receiving end of the transmission line is more than the sending voltage is known as the Ferranti effect.

Ferranti effect occurs of the transmission line due to the charging current.

Such type of effect mainly occurs because of light load or open circuit at the receiving end.


A long transmission line can be considered to compose a considerably high amount of capacitance and inductance distributed across the entire length of the line.


Ferranti Effect occurs when current drawn by the distributed capacitance of the line itself is greater than the current associated with the load at the receiving end of the line (during light or no load).

This capacitor charging current leads to a voltage drop across the line inductor of the transmission line system which is in phase with the sending end voltage. This voltage drop keeps on increasing additively as we move towards that load end of the

Line and subsequently, the Receiving end voltage leading to the phenomena called Ferranti effect in power system.

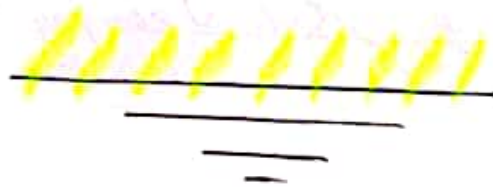Thus both the capacitance and inductor effect of transmission line are equally responsible for this particular phenomena to occur and hence Ferranti effect is negligible in case of general for a 300 km line operating at frequency 50 Hz the no load receiving end voltage has been found to be 5% higher than the sending end voltage.



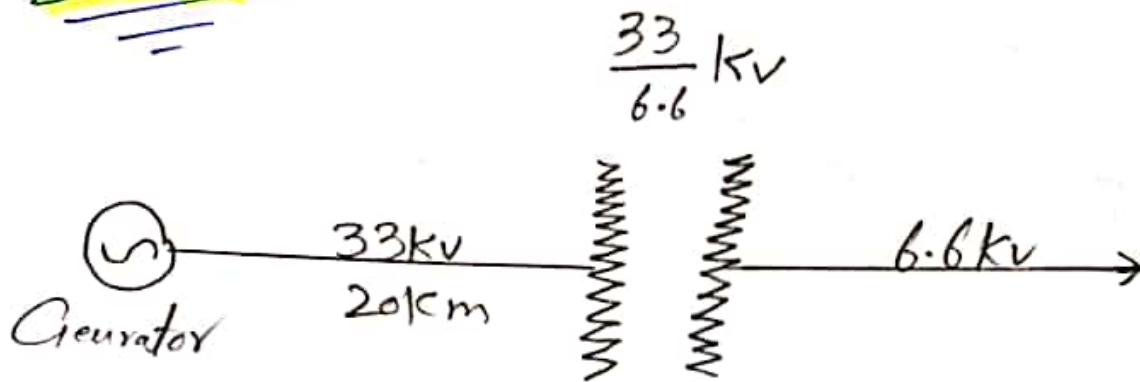Question No 4Sol

The above diagram shows the single transmission system. Here the voltage drop will be due to impedance of transmission line and also due to the impedance of transformer.

$$\Rightarrow \text{Resistance of each conductor} = 20 \times 0.4 = 8 \Omega$$

$$\Rightarrow \text{Reactance of each conductor} = 20 \times 0.5 = 10 \Omega$$

Let us transfer the impedance of transformer secondary to high tension

Side i.e 33 KV side

Equivalent resistance of transformer referred to 33k side

$$= \text{Primary resistance} + 0.35 \left(\frac{33}{6.6} \right)^2$$

$$= 7.5 + 8.75 = 16.25 \Omega$$

= Equivalent reactance of transformer referred to 33KV side

$$= \text{Primary reactance} + 0.65 \left(\frac{33}{6.6} \right)^2$$

$$= 13.2 + 16.25 = 29.45 \Omega$$

Total Resistance of Line and transformer

is $R = 8 + 16.25 = 24.25 \Omega$

Total Reactance of Line and transformer

$$X_L = 10 + 29.45 = 39.45 \Omega$$

Receiving end voltage per phase is

$$= V_R = 33,000 / \sqrt{3} = 19052V$$

$$I = \frac{2000 \times 10^3}{\sqrt{3} \times 33000} = 35A$$

Using the approximate expression for sending end voltage V_S Per Phase.

$$= V_S = V_R + IR \cos \phi_R + IX_L \sin \phi_R$$

$$= 19052 + 35 \times 24.25 \times 0.8 + 35 \times 39.45 \times 0.6$$

$$= 19052 + 679 + 828 = 20559V = 20.559KV$$

Sending end Line voltage

$$= \sqrt{3} \times 20.559KV = 35.6KV$$

Sending end P.f $\cos \phi_S$

$$= \frac{V_R \cos \phi_R + IR}{V_S}$$

$$= \frac{19052 \times 0.8 + 35 \times 24.25}{20559} = 0.7826 \text{ lag}$$

$$\text{Line Losses} = \frac{3I^2R}{1000} \text{ kW} = \frac{3 \times (35)^2 \times 24.25}{1000}$$


$$= 89.12 \text{ kW}$$

$$\text{Output power} = 2000 \text{ KVA} \times 0.8 = 1600 \text{ kW}$$

$$\text{Transmission efficiency} =$$

$$= \frac{1600}{1600 + 89.12} \times 100$$

$$= 94.72 \%$$

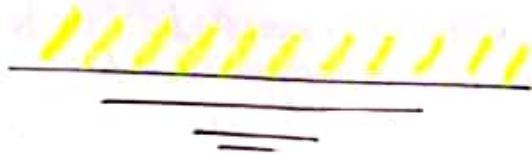

Question No 5

Ans: 5

Q. 5First we find ' γ '

$$\text{So. } \gamma = \frac{1.956}{2} = 0.978 \text{ em}$$

$$\Rightarrow E_0 = \frac{30}{\sqrt{3}} = 21.2 \text{ (r.m.s)}$$

$$\Rightarrow m_0 = 1 \text{ (Smooth Conductor)}$$

$$\Rightarrow \delta = 1 \text{ (standard Pressure and temperature)}$$

$$V_0 = 21.1 \text{ m. } \delta \gamma \ln \frac{d}{r}$$

$$\text{Disruptive voltage / Phase} = \frac{210}{\sqrt{3}} = 121.25 \text{ kV}$$

$$\therefore 121.25 = 21.1 \times 1 \times 1 \times 0.978 \times \ln \frac{d}{r}$$

$$\ln \frac{d}{r} = 5.84 \Rightarrow d = 34 \text{ / em}$$