


Q 1 Rectifier:

It is the electronic device which is used to convert AC into DC is called Rectifier -


① 1- $\phi$  uncontrolled Half wave Rectifier.

A rectifier is a circuit that convert an ac signal into unidirectional signal. Diodes are used commonly is rectifier. A single phase halfwave rectifier is the simplest type is not normally used in industrial applications. However it is useful in understanding the principle of rectifier operation.


Circuit Diagram

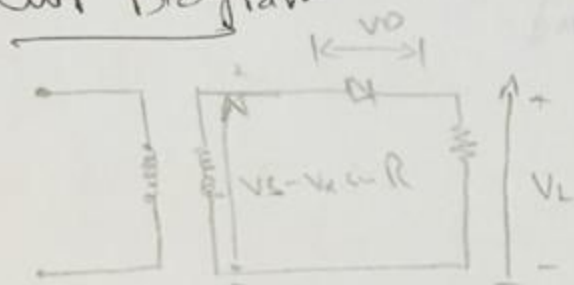


During positive half cycle the input voltage diode  $D_1$  is forward bias and conducts and input voltage appear across the load. During negative half cycle of the input voltage the diode is in blocking condition and output voltage is zero.

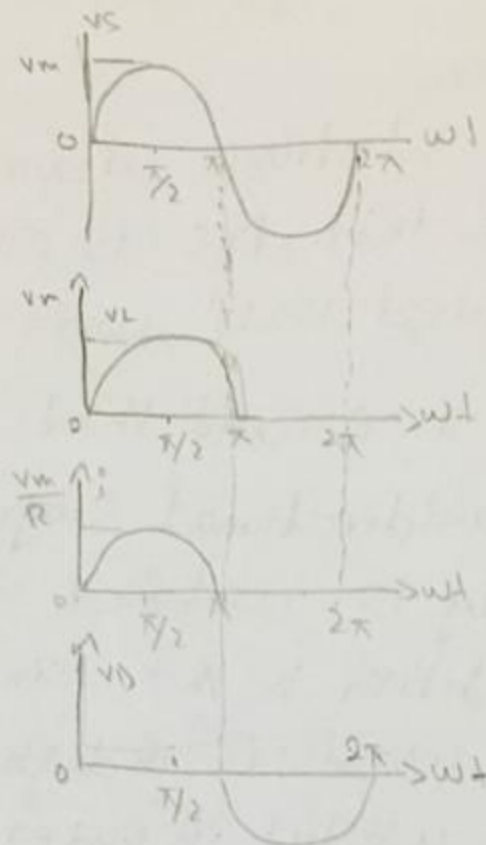wav form

1-  $\Phi$  uncontrolled full wave bridge Rectifier  
we use four diodes in bridge Rectifier circuit.

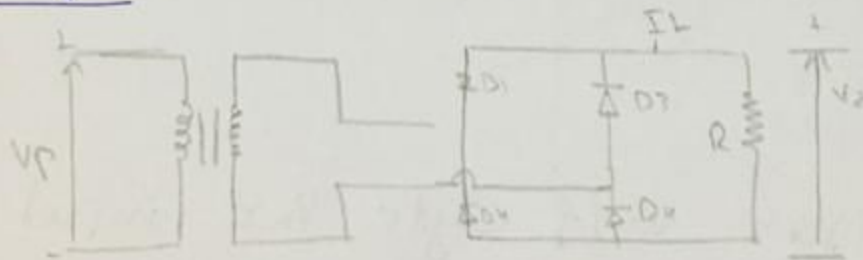Diagram

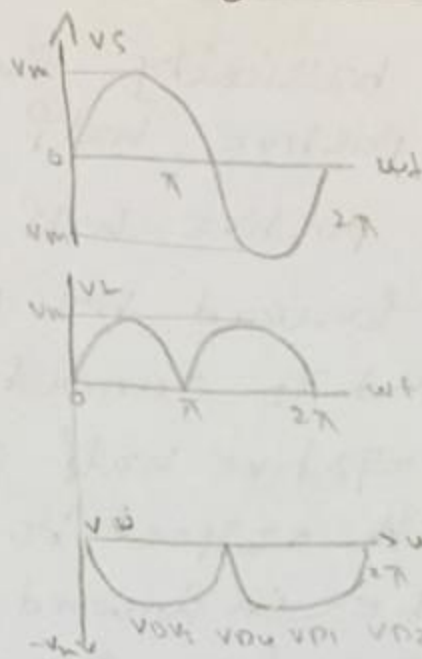During positive half cycle of the input voltage the current flows through the load through diodes  $D_1$  and  $D_2$ . During negative cycle diodes  $D_3$  and  $D_4$  conduct. The peak inverse voltage of a diode is  $V_m$ .




Similarities and differences

Both uses diode

- During positive half cycle both conduct
- During negative half cycle bridge Rectifier conduct & not conducted in half wave Rectifier


2 - 1 - φ controlled bridge rectifier

Circuit diagram

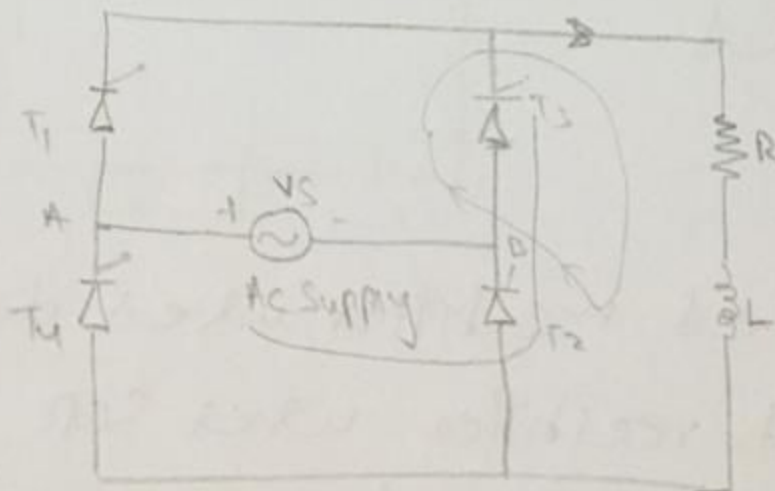

The function is basically subdivided into two parts positive half and negative half cycle. During positive half cycle  $T_1$  and  $T_2$  will become forward bias. If we give gate pulse  $T_1$  and  $T_2$  currents will flow in the loop. During negative half cycle  $T_3$  and  $T_4$  will be in forward bias. If we give gate pulse to  $T_3$  and  $T_4$  current will flow in another loop.

Graph

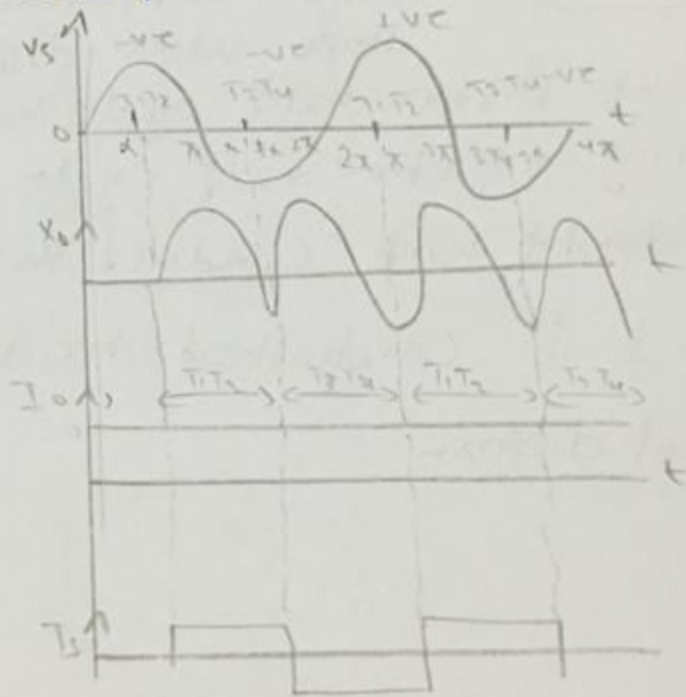

Similarities and differences

- Uncontrolled rectifier uses diodes
- Controlled rectifier uses SCR
- In controlled Rectifier we control the output by using the gate pulse. when we give gate pulse than it triggers otherwise it not.

Q = 02  
Solution



$$V_m = 40V$$

$$R_L = 11\Omega$$

$$I_m = V_m / R_L = \frac{40}{11} = I_m \approx 3.64A$$

Q)  $I_{dc} = ?$

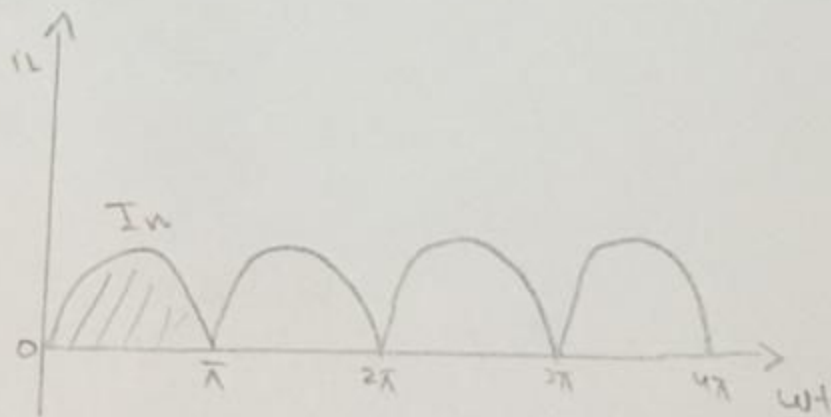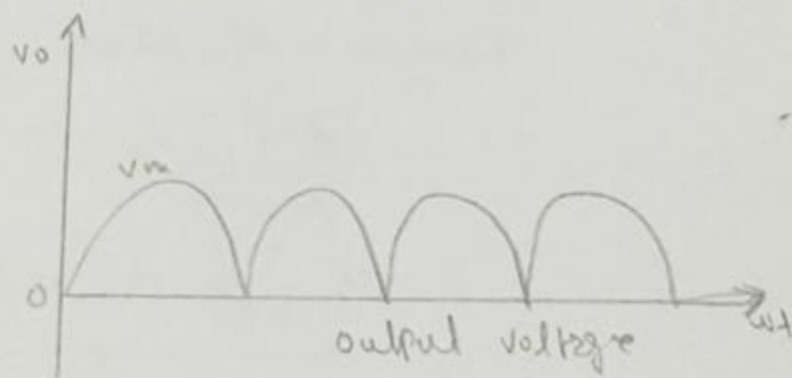First we will find  $I_{dc}$  in full wave rectification



$I_{dc} = \frac{\text{area under the load current over full cycle}}{\text{period of the cycle}}$

A722 Ali 11440

(6)

$$I_{dc} = \int_0^{\pi} \frac{I_m \sin \omega t}{\pi} d(\omega t)$$

$$I_{dc} = \frac{I_m}{\pi} \int_0^{\pi} \sin \omega t d(\omega t)$$

$$I_{dc} = \frac{I_m}{\pi} [-\cos \omega t]_0^{\pi}$$

$$I_{dc} = \frac{I_m}{\pi} [-\cos \pi - (-\cos 0)]$$

$$I_{dc} = \frac{I_m}{\pi} [1 + 1]$$

$$I_{dc} = \frac{2I_m}{\pi}$$

Now put the values



$$I_{dc} = \frac{2(3.5)}{3.14}$$

$$I_{dc} = 0.79 \text{ A}$$

$$V_{dc} = \frac{V_m}{3\pi}$$

$$V_{dc} = \frac{2.40}{3.14}$$

$$V_{dc} = 0.77 \text{ V}$$

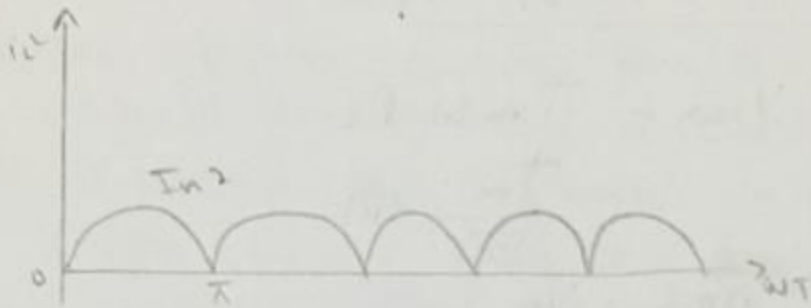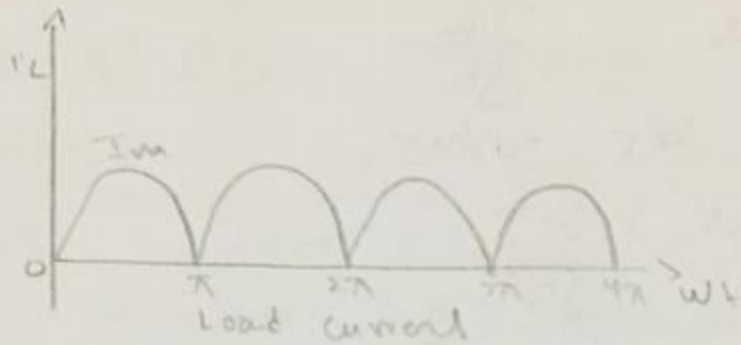③  $I_{rms}$  ?

$I_{rms} = \frac{\text{area of the square of load current over full cycle}}{\text{Period of square wave form}}$

$$I_{rms} = \sqrt{\int_0^{2\pi} \frac{I_m^2}{2\pi} \sin^2 \omega t \, d(\omega t)}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} (1 - \cos 2\omega t) \, d(\omega t)}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \left[ \pi - \frac{\sin 2\pi}{2} - 0 + \frac{\sin 2(0)}{2} \right]^{1/2}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

Put the value

$$I_{rms} = \frac{2.5}{\sqrt{2}}$$

$$I_{rms} = 1.76A$$

$$\text{Ans } V_{rms} = I_{rms} \times R_L$$

$$= \frac{I_m}{\sqrt{2}} \times R_L$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Put the value

$$V_{rms} = \frac{40}{\sqrt{2}}$$

$$V_{rms} = 28.28V$$

Ans  $V_{dc}$ ?

$$V_{dc} = \frac{I_{dc} \times R_L}{\frac{2I_m \times R_L}{\pi}}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

Put the value

$$V_{dc} = \frac{2(40)}{3.14}$$

$$V_{dc} = 25.48V$$




Q3

Principle of Buck Converter


→ The main working principle of Buck Converter is that the inductor in the input circuit resists sudden variations in input current when switch is ON. The inductor stores energy from the input in the form of magnetic energy and discharges it when switch is closed. The capacitor in the output is assumed large enough that the time constant of RC circuit in the output stage is high. The large time constant compared to switching period ensures that in steady state a constant output voltage  $V_o(t) = V_o$  (constant) exists across load terminals.

Working of Buck Converter.

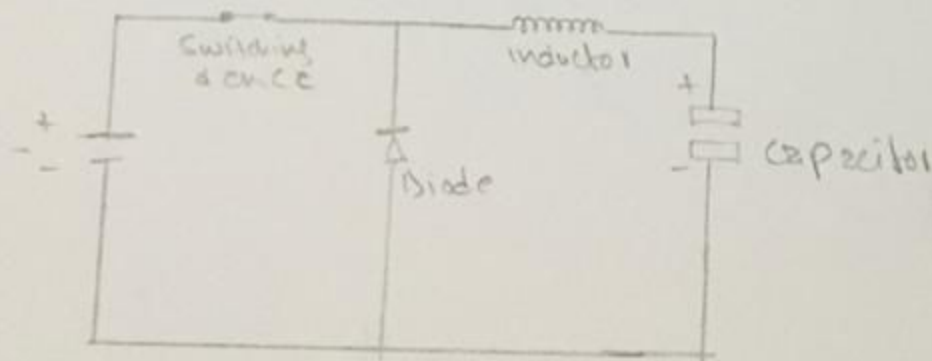The working of a buck converter into a few steps  
 Step 1: The switch on and lets current flow to the output capacitor charging it up since the voltage across the capacitor cannot rise instantly and since the inductor limits the charging current. The voltage across the cap during the switching cycle is not the full voltage of the power source.



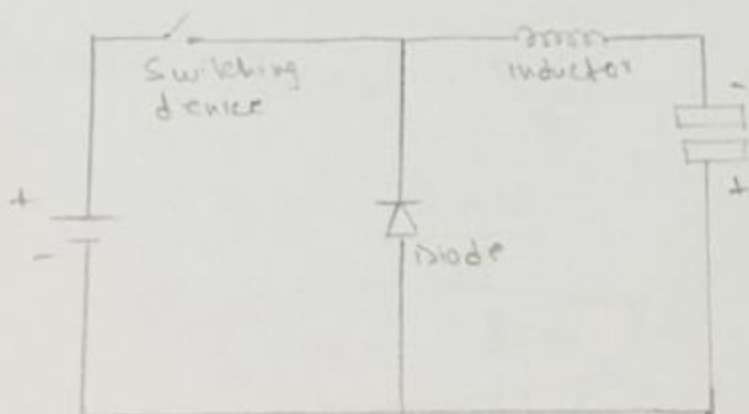Step 2 The switch turns off since the current in an inductor cannot change suddenly. The inductor creates a voltage across it. This voltage is allowed to charge the capacitor and power the load through the diode when the switch is turned off. maintaining current output current throughout the switching cycle.



Q3 = Part 2

Date  $V_{in} = 50V$ duty cycle  $= d = 40\% = 0.40$ 

Last digits of ID (11440)

 $R = 11 \Omega$ 

First digits of ID (11440)

 $f = 20kHz = 20000Hz$ ①  $V_{out} = ?$ 

$$V_o = d(V_i)$$

$$= (0.40)(50)$$

$$V_o = 20V$$

②  $I_{out}$ 

$$I_{out} = \frac{V_o}{R}$$

$$I_o = \frac{20V}{11}$$

$$I_o = 1.81A$$

③  $I_{in} = ?$ 

$$I_{in} = \frac{V_i}{R}$$

$$I_{in} = \frac{50}{11}$$

$$I_{in} = 4.54A$$

④ Inductance (L) = ?

$$L = \frac{T_{OFF}}{2} \times R \quad \text{--- ①}$$

As we know that

$$V_o = dV_i$$


$$d = \frac{V_o}{V_i} = \frac{20}{50} = 0.4$$

Q4


Boost Chopper:

A boost chopper is one of the simplest types of switch mode converter. It takes an input voltage & boost it.

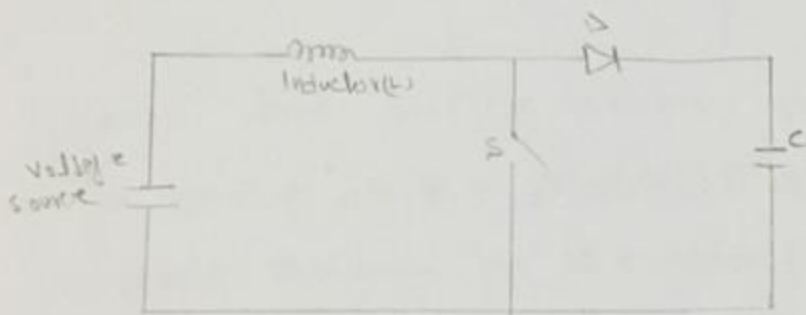
All consist of is an inductor & semi conductor switch, a diode & a capacitor. It is also called as step-up converter.



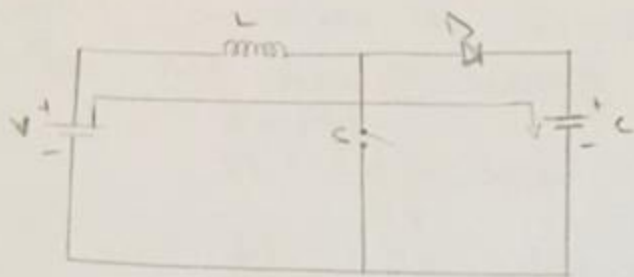Principle The main working principle of boost converter is that the inductor in the input circuit resists sudden variations in input current. When switch is off the inductor stores energy in the form of magnetic energy & discharges it when switch is closed. The capacitor in the output circuit is assumed large enough that the time constant of RC circuit in the output stage is high.



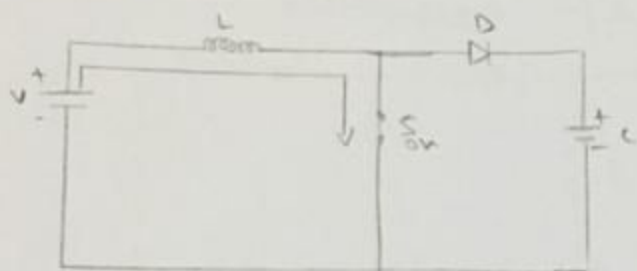The output capacitor is charged to the input voltage minus one diode drop.



When the switch is on our signal source goes high, turning on the MOSFET. All the current is diverted through to the MOSFET through the inductor. The output capacitor stays charged since it can't discharge through the now back-biased diode.

is on for a time  $t_{on}$  & is off for a time  $t_{off}$  we define the time period  $T$ , as  $T = t_{on} + t_{off}$  & the switching frequency

$$f_{\text{switch}} = \frac{1}{T}$$

Now define another term duty cycle

$$D = \frac{t_{on}}{T}$$

Boost converter in steady state operation for this mode using KVL

$$V_{in} = V_L$$


$$V_L = L \frac{di_L}{dt} = V_{in}$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_{in}}{L}$$

Since the switch is closed for a time

$T_{ON} = DT$  we can say that  $\Delta t = DT$
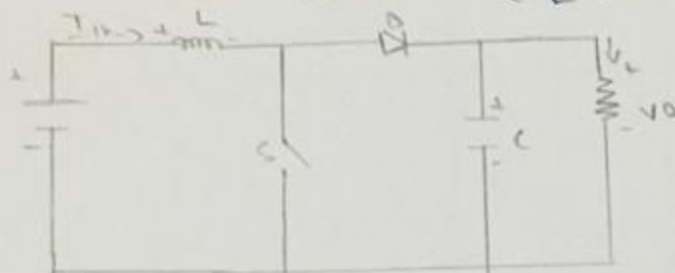
$$(\Delta i_L)_{closed} = \left(\frac{V_{in}}{L}\right) DT$$



In this mode the polarity of the inductor is reversed. The energy stored in the inductor is released & is ultimately dissipated in the load resistance & this helps to maintain the flow of current in the same direction through the load & also step-up the voltage as the inductor is now also acting as a source in conjunction with ~~also acting as a source~~ with the input source.

Analyze the circuit using KVL

Boost converter in steady state operation for mode 2 using KVL

$$V_{in} = V_L + V_o$$

$$V_L = L \frac{di_L}{dt} = V_{in} - V_o$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_{in} - V_o}{L}$$

Since the switch is open for a time  $T_{OFF} =$


$T - T_{ON} = T - DT = (1-D)T$  we can say that

$$\Delta t = (1-D)T$$

Aza & Ali

11440

(15)

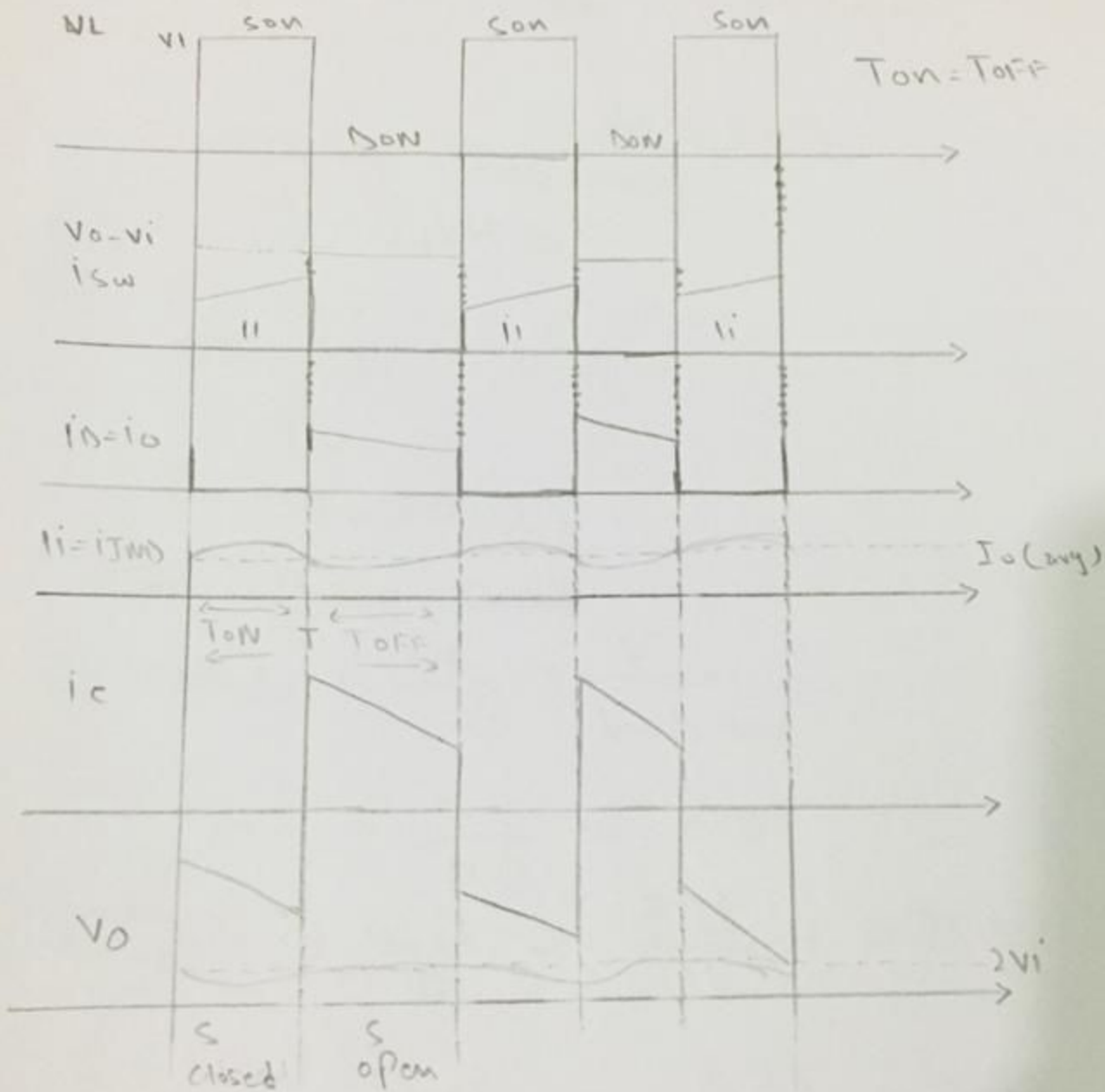

Q4 Part B

$$V_m = 50V$$

$$D = 40$$

$$R = 11\Omega$$

Switching frequency

$$f = 20\text{Hz}$$

find

$$\textcircled{1} V_{out}$$

$$\textcircled{2} I_{out}$$

$$\textcircled{3} I_{in}$$

$$\textcircled{4} \text{Inductor (L)}$$

we know that

$$\textcircled{1} V_{out} = \frac{V_s}{1-D} = \frac{5}{1-0.40}$$

$$= \frac{5}{0.6} = 8.33$$

$$\textcircled{2} I_{out} = \frac{V_{out}}{R} = \frac{8.33}{11} = 0.75A$$

$$\textcircled{3} I_{in} = \frac{I_{out}}{1-D} = \frac{0.75}{1-0.40}$$

$$= \frac{0.75}{0.6}$$


$$= 1.25A$$



## Q5 | Buck-Boost Choppers:

A buck-Boost converter which can operate as a DC-DC step-down upon the duty cycle,  $D$ .


Buck-Boost converter is shown below

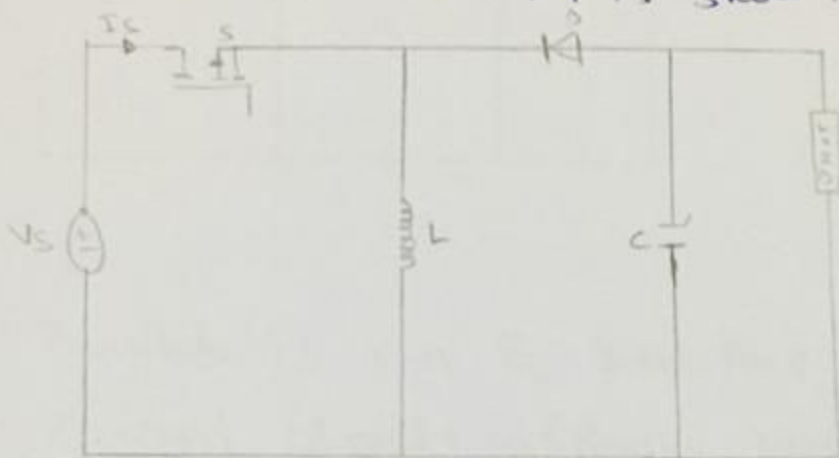

The input voltage source is connected to a solid state device. The second switch is used is a diode. The diode is connected in reverse to the direction of power flow from source to capacitor & the load & the two are connected in parallel as shown in the figure above.


The controlled switch is turned on & off by using pulse width modulation. PWM can be time based or frequency based. Time based is mostly used for DC-DC converters. It is simple to construct & the frequency remains constant in this type of PWM modulation.

Mode 1: Switch is on. Diode OFF

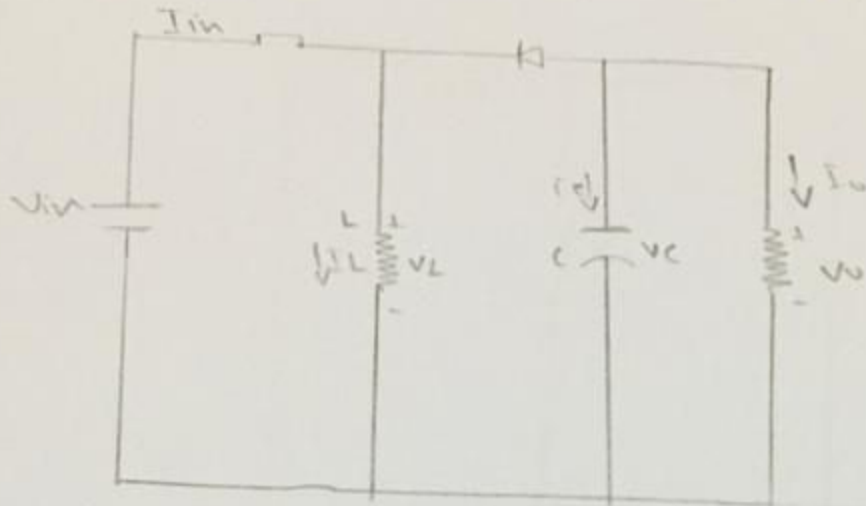

This switch is on & therefore represents a short circuit ideally offering zero resistance to the flow of current so when the switch is on all the current will flow through the switch & the inductor & back to the DC input source. The inductor stores charge during the time the switch is on & when the solid state switch is off the polarity of the inductor reverses so that current flows through the load & through the diode & back to the inductor. So the direction of the current remain same.

MODE II · Switch is off · Diode is ON

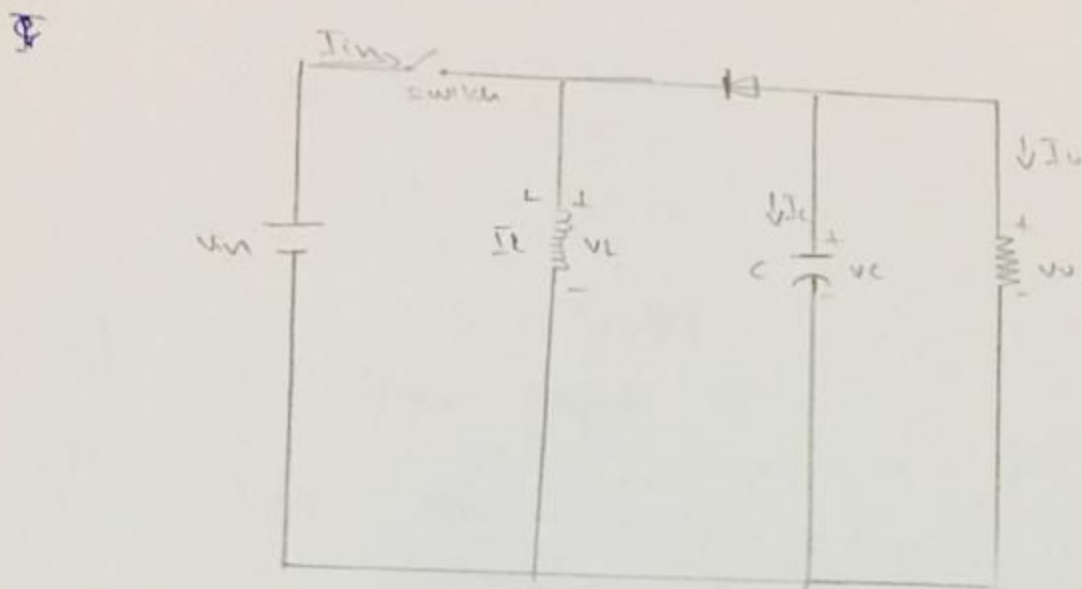

In this mode the polarity of the inductor is reversed & the energy stored in the inductor is released. So the current through the inductor cannot abruptly change the diode must carry the current so it commutates & begins conducting. Energy is transferred from the inductor to the capacitor resulting in a decreasing inductor current & a voltage across the resistor with the opposite polarity compared to  $v_{in}$ .

During steady state the circuit is said to

① In discontinuous conduction mode if the inductor current reaches zero. <sup>operate</sup>

② In continuous conduction mode if the inductor current never reaches zero.

Q 5 Part B

Given Data.  $V_{in} = 50V$ 

$$V_{out} = 40\%$$

$$R = 11$$

$$f = 20Hz$$

Sol we know that

$$① \quad 1 - D = \frac{-V_m}{V_o - V_{in}}$$

$$-D = \frac{-V_{in} - 1}{V_o - V_{in}}$$

$$D = \frac{50V + 1}{0.40 + 5}$$

$$D = 9.44$$

$$② \quad I_{out} = \frac{V_o}{R} = \frac{0.40}{11}$$

$$I_{out} = 0.036 A$$

$$③ \quad I_{in} = \frac{I_o D}{1 - D} = \frac{0.03 \times 9.44}{1 - 9.44}$$

$$I_{in} = 0.896 A$$

$$④ \quad L = \frac{V_{in} D}{f \times \Delta I} = \frac{50 \times 9.44}{20}$$