

Department of Electrical Engineering
Assignment
Date: 20/08/2020

Course Details

Course Title: Electrical Network Analysis
 Instructor: _____

Module: B-tech
 Total Marks: 30

Student Details

Name: Shehriyar khan


Student ID: 13738



Q1	(a)	For the circuit shown below, calculate the voltage V , the conductance G , and the power P . <div style="text-align: center; margin: 10px 0;"> </div>	Marks 05
	(b)	A resistor absorbs an instantaneous power of $20 \cos^2(t) \text{ mW}$ when connected to a voltage source $V = 10 \cos(t) \text{ v}$. Find I and R ?	Marks 05
Q2	(a)	The current in a 4H inductor raises at a rate of 4A/s. Find the voltage across the inductor the energy stored in the magnetic field at after 2sec.	Marks 04
	(b)	A current waveform flowing through an inductor of 1mH is shown in the figure. Obtain and sketch the waveform of voltage across the inductor.	Marks 06
Q3	(a)	A series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of 100uF are connected in series across a 100V, 50Hz supply. Calculate	Marks 07

the total circuit impedance, the circuits current, power factor and draw the voltage phasor diagram.

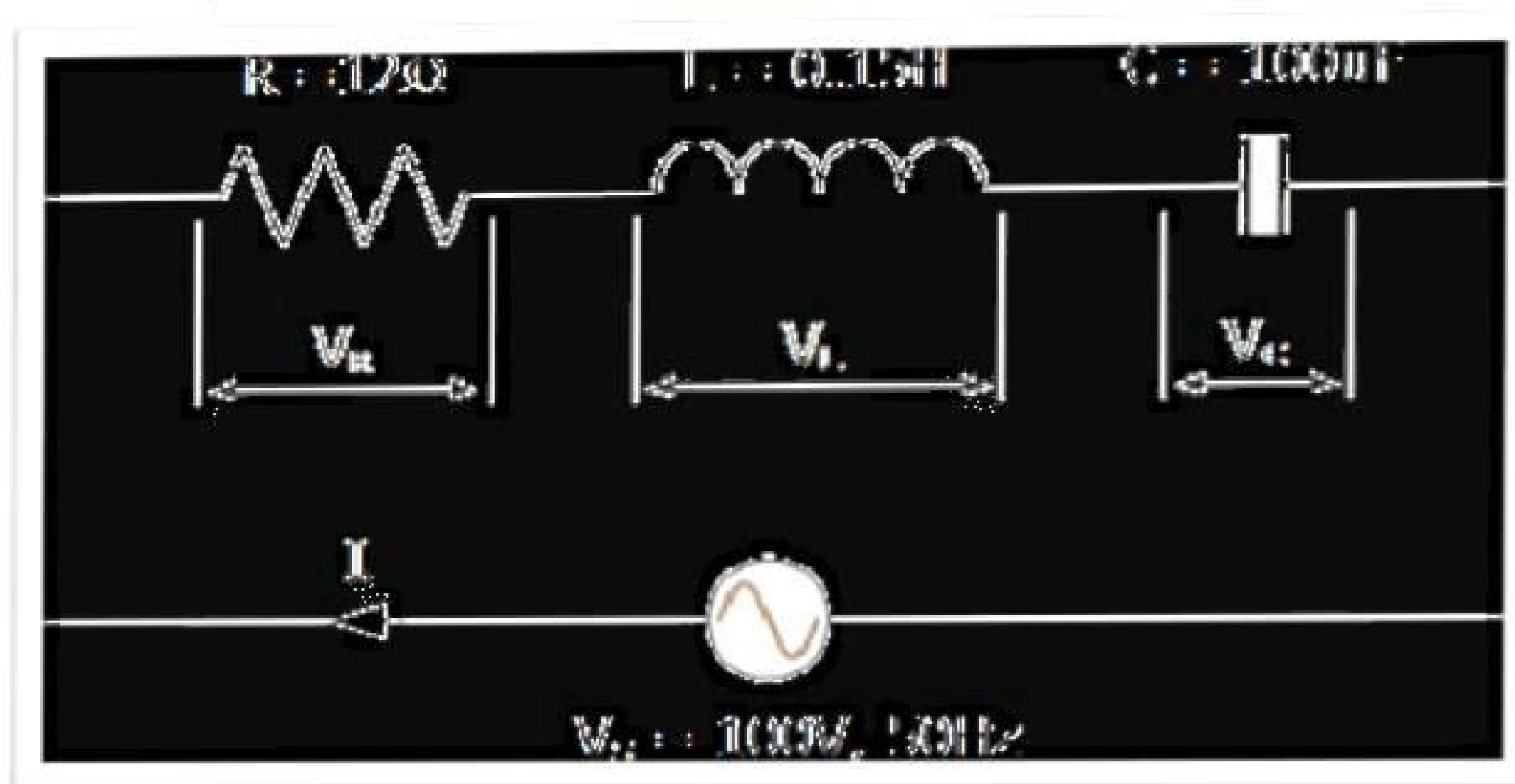$R=12\ \Omega, L=0.15\text{H}, C=100\ \mu\text{F}, V_s=100\text{V}, 50\text{Hz}$



(b) Write a short note on under damped ,over damped and under damped?

Marks 03

☺Good Luck☺

Shehriyar Kham


13738

BE (Electrical)

Qno (1)(a)

Page # 01

Sol:-

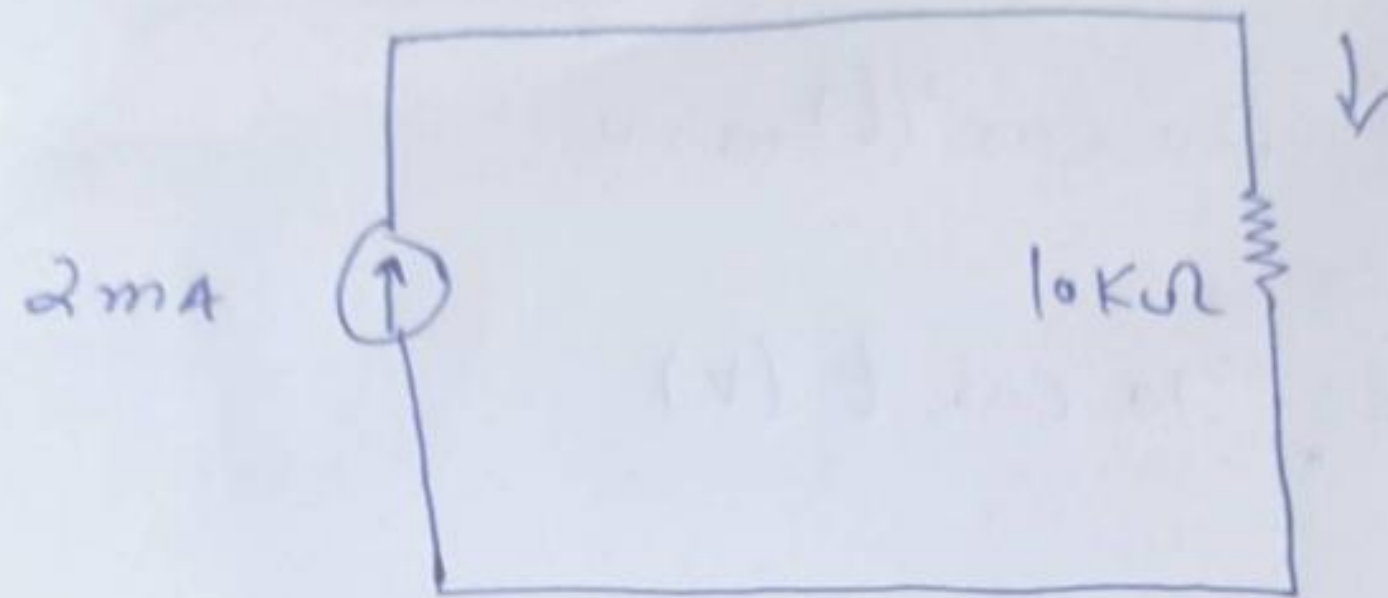

$$I = 2 \times 10^{-3} \text{ A}$$

$$R = 10 \text{ k}\Omega$$

$$V = IR$$

$$V = (2 \times 10^{-3}) (10 \times 10^3 \Omega)$$

$$V = 20 \text{ V}$$

$$V = IR$$

$$R = \frac{V}{I}$$

$$\frac{1}{C} = \frac{V}{I}$$

$$C = \frac{I}{V}$$

$$= \frac{2 \times 10^{-3}}{20}$$

$$C = 0.001$$

$$P = VI = 20 \times 2 \times 10^{-3}$$

$$P = 0.2 \text{ W}$$

Sol:-

$$P = 20 \cos^2(t) \text{ mW}$$

$$V = 10 \cos t \text{ (V)}$$

$$P = Vi$$

$$i = P/V$$

$$i = \frac{20 \cos^2 t \times 10^{-3}}{10 \cos t}$$

$$i = 2 \cos t \times 10^{-3}$$

$$i = 2 \cos t \text{ mA}$$

$$V = IR \Rightarrow R = \frac{V}{I}$$

$$= \frac{10 \cos t \text{ (V)}}{2 \cos t \times 10^{-3}}$$

$$= 5 \times 10^3 \Omega$$

$$R = 5 \text{ k}\Omega$$

Sol:-

$$V = L \frac{di}{dt}$$

$$\Rightarrow 4 \times 4 = 16 \text{ V}$$

$$V = 16 \text{ V}$$

$$W = \frac{1}{2} L i^2 (4)^2$$

$$= \frac{1}{2} \cdot 4 (4)^2$$


$$= 2 \times 16$$

$$W = 32 \text{ J} = 32 \text{ J}$$

Q No 2 (b)

Page # 04

Sol:-

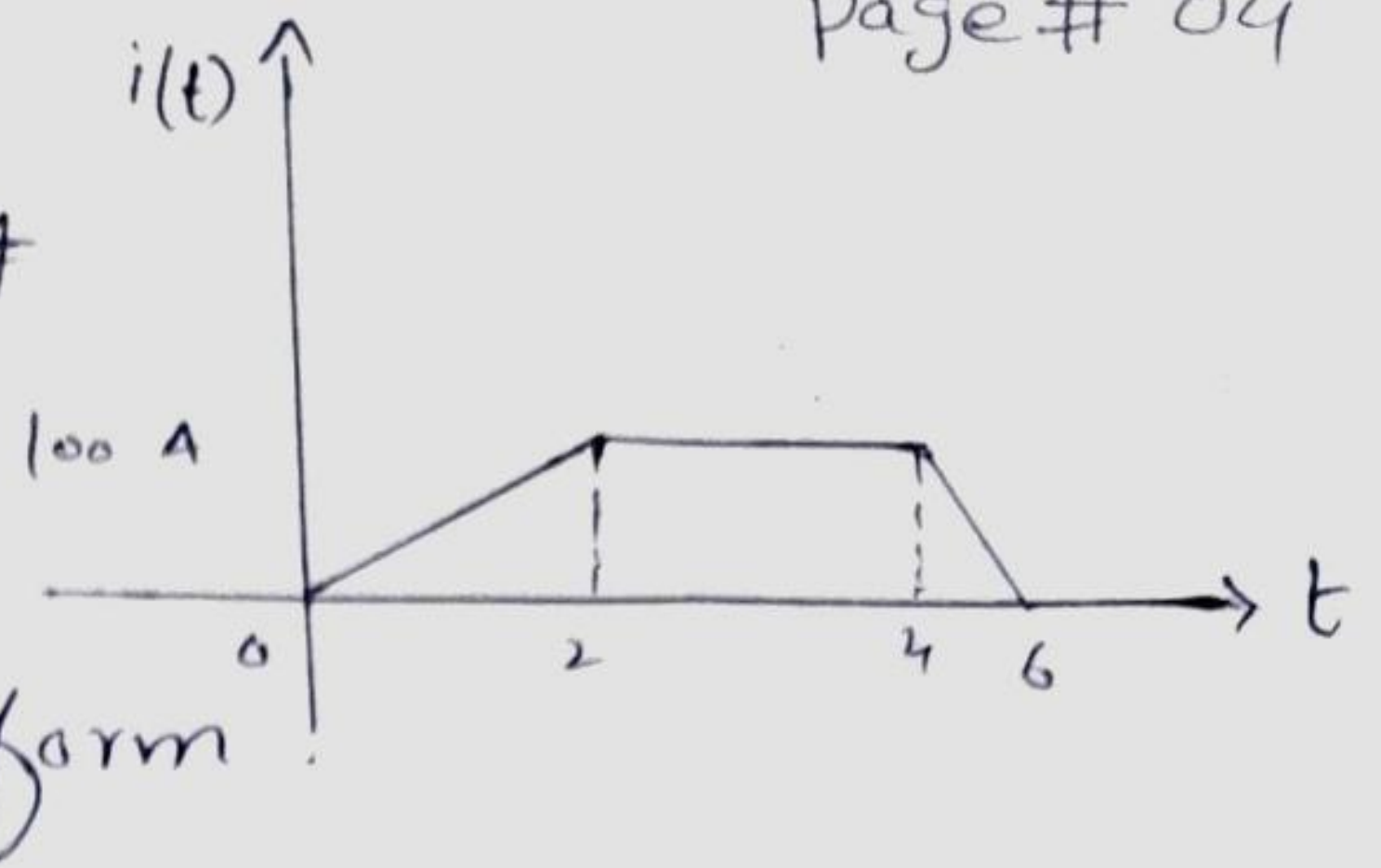

From the given wave form:

for $0 < t < 2$, $i(t)$ is a straight line of slope
 $= (100/2) = 50$

Therefore $i(t) = 50t$ and $\frac{di(t)}{dt} = 50$.

for $2 < t < 4$, $i(t) = 100$ and $\frac{di(t)}{dt} = 0$

for $4 < t < 6$, $i(t)$ is a straight line of slope
 $= -(100/2) = -50$

Therefore, $i(t) = -50t$ and $\frac{di(t)}{dt} = -50$.

Now
$$V_L(t) = L \frac{di(t)}{dt}$$

$$= 1 \times 10^{-3} \times 50 = 0.05 \text{ V} \quad 0 < t < 2$$

$$= 1 \times 10^{-3} \times 0 = 0 \text{ V} \quad 2 < t < 4$$

$$= 1 \times 10^{-3} \times -50 = -0.05 \text{ V} \quad 4 < t < 6$$

$$Q \text{ No } 3(a) \quad L = 0.15 \text{ H} \quad C = 100 \mu\text{F}$$

$$R = 12 \Omega$$

Sol:- Inductive Reactance, X_L

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.15 = 47.13 \Omega$$

Capacitive Reactance,

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83 \Omega$$

Circuit impedance, Z ,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{12^2 + (47.13 - 31.83)^2}$$

$$Z = \sqrt{144 + 234} = 19.4 \Omega$$

Circuit's current I ,

$$I = \frac{V_s}{Z} = \frac{100}{19.4} = 5.14 \text{ amps}$$

Voltage across the Series RLC circuits,
 V_R, V_L, V_C

$$V_R = I \times R = \cancel{5.14} \quad 5.14 \times 12 = 61.7 \text{ volts.}$$

$$V_L = I \times X_L = 5.14 \times 47.13 = 242.2 \text{ volts.}$$


$$V_C = I \times X_C = 5.14 \times 31.8 = 163.5 \text{ volts.}$$

circuits power factor and Phase Angle, θ


$$\cos \phi = \frac{R}{Z} = \frac{12}{19.4} = 0.619$$

$$\cos^{-1} 0.619 = 51.8^\circ \text{ lagging.}$$

Phasor Diagram

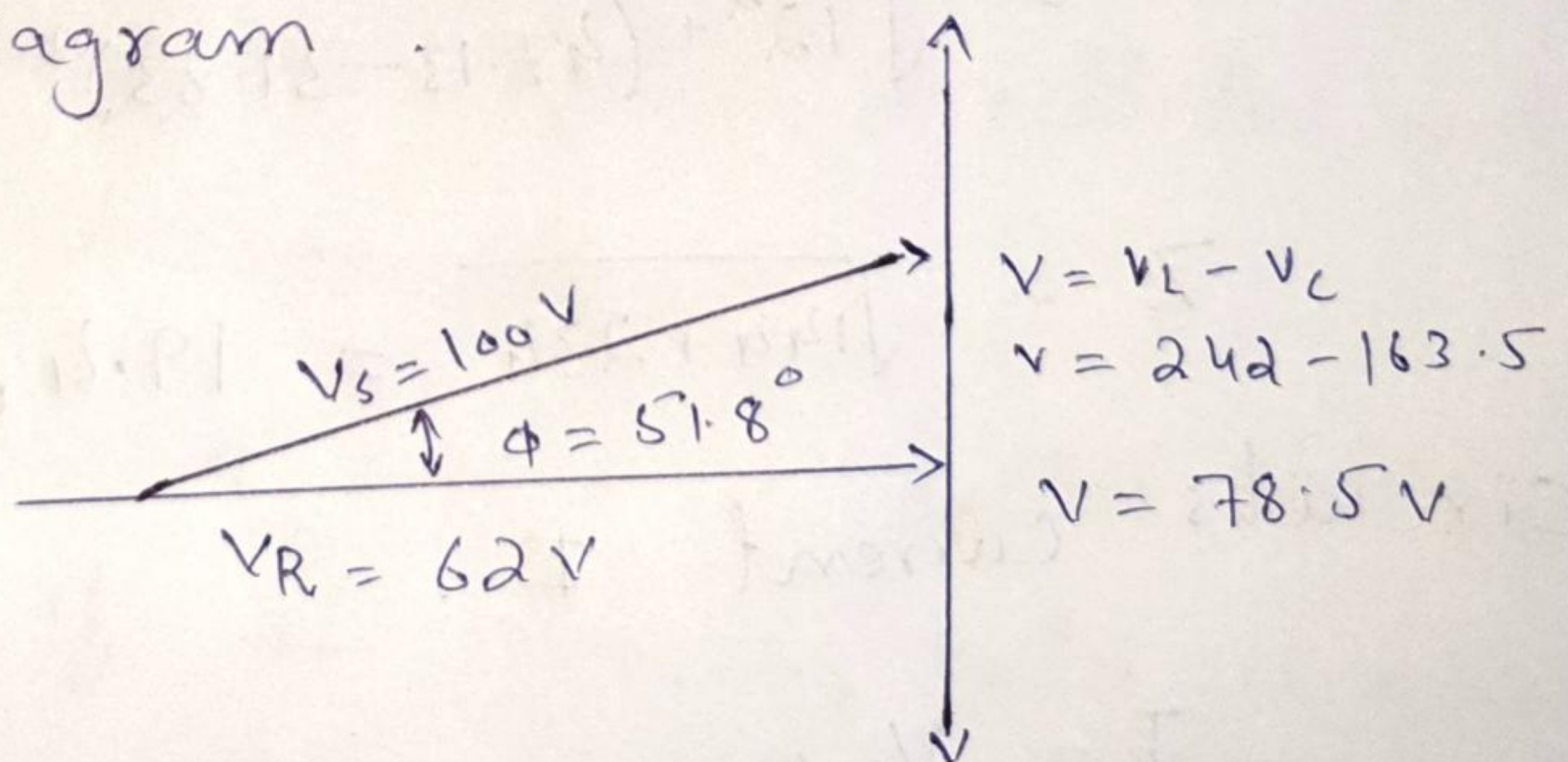

Q No (3) (b)

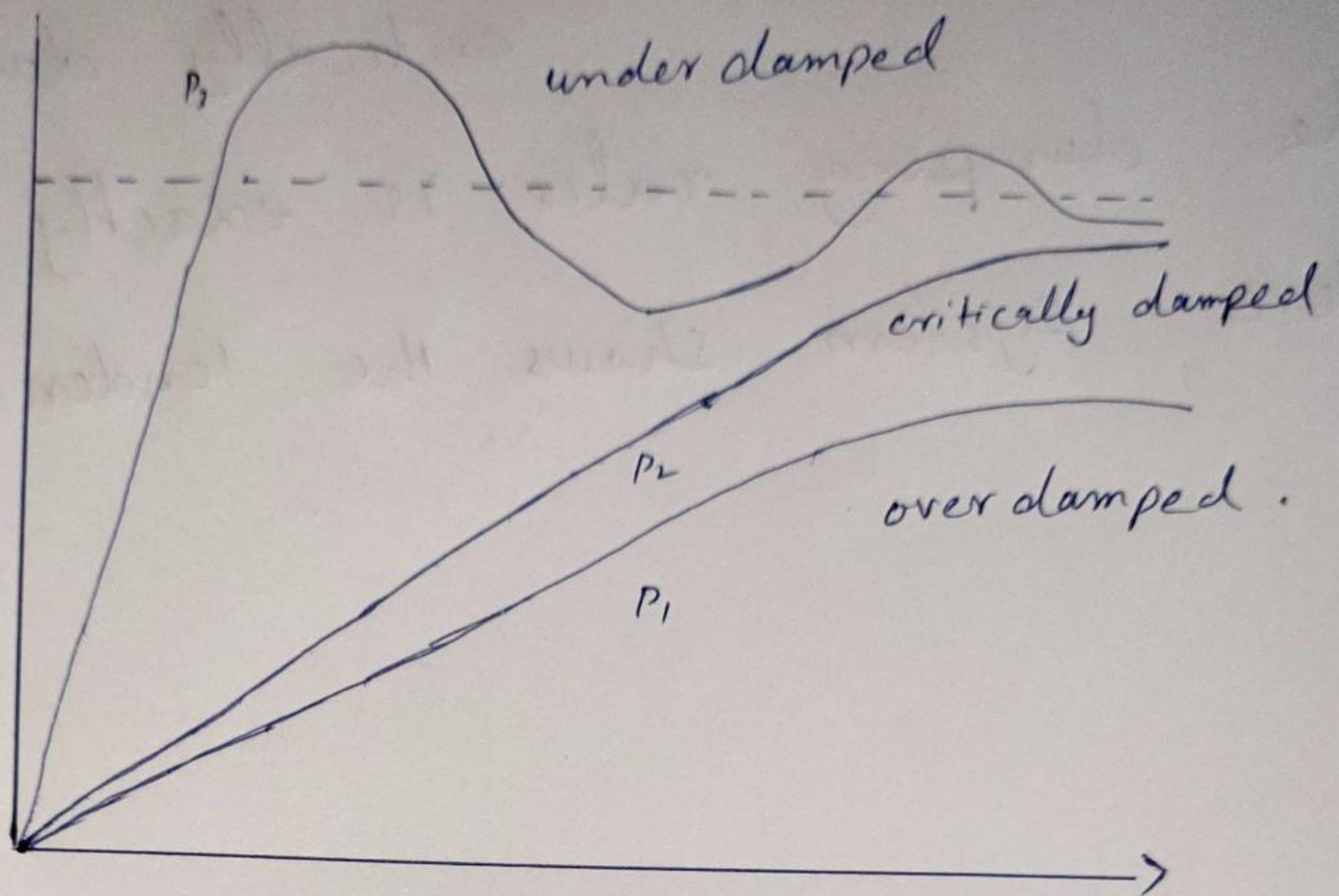

- i) under damped:- A system is called under damped, if the damping ratio is less than 1. Here the system oscillates with a gradual decrements.
- ii) over damped:- A system is called overdamped if the damping ratio is greater than one. Here the system shows tendency to achieve equilibrium without oscillating.

ii) critically damped:- A system is called critically damped if the damping ratio is exactly one. Here system shows the tendencies.

