

Name :#	Ancis	Ghaffar
ID #	15269	
Dep #	Bs cs	
Paper #	Basic	Electronics
Teacher :#	Sir	Khalid Hameed
Semester #.	4 th	



(Q: NO: 1)

(1)

(Q. NO: 1)

Given

(a)

$$I_s = \frac{24V}{470\Omega}$$

$$51.06 \text{ mA}$$

Special Purpose diode

Since the load voltage

is 15

$$I_L = \frac{15V}{1.5 \text{ k}\Omega}$$

$$I_L = 10 \text{ mA}$$

The Zener current is the diff
between two current

$$I_z = 51.06 \text{ mA} - 10 \text{ mA} =$$

$$I_z = 41.06 \text{ mA}$$

← (Q: 1 part b) →

Given data -

$$\text{Load terminal} = 1500\Omega$$

$$\text{input current} = E_1 = 24$$

$$R_{\text{resistor}} = R = 470\Omega$$

Required data

$$\text{load voltage} = V_L = ?$$

As we know that

$$V_L = \frac{R_L E_1}{R + R_L}$$

(2)

Putting values

$$\Rightarrow V_L = \frac{R_L E_i}{R + R_L}$$

$$= V_L = \frac{1500 \times 24}{470 + 1500}$$

$$\Rightarrow V_L = \frac{36000}{1970}$$

$$\Rightarrow V_L = 18.27 \text{ V}$$

$$\text{Result} = V_L = 18.27 \text{ V}$$

(3)

(Q No: 2)

Collector Characteristics Curves.

Consider the circuit of fig (1) which we will use to learn about the operation of the transistor in a circuit by adjusting the voltage source V_{BB} and V_{CC} .


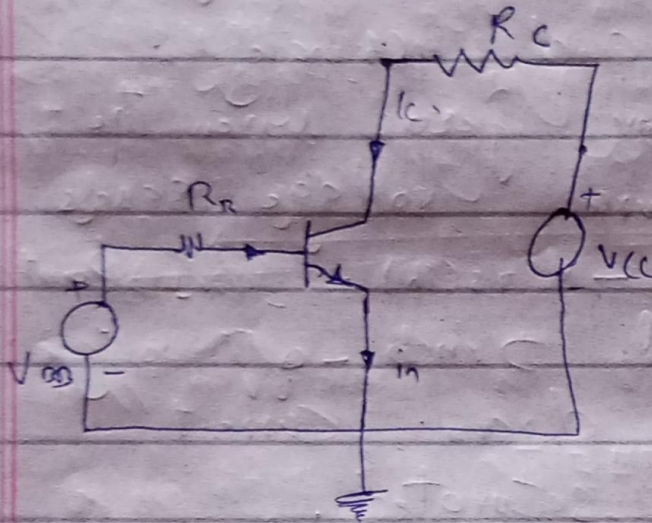


Fig (1)

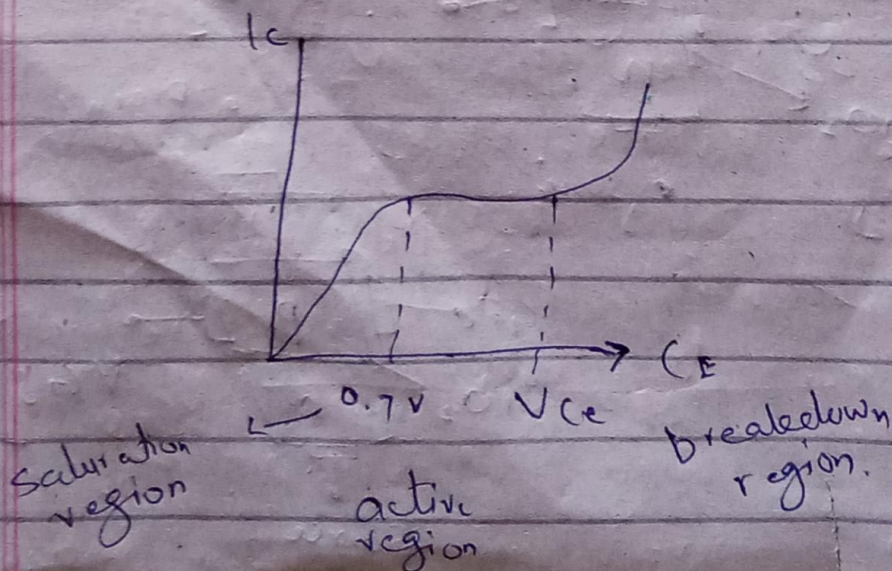A graph of the collector, I_C versus V_{CE} is shown in fig (2)



suppose V_{BB} and V_{CE} are set to produce a current $I_B > 0$ and $V_{CE} = 0V$. Then both BE and BC junction are forward biased. The saturation region corresponds ^{region} to the case where both junction are forward biased.

As V_{CE} increases and reaches about $0.7V$ then BC junction becomes reverse biased.

When V_{CE} exceeds $0.7V$ the transistor goes into the ~~VCE~~ active region or linear region.

Corresponds to the BE junction forward biased and BC reverse biased. This is the normal mode of operation of the transistor.

e.g. as in amplifier. In the active region the collector characteristics is almost flat meaning that I_C is almost constant but V_{CE} can vary.

The value of I_C is determined by I_B .


(4)

if V_{CE} increases too much the transistor goes into the breakdown region. This should be avoided.

Fig C)

Collector Curves for different values of base current. When $I_B = 0$

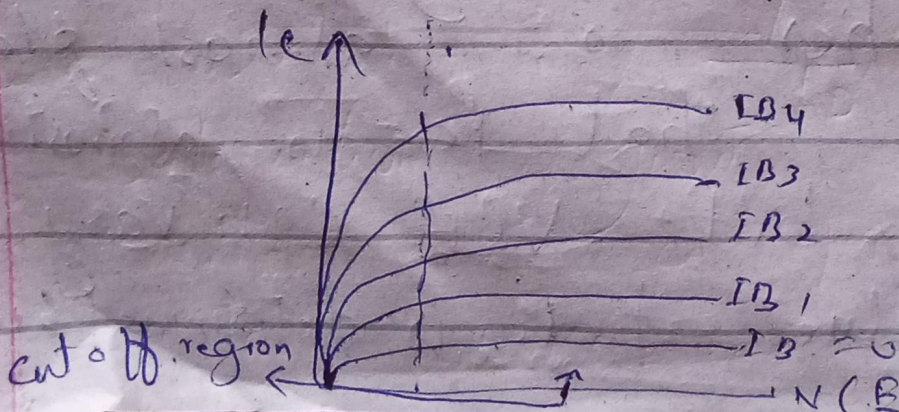A, the transistor is in its cut off region and only a small leakage current flows as I_C .



(5)

When V_{GS} is greater than $V_{GS(th)}$ the curve appears linear and the device begins to conduct and turns 'ON'. Also the drain current is controlled by the gate voltage.

The almost vertical part of the graph is the ohmic region and the almost horizontal parts are the active region.

It is equivalent to a resistor when biased in the active region. It is equivalent to a current source.



In the cutoff region the gate-source voltage is less than the gate threshold voltage and the device is an open circuit or OFF.

In the ohmic region the device acts as a resistor.

equivalent to $\frac{V_{DS}}{I_D}$. In the saturation region the drain current is a function of gate-source voltage.

(6)

Q: No: 3

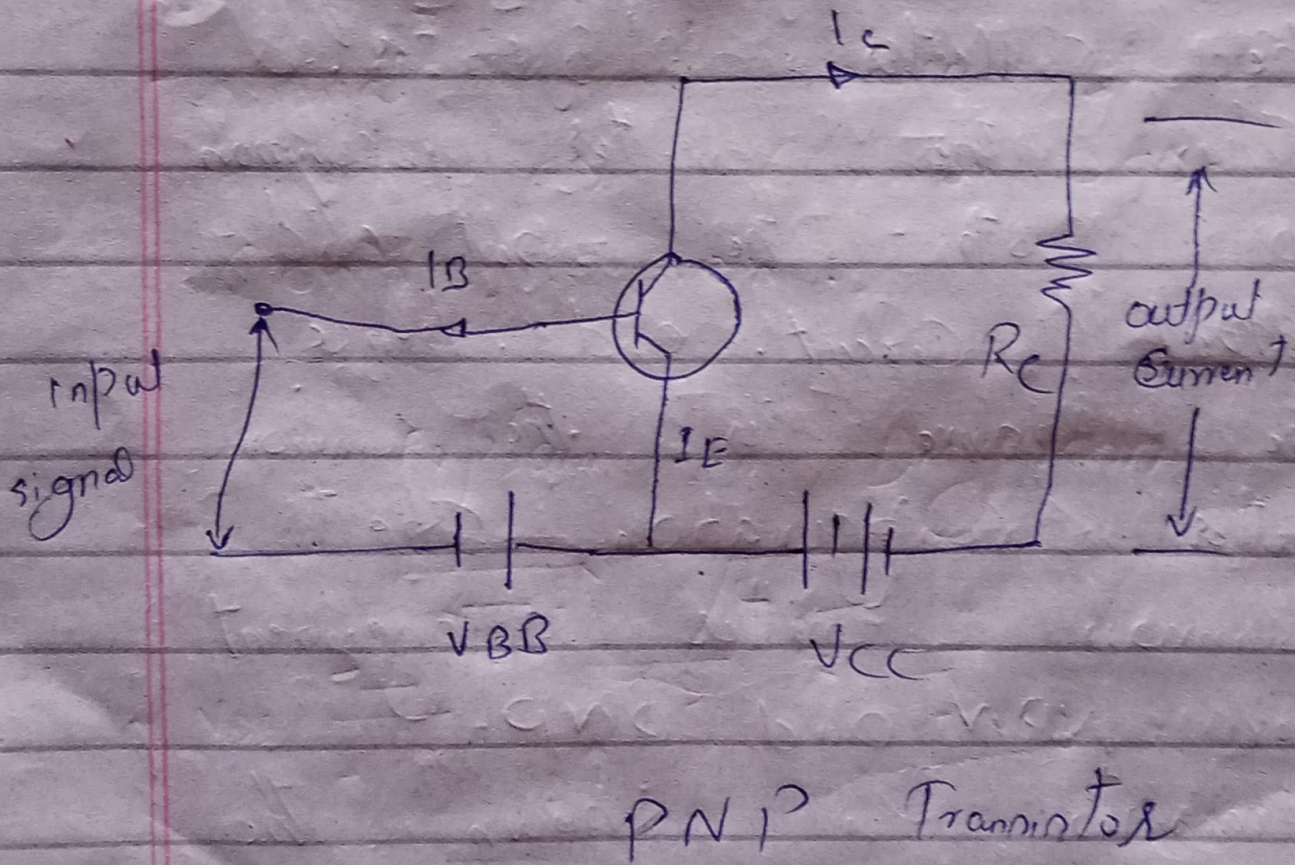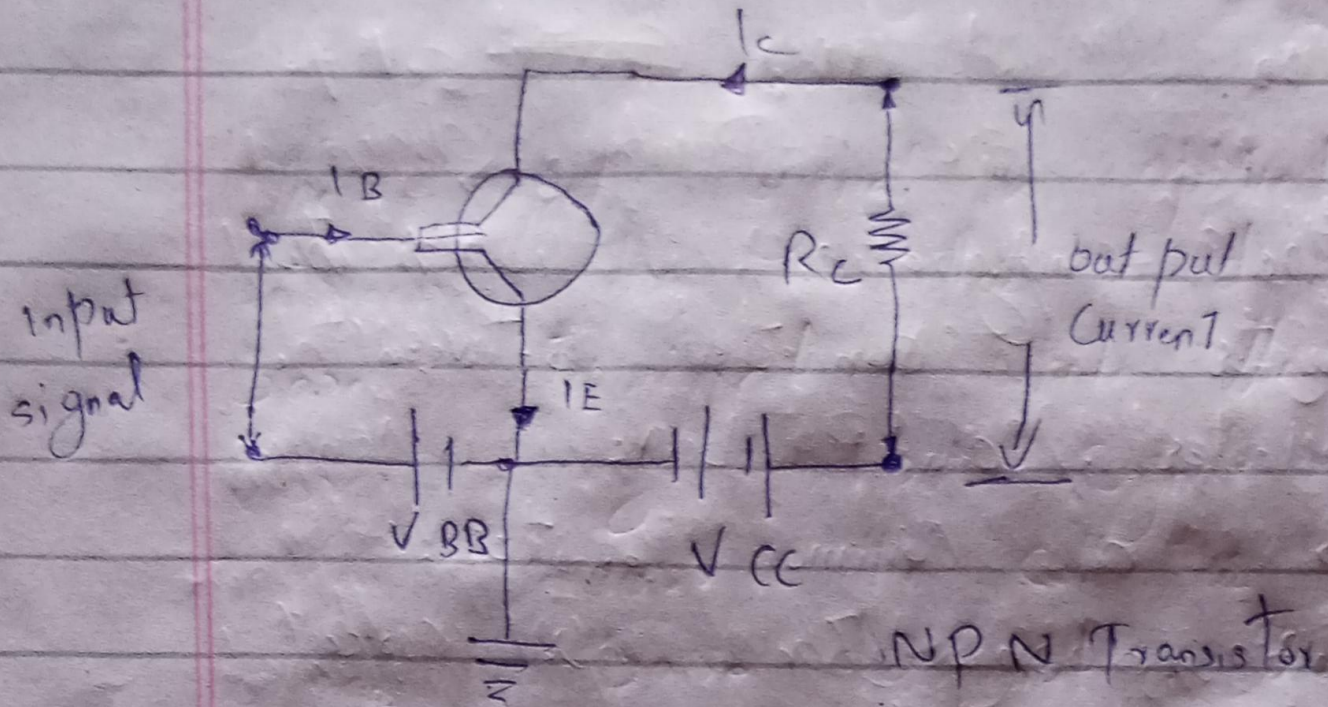


(7)

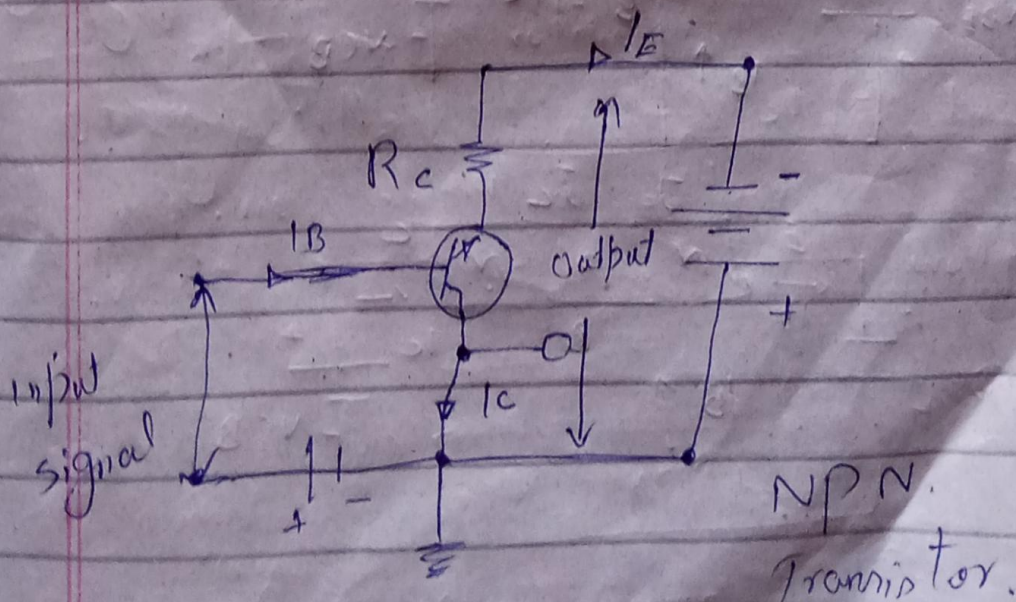2) Common Collector.

The configuration in which the collector is common between emitter and base is known as CC configuration. In CC configuration, the input circuit is connected between emitter and base and the output is taken from the collector and emitter.

The collector is common to both the input and output circuit and hence the name Common collector connection or Common collector configuration.





(8)

Q: No: 3

3- Common Base

The input signal is applied between the emitter and base terminal while the corresponding output signal is taken across the collector and base terminal. Thus the base terminal of a transistor is common for both input and output terminal and hence it is named as common base configuration.

Explain in Diagram

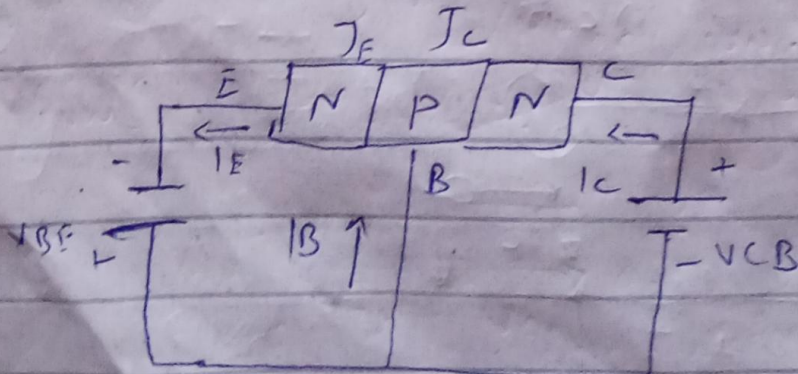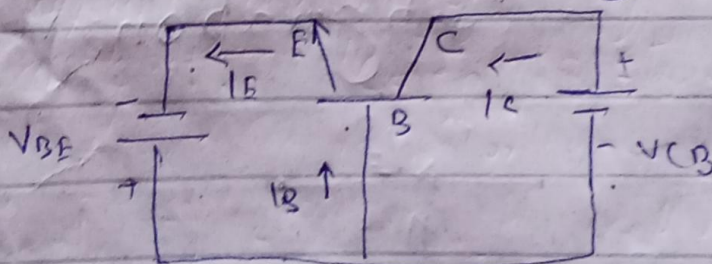

Common base configuration

(9)

(Q: NO: 4)

The E MOSFET in high power application is called the power FET. The set of drain current from an n-channel MOSFET. Normally E MOSFET is an OFF device. The minimum voltage V_{GS} that creates the n-type inversion layer is called the threshold voltage $V_{GS(th)}$. When V_{GS} is less than $V_{GS(th)}$. The drain current is approximately zero. When V_{GS} is greater than $V_{GS(th)}$ the curve appears linear and the device begins to conduct and turns "ON". Also the drain current is controlled by the gate voltage.

The almost vertical part of the graph is the ohmic region and the almost horizontal parts are the active region. It is equivalent to a resistor. When biased in the active region it is

(10)



equivalent to resistor, when biased in the active region. It is equivalent to a current source in the cutoff region. The gate source voltage is less than the gate threshold voltage and the device is an open circuit or (OFF).

In the ohmic region, the device acts as a resistor equivalent to $\frac{V_{DS}}{I_D}$. In the saturation region, the drain current is a function of gate source voltage. When the drain voltage is increased, the positive drain potential opposes the gate voltage bias and reduces the surface potential in the channel. The channel inversion layer charge decreases with increasing drain source voltage equals to $(V_{GS} - V_{GS(th)})$.

(11)

This point the channel
pinch-off voltage where
the drain current

becomes saturated.

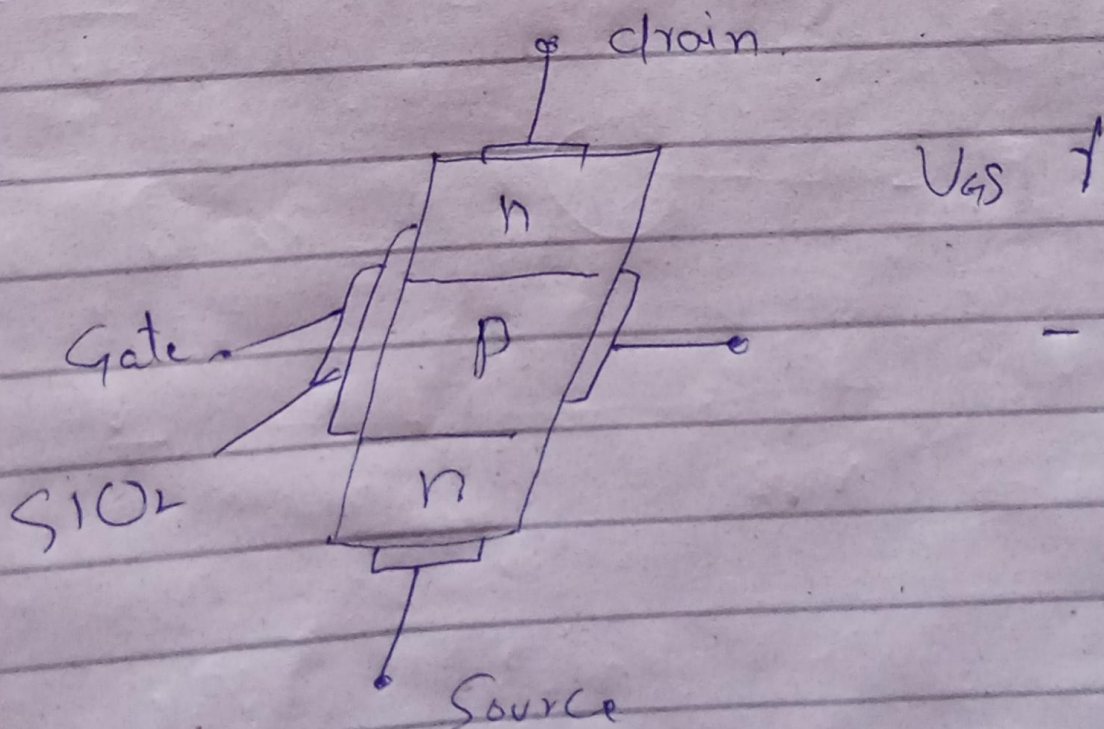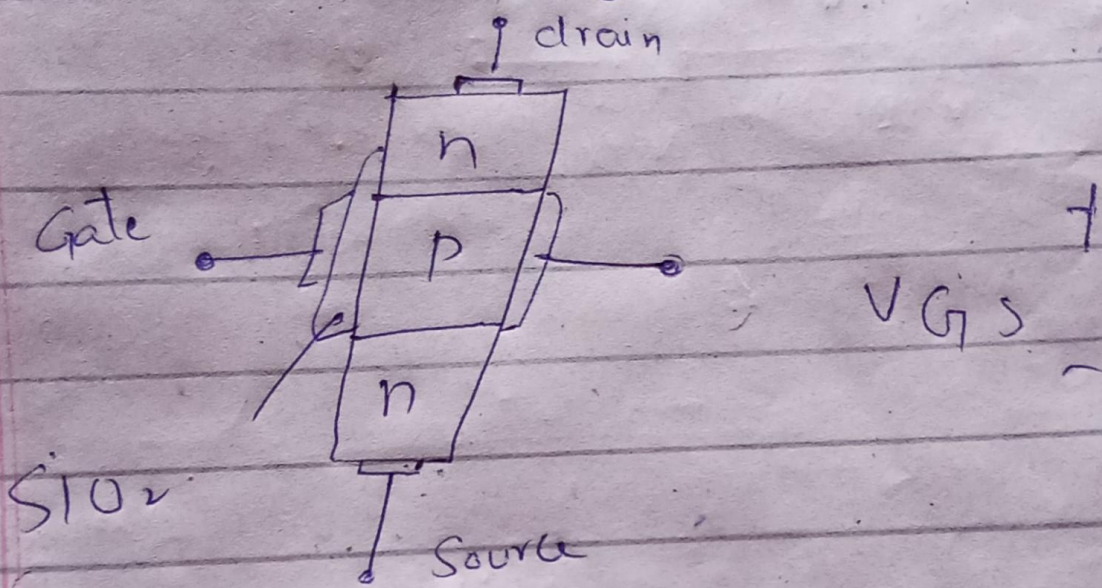

(12)

(QNo: 5. a)

Advantages of BJT.

- ① It has a large gain bandwidth.
- ② It shows the better performance at high frequency.
- ③ It has a better voltage gain.
- ④ It can be operated in low or high power application.
- ⑤ It has high current density.

Disadvantages of BJT.

- ① The BJT is more an effect of radiation.
- ② It has a very complex base control so it may lead to confusion and requires a skilful handling.
- ③ The switching frequency of a BJT is low.
- ④ It more noise produced.
- ⑤ It has a low thermal stability.

(QNO: 5 a)

Advantages of FET.

① FET are voltage sensitive device with high input impedance (10^7 to $10^{12} \Omega$).

② One class of FET generates lower noise than BJT.

③ FET are more temperature stable than BJT.

④ Power FETs can dissipate high power and can switch large currents.

⑤ The high input impedance of FETs permit them to store charge long enough to allow them to be used as storage elements.

⑥ FET are not as sensitive to radiation as BJT. Important consideration for space electronic application.

(14)

(Q: No: 5 a)

Disadvantage of FET:

- ① FETs amplifiers usually exhibit poor frequency response because high input capacitance.
- ② Some types of FET exhibits poor linearity.
- ③ FET can be damaged in handling due to static electricity.

←—————→
(Q: No: 5 b)

The EMOSFET in high power application is called the power FET. The set of drain current from an n-channel MOSFET. Normally EMOSFET is an OFF device. The minimum device voltage V_{GS} that creates the n-type inversion layer is called the threshold voltage $V_{GS(th)}$; when V_{GS} is less than $V_{GS(th)}$. The drain current is approximately zero.

(5)

When V_{GS} is greater than $V_{GS(th)}$ the curve appears linear and the device begins to conduct and turns 'ON'. Also the drain current is controlled by the gate voltage.

The almost vertical part of the graph is the ohmic region and the almost horizontal parts are the active region. It is equivalent to a resistor when biased in the active region. It is equivalent to a current source.

In the cutoff region the gate-source voltage is less than the gate threshold voltage and the device is an open circuit or OFF.

In the ohmic region the device acts as a resistor equivalent to $\frac{V_{DS}}{I_D}$. In the saturation region the drain current is a function of gate-source voltage.

(16)

When the drain ~~current~~ ^{voltage} is increased the positive drain potential opposes the gate voltage bias and reduces the surface potential in the channel. The channel inversion layer charge decreases with increases drain source voltage and ultimately I_d become zero when the drain-source voltage equals to $(V_{GS} - V_{GS(th)})$. This point the channel pinch-off voltage where the drain current becomes saturated.

