

NAME: Muhammad Hamza.

ID: 13136.

Q₁ Convert the following.

a. 101109.

b. 127.

c. 1110100110111.

d. $(170)_{10}$

e. 1111111111111111.

f. 000101010110.

g. 110111.

h.

Q₂ Calculate each of the following.


a. 125

b. 21.


c. 0111.

d. 01111000_2 .

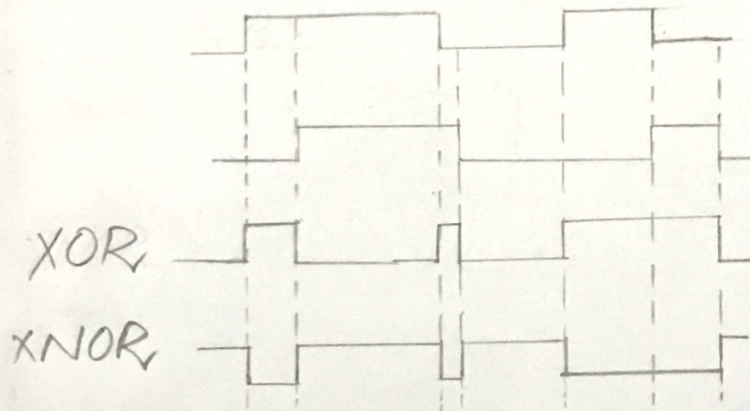Q3 Determine the output waveforms for the XOR & XNOR gates given the input waveforms, A & B, in fig 01.



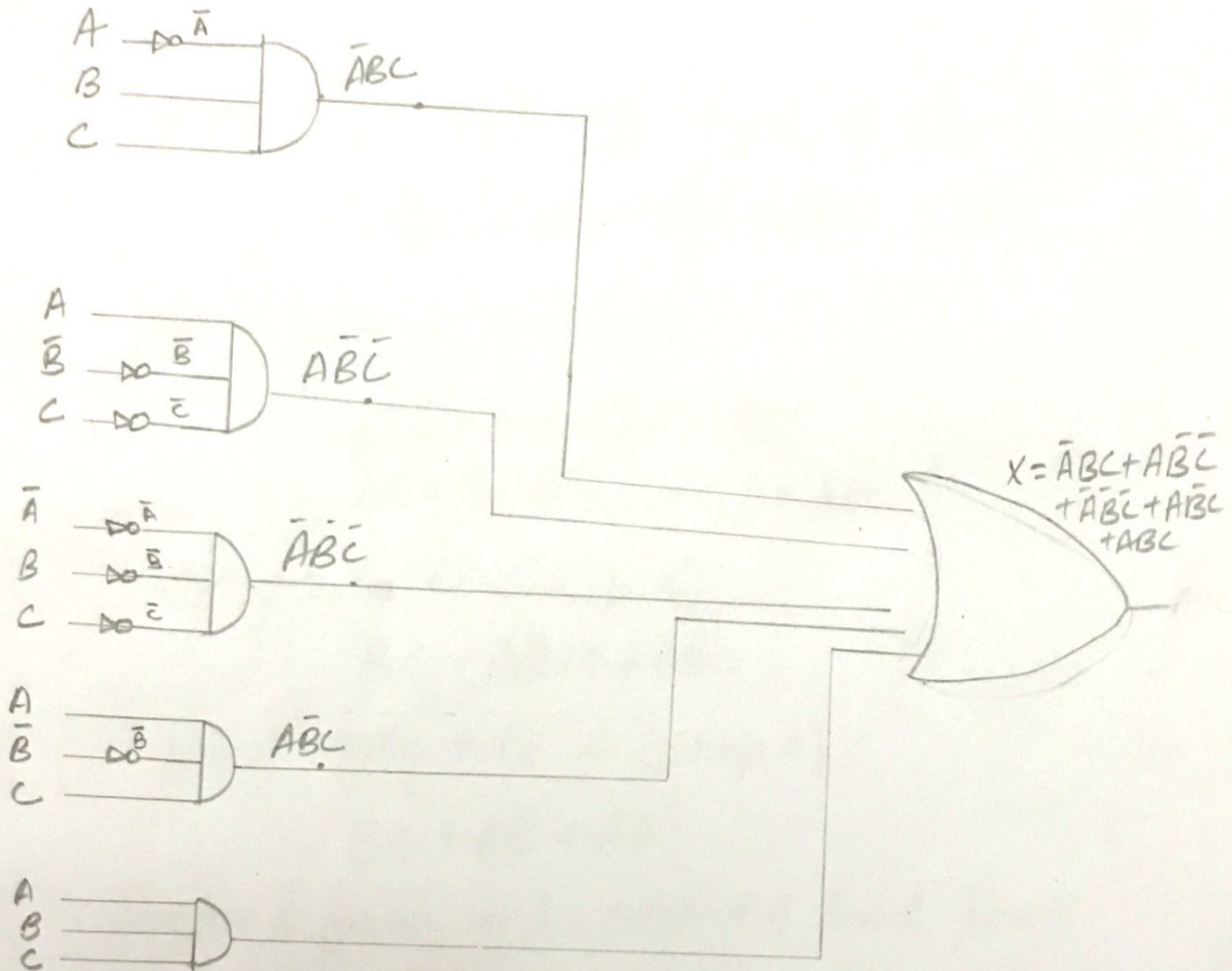Q4
(a) Draw the logic circuit for the following
 $X = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC$.



(b) Using Boolean algebra, simplify the expression in given part a.

$$X = \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$$

Factor BC out of first & last terms.

$$BC(\bar{A} + A) + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C$$

Apply rule 6 ($\bar{A} + A = 1$)

$$BC \cdot 1 + A\bar{B}(\bar{C} + C) + \bar{A}\bar{B}\bar{C}$$

Apply rule 4 (drop 1).

$$BC + A\bar{B} \cdot 1 + \bar{A}\bar{B}\bar{C}$$

Again apply rule 4 (drop 1).

$$BC + A\bar{B} + \bar{A}\bar{B}\bar{C}$$

Factor \bar{B} from the second & third terms.

$$BC + \bar{B}(A + \bar{A}\bar{C})$$

Apply rule 11 ($A + \bar{A}\bar{C} = A + \bar{C}$).

$$BC + \bar{B}(A + \bar{C})$$

Use the distributive & commutative law to get the following.

$$BC + A\bar{B} + \bar{B}\bar{C}$$

Q5
(a)

Convert the following expression to standard SOP form $A = \overline{\overline{X+Y+Z}}$.

Solution:

$$A = \overline{\overline{X+Y+Z}}$$

$$= \overline{(\overline{X+Y+Z})}$$

~~$$= \overline{\overline{X+Y+Z}}$$~~

$$= \overline{X+Y+Z}$$

$$(\because \overline{A+B} = \overline{A} \cdot \overline{B})$$

$$= (\overline{X} + \overline{Y}) \cdot \overline{Z}$$

$$= (X+Y) \overline{Z}$$

$$= X\overline{Z} + Y\overline{Z}$$

$$= X(Y+\overline{Y})\overline{Z} + (X+\overline{X})Y\overline{Z} \quad (\because A+\overline{A} = 1)$$

$$= XY\overline{Z} + X\overline{Y}\overline{Z} + X\overline{Y}\overline{Z} + \overline{X}Y\overline{Z}$$

Q5
(b) Convert the standard SOP expression obtain in part (a) to standard POS form.

Ans: Solution.

Demorgan's

$$(x+y)' = x'y'$$

$$(xy)' = x'+y'$$

Apply demorgan's law.

$$\rightarrow (A') = (xz' + yz')$$

$$A' = (xz')' (yz')'$$

$$A' = (x'+z) (y'+z)$$

$$= x'y' + y'z + x'z + z \cdot z$$

$$A' = x'y' + y'z + x'z$$

again apply demorgan's law

$$(A')' = (x'y' + y'z + x'z)'$$

$$A = (x'y')' (y'z)' (x'z)'$$

$$A = (x+y) (y+z') (x+z')$$

Q5
(c)

Develop a single truth table for the standard SOP & standard POS expressions obtain in part (a) & part (b).

Ans

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

1 shows SOP terms.
 $\Sigma = (2, 4, 6)$

0 shows POS terms.
 $\Pi (0, 1, 3, 5, 7).$

Q6 Use a karnaugh map to find minimum SOP form the following.

$$X = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + ABC + A\bar{B}C.$$

Solution

$$X = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + ABC + A\bar{B}C.$$

000 100 010 110 111 101.

A \ BC	00	01	11	10
0	1			1
1	1	1	1	1

- \bar{C}
- A

SOP form = $X = A + \bar{C}$.

Q6 (b) Determine minimum POS from the karnaugh map used in part (a).

Ans $\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + ABC + A\bar{B}C.$
111 + 011 + 101 + 001 + 000 + 010.

AB \ C	0	1
00	0	0
01	0	0
11		0
10		0

→ $A+B+C$
→ $A\bar{B}+C$
→ $\bar{A}+\bar{B}+\bar{C}$
→ $\bar{A}+B+\bar{C}$.