

Haroon Rashid

Reg# 16549

Semester 6<sup>th</sup>

Assignment: DLD Lab

Submitted to: Sir MUHAMMAD AMIN

Lab 8-2  
HALF Adder

Table 2.1: Output Observation Table

Inputs		Outputs	
A	B	Sum (s)	Carry (c)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1