Department of Electrical Engineering Mid – Term Assignment Spring 2020 Date: 20/04/2020

Course Details

| Course Title: Instructor: | | e Title: ctor: | Microcontroller Systems & Inter | fac | ing Module:06 Total Marks:30 |) |
|------------------------------|-----|--|--|------|---|----------|
| | | | Student D | eta | <u>ills</u> | |
| Na | me | : | Asfandyar Awais | | Student ID:114 | 61 |
| 01 | (a) | 1) Ohm's | Law is an equation that relates the follow | ving | electrical concents: | Marks 10 |
| Z ¹¹ | (u) | a. Voltag | e, current and resistance | b. | Resistance and reluctance | CLO 1 |
| | | c. Currer | nt, power and voltage | d. | Voltage and current | |
| | | 2) If a con been co | nputer uses a 200 W power supply and i nsumed? | t is | activated for 45 minutes, how much energy has | |
| | | a. 540 M | J | b. | 5.4 kJ | |
| | | c. None | of these answers | d. | 540 kJ | |
| | | 3) You we | ould like to set up a circuit with 2 identi | cal | light bulbs and a battery. You hesitate between | |
| | | putting them in series or in parallel. The circuit that dissipates the most power is: | | | | |
| | | a. The sa | me for light bulbs in series and parallel | b. | Light bulbs in series | |
| | | c. Light | bulbs in parallel | d. | Not possible to determine from the given information. | |
| | | 4) For the circuit discussed in Question 3, the circuit for which the lights are the brightest is: | | | | |
| | | a. Light | oulbs in parallel | b. | The same for light bulbs in series and parallel | |
| | | c. Light | bulbs in series | d. | Not possible to determine from the given information | |

| | | 5) The circuit for which the battery will last the longest is | | | |
|-----|-----|--|-------|--|--|
| | | a. The same for light bulbs in series and parallel b. Light bulbs in series | | | |
| | | c. Light bulbs in parallel d. Not possible to determine from the given | | | |
| | | information | | | |
| Q2. | (a) | A parking lot must be automated using an Arduino by counting each car entering the lot and leaving the | | | |
| | | lot. The lot has a total space for 8 cars at a time. On each parking of a car a RED led must be visible to | | | |
| | | show the space has been taken. A GREEN led must be visible to show the space is vacant for a car. | | | |
| | | Write the code in C-language and draw the circuit diagram. | | | |
| Q3. | (a) | A counter must be implemented using an Arduino for a room, whenever a person enters the room and | | | |
| | | presses a button the counter must the counter and display the amount on two 7 segment displays, | CLO 2 | | |
| | | whenever the person leaves the room and presses the second button the counter must be decremented | | | |
| | | and displayed on the 7 segment display. Write the code in C-language and draw the circuit diagram. | | | |

80 0 0 0 0 0 0

Plasmer to Const int parking In = 0; Const int parking In = 0; 2 2: Const Const Parkinjout = 9; led 1 = 1; int Const int led 2 = 2; Const int Const leel 3 23, Const int led 9 24 Const int led 5 = 5; int led 6 26, Const int led 7 = 7; Const int led 8 28; int senser Value, bright; Void Setup () { Schal begin (9600); PinMode (Parking In, INPUT); PinMode (Parking Out, INPUT); PinMode (led1, OUTPUT); Pin Mode (ledz; OUTPUT); Pinklode (lad 3; OUTPUT); PINNade Cledy; OUTPUT); PinMade Cled5; OUTPUT); PinMode (led6; OUTPUT); Pin Mode (leda; OUTPUT); Pin Mode (led 8; OUT PUT); int available Packing 28; 3 Joid loop () q Car car In z analog Read (parking In); car Out - analog Read (parking Out); if (carlo) available Parking ++; 3 25

3 else if (arout) awailable Packing --; fer(ledon=1; ledon <= 8; ledon+) analog White (led, High); analog White (led, HIGH); 52 2

Const int and, const int bed const int de bi const int re 6 const int f = 2 const int J = \$ 1 bool blun + fale, Const int Inclusion Pine to: Const int Dreballon Pine (1) Int button Plush counter = 0) int inclustion state = 0; int last incluston state = 0; int Dec batton state = 0; int last Der butten state = 0; Void Setup () ? Pin Mode Ca, Orapid OUTPUTS PinNode (b), OUTAUT); Pin rede (C, OVTPUT); PinModecd, OUTPUT); PinAlode(e, OUTPUT), Pin Made (f. OUTPUT), Pinnlode (g, OUTPUT); Pinnlade (Inchutton Pin, INPUT_POLLOP), Pin Mode (Dec button Pin, INPUT_PULLUP); Serial begin (9600)+ display Digit (button Pash Counted). N Inclutton State = digital Raid Clinebutton Pink Vaid loop () 8 De button State & digital Read (Dec button An), (check Inc Batton Press (); Check De Button Press ();

it (bPress) { 5 6 Press z false, turn Off (); diplay Piget (button Push (ountex); for (int izo; iclo, itt) display Digit (i); delay (1000); turnoff; S Void check Inc Button Press () Se If (Incouttonstate 12 last button state) if (Inchatton state== how) { b Press 2 true; if (button Rush counters 4) button Push counter 20; Secial Prent In ("on"); 3 else { Secial Print [In("Off); 3 delay (50); last Inchutton State 2 Inchitton State; 3 Void chark Per Button Press() 3 if (Perbuttonstate != last Derbutton state) { if (Derbuttonstate zzhow) { ppress 2 true; button Push Counter -- ;

of Chutton Plush Counter = 0) Inston Push Counter = 9; Secial - Print in Con?); else ? Second printer ("Ost"); 3 detay (50); 2 last Dec button State = Dec batton Scate; Void duplay Digit (int digit) 3 1+ Colugit != 1 88 digit 1=9) digital white Ca, Hight - HIMH 27 Coligit 1=5 88 digit 1=6) digital white Cb, Highin HIGH if (digit 1-2) digital white (GiHiGiHI); if (digit 1 =1 && digit 1=4 && digit (=7) digital Write (d, HIGH); if (digit = 2 11 digit = = 6 11 digit = 28 11 digit = 20) if Cdigit != 1 88 digit 1=2 88 digit != 3 88 digit != 7) digital white (f, HIGH); 17 (digit 120 88 digit 121 88 digit 1=7) digital Write (JoHIGIH); 2 Void turnoff() digital White (a, LOW); digital Nrite (b, NOW); digital white ((, how); digital white (d, how);

