

NAME

Muhammad ILYAS

Degree

B.S (software Engr)

ID.No

15392

Assignment

5

TEACHER

Siv. M. Amin

Q1: Determine the output of a full-adder for the following input $A=1$, $B=0$, $C_{in}=1$

Ans:-

$\Sigma = (A \oplus B) \oplus C$	$C_{out} = AB + (A \oplus B)C_{in}$
$\Sigma = (1 \oplus 0) \oplus 1$	$C_{out} = (1)(0) + (1 \oplus 0)1$
$\Sigma = (1) \oplus 1$	$C_{out} = 0 + (1)(1)$
$\Sigma = 0$	$C_{out} = 1$

Q2: In what are the half-adder inputs that will produce the following output $\Sigma = 0$, $C_{out} = 0$

Ans:-

$$\Sigma = 0, \quad C_{out} = 0$$

$$A = ? \quad B = ?$$

for Σ and C_{out} both to be zero the A and B must be zero.

$A=0$	$\Sigma = A \oplus B$	$C_{out} = AB$
$B=0$	$0 = 0 \oplus 0$	$C_{out} = 0 \cdot 0$


Ans.

Q3: Determine the output of a full adder for the following inputs.

Ans:- $A=1$, $B=1$, $C_{in}=1$

$\Sigma = (A \oplus B) \oplus C_{in}$	$C_{out} = AB + (A \oplus B)C_{in}$
$\Sigma = (1 \oplus 1) \oplus 1$	$C_{out} = 1 \cdot 1 + (1 \oplus 1)1$
$\Sigma = (0)$	$C_{out} = 1 + (0)1$
<u>Ans.</u>	$C_{out} = 1$

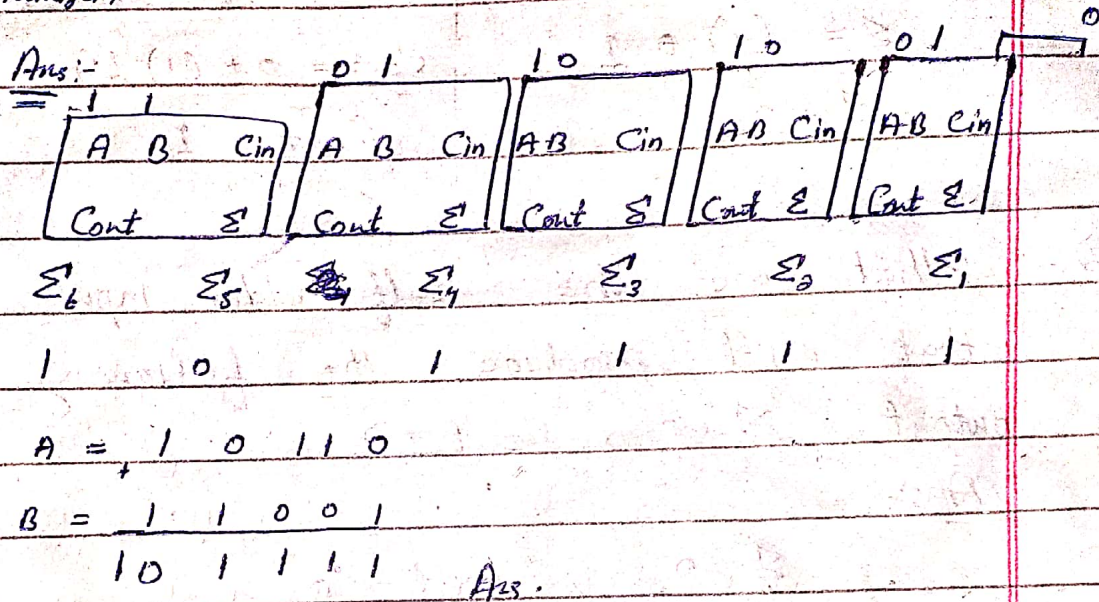Q4:- For the parallel adder in figure 01 determine the complete sum by analysis of the logical operation of the circuit. verify your result by longhand addition of two input numbers.



QUESTION-5

PART 'A':-

When the Add/sub is high the input bits of will be complemented and the resulting Σ will be the subtraction of the input bits.

PART 'B':

When the Add/sub is low the input bits of B will not be changed and the circuit will work as a parallel adder for the input bits.

Q 6:- For the circuit in Figure 02, assume the input are $\overline{\text{Add/sub}} = 1$, $A = 1010$, and $B = 1101$, what is the output.

Ans:-

$$\overline{\text{Add/sub}} = 1, A = 1010, B = 1101$$

$$\text{for } \Sigma_0: A_0 = 0, B_0 = 1 \oplus 1, C_{in} = 1$$

$$\Sigma_0 = 0 + 0 + 1 = 1, \text{Carry} = 0$$

$$\text{for } \Sigma_1: A_1 = 1, B_1 = 1 = 1 \oplus 0, C_{in} = 0$$

$$\Sigma_1 = 1 + 1 + 0 = 0, \text{Carry} = 1$$

$$\text{for } \Sigma_2: A_2 = 0, B_2 = 1 \oplus 1, C_{in} = 1$$

$$\Sigma_2 = 0 + 0 + 1 = 1, \text{Carry} = 0$$

$$\text{for } \Sigma_3: A_3 = 1, B_3 = 1 \oplus 1, \text{Carry} = 0$$





$$\Sigma_3 = 1 + 0 + 0 = 1, \text{Carry} = 0$$

$$\Sigma = \Sigma_3 \Sigma_2 \Sigma_1 \Sigma_0 = 1101, \text{Carry} = 0$$

Ans:-

Q 7:- The input waveform in figure are applied to a 2-bit adder. Determine the waveforms for the sum and the output carry in relation to the inputs by constructing a timing diagram.

Ans:

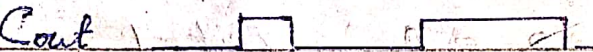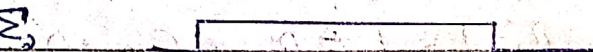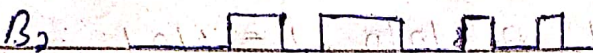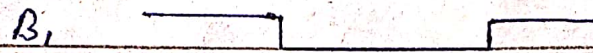

Q 8:

$A_1 = 1010, A_2 = 1100, A_3 = 0101$

$A_4 = 1101$

$B_1 = 1001, B_2 = 1011, B_3 = 0000, B_4 = 0001$

Sol:

$A_4 A_3 A_2 A_1 + B_4 B_3 B_2 B_1 = \Sigma_5 - \Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1$

$1 \ 0 \ 1 \ 1 \quad 0 \ 0 \ 1 \ 1 \quad 0 \ 1 \ 1 \ 0$

$1 \ 1 \ 1 \ 0 \quad 0 \ 0 \ 0 \ 0 \quad 0 \ 1 \ 1 \ 0$

$0 \ 0 \ 0 \ 1 \quad 0 \ 0 \ 1 \ 0 \quad 0 \ 0 \ 1 \ 1$

$1 \ 1 \ 0 \ 0 \quad 1 \ 0 \ 1 \ 1 \quad 1 \ 0 \ 1 \ 1$

$\Sigma_5 = 0 \ 0 \ 0 \ 1$


$\Sigma_4 = 1 \ 1 \ 0 \ 0$

$\Sigma_3 = 1 \ 1 \ 0 \ 1$

$\Sigma_2 = 1 \ 1 \ 1 \ 1$


$\Sigma_1 = 0 \ 1 \ 1 \ 1$

Q10:-

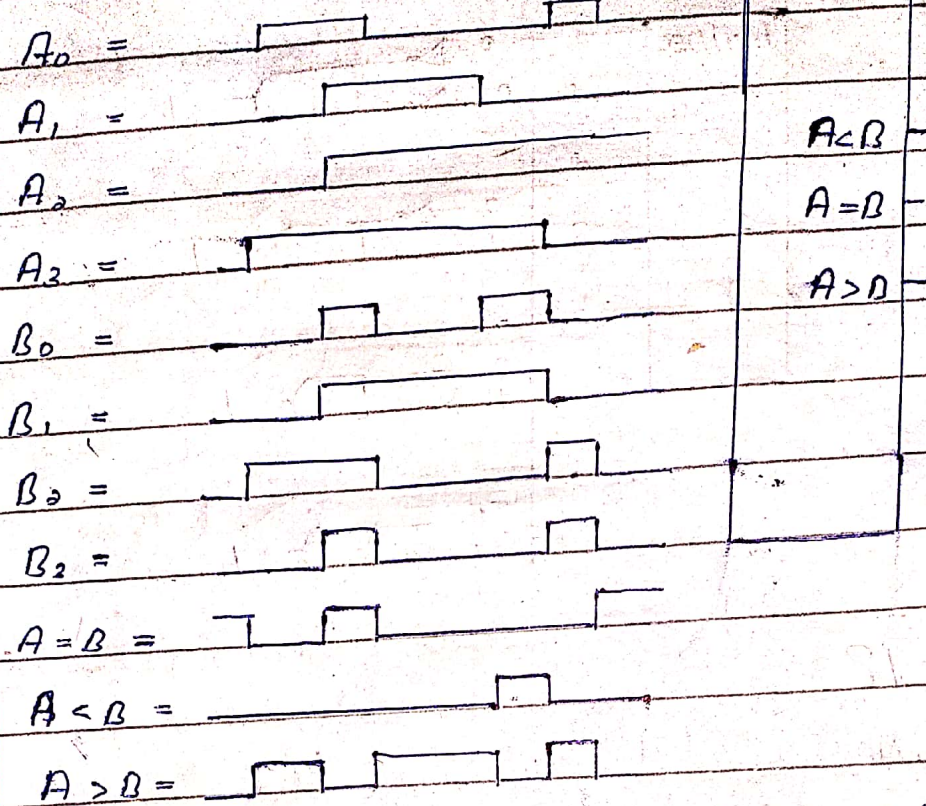

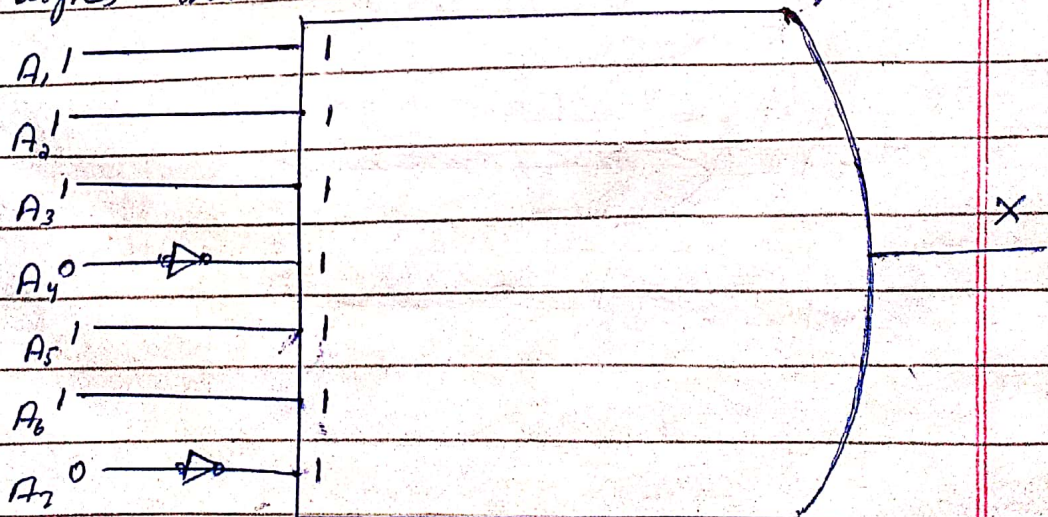Q11:- Show the decoding logic for the following codes if an active-HIGH (1) output is required: 1110110


Ans:- For the output to be High for the given code 1110110 following is the decoding logics that can be used to decode the given code.



$$X = \bar{A}_7 A_6 A_5 \bar{A}_4 A_3 A_2 A_1 A_0$$


Q12: Draw logic diagram for 2 to 4 line decoder.

Ans:

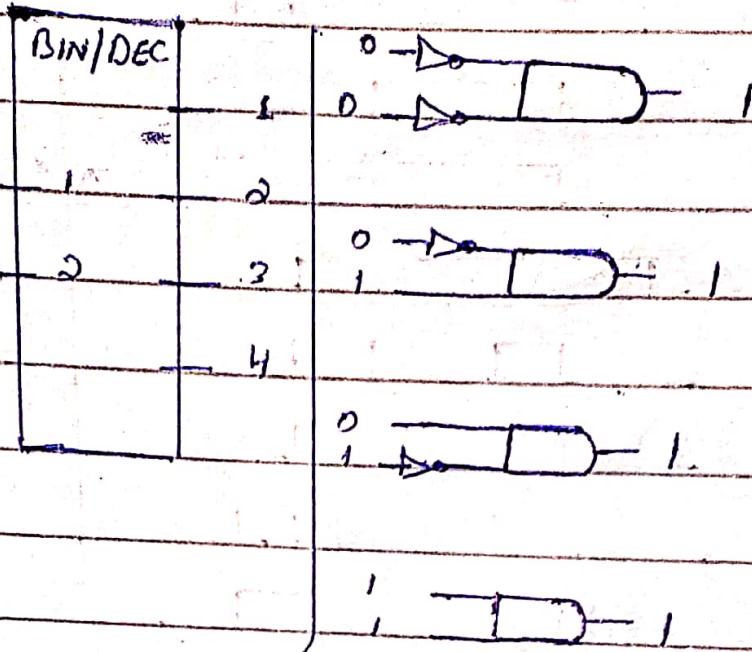


Q13:-


Ans:-

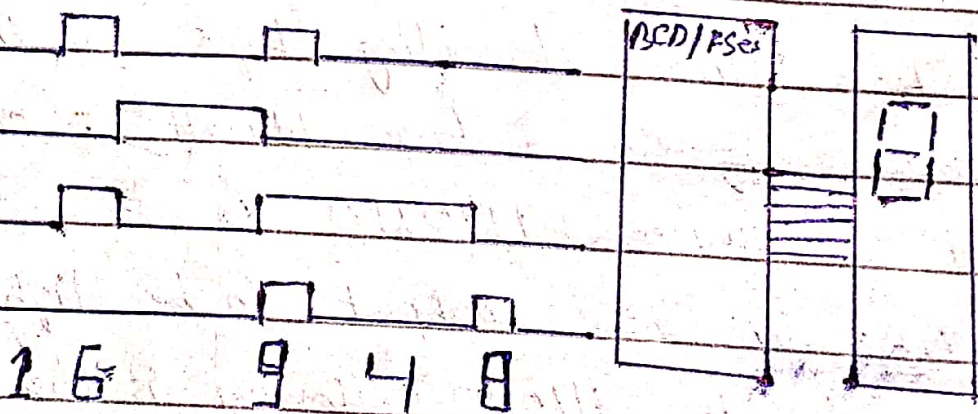

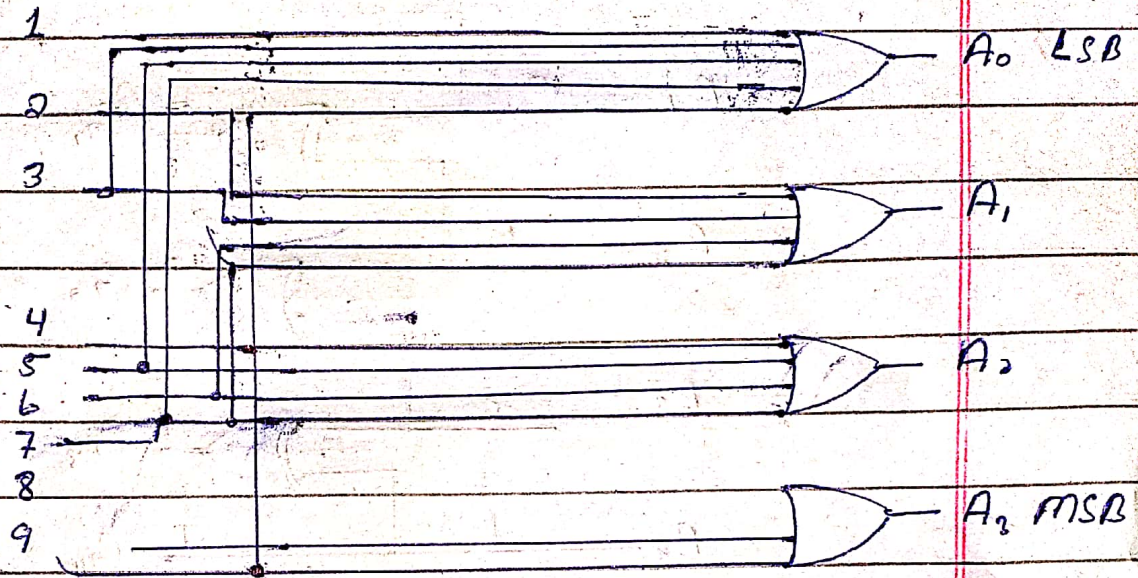Q14:- Draw logic diagram for decimal to BCD encode.




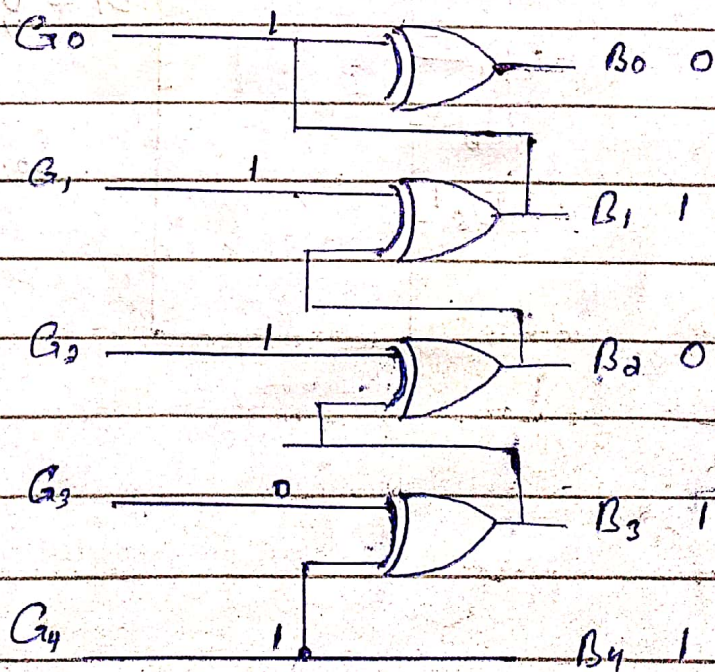Q16:- Show the logic required to convert a 5-bit Carry code to binary and use that logic to convert the following Carry code words to binary 1011.




$$1011_2 = 11010_2$$

Q 15 :-

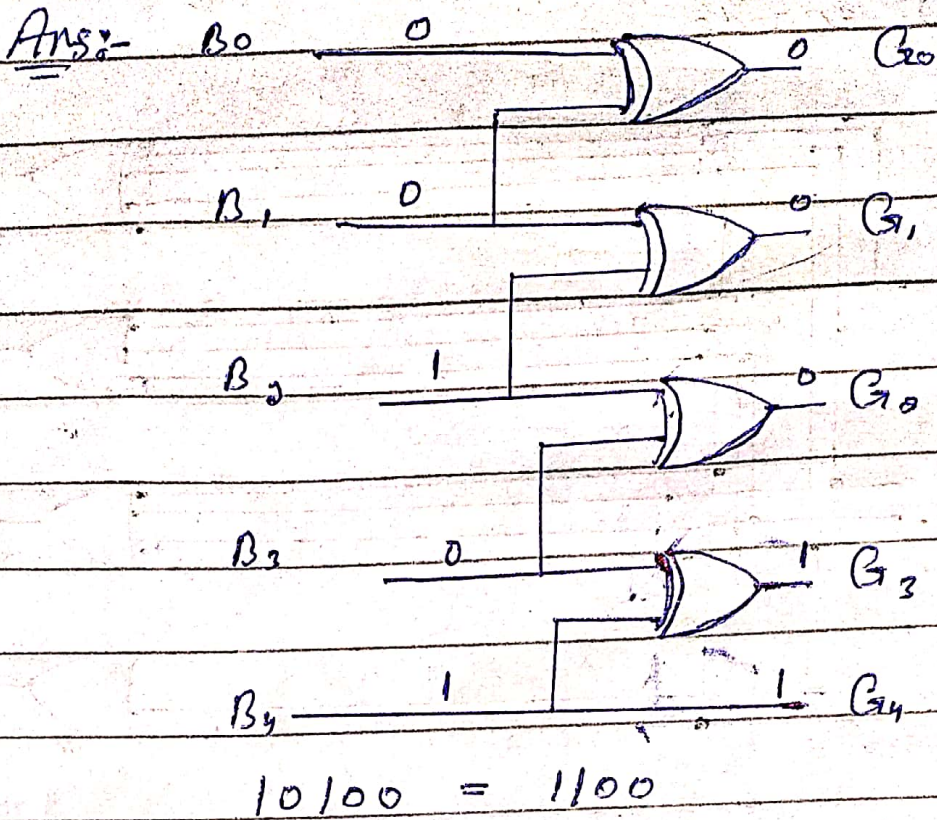


Q 17 :-

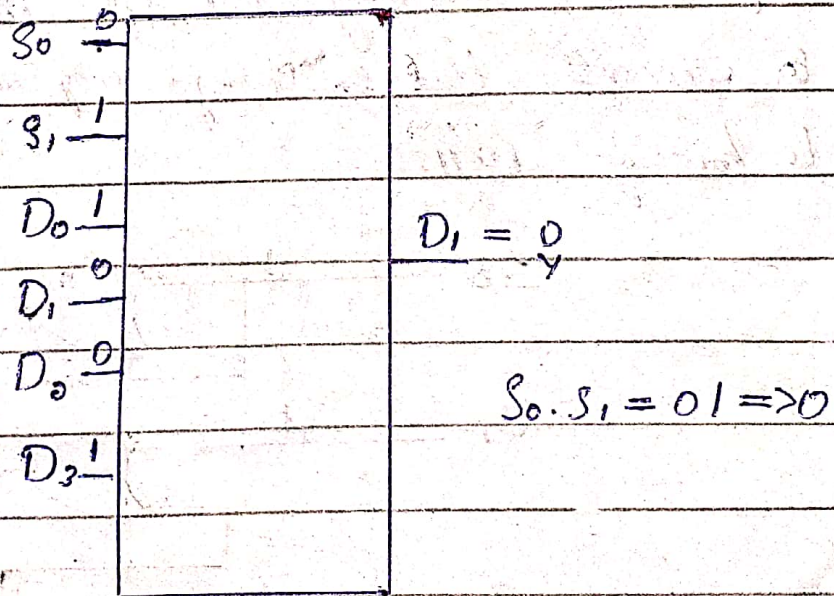

Q18:-


Ans:-

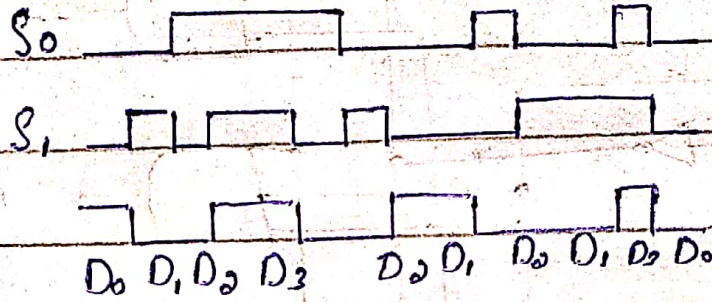

Q19:-

Draw logic diagram for 4 to 1 line multiplexer.

Ans:-

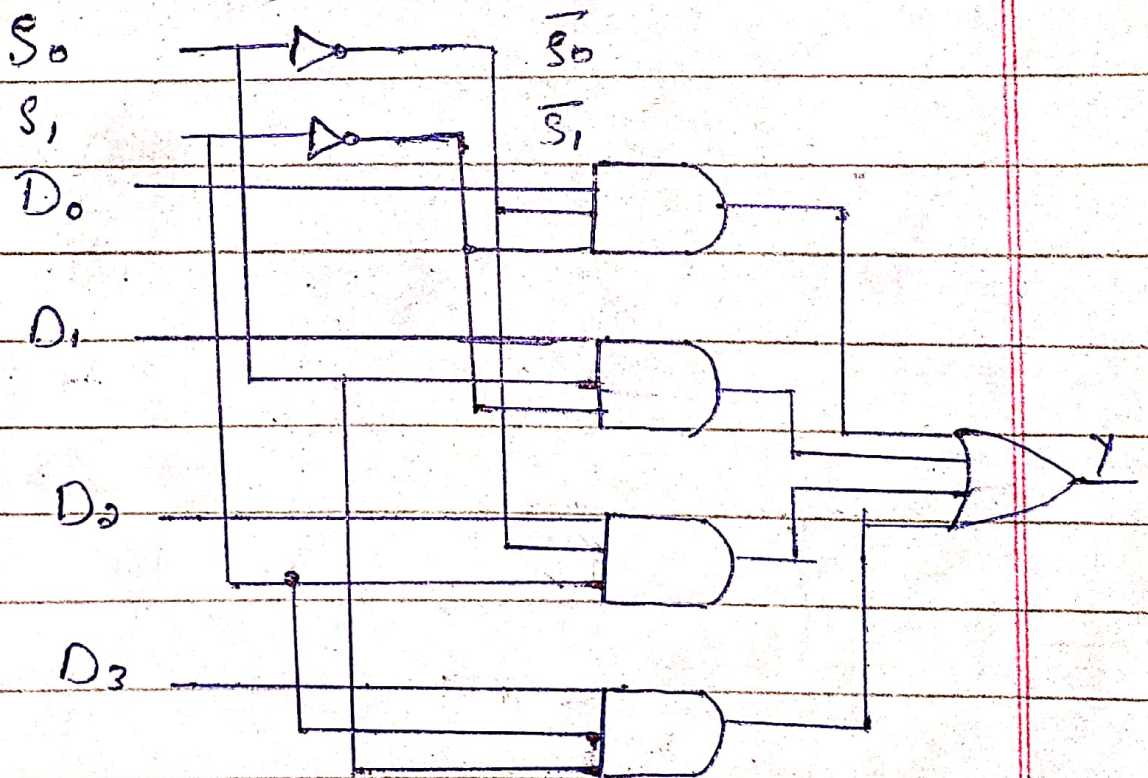

Q 20:

Ans:

