

DIGITAL LOGIC DESIGN

ASSIGNMENT: 6.


Sir. Muhammad Amin.

NAME: M. Hassan Adeel.



ID: 15437.

DEPARTMENT: CS.


Q: 1.

 


Q: 2

 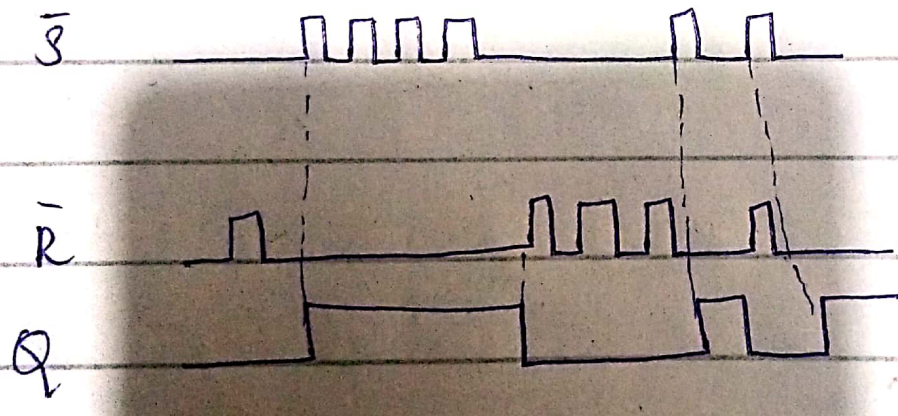


Q:3)

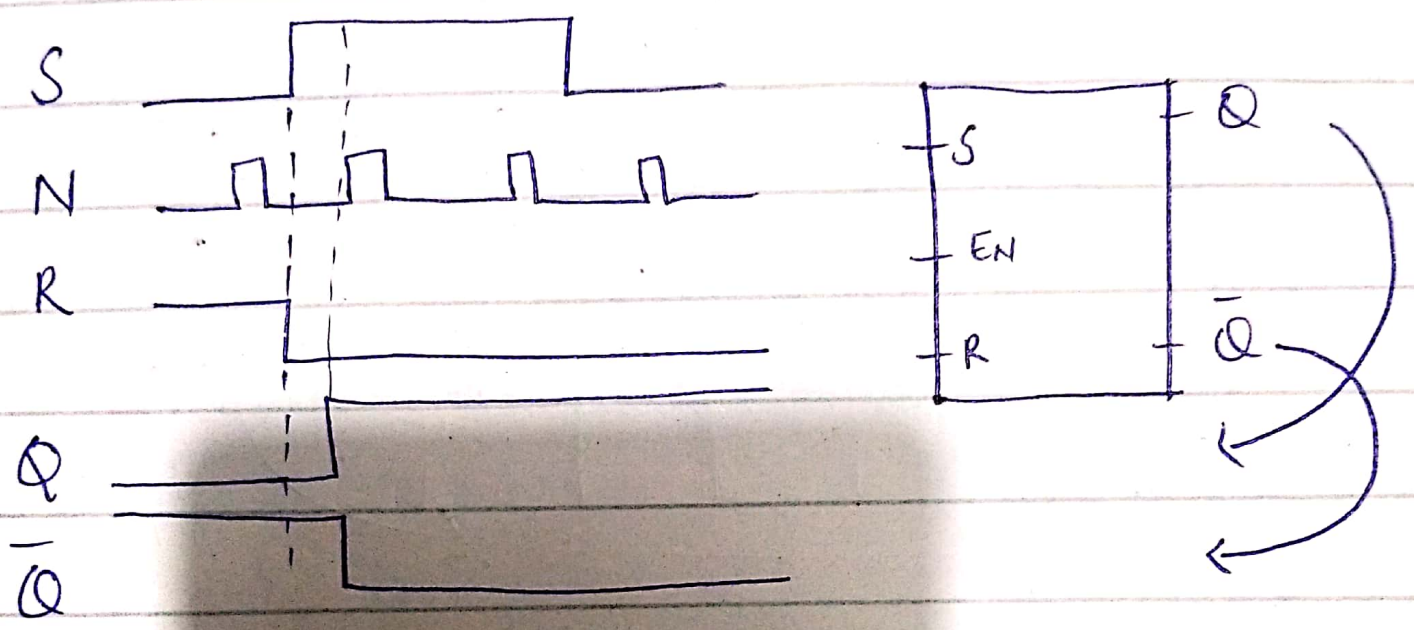

Q:4)

 


Q: 5:

 


The main difference between (a) and (b) edge triggered JK-flip-flops is that "The flip flop (a) on the negative edge of the clock pulse, while. The flip flop (b) triggers on the positive edge of the clock pulse"


(b)

 


Q: 7.

 


Q: 8 :-

 


Q: 9)

 


Q: 10:

 

Q: 11:

 

Q: 12:

 

Q: 13)

Q

$$\bar{J}_1 = 1010011$$

$$\bar{J}_2 = 0111010$$

$$\bar{J}_3 = 1111000$$

$$J = 0010000$$

$$k_1 = 0001110$$

$$k_2 = 1101100$$

$$k_3 = 1010101$$


$$k = 0000100$$

$$J = 0010000$$



$$k = 0000100$$

$$Q = 0011000$$


Q: 15)

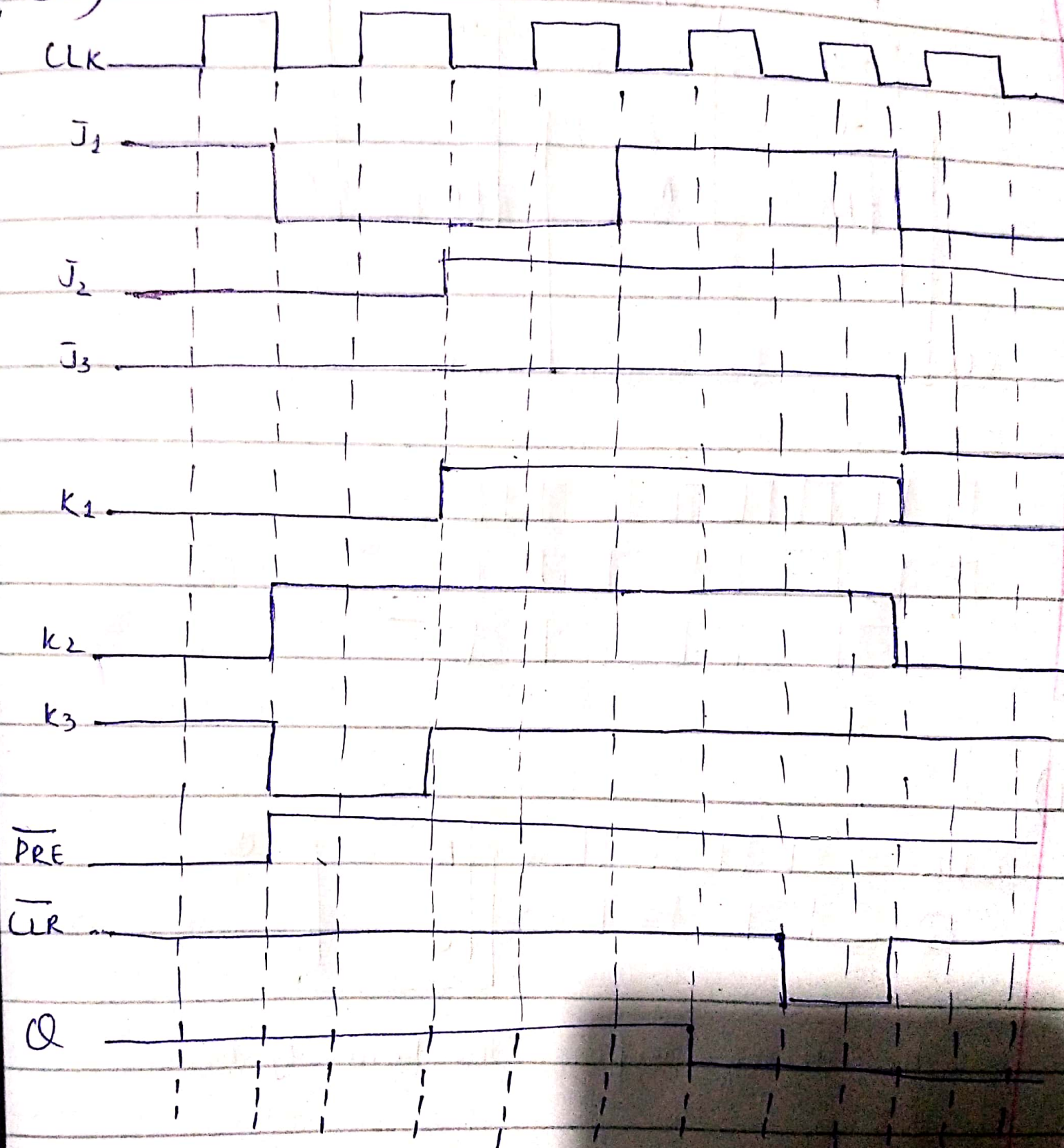

Q: 16)

 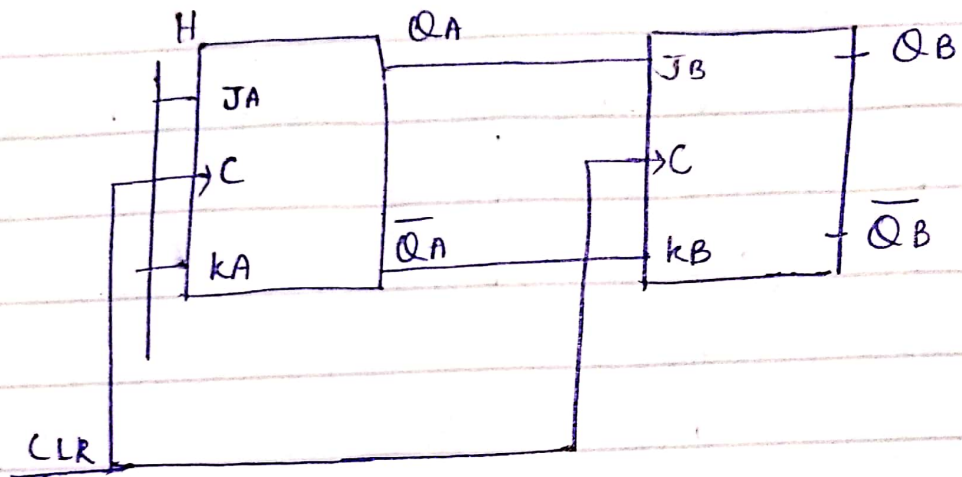


Q: 17)

 


The device performs the Divide-by-two function.

Q: 18)

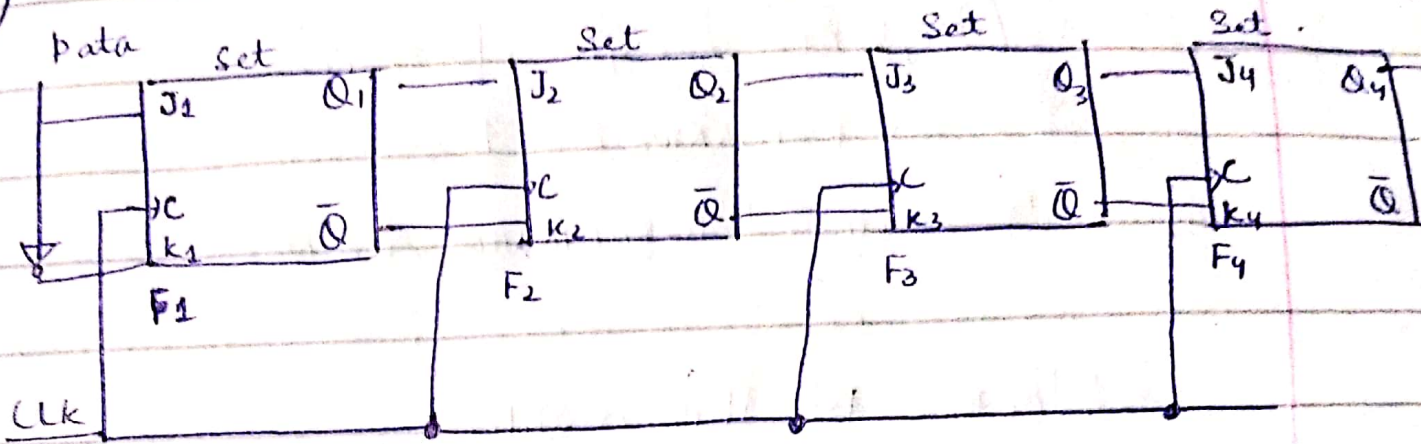

Q: 19)

 

Here if the input frequency is 8 kHz then at given modes frequency will be as follows.

$$Q_A = \frac{f}{2} = 4 \text{ kHz}$$

$$Q_B = \frac{f}{4} = 2 \text{ kHz}$$

$$Q_C = \frac{f}{8} = 1 \text{ kHz}$$