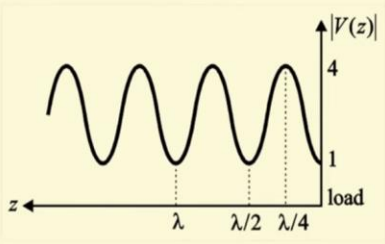


	(b)	Derive transmission line equation and describe what it says	Marks 4 CLO 1
Q3.	(a)	<p>Voltage standing wave pattern in a lossless transmission line with characteristic impedance 50Ω and resistive load is shown in the figure.</p>  <p>Qu. The reflection coefficient is given by</p> <p>(A) -0.6 (B) -1 (C) 0.6 (D) 0.2</p>	Marks 4 CLO 2
	(b)	Explain two Impedance Matching techniques in detail?	Marks 6 CLO 2


Name:- Umar Khan

ID :- 13079

Date :- 17-4-2020

Course title:- Antenna & wave propagation

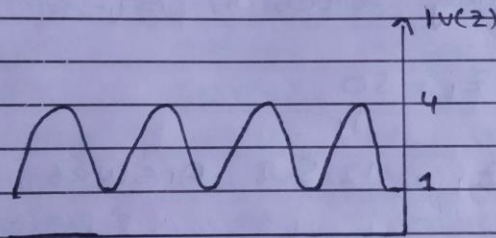(a)
Q1 Voltage standing wave pattern in a lossless transmission line with characteristic impedance 50Ω & resistive load as shown in figure.



Solution:-

Given data

$$Z_0 = 50\Omega$$

$$V_{max} = 4$$

$$V_{min} = 1$$

Required data:-

$$Z_L = ?$$

$$S. \text{ wave ratio} = ?$$

As we know that

$$S. \text{ wave ratio} = \frac{V_{max}}{V_{min}} \quad (1)$$

Putting values in eq. (1)

$$= \frac{4}{1}$$

S. wave ratio = 4

Now find Z_1

$$S. \text{ wave ratio} = \frac{Z_0}{Z_1}$$

$$Z_1 = \frac{Z_0}{S. \text{ wave ratio}} \quad - (2)$$

Putting values in eq. (2)


$$Z_L = \frac{50}{4}$$

$$Z_L = 12.5 \Omega \text{ Answer.}$$

(b)
Q1

Draw & explain equivalent circuit model of transmission line.

Ans:-

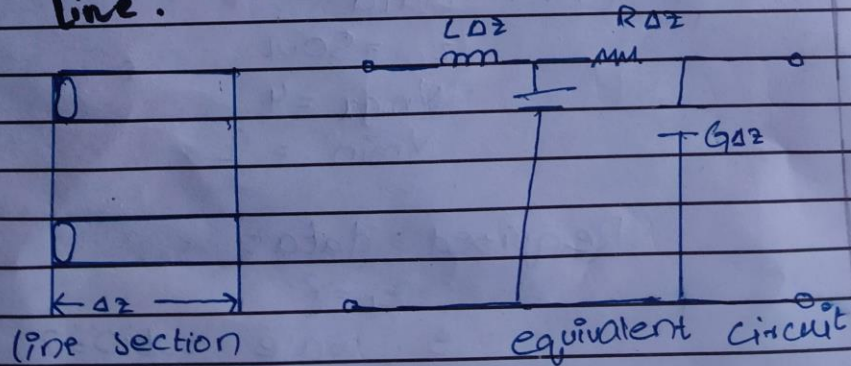

Explanation:

R, L, G, C are primary line constant

Since the voltage & current of a transmission line vary with position z (and time t) we have no characterized it by a distributed circuit model. Consider an infinitesimal line of length Δz , the current set up magnetic field between the conductors (by ampere's law) causing magnetic flux. When current are time varying. So the magnetic flux & a voltage variation along the conductor emf is included in an attempt to derive the current oppositely.

$$V = L \frac{di}{dt}$$

Q.3

Solution:-

As we know that

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}, \quad f = 1 \text{ GHz}$$

In this case $\Gamma = 0$

$$Z_a = 50$$

$$Z_b = jZ_0 \cot \beta L$$

$$Z_{\text{eqt}} = Z_a \parallel Z_b = 50$$

$$Z_b = \alpha$$

Now

$$Z_b = -jZ_0 \cot \frac{2\pi}{\lambda} \cdot L$$

$$Z_b = -j50 \cot \frac{2\pi}{\lambda} \cdot L$$

$$\cot \frac{2\pi}{\lambda} \cdot L = \alpha$$

$$\text{i.e. } L = \lambda/2$$

$$\text{cut } \frac{2\pi}{\lambda} = \frac{\pi}{2} = \pi$$

Now

$$l = \lambda/2$$

$$v_p = 2 \times 10^8$$

$$w = 2 \times 10^8$$

B

$$\frac{2\pi f \times \lambda}{2\pi} = 2 \times 10^8$$

At $f = 1 \text{ GHz}$

$$\lambda = \frac{2 \times 10^8}{1 \times 10^9}$$

$$\lambda = 0.2 \text{ m}$$


Now

$$L = \lambda/2$$



$$= 0.2/2$$

$$L = 0.1 \text{ m} \rightarrow \text{Ans}$$

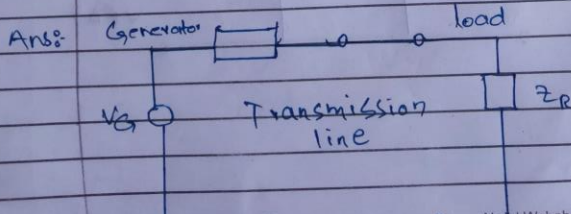(b) Define transmission line equation & describe what it says.



Transmission time effect

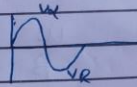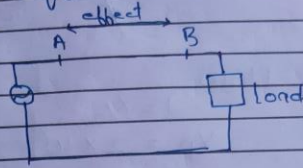

$$t_r = \frac{D}{v}$$

$$T \gg t_r$$


$$T \gg \frac{D}{v}$$

$$V_f \gg \frac{P}{V}$$


$$\frac{v}{f} \gg l$$

$$\lambda \gg l$$

Primary constant of transmission line

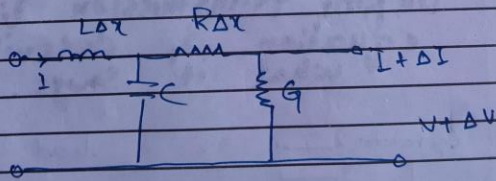

Transmission line equation

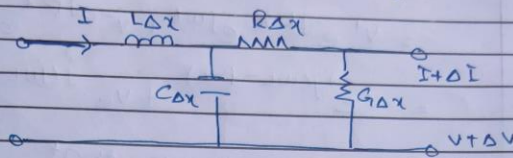

$$\Delta I = -(G\Delta x + j\omega C\Delta x)V$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C)V$$

$$\frac{dI}{dx} = -(G + j\omega C)V \quad \text{---(1)}$$

$$\Delta V = -(R\Delta x + j\omega L\Delta x)I$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = -(R + j\omega L)I$$

$$\frac{dV}{dx} = -(R + j\omega L)I \quad \text{---(2)}$$

After diff

$$\frac{d^2V}{dx^2} = -(R + j\omega L) \frac{dI}{dx}$$

$$\frac{d^2V}{dx^2} = (R + j\omega L)(G + j\omega C)V$$

$$\frac{d^2V}{dx^2} = V^2 \gamma$$

$$\begin{aligned}
 v(x,t) &= (V^+ e^{-\gamma x} + V^- e^{+\gamma x}) e^{j\omega t} \\
 &= V^+ e^{-j\beta x} e^{j\omega t} + V^- e^{+j\beta x} e^{j\omega t} \\
 &= V^+ e^{+j(\omega t - \beta x)} + V^- e^{-j(\omega t + \beta x)}
 \end{aligned}$$

Now we know that

$$\vec{E} = E_0 e^{-\alpha z} \cos(\omega t - \beta z) \hat{x}$$


Final equation

$$v(x,t) = V^+ \cos(\omega t - \beta x) + V^- \cos(\omega t + \beta x)$$

Transmission of a signal from a generator to a load. A transmission line is a part of the circuit that provides the direct link b/w generator & load. Transmission line can be realized in a number of ways.

Common examples are parallel wire line & the coaxial cables.

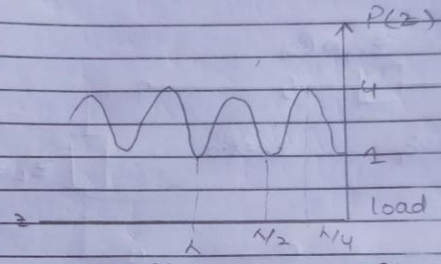Q3 (a) Voltage standing wave pattern in a lossless transmission line with characteristic impedance Z_0 & resistive load



Q4 The reflection coefficient
 (a) -0.6 (b) -1 (c) 0.6 (d) 0.2

Solution


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= \frac{12.5 - 50}{12.5 + 50}$$

$$= \frac{-37.5}{62.5}$$

$$\Gamma = 0.6 \text{ Ans}$$

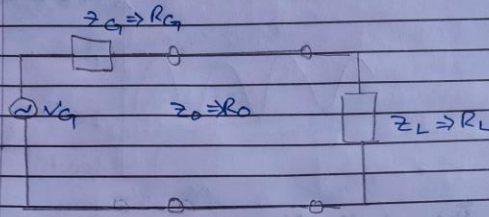36 Explain two impedance matching technique.



$$Z_L = Z_G$$

$$Z_G \neq R_G$$

$$I = I_0$$

$$Z_{in} = Z_0^2 \frac{Z_L}{Z_0}$$

$$R_{in} = R_0^2 \frac{R_L}{R_0} = R_G$$

$$\left(\frac{R_G}{R_0} \right) = \left(\frac{R_L}{R_0} \right)$$

$$R_0 = \sqrt{R_L R_G}$$

⇒ The operation of an antenna systems over a frequency range is not completely depend upon the frequency response of the antenna element itself but rather on the frequency characteristics.

of the transmission line antenna element combination.

→ In the practice the characteristic impedance of the transmission line is usually real whereas that of the antenna element is complex. Also the variation of each as function of frequency is not the same.