

## Department of Electrical Engineering

### Assignment

Date: 14/04/2020

#### Course Details

Course Title: Electronic Circuit Design  
 Instructor: Engr.Mujtaba Ihsan Sir

Module: 04  
 Total Marks: 30


#### Student Details

Name: Asad shoib khalil


Student ID: 13095

|    |     |   |             |
|----|-----|---|-------------|
| Q1 | (a) | <p><b>Explain</b> the drain characteristic curve of D-MOSFET given below.</p> <div style="text-align: center;"> </div>  | Marks<br>07 |
|    |     |   | CLO 1       |
|    | (b) | <p><b>Sketch</b> the hybrid model and write equations for the transistor in common emitter configuration.</p>   | Marks<br>06 |
|    |     |   | CLO 1       |
| Q2 |     | <p>A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. <b>Evaluate</b> the CMRR &amp; express it in decibels.</p>            | Marks<br>05 |
|    |     |   | CLO 2       |
| Q3 | (a) | <p><b>Explain</b> the concept behind negative feedback in operational amplifiers.</p>   | Marks<br>06 |
|    | (b) | <p><b>State</b> the following statement as <b>True</b> or <b>False</b> and also give the reason for your answer:<br/>                     "The output of a summing amplifier is positive"</p> | Marks<br>06 |
|    |     |   | CLO 2       |

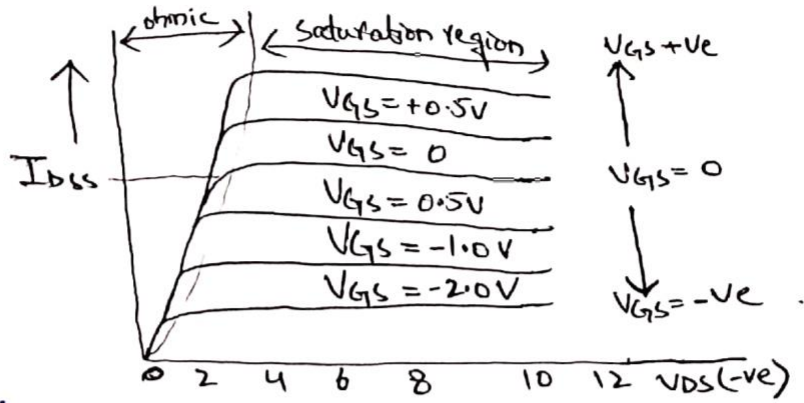
Q1 (a) :- Explain the drain characteristic curve of D-MOSFET given below



ANSWER

 

N-channel

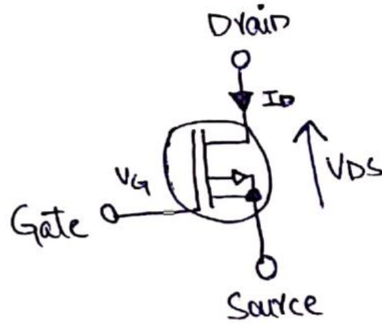

P-channel.


The characteristic mainly gives the relationship b/w drain-source voltage ( $V_{DS}$ ) & Drain current ( $I_D$ ). The small voltage at the gate controls the current flow through the channel. The channel b/w drain & source acts as a good conductor with zero bias voltage at gate terminal. The channel width & drain current increases if the gate voltage is positive & these two decreases if the gate voltage is negative.

Question # 1 } Sketch the hybrid model & write equations  
 Part (b) :- } for the transistor in common emitter configuration.

Answer:- In common emitter transistor configuration the input signal is applied b/w the base & emitter terminals of the transistor & output appears b/w the collector & emitter terminals. The input voltage ( $V_{be}$ ) & output current ( $i_c$ ) are given.

$$V_{be} = h_{ie} \cdot i_b + h_{re} \cdot V_c$$
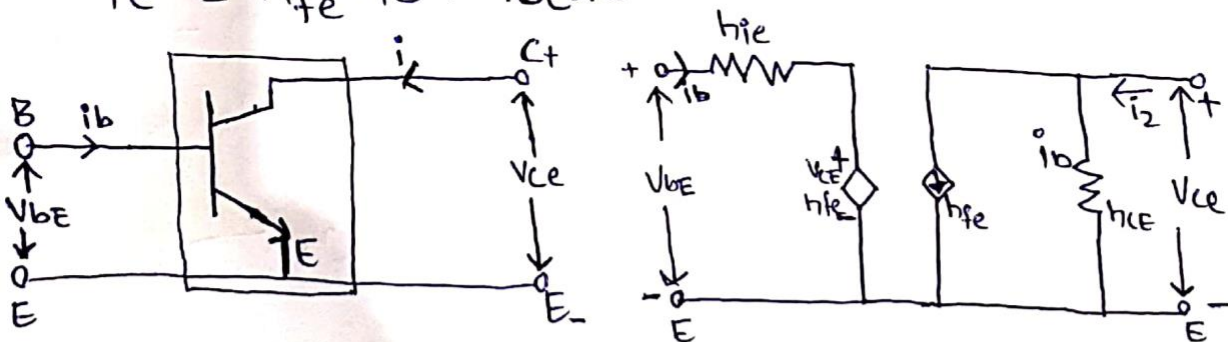
$$i_c = h_{fe} \cdot i_b + h_{oe} \cdot V_c$$



where,  $h_{ie} = (\partial i_1 / \partial i_B) V_c = (\partial V_B / \partial i_B) V_c = (\Delta V_B / \Delta i_B) V_c = (V_b / i_b) V_c$

$h_{re} = (\partial i_1 / \partial V_c) I_B = (\partial V_B / \partial V_c) I_B = (\Delta V_B / \Delta V_c) I_B = (V_b / V_c) I_B$

$h_{fe} = (\partial i_2 / \partial i_B) V_c = (\partial i_c / \partial i_B) V_c = (\Delta i_c / \Delta i_B) V_c = (i_c / i_b) V_c$

$h_{oe} = (\partial i_2 / \partial V_c) I_B = (\partial i_c / \partial V_c) I_B = (\Delta i_c / \Delta V_c) I_B = (i_c / V_c) I_B$

Question #2:- A certain operational amplifier has a common mode gain of 0.6 & an open loop differential voltage gain of 40,000.  
Evaluate the CMRR & express it in decibels.

Solution:- Given data .

$$A_{ol} = 400,000$$

$$A_{cm} = 0.6$$

Required

$$\rightarrow \text{CMRR} = ?$$

$$\text{Formula: As } \text{CMRR} = \frac{A_{ol}}{A_{cm}}$$

$$\rightarrow \text{Therefore } \text{CMRR} = \frac{400,000}{0.6} \\ = \boxed{666,666.666}$$

$\rightarrow$  CMRR in describe:

$\rightarrow$  Formula


$$\text{CMRR} = 20 \log (A_{ol}/A_{cm}) \\ = 20 \log (666,666.666)$$

$$= \boxed{116.478 \text{ dB}}$$

Answer.

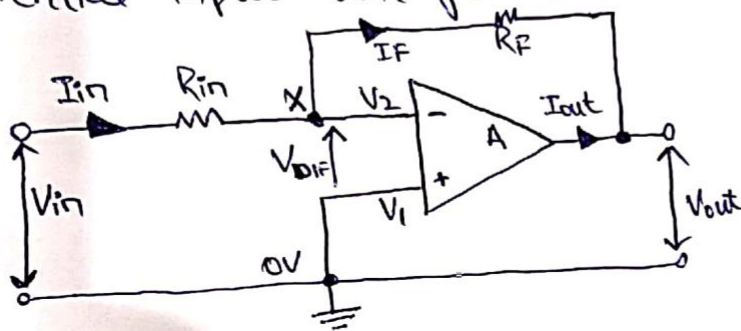Question# 3  
part (a) :- Explain the concept behind negative feedback in operational amplifiers.

Answer :- Negative feedback is the process of "feeding back" a fraction of the output signal back to the input, but to make the feedback negative, we must feed it back to the negative or "inverting input" terminal of the op-amp using an external feedback resistor called  $R_f$ . This feedback connection b/w the output & the inverting input terminal forces the differential input voltage towards zero.



Question #3 :- State the following statement as True or False  
part (b) } & also give the reason for your answer.

Answer :- The answer is "TRUE"

When the summing point is connected to the non-inverting input of the op-amp, it will produce the positive sum of the input voltages. This allows the output voltage to be easily calculated if more input resistors are connected to the amplifier inverting input terminal.

