



Department of Electrical Engineering

Subject: Power Electronics

Spring: 2020

Date: 19/04/2020


Instr: Sir, Shayan Khan

ID: 13045

Student Name : Muhammad Numan Asad

Q1	(a) An appliance circuit has a R-L connected in series with a diode. After some time, modification is done to the circuit and a free-wheeling diode added in parallel to the R-L. Will it have any impact on the performance and output of the circuit. Back your answer with before & after data, facts and figures. Does adding a free-wheeling diode in parallel to a R-C circuit have the same effect, different effect or no effect.	Marks, 7 CLO 1
----	---	-------------------



Ans:

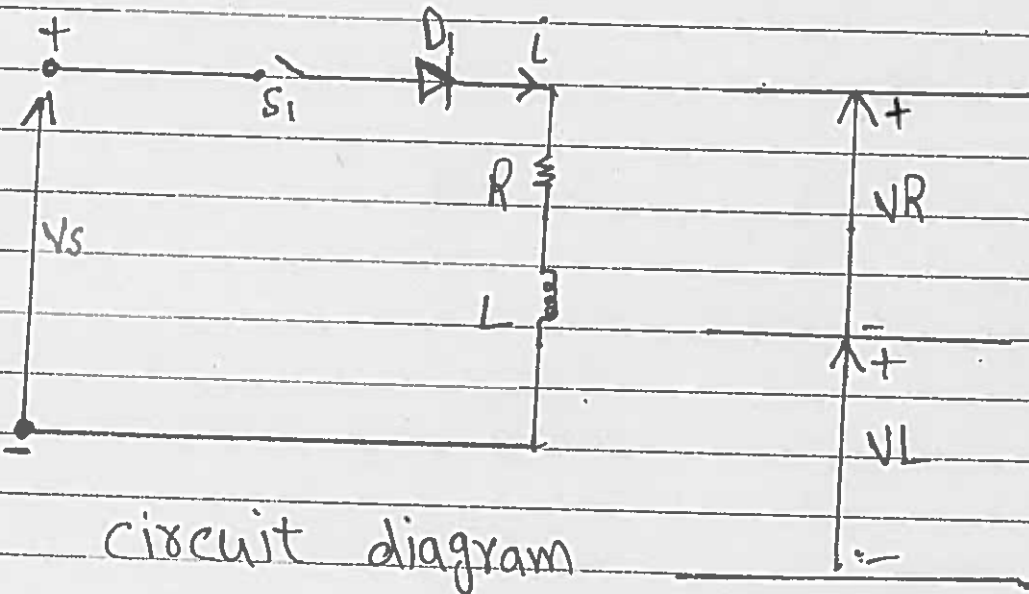

circuit diagram

The circuit consists of resistor and inductor connected in series. If we use one fan in the circuit. As we know that AC voltage is always up and down time by time if the voltage is suddenly high then the circuit will be

Page 2

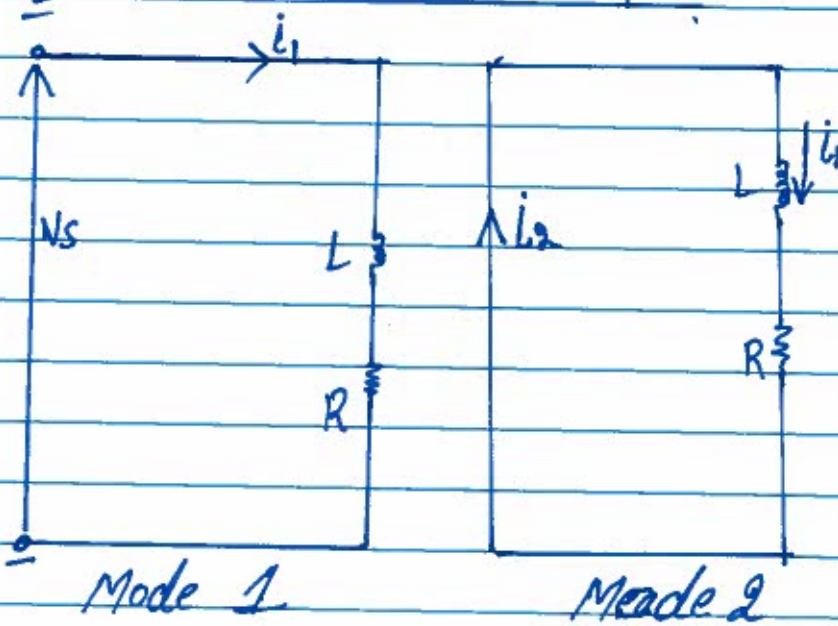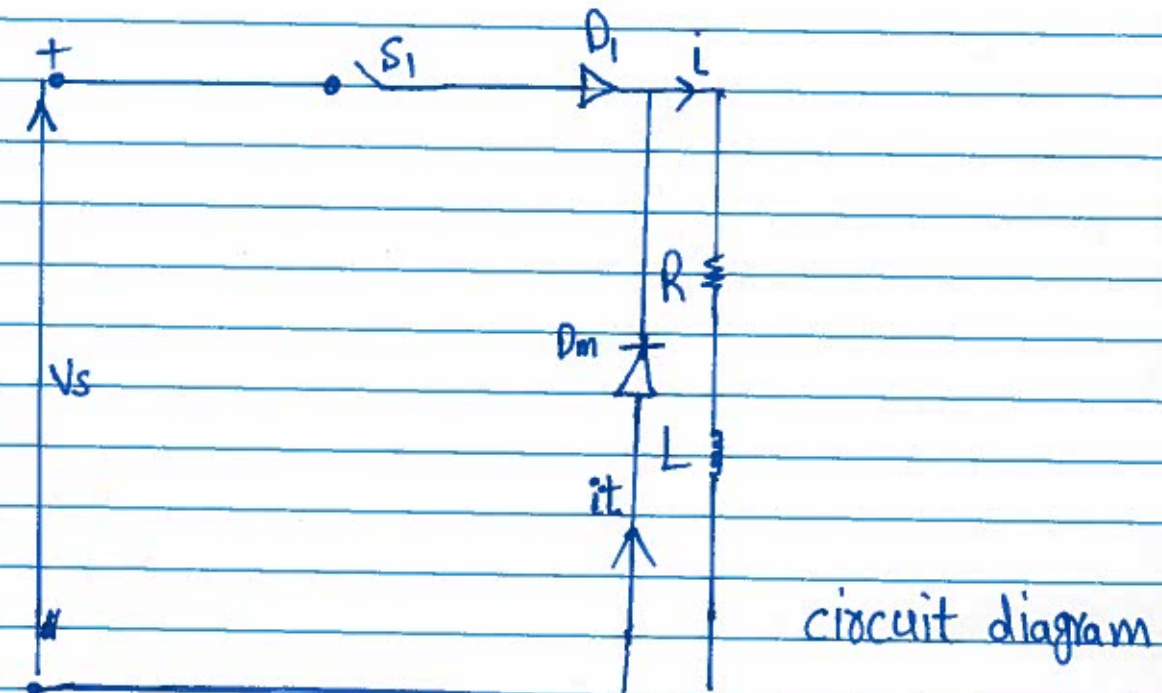

Page 3

damaged soon because there is no safety component in the circuit to control the high voltage the circuit will be damaged so the circuit is not safe. The circuit B consists of resistor and inductor connected in series and free wheeling diode is placed in parallel to RL. Free wheeling diode are basically connected across inductive coil to prevent from voltage spikes in case of power getting turned off to the device if the voltage is suddenly high i.e. (440). The voltage is divided into two parts half voltage moves towards free wheeling diode and half moves towards RL. So the circuit remains safe from damaging.

$$i_1(t) = \frac{V_s}{R} (1 - e^{-tR/L})$$

all switch is open at $t = t_1$

Page 4


$$i_1 = i_1(t=t_1) = \frac{V_s}{R} (1 - e^{-tR/L})$$

The switch is opened and the load current starts to flow through the free wheeling diode D_m .

$$0 = L \frac{di_2}{dt} + Ri_2$$

initial condition $i_2(t) = 0 - i_1$

$$i_2(t) = i_1 e^{-tR/L}$$

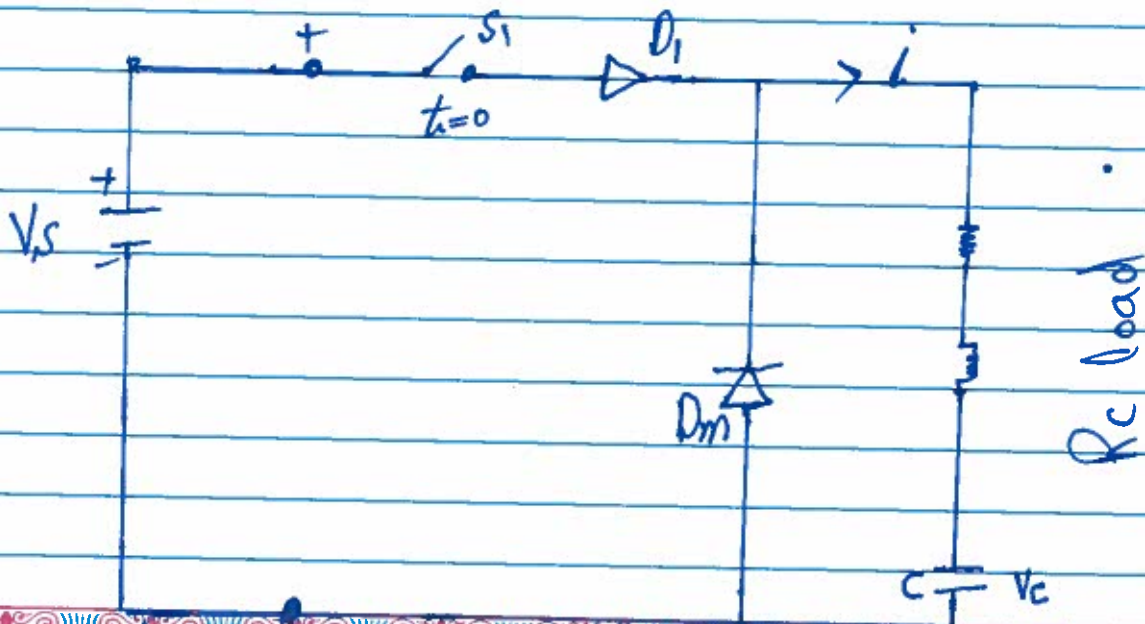

Page 5

$$\frac{di}{dt} = \frac{V_s}{L} e^{-tR/L}$$
$$\text{at } t=0 \quad = \frac{di}{dt} \Big|_{t=0} = \frac{V_s}{L}$$


$$V_L(t) = L \frac{di}{dt} = V_s e^{-tR/L}$$

LLR

$$V_s = V_R + V_L = V_R + L \int_{-t_0}^t i dt + V_L(t) = 0$$

$$V_R = Ri$$

The inductor has property to store energy. In AC current during positive half cycle the inductor stores energy. In negative half cycle in free-wheeling diode because forward bias so the current will flow through diode.

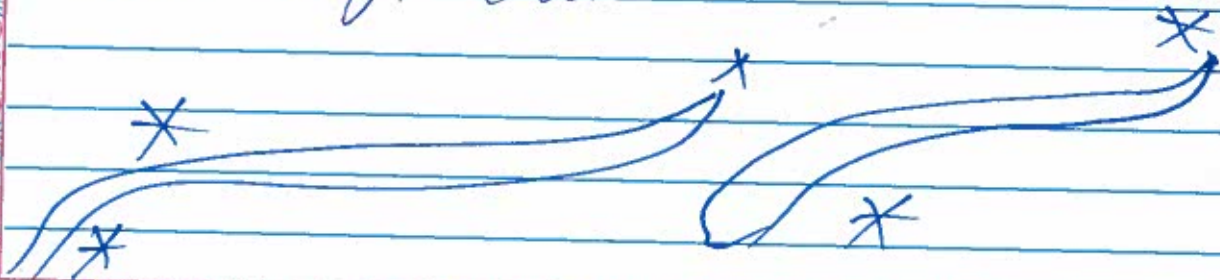

Page 6

Q 1(B)

- (b) In the above appliance (Q2.a) if the P.Mosfet is replaced with a Silicon Controlled Rectifier what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.

Marks 5

CLO 1

Solution:

Give data

Student ID = 13045

$$V_T = 3V$$

$$V_{DS} = 45$$

*

Required data

$$V_{GS} = ?$$

Solution:- As we know that

$$V_{DS} = V_{GS} - V_T$$

$$V_{GS} = V_{DS} + V_T \Rightarrow 45 + 3$$

$$V_{GS} = 48V$$

Ans:

Page 7

Q2 (a) A Power Electronics appliance of 500W, 220V, 500KHz rating is using a Power Mosfet for switching purpose. If the P.Mosfet is replaced with a Power Bipolar Junction Transistor what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.

Marks 5

CLO 1

Solution:



BJT has higher switching losses but lower conduction losses while p-mosfet has lower switching losses and higher conduction losses.

BJT is a current controlled device in BJT the operation is controlled by base current. BJT has negative temperature coefficient so current sharing resistor are mandatory. BJT suffer from secondary breakdown issue while p-mosfet have no breakdown issue.

Losses in BJT are low as compared to p-mosfet have higher power application while p-mosfet are used in low power application. BJT have high voltage and current rating p-mosfet have less voltage and current rating. There is saturation region in BJT. There is not ohmic

Shaiq Notes

Page 8

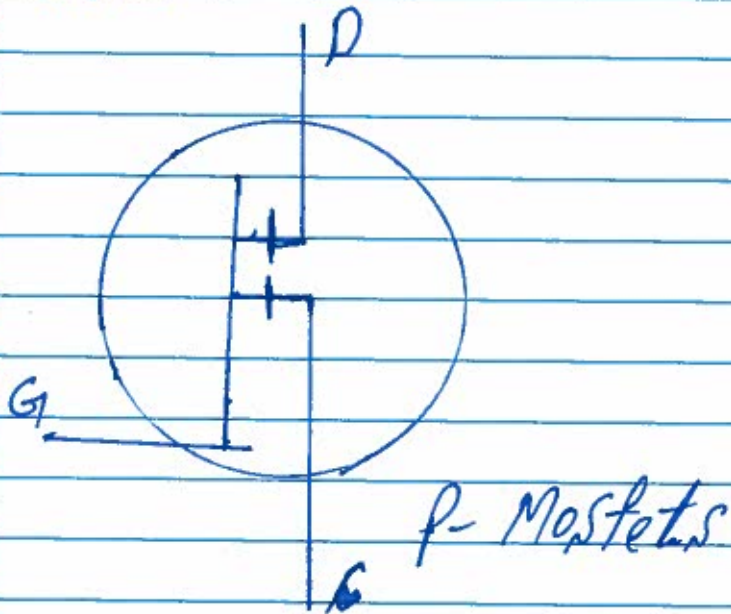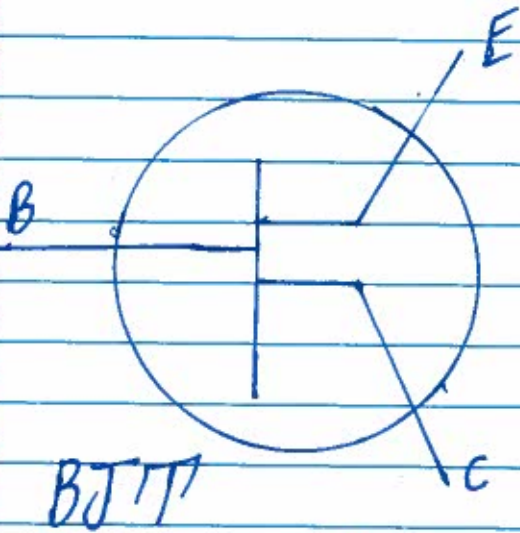

Page 9

region in BJT.


BJT have lower switching frequency than MOSFET. BJT is ON in saturation region, so paralleling of BJT is difficult.

BJT is slower than p-MOSFET BJT device switching is slower than p-mosfet.

BJT is used in switching power supply SMPS.

BJT are more noisy than

p-mosfet so it is less suitable for signal processing application or for voltage amplifiers. BJT is difficult manufacture than MOSFET.

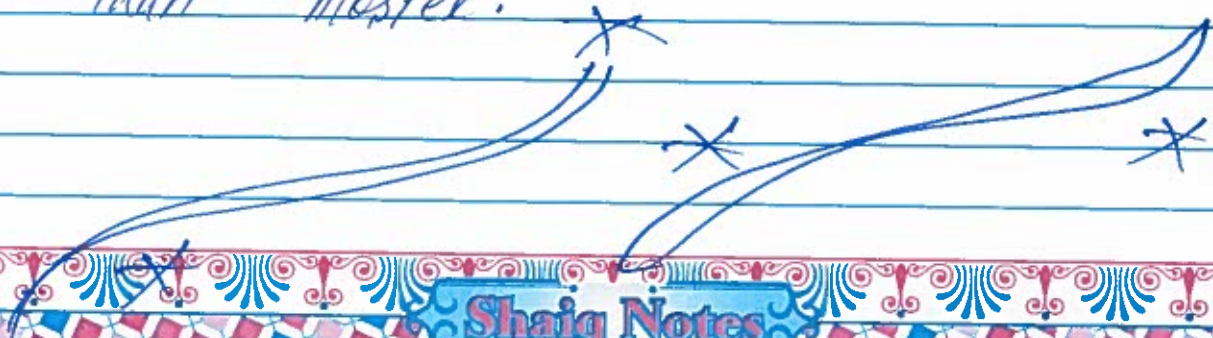

Page 10

Q2 Part (B):

A Power Mosfet is connected in a circuit.
The Drain to Source voltage, V_{DS} = (Last 2 digits of your student ID) V and
Threshold Voltage, V_T = (Last 1 digits of your student ID) V.
What is the minimum Gate to Drain Voltage, V_{GS} required for the P.Mosfet to be
in saturation mood.

Marks 3

CLO 1

Ans: Silicon controlled rectifier:-

SCR is a semiconductor switch that is used to control switch amount of power with small signal input it is turned off by the zero current through it naturally becoming zero.

SCR cannot be used for amplification.

The SCR is an unidirectional semiconductor which allows current SCR to flow in one



Page 11

direction (act as a switch).

SCR control high voltage and power.
The SCR require a gate signal to turn it "ON" and once "ON" its function like a rectifying diode. There are three major part of SCR. Gate control flow of current (Anode and cathode)

Anode positive and cathode negative terminal.

The SCR works by applying positive current or application to gate in order to raise unity.

SCR have low frequency ($400-500\text{Hz}$) than p-mosfet (100kHz)

SCR is current controlled need signal pulse to turn ON.


SCR is a minority carrier device.
SCR is current controlled device.
SCR have negative temperature coefficient.

So due to all these facts p-mosfet is better than SCR.

Page 12

The efficiency of sch is higher
of sch is less better

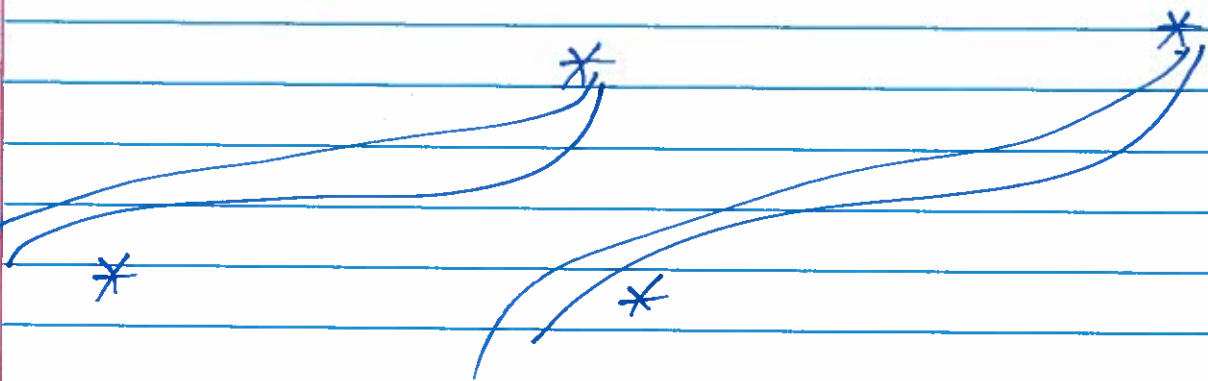
than the p. Mastet more losses
occur in sch as compared
to p. Mastet.



Q3 (a) The bipolar transistor in the Figure below is specified to have β_F in the range of 8 to 40.
 The load resistance, $R_C =$ (Last 2 digits of your student ID) Ω .
 The dc supply voltage, $V_{CC} =$ (Last 3 digits of your student ID) V and the input voltage to the base circuit, $V_B = 10$ V.
 If $V_{CE} =$ (First digits of your student ID) V and $V_{BE} = 1.5$ V, find
 (a) The mode of operation of the transistor
 (b) the value of R_B that results in saturation with an ODF of 5,
 (c) the β_{forced} ,
 (d) the power loss, P_T in the transistor.

Marks
10

CLO 1

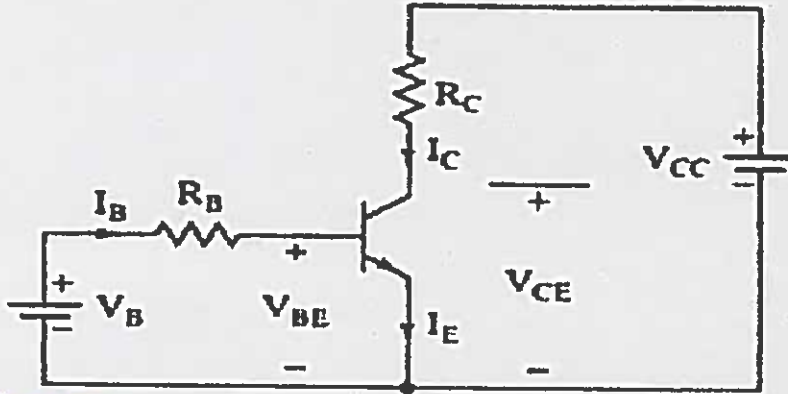

~~Solution:~~
 Solution:

Give date

Student ID = 13045

$R_C = 45 \Omega$

$V_{CC} = 0.45$

$V_B = 10V$

$V_{CS} = 6.0V$

$\beta_{min} = 8$, $\beta_{max} = 40$

ODE = 5

$V_B = 10V$

If V_{CE} and $V_{BE} = 1.5V$

Solution: As we know that

Formula

(A)

$$I_{CS} = \frac{V_{CC} - V_{CS}}{R_C}$$

$$\frac{0.45 - 6}{45} = 0.866A$$

$$I_{CS} = 0.866A$$

Page 14

Base current:

$$I_{BS} = \frac{I_{CS}}{\beta_{min}} = \frac{0.866}{8}$$

$$I_{BS} = 0.1083 \text{ A}$$

$$ODF = \frac{I_B}{I_{BS}}$$

$$I_B = ODF \times I_{BS}$$

$$I_B = 5 \times 0.1083 = 0.54 \text{ A}$$

$$I_B = 0.54 \text{ A}$$

(B) Value of R_B

$$I_B = \frac{V_B - V_{BS}}{R_B}$$

$$0.54 = \frac{10 - 1.5}{R_B} \Rightarrow 7R_B = 10 - 1.5$$

$$R_B = \frac{10 - 1.5}{0.54} = 15.74$$

Page 15

$$R_B = 15.740 \text{ A}$$

(c)

$$B_{\text{forced}} = \frac{I_{C5}}{I_B} = \frac{0.866}{0.54}$$

$$B_{\text{forced}} = 1.603$$

(d) Power Loss P_T

$$P_T = V_{BE} I_B + V_{CE} I_C$$

$$P_T = (1.5)(0.54) + (6.0) \text{ ~~(1.5)~~ (0.866)}$$

$$= 0.81 + 5.196$$

$$P_T = 6.006 \text{ W} \rightarrow \text{Ans}$$

$$P_T = 6.006 \text{ W Ans}$$

The END: