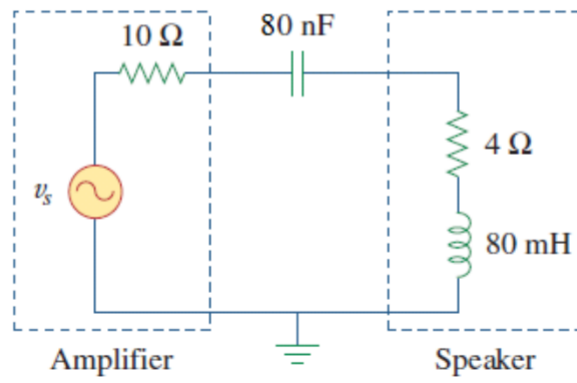


(a)



Q1.	Assume that a 2000-kW turbine-generator of 0.85 power factor operates at the rated load. An additional load of 300 kW at 0.8 power factor is added. What kVAR of capacitors is required to operate the turbine generator but keep it from being overloaded?	Marks 10
		CLO 03

Sol:-

Given data:-

$$P_1 = 2000 \text{ kW}, \quad \cos \alpha_1 = 0.85$$

$$S_1 = \frac{P_1}{\cos \alpha_1} = 2352.94 \text{ kVA}$$

$$Q_1 = \sqrt{S_1^2 - P_1^2} = 129.49 \text{ kVAR}$$

Additional load

$$P_{\text{add}} = 300 \text{ kW} \quad \& \quad \cos \alpha_{\text{add}} = 0.8$$

$$S_{\text{add}} = \frac{P_{\text{add}}}{\cos \alpha_{\text{add}}} = 375 \text{ kVA}$$

$$Q_{\text{add}} = \sqrt{S_{\text{add}}^2 - P_{\text{add}}^2} = 295 \text{ kVAR}$$

Total load

$$P_2 = P_1 + P_{\text{add}} = 2300 \text{ kW}$$

$$Q_2 = Q_1 + Q_{\text{add}} = 1764.49 \text{ kVAR}$$

$$S_2 = S_1 + S_{\text{add}} = 2727.94 \text{ kVA}$$

turbine generator from  
being overloaded, total complex power  
has to be equal to the complex  
power of a rated load.

$$S_2' = S_1$$

We have to add capacitor  
with reactive power  $Q_c$

$$S_2 + jQ_c = S_1$$

$$P_2 + jQ_2 + jQ_c = S_1$$

$$Q_2' = \sqrt{S_1^2 - P_2^2} = 498.37 \text{ kVAR} \text{ where}$$

$Q_2'$  is  $Q_2 + Q_c$

$$Q_c = Q_2' - Q_2 = -968.18 \text{ kVAR}$$

we need capacitor with  
reactive power of 968.18 kVAR

Q2.

A balanced  $abc$  sequence, one line voltage of a balanced Y-connected source is  $V_{AB} = 180 \angle -20^\circ$  V. If the source is connected to a  $\Delta$ -connected load of  $20 \angle 40^\circ \Omega$ , find the phase and line currents.

Marks 10

CLO 02

line voltage =  $V_{AB} = 180 \angle -20^\circ$  V

$Z_{\Delta} = 20 \angle 40^\circ \Omega$

$V_L = \sqrt{3} V_P \angle 30^\circ \Rightarrow V_P = \frac{V_L}{\sqrt{3} \angle 30^\circ}$

Phase voltage

$$V_{an} = \frac{180 \angle -20^\circ}{\sqrt{3}} \quad \angle = 30^\circ = 103.9 \angle -50^\circ$$

$$Z_Y = \frac{Z_{\Delta}}{3} = \frac{20 \angle 40^\circ}{3} = 6.67 \angle 40^\circ \Omega$$

Line current

$$\bar{I}_a = \frac{V_{an}}{Z_a/3} = \frac{103.9 \angle -50^\circ}{6.67 \angle 40^\circ}$$

$$\bar{I}_a = 15.57 \angle -90^\circ \text{ A}$$

$$\bar{I}_b = \bar{I}_a \angle -120^\circ = 15.57 \angle +150^\circ \text{ A}$$


$$\bar{I}_c = \bar{I}_a \angle +120^\circ = 15.57 \angle 30^\circ \text{ A}$$

Phase current

$$\bar{I}_{AB} = \frac{15.57 \angle -90^\circ}{\sqrt{3}} \angle 30^\circ = 9 \angle -60^\circ \text{ A}$$

$$\bar{I}_{BC} = \bar{I}_{AB} \angle -120^\circ = 9 \angle -180^\circ \text{ A}$$
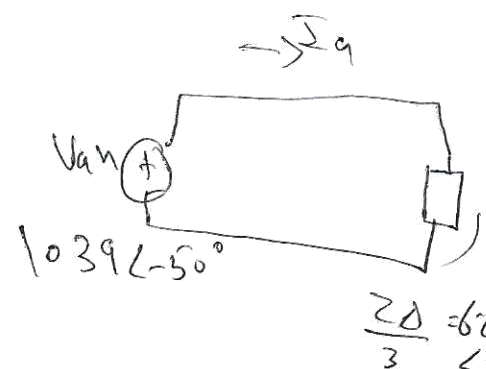
$$\bar{I}_{CA} = \bar{I}_{AB} \angle +120^\circ = 9 \angle 60^\circ \text{ A}$$



Q3.	Consider a load with value of, $V_{rms} = 110 \angle 85^\circ \text{ V}$ , $I_{rms} = 0.4 \angle 15^\circ \text{ A}$ . Calculate the following: a) The complex and apparent powers b) The real and reactive powers, and c) The power factor and the load impedance.	Marks 10 CLO 01
-----	--	--------------------

Q3

Sol:-  $V_{rms} = 110 \angle 85^\circ \text{ V}$   
 $I_{rms} = 0.4 \angle 15^\circ \text{ A}$

Step 2

a) complex power is

$$S = V_{rms} I_{rms}$$

$$S = (110 \angle 85^\circ)(0.4 \angle -15^\circ)$$

$$S = 110 \times 0.4 \angle (85^\circ - 15^\circ)$$

$$S = 44 \angle 70^\circ \text{ VA}$$

apparent power is

$$S = |S|$$

$$S = 44 \text{ VA}$$

Step 3

Express in complex power in Rectangular form

$$S = 44 \angle 70^\circ$$

$$S = 44 [\cos(70^\circ) + j \sin(70^\circ)]$$

$$S = 44 [0.3420 + j 0.9397]$$

~~$$S = 15.05 + j41.33$$~~

since  $S = P + jQ$

Real Power is

$$P = 15.05 \text{ W}$$

reactive power is

$$Q = 41.35 \text{ VAR}$$

Step 4 is The power factor is

$$P_f = \cos(70^\circ)$$

$$P_f = 0.342 \text{ (lagging)}$$

power factor is lagging as the reactive power is five

The load impedance is

$$Z = \frac{V}{I}$$

$$V = \sqrt{2} V_{rms}$$

$$I = \sqrt{2} I_{rms}$$

$$Z = \frac{170 \angle 85^\circ}{0.4 \angle 15^\circ}$$

$$Z = 275 \angle 70^\circ \Omega$$

$$Z = 275 [\cos(70^\circ) + j \sin(70^\circ)]$$

$$Z = 275 (0.342 + j0.9337)$$

$$Z = (94.05 + j258.4) \Omega$$


Step 5

Q4.

Apply Laplace transform and calculate the output voltage  $v_o(t)$  in the circuit of figure below:

Marks 10

CLO 01

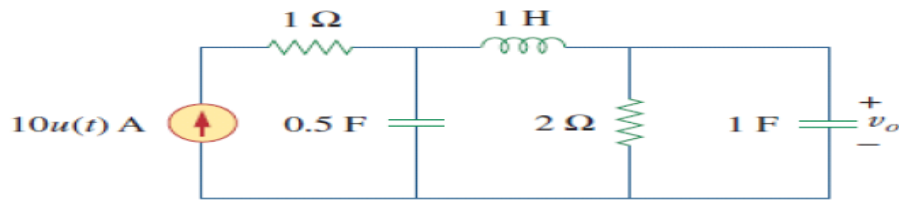

Figure

1. Since there is nothing said about the initial charge on the inductor and the capacitor before  $t=0$  we assume that the initial condition on both of them is 0.

2) Converting the element of the circuit from time domain to the s-domain.

$$1\ \Omega \Rightarrow 1\ \Omega$$


$$2\ \Omega \Rightarrow 2\ \Omega$$

$$1\text{ H} \rightarrow s$$

$$1\text{ F} \rightarrow \frac{1}{s}$$

$$0.5\text{ F} \Rightarrow \frac{2}{s}$$
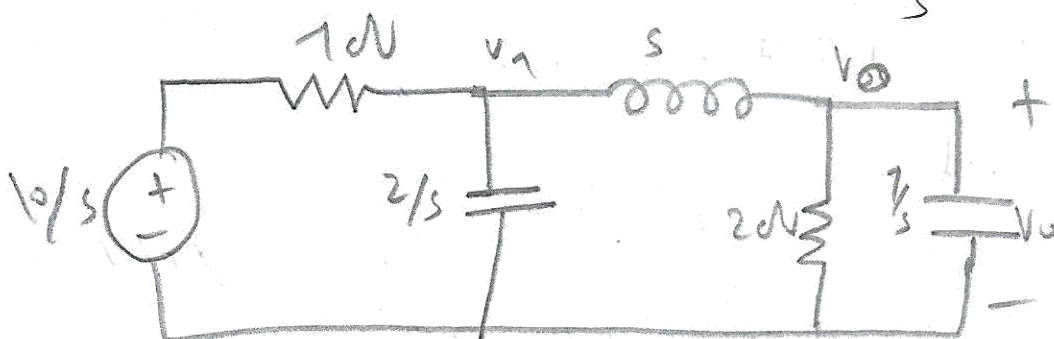
$$10u(t)\text{ V} \Rightarrow \frac{10}{s}$$





to the  $s$  domain will look like  
the one show in the above fig

5. At node 1, applying KCL &  
ohm's law gives .

$$\frac{V_1}{2/s} + \frac{V_1 - V_0}{s} + \frac{V_1 - \frac{10}{s}}{1} = 0$$

Multiplying by  $2s$  and simplifying

$$(s^2 + 2s + 2)V_1 - 2V_0 = 20$$

Applying KCL to node 0

$$\frac{V_0}{2} + \frac{V_0 - V_1}{s} + \frac{V_0}{1/s} = 0$$

Multiplying by  $s$  & simplifying

$$V_1 = (s^2 + 0.5s + 1)V_0$$

Substituting Eq (2) in Eq 1 yield

$$(s^2 + 2s + 2)(s^2 + 0.5s + 1)V_0 - 2V_0 = 20$$

$$V_0 = \frac{20}{s(s^3 + 2.5s^2 + 4s + 3)}$$

$$= \frac{20}{s(s + 1.2306)(s^2 + 1.2694s + 2.4377)}$$

Now break down  $V_0(s)$

$$\frac{20}{s(s + 1.2306)(s^2 + 1.2694s + 2.4377)} = \frac{A}{s} + \frac{B}{s + 1.2306} + \frac{Cs + D}{s^2 + 1.2694s + 2.4377}$$

By residue method

$$A = (s) \left( \frac{20}{s(s + 1.2306)(s^2 + 1.2694s + 2.4377)} \right)_{s=0}$$

$$= 6.667$$

$$B = (s + 1.2306) \left( \frac{20}{s(s + 1.2306)(s^2 + 1.2694s + 2.4377)} \right)$$

$$= -6.8$$

By algebraic method find C&D

$$20 = A(s+1.2306)(s^2 + 7.2694s + 2.4377) + B(s)(s^2 + 7.2694s + 2.4377) + (C+sD)(s)(s+1.2306)$$

$$20 = 6.667(s+1.2306)(s^2 + 7.2694s + 2.4377) - 6.8(s)(s^2 + 7.2694s + 2.4377) + (C+sD)(s)(s+1.2306)$$

$s^3$

Coefficient

$$0 = 6.667 - 6.8 + C = 0.133$$

$s^2$

$$0 = -8.199 + D = -8.199$$

hence

$$V_0(s) = \frac{6.667}{s} + \frac{0.133s - 8.199}{s^2 + 7.2694s + 2.4377}$$

$$V_0(s) = \frac{6.667}{s} = \frac{6.8}{s+1.2306} + \frac{0.133s - 8.199}{s^2 + 1.2694s + 2.4377}$$

$$= \frac{6.667}{s} = \frac{6.8}{s+1.2306} + \frac{0.133(s+0.6347)}{(s+0.6347)^2 + (7.4265)^2}$$

taking inverse Laplace  $\frac{8.2834}{(s+0.6347)^2 + (7.4265)^2}$

$$V_0(t) = \mathcal{L}^{-1}\{V_0(s)\}$$

$$= \mathcal{L}^{-1}\left[\frac{6.667}{s}\right] - \mathcal{L}^{-1}\left[\frac{6.8}{s+1.2306}\right] + \mathcal{L}^{-1}\left[\frac{0.133(s+0.6347)}{(s+0.6347)^2 + (7.4265)^2}\right] - \mathcal{L}^{-1}\left[\frac{8.2834}{(s+0.6347)^2 + (7.4265)^2}\right]$$

$$= 6.667u(t) - 6.8e^{-1.2306t}u(t) + 0.133e^{-0.6347t}\cos(7.4265t)u(t) - 5.80608e^{-0.6347t}\sin(7.4265t)u(t) \text{ V}$$

Result

~~$$V_0(t) = 6.6667 - 6.8e^{-1.2306t} + 0.133e^{-0.6347t}\cos(7.4265t)$$~~

Result

$$v_o(t) = \left( 6.667 - 6.8e^{-7.2306t} + e^{-0.6347t} \left( 0.133 \cos(1.4965t) - 5.8068 \sin(1.4965t) \right) \right) u(t) \text{ (V)}$$

Q5.

For the circuit given in figure below, the speaker works as load while the amplifier and the capacitor act as the source. To block dc current from an amplifier, a coupling capacitor of 80 nF is used ( see figures below). Calculate the following:

Marks 10

CLO 03

- a) At what frequency is maximum power transfer to the speaker?  
 b) If  $V_s = 5 \text{ V}_{\text{rms}}$ , how much power is delivered to the speaker at that

Q5) Source impedance  $Z_b = R_s - jX_c$   
 Load impedance  $Z_L = R_L + jX_L$   
 for maximum load transfer

$$Z_L = Z_s \rightarrow R_s = R_L, X_c = X_L$$

$$X_c = X_L \rightarrow \omega L = \frac{1}{\omega C} \rightarrow \omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

$$f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(80 \times 10^{-3}) (40 \times 10^{-9})}}$$

$$= 2.81415 \text{ Hz}$$

$$b) P_L = \left( \frac{V_s}{(10+4)} \right)^2 \times 4 = \left( \frac{4.0}{14} \right)^2 \times 4 = 437.8 \text{ mW}$$

since  $V_s$  is in  $\text{V}_{\text{rms}}$