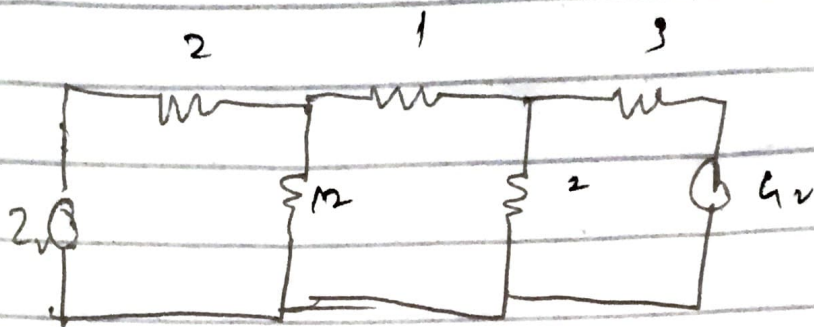


Name = Hassam Khom .

ID = 6620


submit to = Engr. Waleed Jan

# Question No # 1



sol:  $\rightarrow$

Using Superposition theorem.

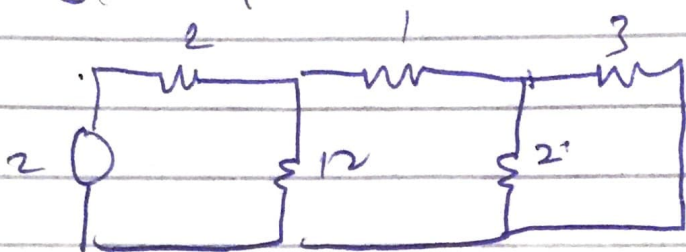

VARS  $\Rightarrow$

using Nodal analysis

$$\frac{V_1 - 2}{2} + \frac{V_1}{12} + \frac{V_1 - V_2}{1} = 0$$

$$6V_1 - 12 + V_1 + 12V_1 - 12V_2 = 0$$

$$19V_1 - 12V_2 = 12 \rightarrow (1)$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2}{3} = 0$$

$$6V_2 - 6V_1 + 3V_2 + 2V_2 = 0$$

$$-6V_1 + 11V_2 = 0$$

$$V_2 = \frac{6V_1}{11} \rightarrow (2)$$

put in (1)

$$19V_1 - 12 \left[ \frac{6V_1}{11} \right] = 12$$


$$V_1 = 0.9635V$$

$$V_2 = 0.52554V$$

$$V_{AB}' = V_2 - 0 = 0.5295V$$

Now

$2V$  is short ckt.

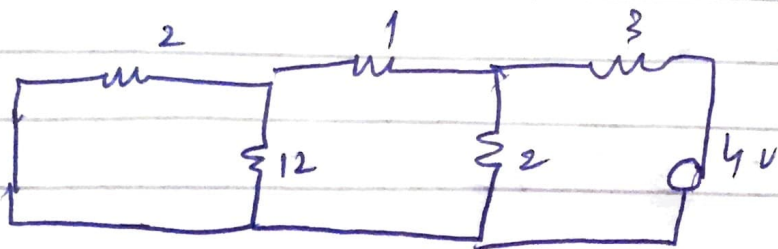


$$R_{12} = 2 \parallel 12$$

$$R_{123} = 2 \parallel 12 + 1$$

$$R_{123} = 1.5 + 1 = 2.5 \Omega$$

Now

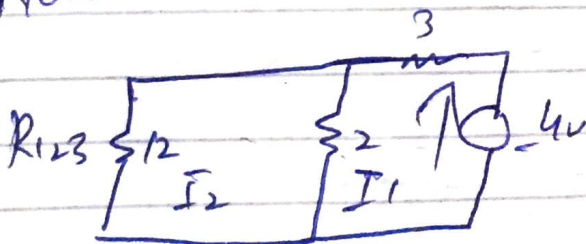

$$V_{AB}^4 = I_1 (2) - 4$$

$$I = \frac{4}{2.5 \parallel 2 + 3} = \frac{4}{4.111} = 0.972 A$$

using current division.

rule.

3

$$I_1 = \left( \frac{2.5}{2+2.5} \right) I = 0.5405 A$$

$$V''_{AB} = I_1 (2) = (0.5405) (2) \\ = 1.081 V$$

So

Net voltage

$$V_{AB} = V_{AB}' + V''_{AB}$$


$$= 0.525 + 1.081 V$$

$$V_{AB} = 1.6035 V$$




Question No # 2.

Step 1.

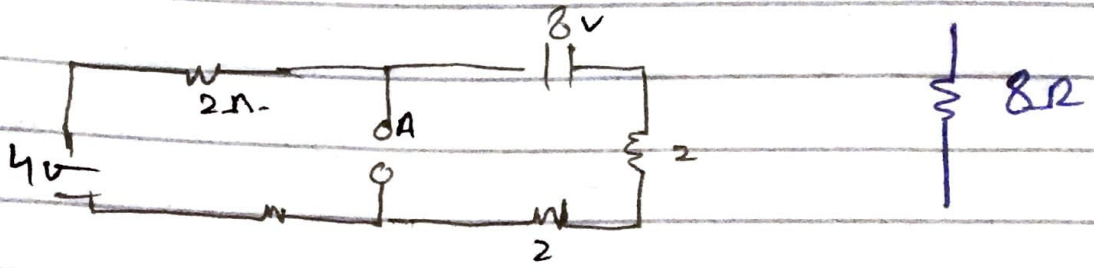

Step 2

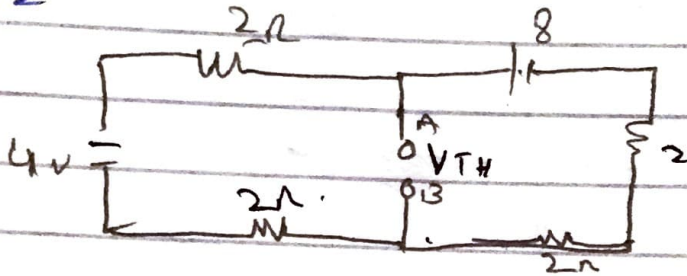


$$4 - 2I - 8 - 2I - 2I - 2I = 0$$

$$-8I - 4 = 0$$

$$I = \frac{4}{8} = \boxed{I = -\frac{1}{2} \text{ A}}$$

Step 3

To find  $V_{TH}$ .

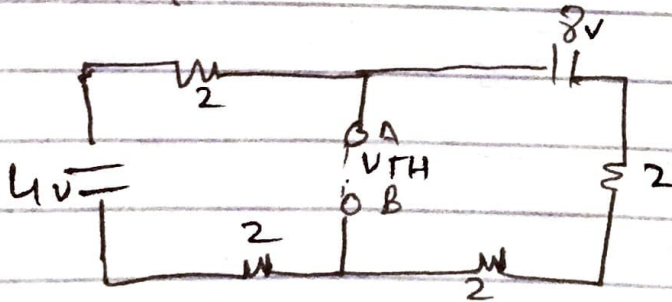



$$4 - 2I - V_{TH} - 2I = 0$$

$$V_{TH} = 4 + 4$$

$$V_{TH} = -4\left(\frac{1}{2}\right) + 4$$

$$V_{TH} = 2 + 4 = 6 \text{ V.}$$


Now find  $R_{TH}$ .

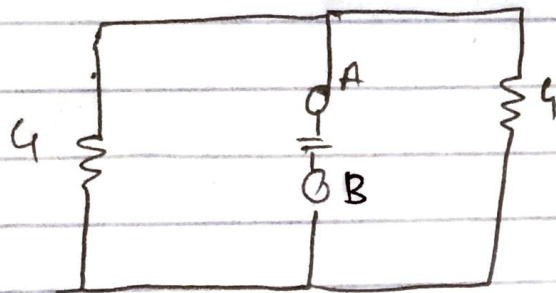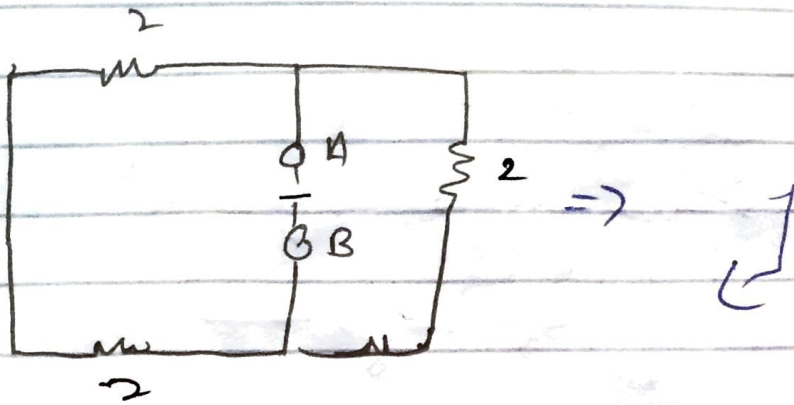

$$R_{TH} = \frac{4 \times 4}{4 + 4} = \frac{16}{8}$$

$$R_{TH} = 2 \Omega$$

Now step 5

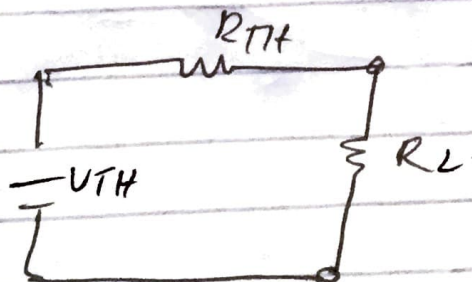


$$I = \frac{V_{TH}}{R_{TH} + R_L} = \frac{6}{2 + 8} \Rightarrow \frac{6}{10}$$

$$= 0.6 \text{ A}$$





Question no # 3.

Sol: →

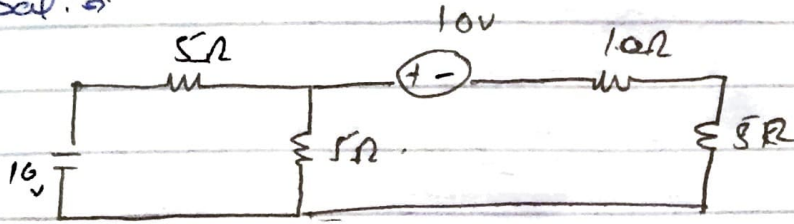

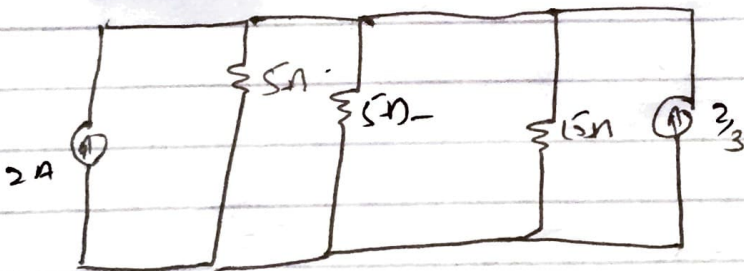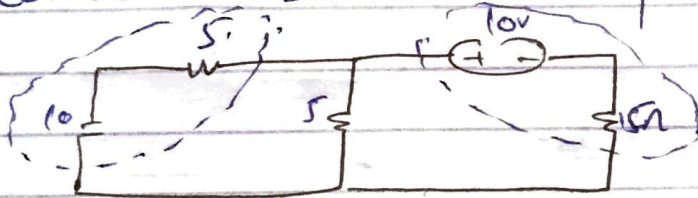
The terminal of the 10V source is placed to the left because the current source was pointing left.



$$I = \frac{10}{5} = \boxed{2A}$$

$$I = \frac{10}{15} = \boxed{\frac{2}{3}A}$$

Now

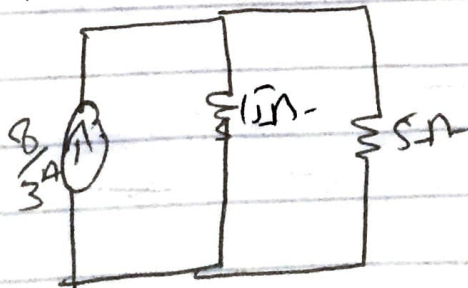


6

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{15}$$

$$= \frac{3+1}{15} = \frac{4}{15}$$

$$R_{eq} = \frac{15}{4} \Omega$$

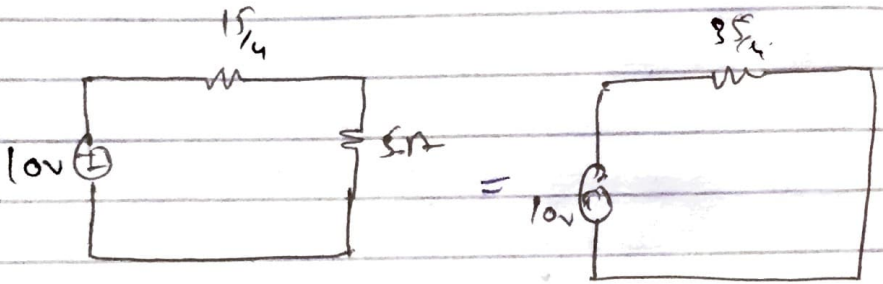


$$\frac{8 \times 15}{3 \times 4} = 10V$$

$$\frac{15}{4} + 5 = \frac{15 + 20}{4} = \frac{35}{4}$$

NOW.

$$i = \frac{10}{\frac{35}{4}} = \frac{10 \times 4}{35}$$


$$= 8 A \quad \text{Ans.}$$

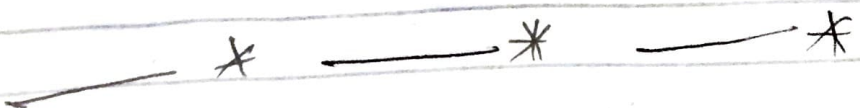



7


Question 4 A.

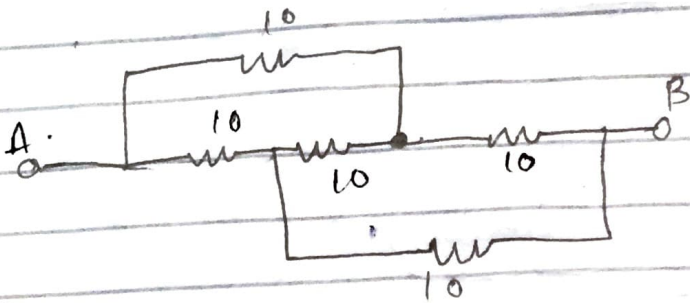


Sol.

$$A = VA$$


$$B = VB$$

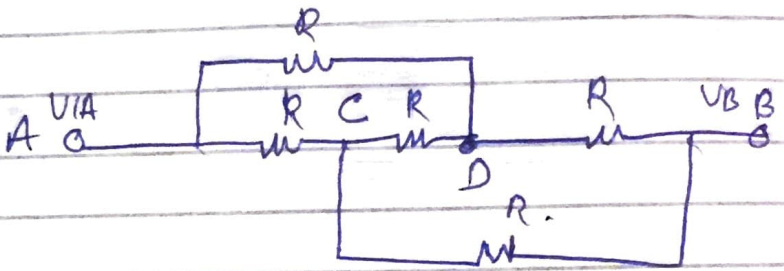

Now Modified the circuit

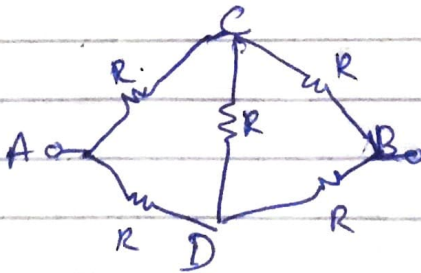

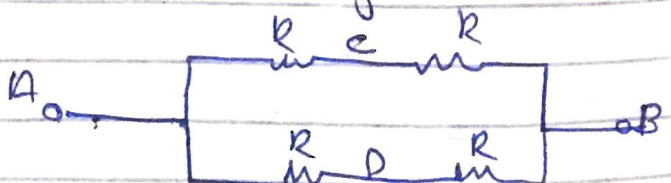Circuit is balanced now from wheat stone bridge.



Now


$$R_{eq} = \frac{2R \times 2R}{2R + 2R} = \frac{2(10) \times 2(10)}{2(10 + 2(10))}$$

$$Req = \frac{400}{40} = 10$$

$$\boxed{Req = 10} \quad \text{Ans}$$




Question 4b

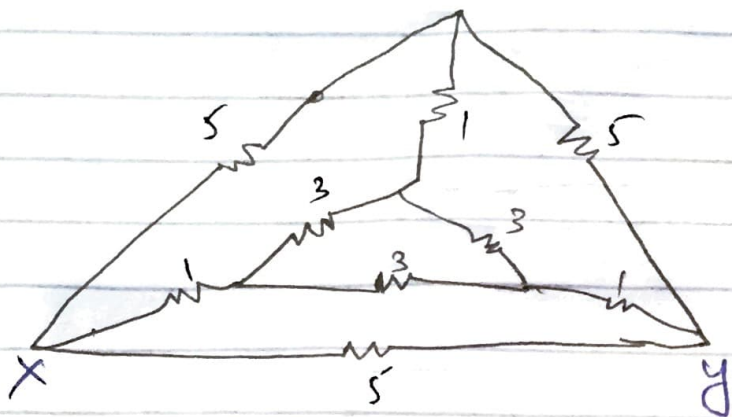


$$R_1 = \frac{3 \times 3}{3 + 3 + 3} = \frac{9}{9} = 1$$

$$R_2 = 1$$


$$R_3 = 1$$


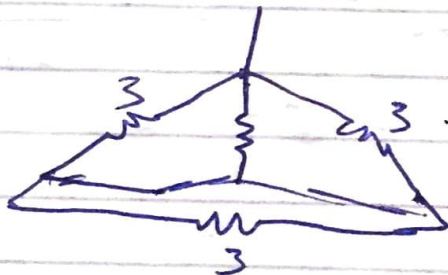


$\Delta \rightarrow Y$

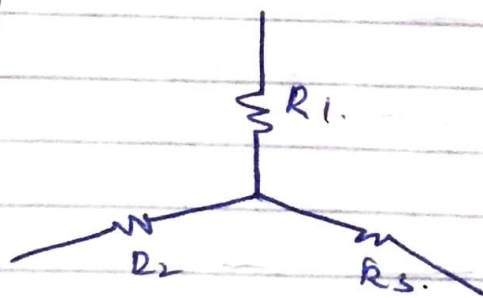

Now

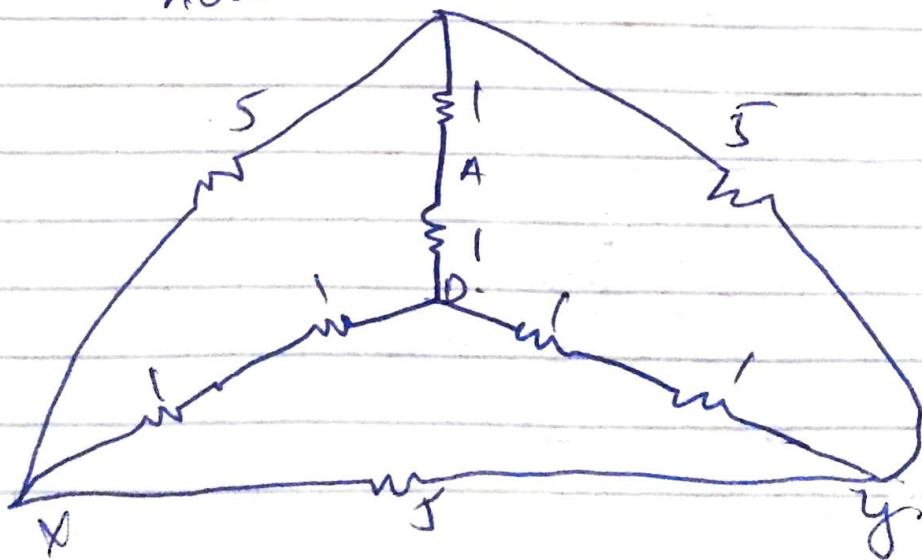


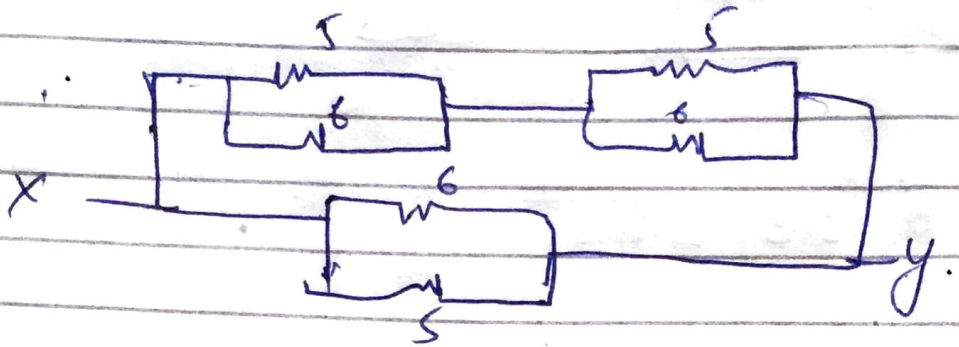
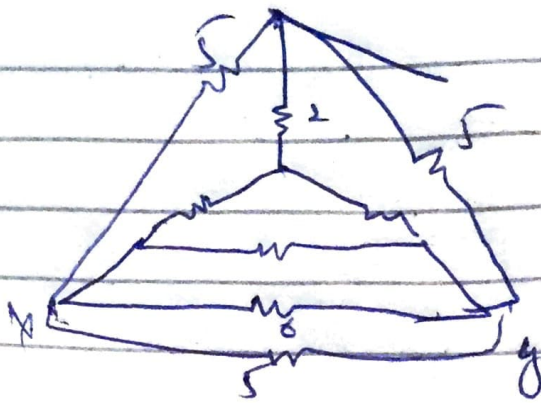


So Req

$$= 5 // R_c = 5 // 6 = \frac{5 \times 6}{5 + 6} = \frac{30}{11}$$

$$R_{eq} = \frac{30}{11} = 2.727 \Omega$$

$$2.727 + 2.727 \Omega$$

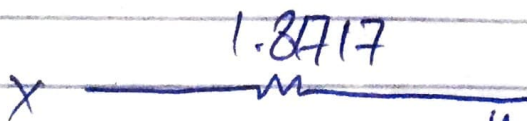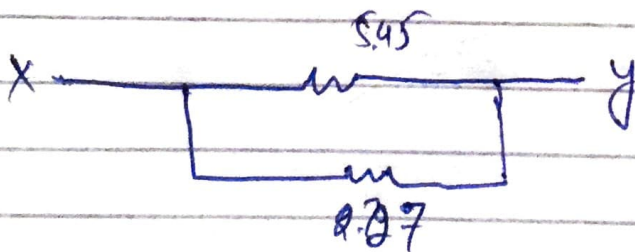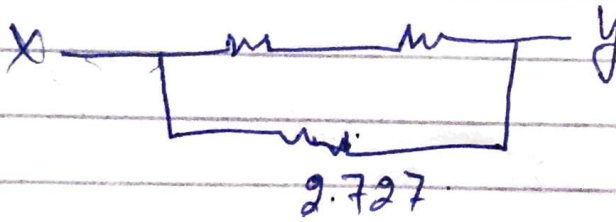

$$= \frac{5.45 \times 2.727}{5.45 + 2.727}$$

$$R_{eq} = 1.81717 \Omega$$