

Name :- Abdus-Rahman

ID :- 7826

Module :- 6th

Subject :- Basic Electro Mech

Submitted :- Engr Ashraf Ali.
to

Date :- 22 - 08 - 20

MID TERM EXAM.

Q1) a) There are two well-known formulae for calculating the total Resistance of parallel-connected resistance. One of these works only for two resistances while the other works for any number of parallel resistances. Write these two formulae:-

Ans:- "For two numbers:-"

$$\rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} -$$

"For any numbers:-"


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \dots \frac{1}{R_n} -$$

b) With parallel resistors the number of total resistance decreases since the total resistance is in reciprocal form so it divides into intervals as shown below:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

While the total Conductance will increase because total Conductance is the reciprocal of total resistance so there is smooth or more flow of electrons. $G_T \propto \frac{1}{R} -$

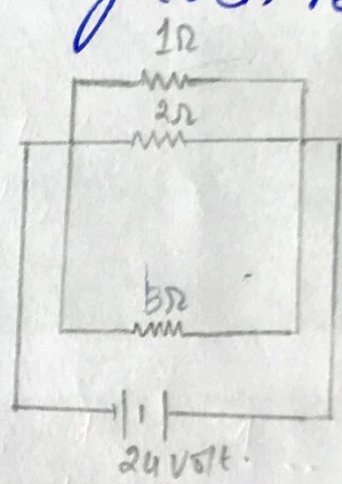Q2) In a given circuit, three resistors receive the same amount of voltage (24 volt) from single source. Calculate the amount of current "drawn" by each resistor, as well as the amount of power dissipated by each resistor



Sol: Since R_1 is in parallel so $\therefore V_T = V_1 = V_2 = V_3$
 $= \frac{1}{R_1}$

Thus $I_1 = \frac{V_1}{R_1}$

$I_1 = \frac{24}{1} = 24 \text{ amp}$

\rightarrow As R_2 is in series so
 $= R$

Thus $I_2 = \frac{V_2}{R_2}$

$$I_2 = \frac{24}{2} = 12 \text{ amp}$$

→ At R_3 is in parallel series so

$$I_3 = \frac{V_3}{R_3} = \frac{24}{3} = 8 \text{ amp}$$

→ Power dissipated by each resistor

$$P = VI$$

$$P_1 = V_T I_1$$


$$P_1 = 24 \times 24 = 576 \text{ W}$$

$$P_2 = V_T I_2$$

$$P_2 = 24 \times 12 = 288 \text{ W}$$

$$P_3 = V_T I_3$$

$$P_3 = 24 \times 8 = 192 \text{ W}$$

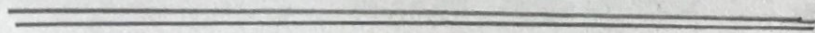

Q3) Differentiate b/w the following.

a) Current & Voltage.

Current

Voltage

- | | |
|--|--|
| <ul style="list-style-type: none"> • It is the flow of electrons across the closed circuit. • It is denoted by "I" • Its unit is ampere "A" | <ul style="list-style-type: none"> • It is defined as the effect to push the electron in circuit. • It is denoted by "V" • Its unit is Volt "V" |
|--|--|

b) Resistance & Conductance.

Resistance

Conductance

- | | |
|--|---|
| <ul style="list-style-type: none"> • It is blockage to the flow of the current • It is denoted by "R" • Its unit is Ohm Ω | <ul style="list-style-type: none"> • Conductance is the reciprocal of the resistance and is the amount of flow of charge. • It is denoted by "G" • Its unit is $\frac{1}{\Omega}$ |
|--|---|

c) Power & Energy -

5

Power

- It is rate of change of energy OR
- It is product of Voltage & current
- Its unit is Watts.
- It is denoted by "W"

Energy

- It is the ability to do work.
- Its S.I unit is J (Nm)
- It is also defined as the product of power & time as $\therefore W \times S = J$.

d) Inductance & Capacitance

Inductance

- It is the property of Conductor which causes e.m.f to generate by change in current flowing
- Its unit is Henry. "H"
- It is denoted by "E"

Capacitance

- It is the property of Conductor which has the ability to store charge
- It is denoted by "C"
- Its unit is Farad "F"
- $\therefore C = \frac{Q}{V}$

e) Synchronous Motor & Asynchronous motor. ⑥

Synchronous Motor

- It has complicated construction.
- Not self starting.
- Motor is sensitive to sudden load change.
- Motor is costly & requires frequent maintenance.

Asynchronous motor

- Its construction is simpler.
 - Self starting.
 - Hunting phenomena is absent.
 - Motor is cheap & cage motor are maintenance free.
-