

Name: Nadeem Ullah Khan

ID # 6873

Assignment # 3

Subject: Power electronics

Submitted To: Sir Shayan Farid

Date: 27/06/2020



Semester: 8th

Nadeem

27/06/2020

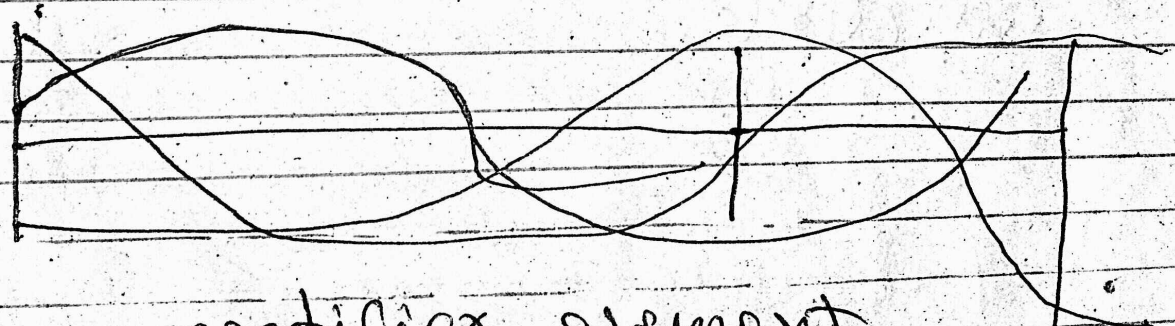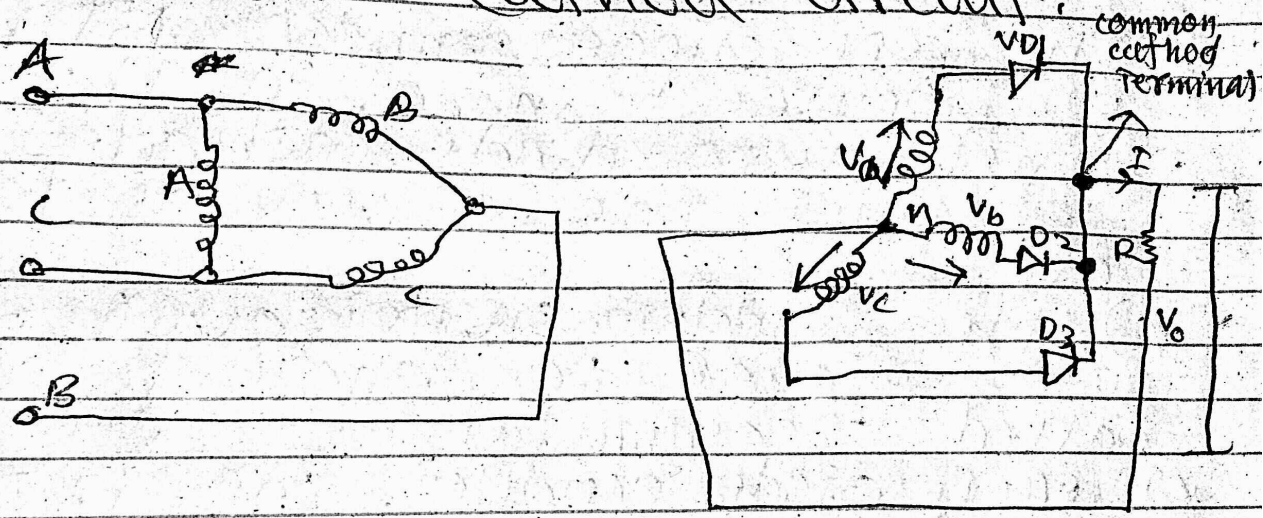Q13 - ϕ Half wave uncontrolled Rectifier:

it uses a $3-\phi$ transformer with primary in Delta and secondary in star connection. D_1, D_2 and D_3 have common connected cathode to common load R and all diodes are oriented in different phases and therefore called as common-cathode circuit.



*) The rectifier element connected to the line at the highest +ve instantaneous voltage can only conduct and pulsate

page (2)

b/w V_{max} and $0.5 V_{max}$.

* it is called 3- ϕ pulse rectifier as the o/p is repeated thrice in every cycle of V_s .

* the ripple frequency (f_r) of o/p voltage is

$$f_r = n f_s \quad , \quad n = \text{No. of diodes}$$
$$f_s = \text{AC supply freq.}$$

the on diode connects its most two source terminal to the other two diode cathodes keeping the other diodes off.

* the sudden switch over from one diode to another is called "commutation".

* each diode conducts for 120 intervals.

⇒ Full wave uncontrolled bridge rectifier:

- * On the positive half cycle of the transformer secondary supply voltage, diodes D_1 and D_2 conduct supplying the voltage to the load.
- * On the -ve half cycle of supply voltage, diodes D_3 and D_4 conduct supplying this voltage to the load.
- * It can be seen from the waveform that the peak inverse voltage of the diodes is only V_m .

Peak Rectifier diode current.

$$= \frac{V_m}{R}$$

Q2) Part (B)

⇒ Phase control rectifiers:

- * Unlike diode, an SCR does not become conducting immediately after its voltage becomes +ve.
- * It requires triggering by means of pulse at the gate.
- * So it is possible to make the thyristor conduct at any points.

Point on the half wave which applies the voltage at its anode.

* Thus output voltage is controlled.

⇒ Phase control Rectifier - Application

* Still rolling mills, paper mills, text mills where controlling of DC motor speed is necessary.

* Electric traction * High voltage DC Transmission
* Electromagnet power supply.

⇒ ϕ uncontrolled Rectifier:

* ϕ Rectifier offers the following advantages.

- (1) Higher d/p voltage for a given i/p voltage.
- (2) Lower amplitude ripple i.e. output voltage is smoother.
- (3) Higher frequency ripple simplifying filtering.
- (4) Higher overall efficiency.

⇒ uncontrolled Rectifier: (classification)

they are generally of four types:

- (1) ~~3~~ ϕ Half wave rectified.
- (2) ~~3~~ $3-\phi$ mid-point ϕ pulse rectified.
- (3) $3-\phi$ Bridge rectified.
- (4) $-\phi$ 12 pulse rectified.

Q No 28 - Given Data -

$$V_m = 73 \text{ V}$$

$$R = 68 \Omega$$

Solutions -

(1) V_{dc}

$$= V_{dc} = \frac{V_m}{\pi} = \frac{73}{3.1428}$$

$$V_{dc} = 23.24 \text{ V}$$

$$(2) I_{dc} = \frac{V_m}{\pi R} = \frac{73}{3.14 \times 68}$$

$$I_{dc} = 0.341 \text{ A}$$

$$(3) V_{rms} = \frac{V_m}{2} = \frac{73}{2}$$

$$V_{rms} = 36.5 \text{ V}$$

$$(4) I_{rms} = \frac{V_m}{2R} = \frac{73}{2 \times 68}$$

$$I_{rms} = 0.5367 \text{ A}$$

Page (6)


(5) whereas in center tapped rectifiers, the inverse voltage coming across each diode is double the maximum voltage across the half of the secondary winding. The transformer utilization factor (TUF) also more in bridge rectifier as compared to the center tapped or full wave rectifier, which makes it more advantages.

Q No 30- Principle and working of Buck converter

⇒ working of Buck converter:-

it works by switching on and off. so it can get a much higher power efficiency than a linear power supply. which it step down voltage from a high input to a low voltage output. while it will step up output current to load. so it lets save power source.

⇒ Principle of Buck converter

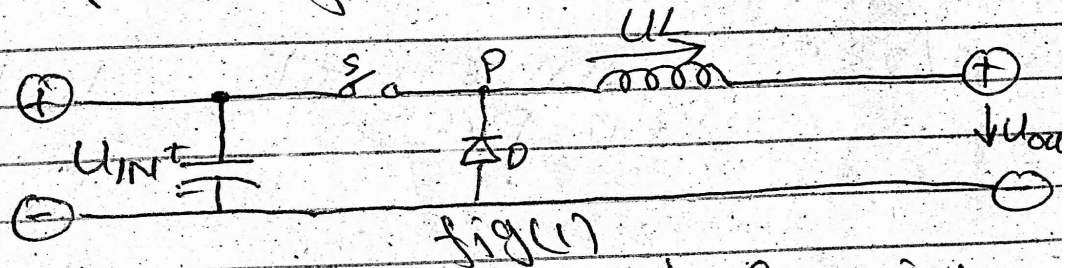

The DC to DC converter will change the voltage source. To higher or lower or something else. By purpose of the designer or our circuit ideas. when we see a basic buck converter circuit as fig(1). it is easy to understand with.

* V_{in} is an input voltage as popular of a European country and " V_{in} " of the United States.

* V_{out} is an output voltage European countries and " V_{out} " on the United States.

In this circuit, it consists of 3 main components only.

* S is a switch, in the real circuit, we use a transistor.

* D is a Diode.

* L is a coil or inductor.

* C is a capacitor.

*

Q No 33 - Numerical Solution :-
Given Data:

$$V_{in} = 50V$$

$$D = 73\%$$

$$\text{load of } R = 68\Omega$$

$$\text{switching } f = 20 \text{ Hz}$$

find

(1) V_{out} (2) I_{out}

(3) I_{in} (4) inductor (L)

Solutions:-

(1) we know that

$$V_{out} = DV_s$$

$$V_{out} = 73\% \times 50 = 0.73 \times 50$$

$$V_{out} = 36.5 \text{ V}$$

$$(2) I_{out} = \frac{V_o}{R} = \frac{36.5 \text{ V}}{68}$$

$$I_{out} = 0.5367 \text{ A}$$

$$(3) I_{in} = \frac{V_{in}}{R} = \frac{50 \text{ V}}{68}$$


$$I_{in} = 0.7352 \text{ A}$$

$$(3) I_{in} = DI_o = 73\% \times 0.5367 \text{ A}$$

$$I_{in} = 0.3917 \text{ A}$$

~~Q48 - Buck Conv~~

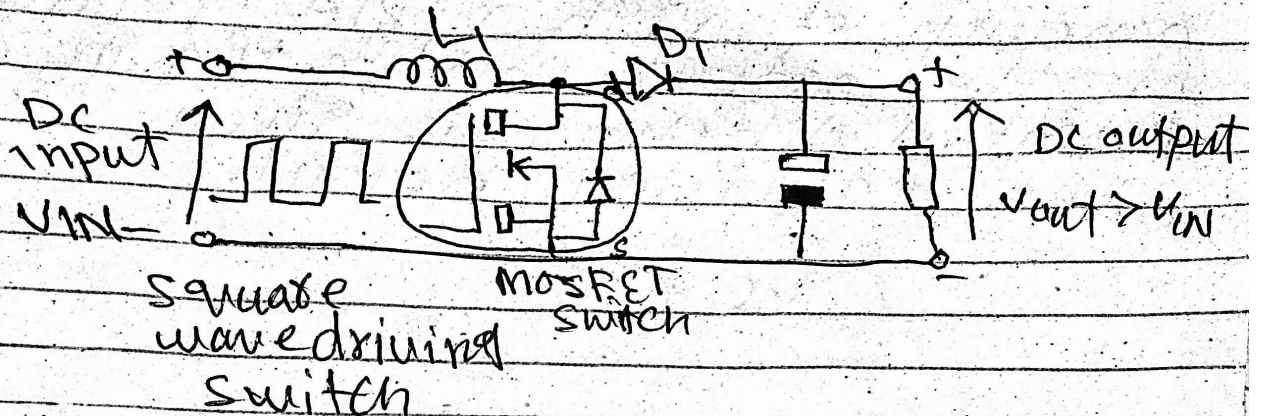Q48 - Boost converter working and principle



In this converter the first transistor is switched ON continuously and for the second transistor the square wave of high frequency is applied to the gate terminal. The second transistor is in conducting when the ON state and the input current flow from the inductor L through the second transistor. The negative terminal charging up the magnetic field around the inductor. The D_2 diode cannot conduct because the anode is on the potential ground by highly conducting the second transistor. By charging the capacitor C the load is

Page (11)

applied to the entire circuit in ON state and it can construct earlier oscillator cycles. During the ON period the capacitor C can discharge regularly and the amount of high ripple frequency on the output voltage. The approximate potential difference is given by the equation below.

$$V_S + V_L$$

Q4) Numerical part

Given Data's -

$$V_{IN} = 50V$$

$$D = 73\%$$

$$R = 68 \Omega$$

Switching frequency.
 $f = 20 \text{ kHz}$

find

(1) V_{out} (2) I_{out} (3) I_{in}

(4) Inductor (L)

Solutions:-

(1) We know that

$$V_{out} = \frac{V_s}{1-D} = \frac{50}{1-0.73}$$

$$V_o = 185.18 \text{ V}$$

$$(2) I_{out} = \frac{V_{out}}{R} = \frac{185.18 \text{ V}}{68}$$

$$I_{out} = 2.7233 \text{ A}$$

$$(3) I_{in} = \frac{I_{out}}{1-D} = \frac{2.7233}{1-0.73}$$


$$I_{in} = 10.086 \text{ A}$$

$$(4) L = \frac{V_{in} (V_o - V_{in})}{f(\Delta I) \times V_o}$$

QNO40- Principle and working of Part(A) Boost converter.


* Working and principle of Boost ^{converter} most of the electrical power circuit designer will choose the Boost mode converter because the output voltage is always high when compared to source voltage. in this circuit power stage can be operated in two modes:

1) continuous conduction mode (CCM)

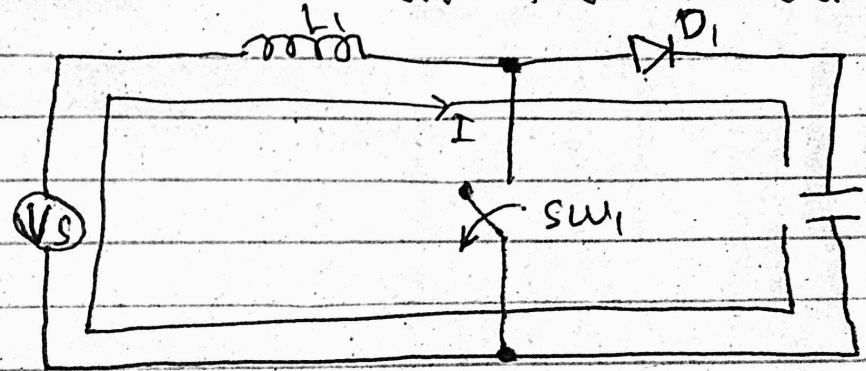

Boost converter continuous conduction mode.

2) Discontinuous conduction mode (DCM)


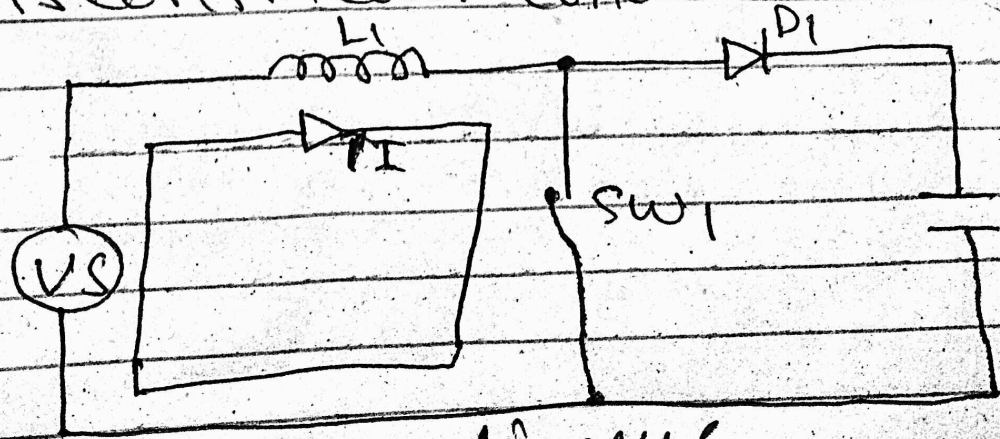


Discontinuous

Q No 50 - Principle and working of Buck boost converter.

⇒) working of Buck Boost converter.

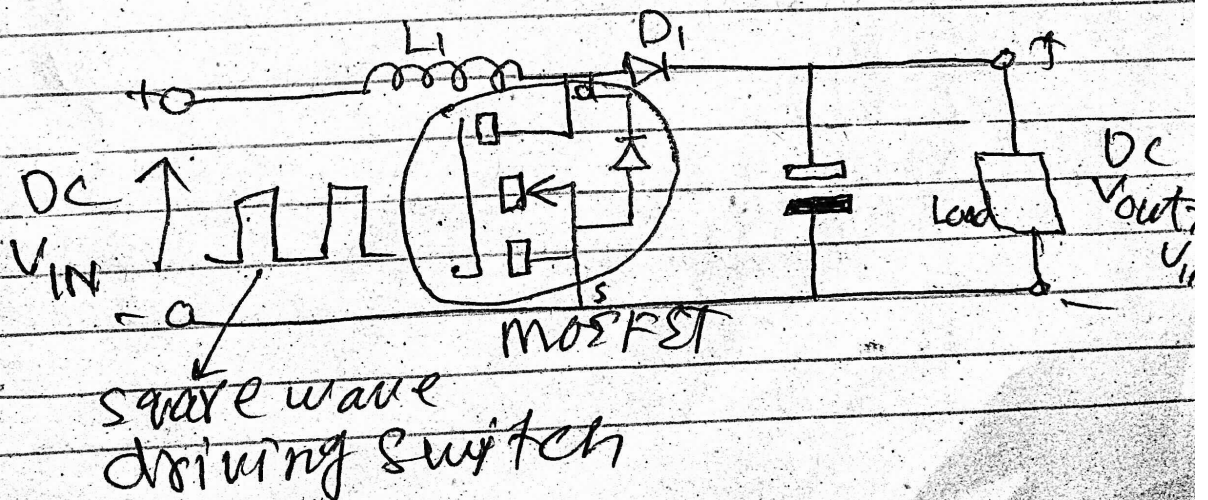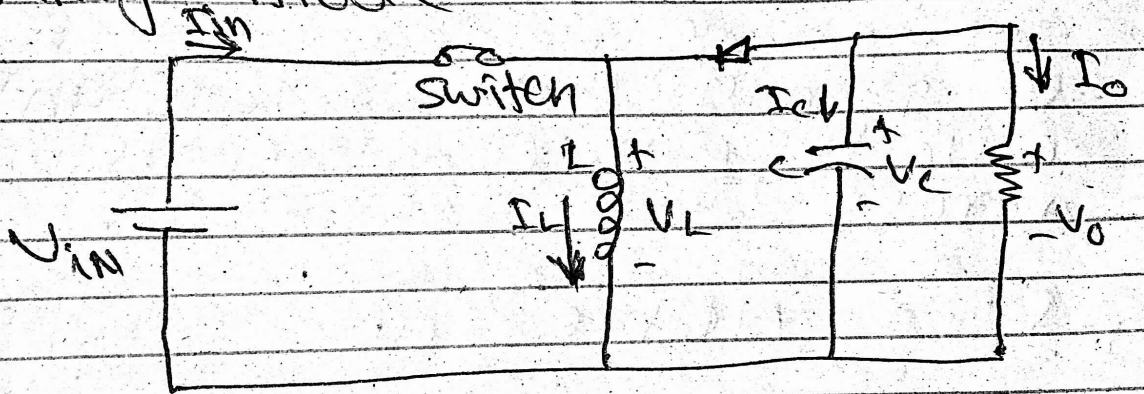A buck Boost converter transform a positive DC voltage at the input to a negative DC voltage at the output. The circuit operation depends on the conduction state of the MOSFET: ON state: the current through the inductor increases and the diode is in blocking mode.



The main working principle of buck booster converter is that the inductor in the input circuit resists sudden variation in input current. When a switch is ON the inductor stores energy from the input in the form of magnetic energy and discharges it when switch is closed. The capacitor in the output circuit is assumed large enough that the time constant of RC circuit in the output stage is high. The large time constant compared to switching period ensures that in steady state a constant output voltage $V_o(t) = V_o(\text{constant})$ exist across load terminal.

Q 5:- Numerical part:-

Given Data:

$$V_{in} = 50V$$

$$V_{out} = 73.90$$

$$R = 68\Omega$$

$$f = 20Hz$$

solutions-

we know that

find (1) duty cycle

$$(1) \quad 1-D = \frac{-V_{in}}{V_o - V_{in}}$$

$$1-D(V_o - V_{in}) = -V_{in}$$

~~$$V_o - V_{in} = \frac{-V_{in}}{1-D}$$~~

~~$$V_o = -V_{in} + V$$~~

~~$$V_o = \frac{1}{1-D} = \frac{1}{1-}$$~~

$$(1) \quad 1-D = \frac{-V_{in}}{V_o - V_{in}}$$

~~$$-D = \frac{-V_{in} - 1}{V_o - V_{in}}$$~~

$$D = \frac{V_{in} + 1}{V_o + V_{in}}$$

$$D = \frac{50V + 1}{0.73 + 50}$$

$$D = 1.0053$$

Page (17)

$$(2) I_{out} = \frac{V_o}{R} = \frac{0.73}{68}$$

$$I_{out} = 0.01073 \text{ A}$$

$$(3) I_{in} = \frac{I_o D}{1-D} = \frac{0.01073 \times 1.0053}{1 - 1.0053}$$

$$I_{in} = 2.03525 \text{ A}$$

$$(4) L = \frac{V_{in} \times D}{f \times \Delta I}$$

End