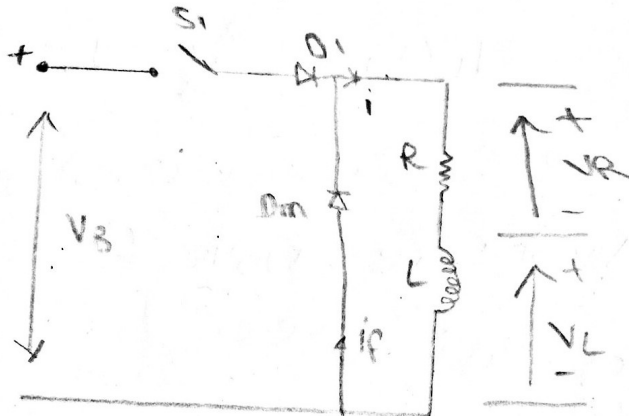


Q1

Ans

A diode circuit with an RL load



When switch \$S_1\$ is closed at \$t=0\$ the current through the inductor increase and is expressed as

$$V_s = V_L + V_R = L \frac{di}{dt} + Ri$$

With the initial \$i(t=0) = 0\$ \$i(t)\$ is expressed

$$i(t) = \frac{V_s}{R} (1 - e^{-tR/L})$$

The rate of change of this current can be obtained from

$$\frac{di}{dt} = \frac{V_s}{L} e^{-tR/L}$$


the initial rate of rise of the current at \$t=0\$ is obtained

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_s}{L}$$

The voltage across the inductor is

$$V_L(t) = L \frac{di}{dt} = V_s e^{-tR/L}$$

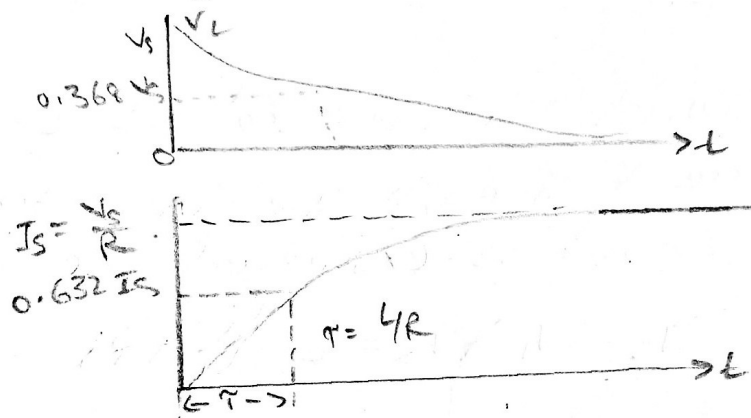Where $L/R = \tau$ is the time constant of an RL load. The wave forms for the voltage and current



Free Wheeling Diode

- A free wheeling diode is basically a diode connected across the inductive load terminals to prevent the development of high voltage across the switch.
- When the inductive circuit is switched off this diode gives a short circuit path for the flow of inductor decay current and hence dissipation of stored energy in the inductor.
- This diode is also called flywheel or fly back diode.

ID = 13132

Subject = Power electronic

Name = Ahmad Zaib

Page = 03

Q 1 (b) Given

$$V_{DS} = 32V$$

$$V_T = 2V$$

Find:

$$V_{GS} = ?$$

Sol.

As we know that.

where for saturation.

$$V_{DS} \geq V_{GS} - V_T$$

$$V_{DS} = V_{GS} - V_T$$

where

$$V_{GS} = V_{DS} + V_T$$

Putting value we get

$$V_{GS} = 32 + 2$$

$$\{V_{GS} = 34V\} \text{ Ans.}$$

Subject = Power electronic

page = 004

Q2 (a) A power electronic appliance of 500W 220V, 50 KHz rating is using a power MOSFET for switching purpose. The power MOSFET is replaced with power bipolar junction transistor. Its effect on its performance and losses and efficiency on the appliance. The switching frequency will be lower of appliance because MOSFET have high switching frequency the BJT. The losses will be low because losses in BJT is less than MOSFET have high switching frequency than BJT loss in appliance will be low another reason losses. The BJT cannot operate at high frequency one of the impact on performance 500KHz. on state voltage low for BJT so the frequency of the impact on performance the appliance improve. The switching losses will increase.

due to Bjt in appliance,
But conduction losses will be
decrease because of Bjt replace
ment in appliance.

on the high frequency Bjt
are less efficient that also effect
on its performance.

The frequency of appliance is
high and Bjt have low frequency
rate and switching frequency need
to adjust frequency because is
so high.

Q2 (B) The above appliance is if the
mosfet replaced with SCR as
switch and impact its performance
losses and efficiency is given.

The SCR have no capabilities
to handle high frequencies and
will impact on its performance
The SCR can handle more power
voltage current which increase
the efficiency of the appliance
and one of the advantages
efficiency.

ID = 13132

Ahmad Zaib.

Subject = P-F

Page = 06.

The SCR can protected because of the fuse, which can decrease losses used as the performance of the appliance improve.

ID=13132

subject= Power electronic

Name= Ahmael Zaib.

page= 07

Q3 (a) Given

βF range 8 to 40

$$R_C = 32 \Omega$$

$$V_{CC} = 132V$$

$$V_B = 10V$$

$$V_{CE} = 1V$$

$$V_{BE} = 1.5V$$

Find

(a) the mode of operation of the transistor

(b) the value of R_B that results in saturation with an ODF of 5

(c) the β forced

(d) the power loss P_T in the transistor.

Sol

As we know that

$$I_{CS} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$= \frac{132 - 1}{32}$$

$$I_{CS} = 4.0A$$

Therefore

$$I_{BS} = \frac{I_{CS}}{\beta_{min}}$$

ID = 13132

Subject = Power electronic

Name = Ahmad Zaib

Page = 08

$$= \frac{4.0 \text{ A}}{8}$$

$$I_{BS} = 0.5 \text{ A}$$

$$I_B = 0.07 \times I_B$$

$$= 5 \times 0.5$$

$$I_B = 2.5 \text{ A}$$

$$I_B = \frac{V_B - V_{BE}(\text{sat})}{R_B}$$

Therefore

$$R_B = \frac{V_B - V_{BE}(\text{sat})}{I_B}$$

$$= \frac{10 \text{ V} - 1.5 \text{ V}}{2.5}$$

$$\{R_B = 3.4 \Omega\}$$

B) therefore

$$\beta_F = \frac{I_{CS}}{I_B}$$

$$= \frac{4.0}{2.5}$$

$$\{\beta_F = 1.6\}$$

$$C) P_T = V_{BE} I_B + V_{CE} I_C$$

$$P_T = 1.5 \times 2.5 + 1 \times 4.0$$

ID = 13132.

Page = 09.

$$= 3.75 + 4$$

$$\left. \begin{aligned} \text{MST} \\ \text{L} \end{aligned} \right\} = 7.75 \text{W}$$