

NAME: FAWAD REHMAN

ID: 5053

PAPER: PSA

INST: ENGR. Shahyan Tariq

DATE: 19/08/2020

Question No. 1.

(a).

Answers:

→ Four conditions to connect generator to the grid.

1. The three-phase voltage must have the same frequency as the grid.
2. The three-phase voltage must have the same amplitude at its terminals as the one of the grid voltage.
3. The three-phase voltage must have the same phase sequence as the grid voltage.
4. The three-phase voltage must be in phase with the grid voltage.



Question No. 1.

(b)

Answer:

→ A generator cannot deliver power to an electrical power system unless all the aforementioned parameters exactly match those of the network. The need for synchronization arises when two or more alternators work together to supply the power to the load. Since electrical load does not remain constant, the two or more generators supplying the power needed to be interconnected and operate in parallel to handle larger loads.


→ The active power and reactive power can be outputted simultaneously. If the generator is made into an asynchronous generator, the generator will absorb a large number of reactive power after grid connection, which will reduce the system voltage and make the power grid reactive power gap too large to maintain the qualified voltage.



Question No 2.

(a)

Solution:

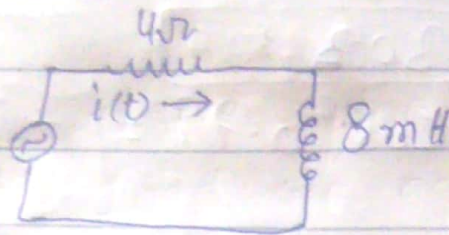

$$V = 110 \angle 50^\circ$$

$$f = 60 \text{ Hz}$$

$$R = 4 \Omega$$

$$X = \omega L = 3$$

$$|Z| = \sqrt{4^2 + 3^2} = 5 \quad \phi = 36.9^\circ$$

$$I = \frac{V}{Z} = \frac{110 \angle 50^\circ}{5 \angle 36.9^\circ}$$

$$= 22 \angle 13.1^\circ$$

$$I = 22 \angle 13.1^\circ \quad \text{current}$$

$$P = (V) (I)$$

$$P = 110 \angle 50^\circ \times 22 \angle 13.1^\circ = 2420 \angle 63.1^\circ$$

$$\Rightarrow \phi = \phi_V - \phi_I$$

$$= 50^\circ - 13.1^\circ$$

$$= 36.9^\circ$$

$$P.F = \cos \phi$$

$$= \cos 36.9^\circ$$

$$P.F = 0.79$$

Power Factor

$$P = |S| \cos \phi$$

$$S = \frac{P}{\cos \phi}$$



$$S = \frac{2420 \angle 63.1^\circ}{0.79}$$

$$S = 3063 \text{ KVA}$$

$$\theta = \cos^{-1} 0.79 = -37^\circ$$

$$Q = |S| \sin \theta$$

$$= 3063 \sin -37$$

$$Q = 1843 \text{ Kvar}$$

Question No 2:

(b).

Solution:

$$S = 42.5 + j26$$

$$\theta = \cos^{-1} 0.85 = 31.78^\circ$$

$$\text{PF of } 0.95 \text{ requires } \theta \text{ desired} = \cos^{-1} 0.95 = 18.2^\circ$$

$$S_{\text{new}} = 42.5 + j(26 - Q_{\text{cap}})$$

$$\frac{26 - Q_{\text{cap}}}{42.5} = \tan 18.2^\circ$$

$$42.5$$

$$= 13.80 = 26 - Q_{\text{cap}}$$

$$Q_{\text{cap}} = 26 - 13.80$$

$$= 12.20 \text{ Kvar} \quad \underline{\underline{\text{Ans}}}$$



Question No 3.

(a)

Answer:

The balance system is one in which the load are equally distributed in all the three phases of the system. the magnitude of voltages remains same in all the three phases and its is separated by an angle of  $120^\circ$

It is one in which the impedances in the three phases are identical.

It is the sinusoidal voltages of same amplitude, frequency, but differing by  $120^\circ$  phase difference with one another.



① Question No 3.

(b)

Solution:

Currents:

$$I_{AB} = \frac{V_{ab}}{Z_A}$$

$$I_{BC} = \frac{V_{bc}}{Z_A}$$

$$I_{CA} = \frac{V_{ca}}{Z_A}$$

Voltages:

$$V_{ab} = \sqrt{3} V_L \angle 30^\circ$$

$$= 190.53 \angle 30^\circ \text{ V}$$

$$V_{bc} = 190.53 \angle -90^\circ \text{ V}$$

$$V_{ca} = 190.53 \angle 150^\circ \text{ V}$$

$$I_{AB} = \frac{190.53 \angle 30^\circ}{60 \angle 40^\circ} = 3.1755 \angle 15^\circ \text{ A}$$

$$I_{BC} = \frac{190.53 \angle -90^\circ}{60 \angle 40^\circ} = 3.1755 \angle -35^\circ \text{ A}$$

$$I_{CA} = \frac{190.53 \angle 150^\circ}{60 \angle 40^\circ} = 3.1755 \angle 105^\circ \text{ A}$$

$$P = V I$$

$$P = 190.53 \times 3.1755$$

$$P = 602.3$$

$$P.F. = \cos \theta = \cos 0$$

$$= -0.46$$