

# Assignment

NAME : Muhammad HAROON


Course title : Linear circuit Analysis

Instructor : Engr. Waleed Jan

Student ID : 16216

Summer final term 2020

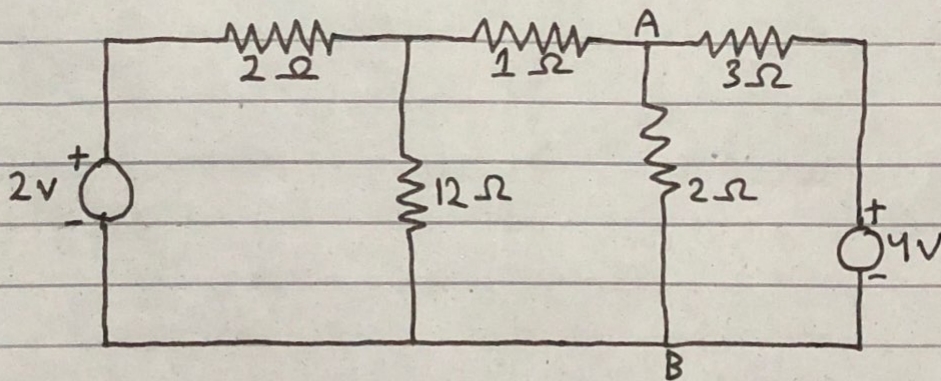Q1: Using superposition principle, determine the current through  $2\ \Omega$  resistor connected between terminal A and B in the circuit shown below:



Solution: Required  $V_{AB} = ?$

using superposition theorem  
Suppose to use 2V source and  
short ckt

$V_{AB} = ?$

using nodal Analysis

VI

ID: 16216

Name: M. HAROON

$$\frac{V_1 - 2}{2} + \frac{V_1}{12} + \frac{V_1 - V_2}{1} = 0$$

$$6V_1 - 12 + V_1 + 12V_1 - 12V_2 = 0$$

$$19V_1 - 12V_2 = 12 \rightarrow \textcircled{1}$$

V<sub>2</sub>

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2}{3} = 0$$

$$6V_2 - 6V_1 + 3V_2 + 2V_2 = 0$$

$$-6V_1 + 11V_2 = 0$$

$$V_2 = \frac{6V_1}{11} \rightarrow \textcircled{2} \text{ put in } \textcircled{1}$$

$$19V_1 - 12(6V_1) = 12$$

$$V_1 = 0.9635 \text{ V}$$

$$V_2 = 0.525549 \text{ V}$$

$$V_{AB} = V_2 - 0 = 0.5225 \text{ V}$$


Now

2V is short cut

ID: 16216

Name: M. HAROON

and 4v act as source

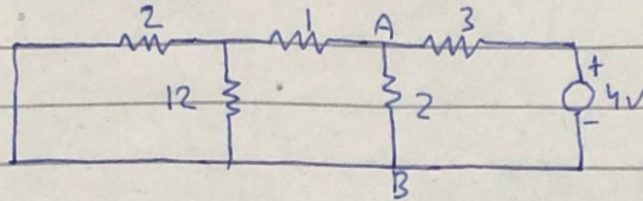
after parallel and sources simpli  
ficator

$$= 2 \parallel 12$$

R12

$$R_{123} = 2 \parallel 12 + 1$$

$$R_{123} = 1.5 + 1 = 2.5 \Omega$$

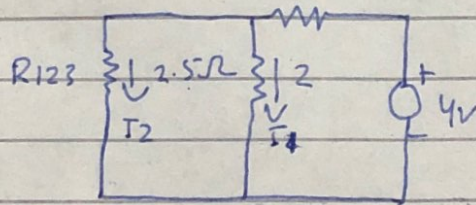

$$V_{AB} = I_1 (2) \rightarrow (A)$$

$$I = \frac{4}{2.5 \parallel 2 + 3} = \frac{4}{4.111} = 0.9724 \text{ A}$$

using current division method

$$I_1 = \left( \frac{2.5}{2 + 2.5} \right) I = 0.5405 \text{ A}$$

$$V_{AB} = I_1 (2) = (0.5405)(2) = 1.081 \text{ V}$$

So

Not voltage

4

ID:16216

Name: M. HAROON

$$V_{AB} = V_{AB}' + V_{AB}'' = 0.5225 + 1.081 \text{ V}$$

$$V_{AB} = 1.6035 \text{ V}$$


$$\boxed{V_{AB} = 1.6035 \text{ V}}$$

(    )

ID: 16216

Name: M. HAROON

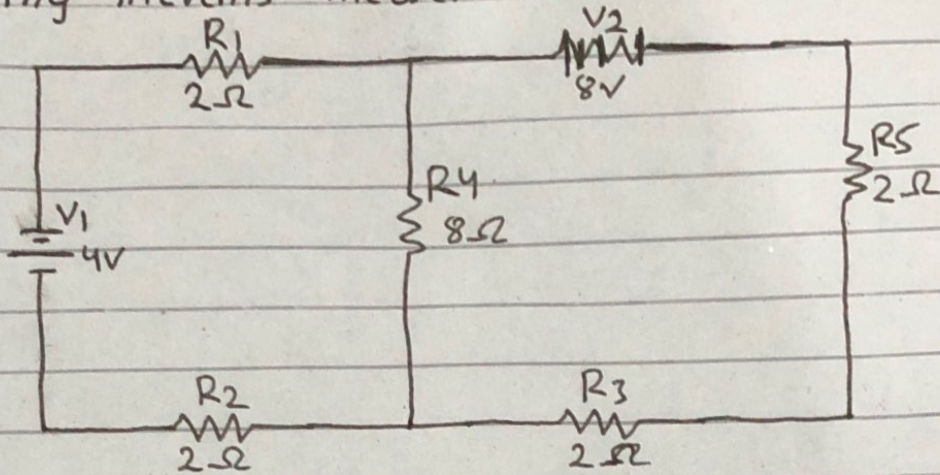Q2: Find the current in  $8\Omega$  resistor using Thevenin's theorem:



Sol:

$$V_{\text{total}} = 4 \quad R_{\text{total}} = 8\Omega$$

$$I = \frac{V}{R} \quad (\because V = IR)$$

$$I = \frac{4}{8} = 0.5\text{A}$$

$$V_1 = 1\text{V}$$

$$V_2 = 1\text{V}$$

$$V_3 = 1\text{V}$$

$$V_4 = 1\text{V}$$

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{4}$$

$$\frac{4+1}{4} = \frac{5}{4} = \frac{4}{5}$$

ID: 16216


Name: M. HAROON

$$V_{in} = 6V$$

$$R_{Th} = 2\Omega$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$

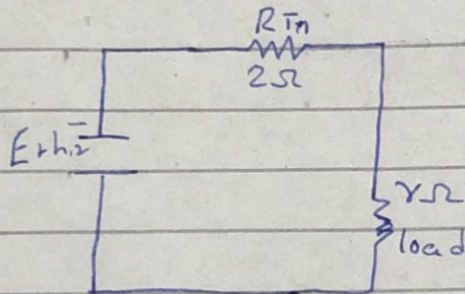
$$\frac{1}{R} = \frac{1+1}{4} = \frac{2}{4} = \frac{1}{2} = \frac{1}{R}$$



$$V = IR$$

$$I_{in} = \frac{V}{R} = \frac{6}{10} = 0.6A$$


$$I = 0.6A$$

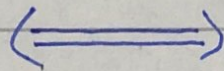


ID: 16216

Name: M. HAROON

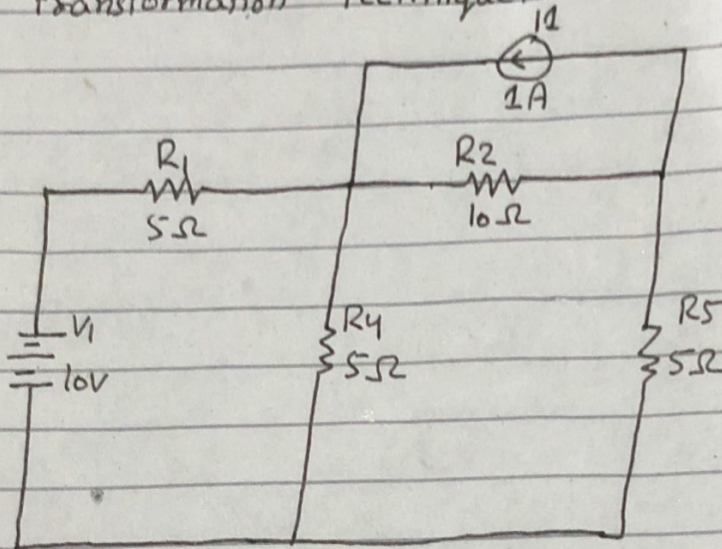Q3: Find the current through the central  $5\text{-}\Omega$  resistor using source transformation technique:







Ans: Sol:

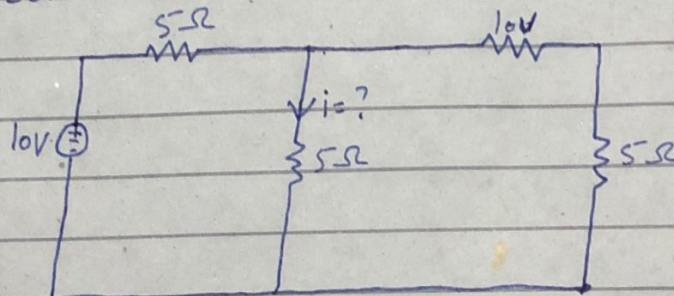


Note that the +ve terminal of the 10V source is placed to the left because the current source arrow was pointing to the left.

ID: 16216

Name: M. HAROON

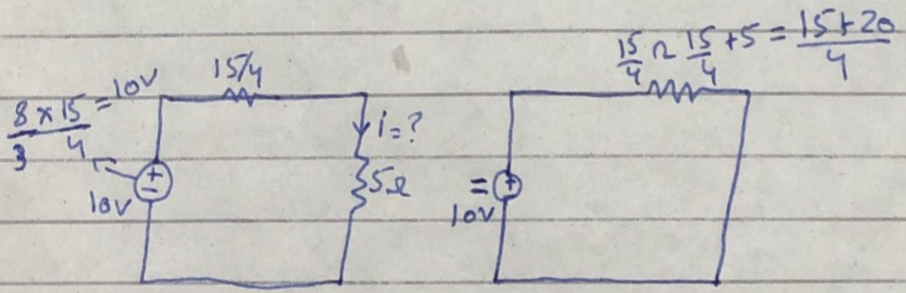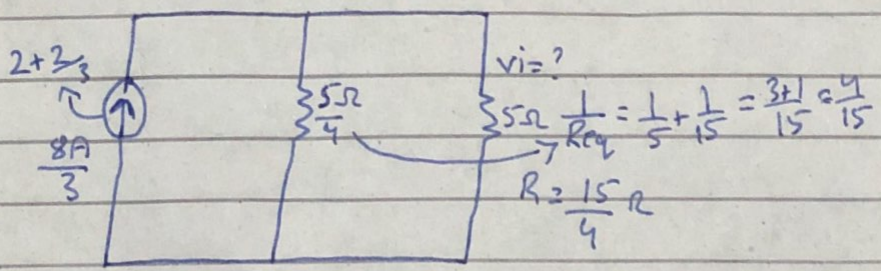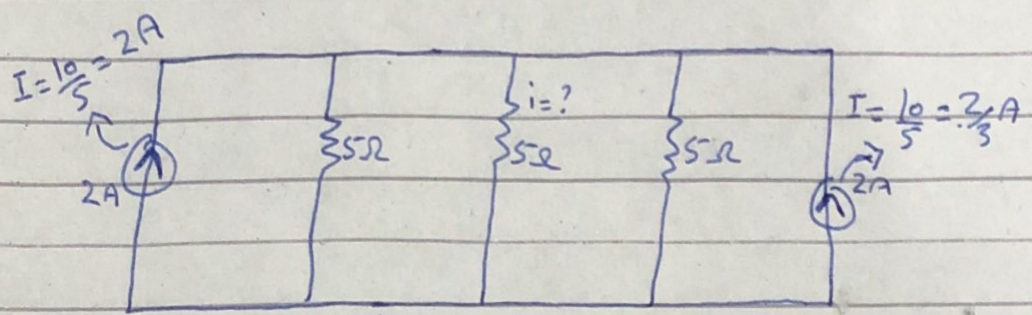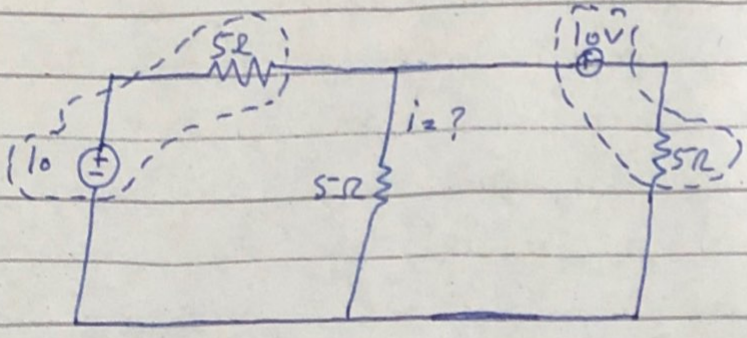
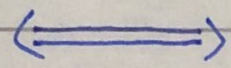
$$i = \frac{10}{35} = \frac{10 \times 4}{35} = \frac{8A}{7} = 1.143 A$$






ID: 16216

Name: M. HAROON


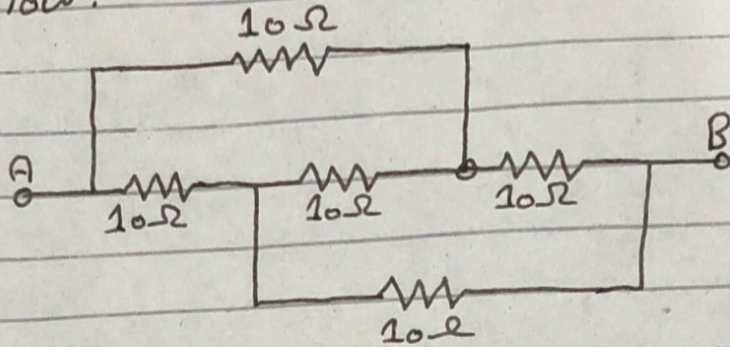
Q4: (a) Calculate the resistance between terminal A and B for the circuit shown below:




Sol:

$$A = VA$$

$$B = VB$$

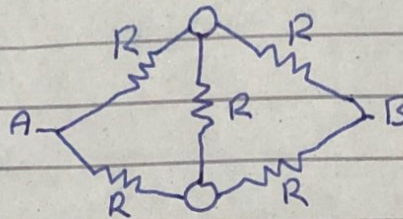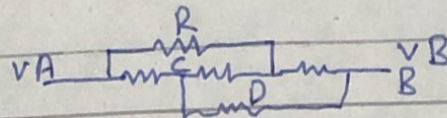


all have same values

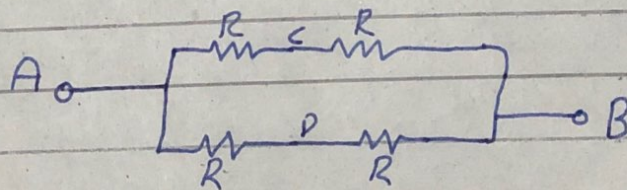

$$R_{eq} = \frac{2R \times 2R}{2R + 2R}$$

$$R_{eq} = \frac{2(10) \times (2(10))}{2(10) + 2(10)}$$


$$R_{eq} = R$$

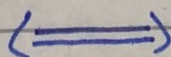

ID: 16216

Name: M. HAROON

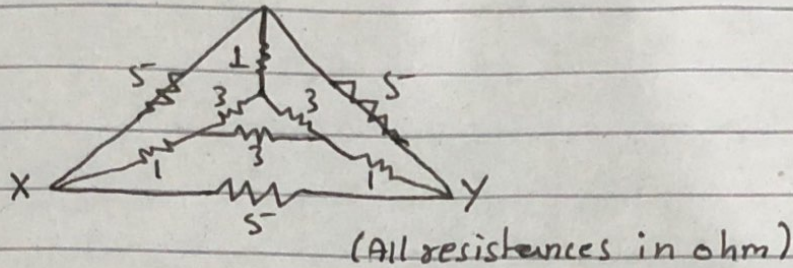Q4:(b) Determine the resistance between terminal x and y for the circuit shown in the figure below:







Solution:

$$R_1 = \frac{3 \times 3}{3+3+3} = \frac{9}{9} = 1$$

$$R_2 = 1$$

$$R_3 = 1$$

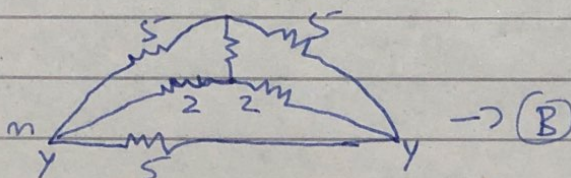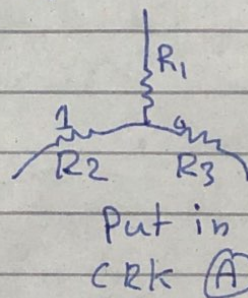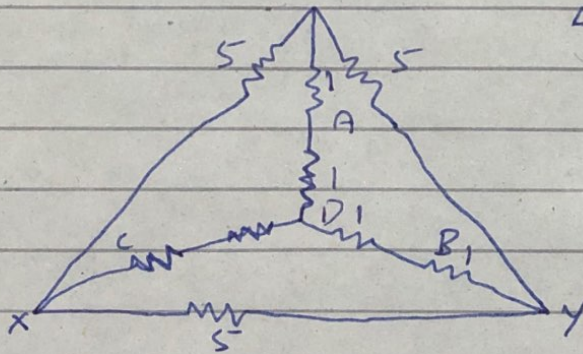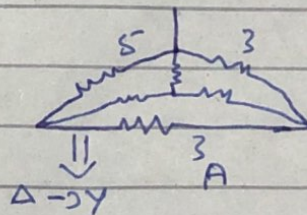

$$R_y = 2 + 2 + \frac{2 \times 2}{2}$$




ID: 16216

Name: M. HAROON

$$R_4 = 4 + 2 = 6 \Omega$$

$$R_5 = 4 + 2 = 6 \Omega$$

$$R_6 = 6 \Omega$$

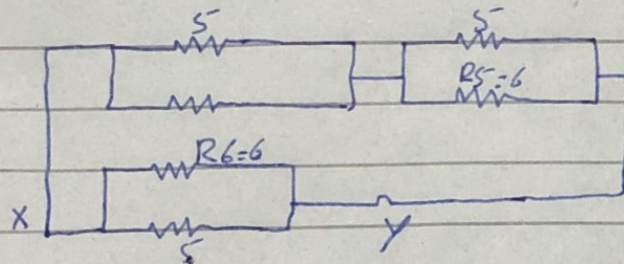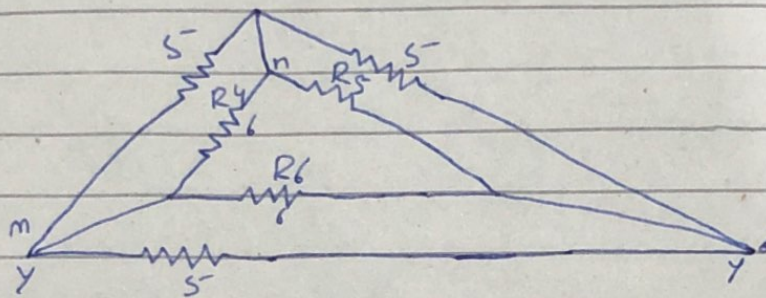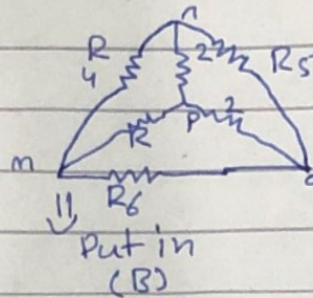


So


$$R_{eq} = 5 \parallel R_6 = 6 \parallel 6 = \frac{5 \times 6}{5 + 6} = \frac{30}{11}$$

$$R_{eq} = \frac{30}{11} = 2.727 \Omega$$

$$2.727 + 2.727$$

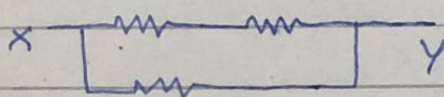


$$2.727$$

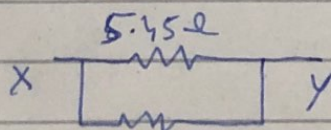

$$2.725 \Omega$$

ID: 16216

Name: M. HAROON

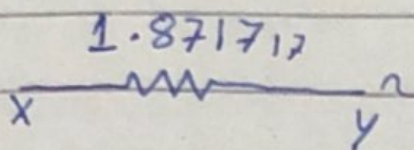

$$= \frac{5.45 \times 2.725}{5.45 + 2.725}$$

$$Z_{eq} = Z_{ny} = 1.81717 \Omega$$

