

Name Muhammad Ali Khan


RegNo 16550

Dld Assignment


NAME: Muhammad Ali Khan
 Reg No: 16550

Q1

a)

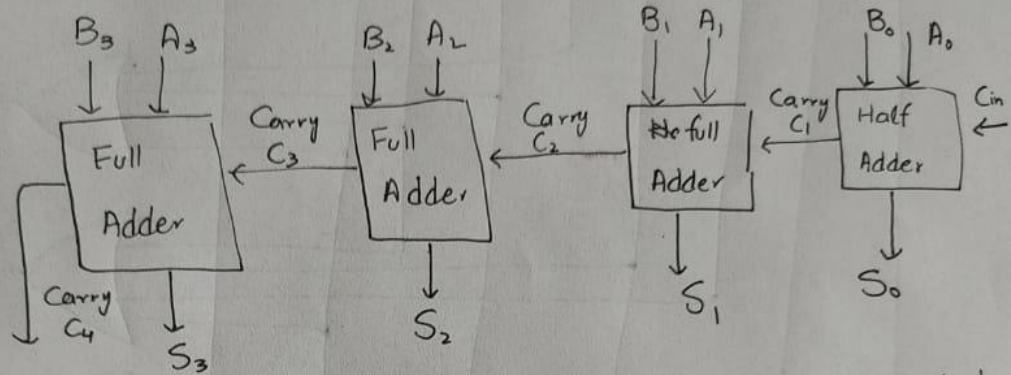

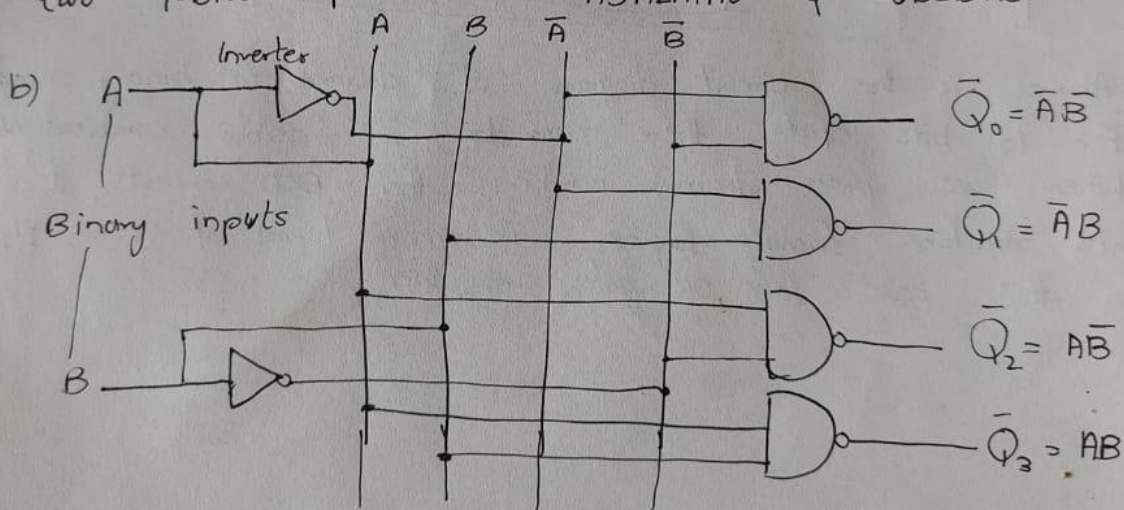
The figure is 4-bit parallel binary adder which has two 4-bits inputs as $A_3A_2A_1A_0$ & $B_3B_2B_1B_0$.



This consists of four AND gates. The binary 2 inputs A & B are decoded into one of 4 outputs, hence description of 2-to 4-binary decoder.

NAME: Muhammad Ali Khan
Reg No: 16550

c)

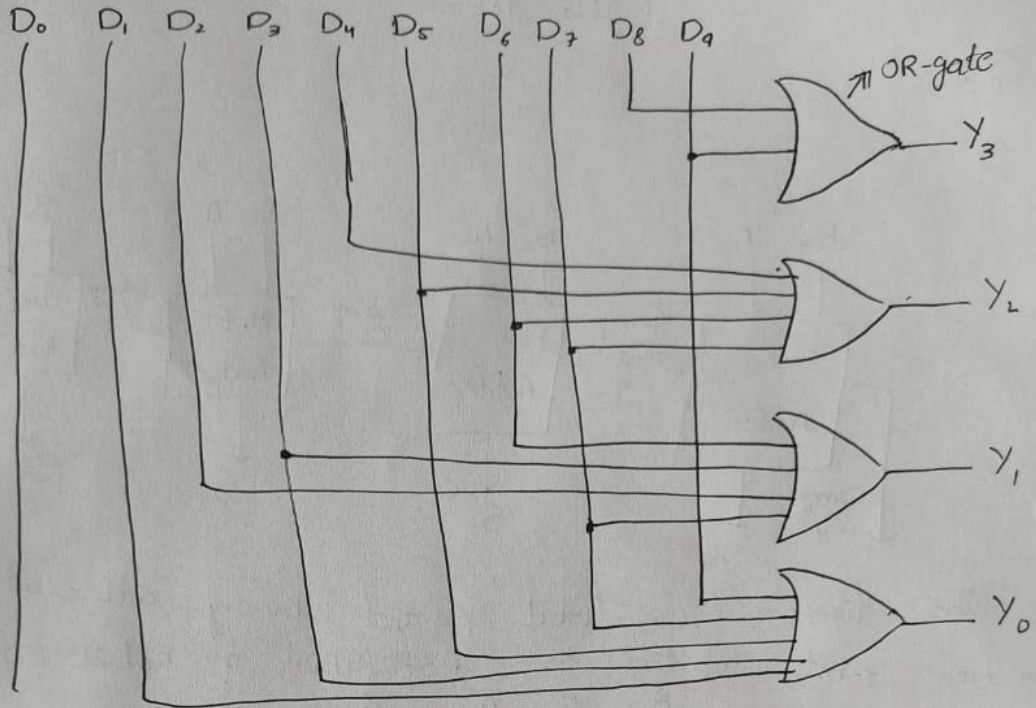

Above is the circuit diagram of decimal to binary encoder. For 10 bits inputs there can be 2^{10} possible combinations. When we press decimal numbers then BCD converts it into machine friendly language i.e. in terms of '0' & '1'. In this case four OR gates are used.

NAME: Muhammad Ali Khan
Reg No: 16550

Q2:

(a) In case of 4×1 Multiplexer.
When $S_0 = 0$ and $S_1 = 0$ then output is D_0 .

S_0	S_1	Output
0	0	D_0

So output is 0

S_0	S_1	Output
0	1	D_1


So the output is 1 as $D_1 = 1$

S_0	S_1	Output
1	1	D_2

So the output is $D_2 = 0$

S_0	S_1	Output
1	0	D_3

So the output is $D_3 = 1$

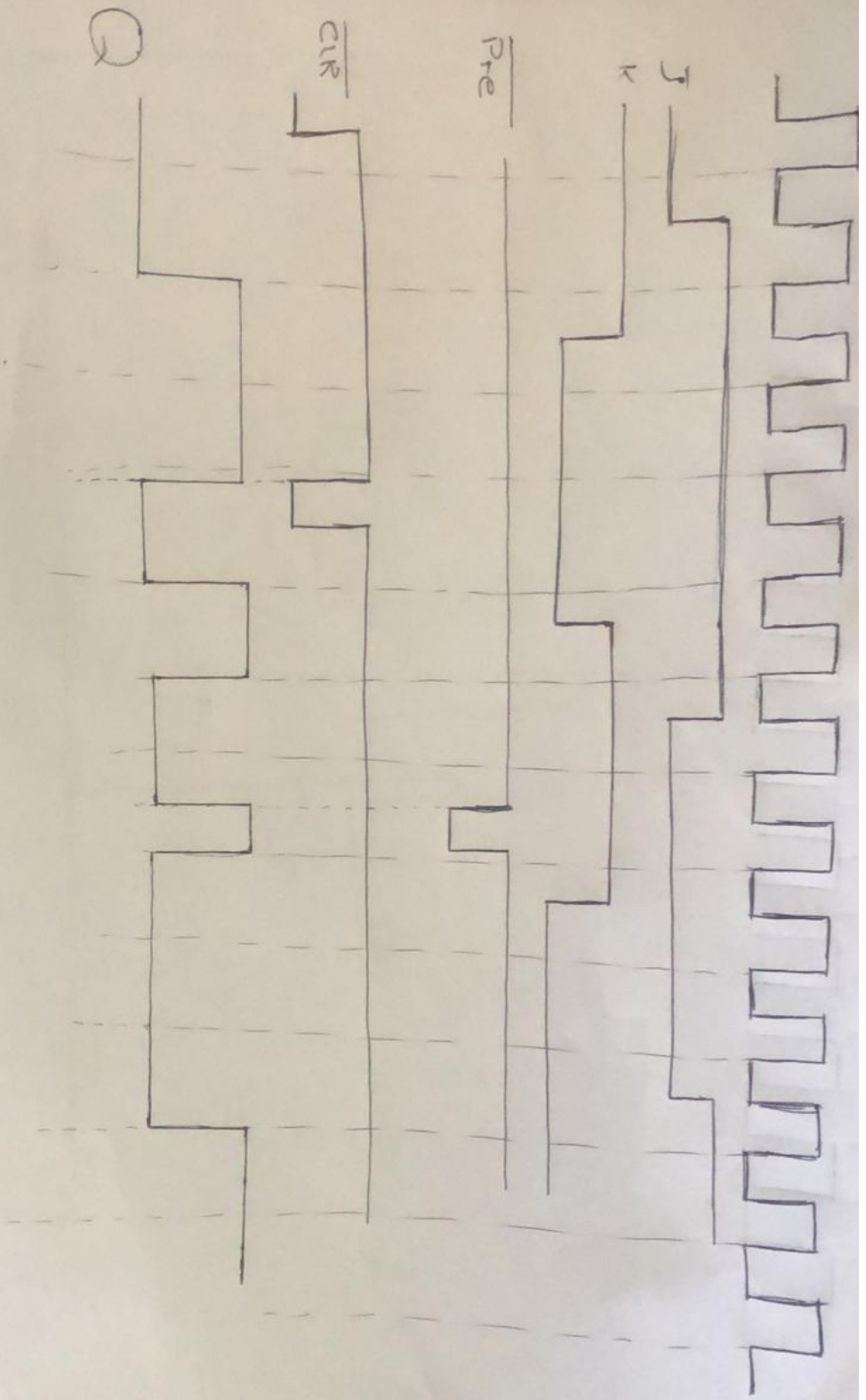


Question # 4


M. Ali Khan

Reg 16550

NAME: Muhammad Ali Khan
Reg No: 16550

Q5:

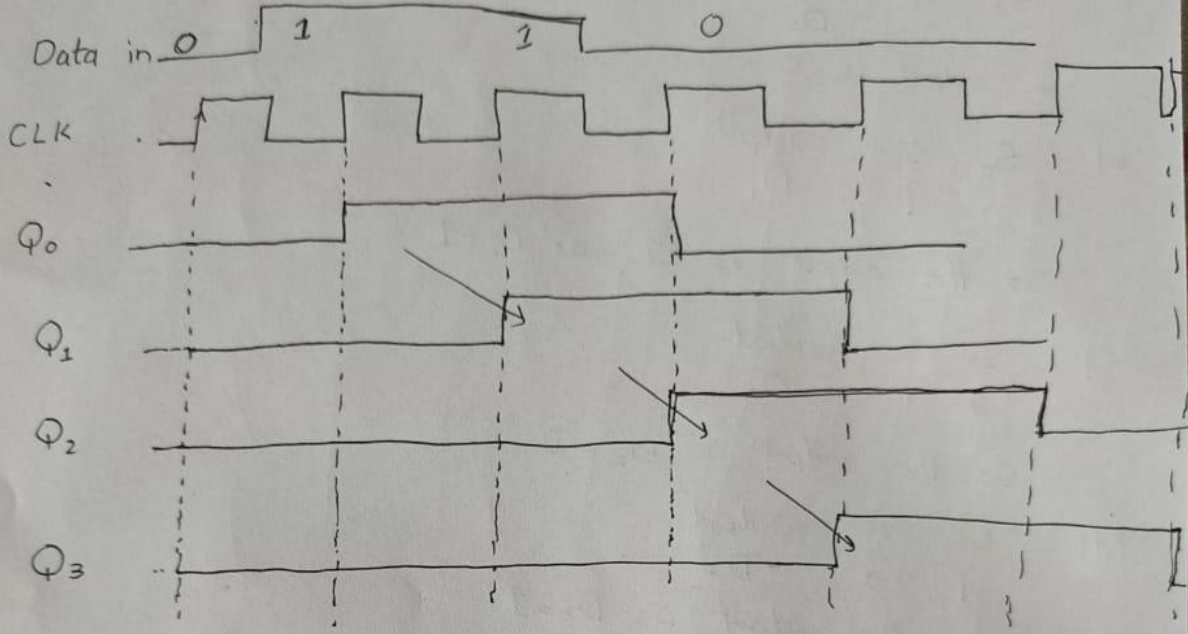

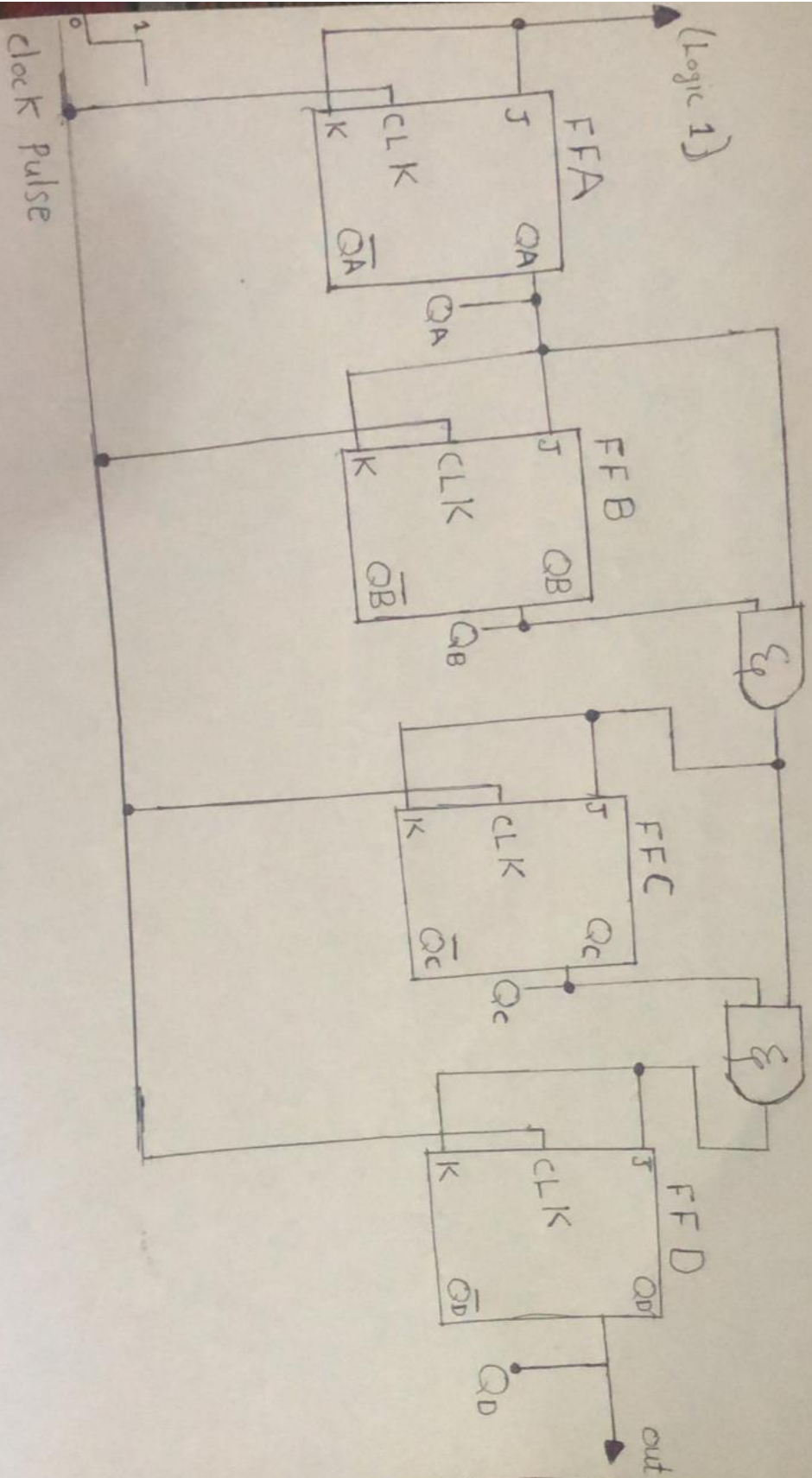


Question # 6
 M. Ali Khan Reg 16550

Name : Muhammad Ali Khan

16650

4-bit Synchronous Counter Waveform

 

Because this 4-bit synchronous counter counts sequentially on every clock pulse the resulting outputs count upwards from 0 (0000) to 15 (1111). Therefore, this type of counter is also known as 4-bit synchronous up counter.

However, we can easily construct a bit 4-bit synchronous down counter by connecting.