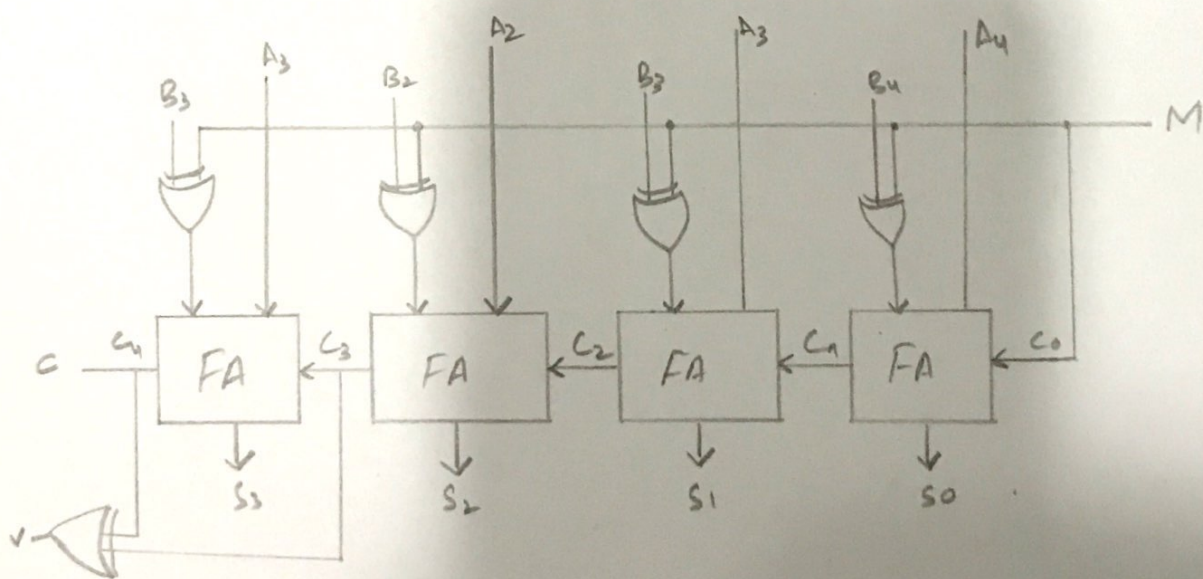


Q₂ Draw & explain the logic diagrams for each of the following.


a) - Four-Bit Adder-Subtractor

The addition & subtraction operation can be combined into one circuit with one common binary adder by including an exclusive-OR gate with each full adder. A four-bit adder-subtractor circuit is given below.



Q1

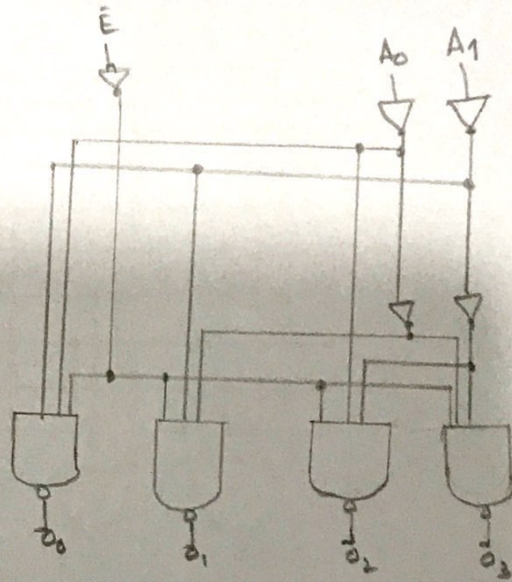
b) - Notice how NAND gates are used instead of ANDs as I have used in part a. That's why decoder outputs are typically active low. Recall that NAND gates are the simplest gates to make, requiring fewer transistors & less space.



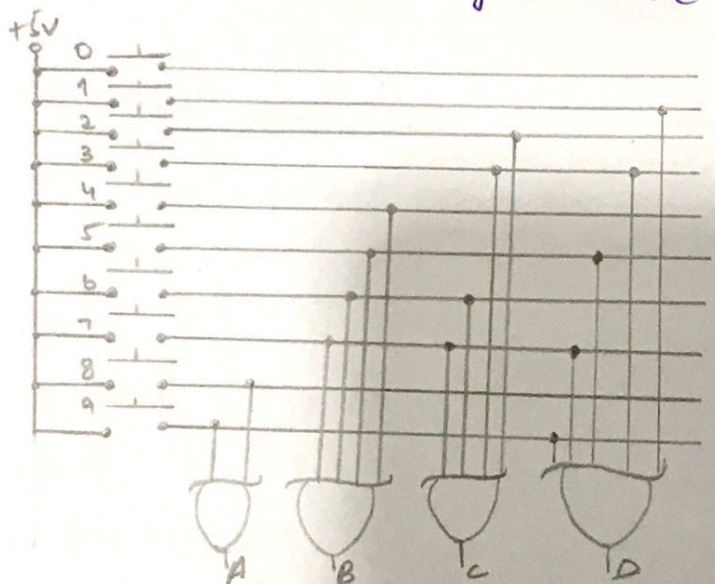Q1

C1- Decimal to BCD Encoder.

Encoders are the electronic equipment which converts one form of input into another one. Encoders are used to generate a coded output from a single active numeric input.



In Decimal to BCD encoder binary output in the form of '1's & '0's which is calculated in encoder as below.

Equations:

$$A = 8 + 9$$

$$B = 4 + 5 + 6 + 7$$

$$C = 3 + 4 + 6 + 7$$

$$D = 1 + 3 + 5 + 7 + 9$$

Q2 for the 4-input multiplexer, data inputs are given as.

Answer.

In multiplexer, the output Y takes the value of the input corresponding to the select bits. Select bits are S_1S_0 .

Using this we can find the value of Y given the select inputs.

a) $S_0 = 1, S_1 = 0$.

$$S_1S_0 = 01 \text{ (1 in decimal)}$$

$$\text{Thus, } Y = D_1 = 1.$$

b) $S_0 = 0, S_1 = 1$.

$$S_1S_0 = 10 \text{ (2 in decimal)}$$

$$\text{Thus, } Y = D_2 = 0.$$

c) $S_0 = 1, S_1 = 1$.

$$S_1S_0 = 11 \text{ (3 in decimal)}$$

$$\text{Thus, } Y = D_3 = 1.$$

d) $S_0 = 0, S_1 = 0$.

$$S_1S_0 = 00 \text{ (0 in decimal)}$$


$$\text{Thus, } Y = D_0 = 0.$$

Q3 Timing diagrams in Figure 09 shows inputs to a 9-bit parity checker. Draw the Σ Even & Σ odd output for the even parity checking.

Answer

For 9 bit parity checker circuit,

 
output is "1" when there are odd numbers of 1's in 9 bits otherwise output is "0".
we will plot waveform based on above criteria.



From plot, we get
its even for bit
time 1, 2, 3, 6, 7, 8 & 1
odd for 4, 5, 6
Even = 6
odd = 3.



Q4 The wave in the figure 02 are applied to the $J, K, CLK, \overline{PRE}$ & \overline{CLR} inputs as indicated. Determine the Q output, if the flip-flop is initially REST.

Answer.

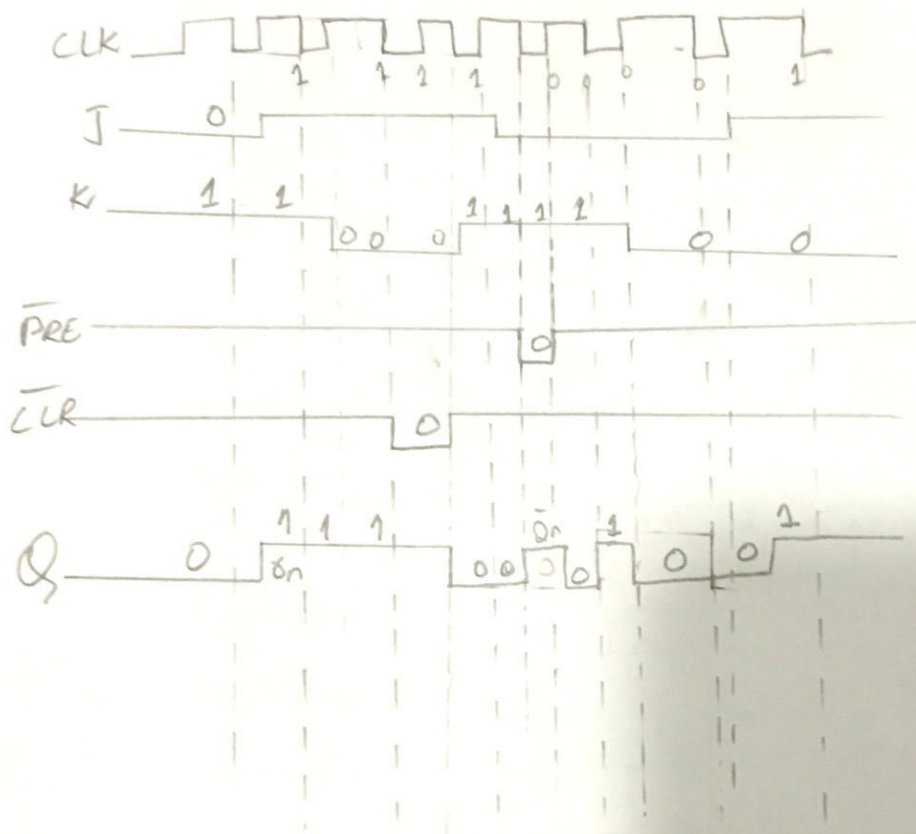

$\overline{PRE} = 0 \quad O/P Q = 1$
 $\overline{CLR} = 0 \quad O/P Q = 0$
} for one clock pulse.

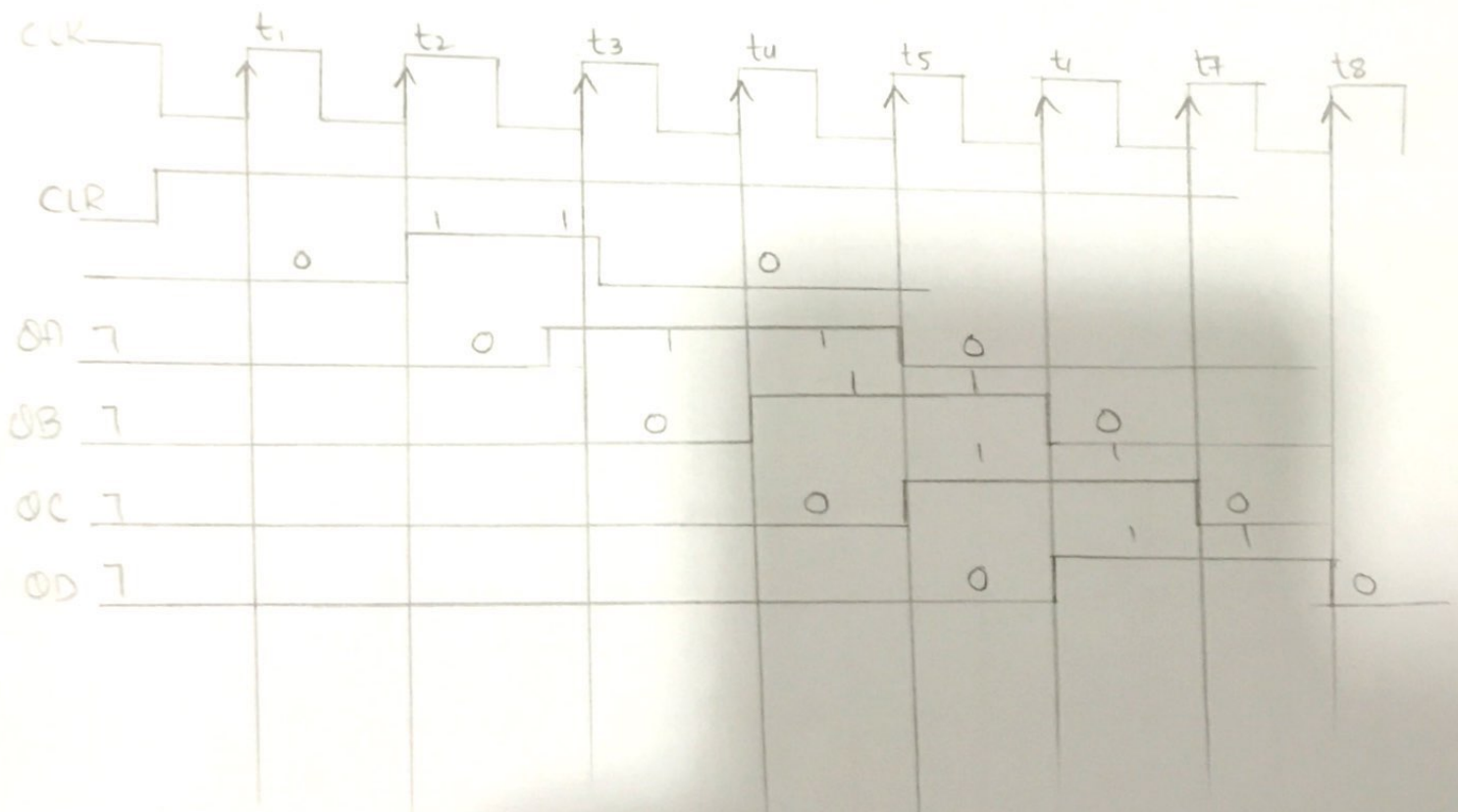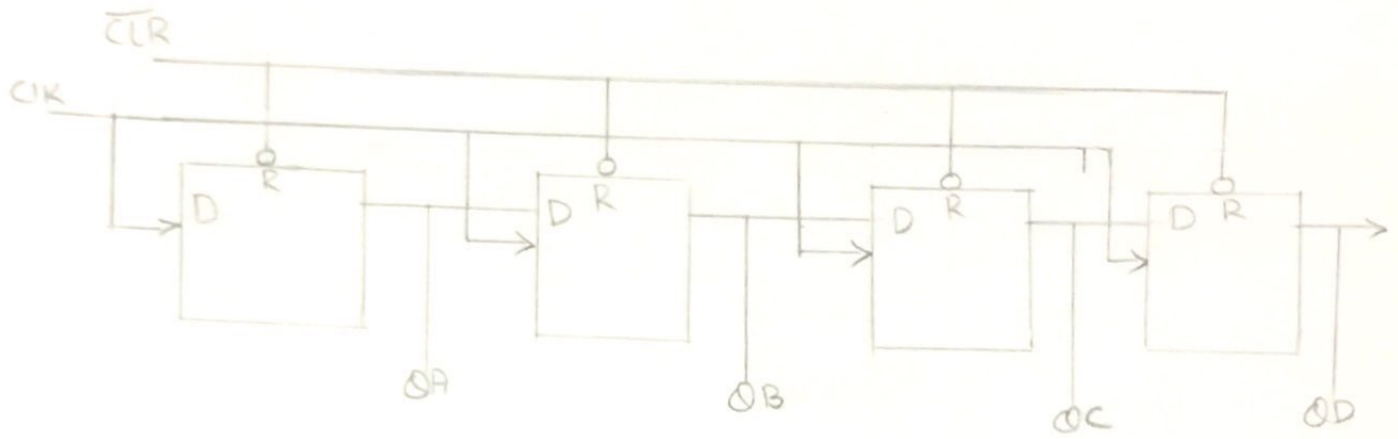Q5 Use the waveforms in figure 03 to draw the timing diagram for the parallel outputs (Q_1, Q_2, Q_3, Q_4) for the shift register. Assume that register is initially cleared.



Q6 Draw the logic diagram & timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

