

Haroon Rashid

Reg#16549


Semester: 6th

Subject: DLD Lab-9

Submitted to: Sir MUHAMMAD AMIN

Lab 10: Gray to Binary Code

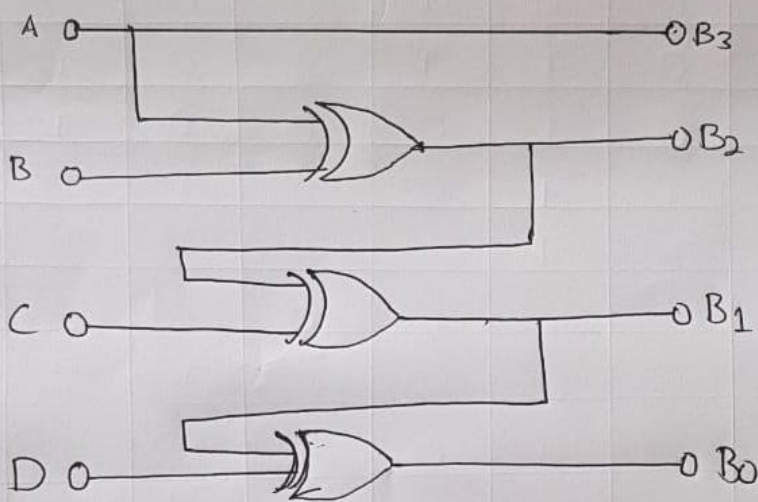Circuit Diagram of Binary to Gray Code Converter



Observation Table:

Input Variable: A B C D

Output Variable: B₃, B₂, B₁, B₀

KMAP Simplification:

For B₃

For B₂

For B₁

For B₀

Boolean Expression:


B₃? B₂? B₁? B₀?

Observation Table


Gray				Binary			
Inputs				Outputs			
A	B	C	D	B ₃	B ₂	B ₁	B ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

KMAP Simplification


Simplification for B₃

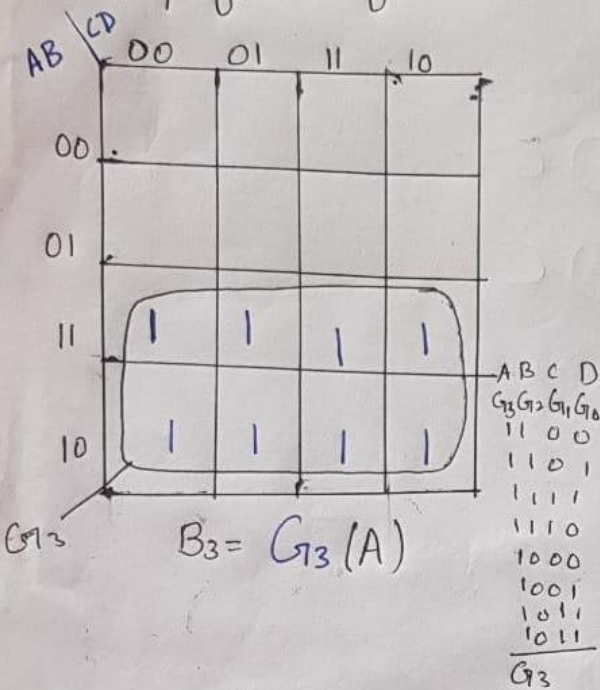


Simplification for B₂

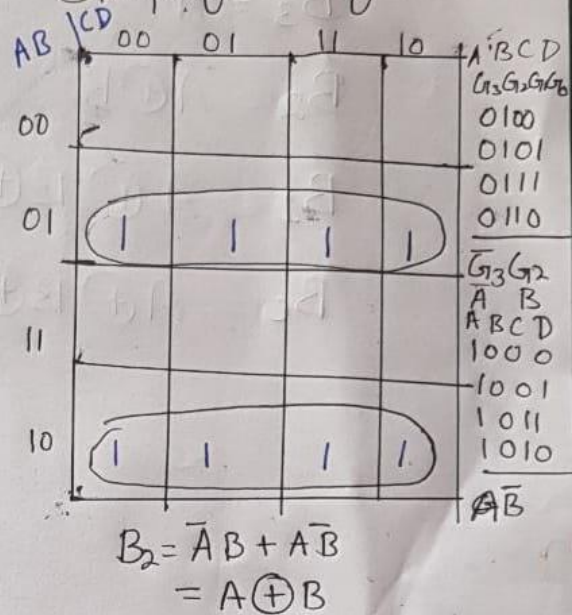

Simplification for B₁

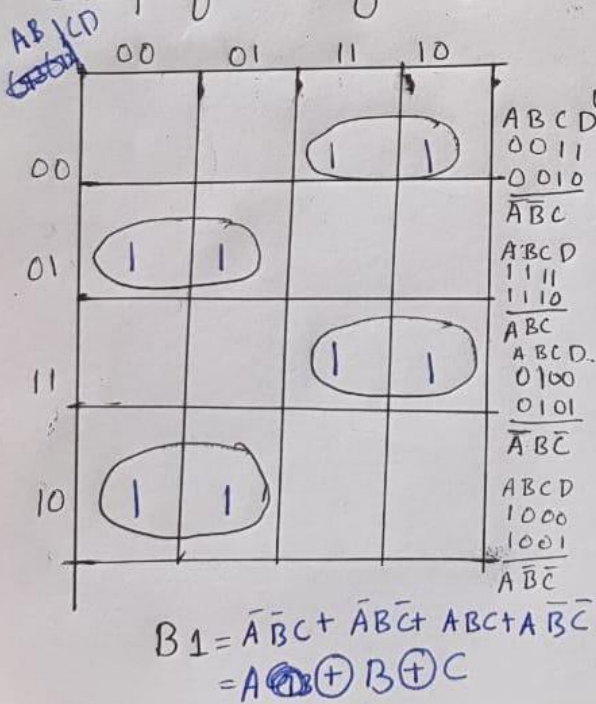

Simplification for B₀

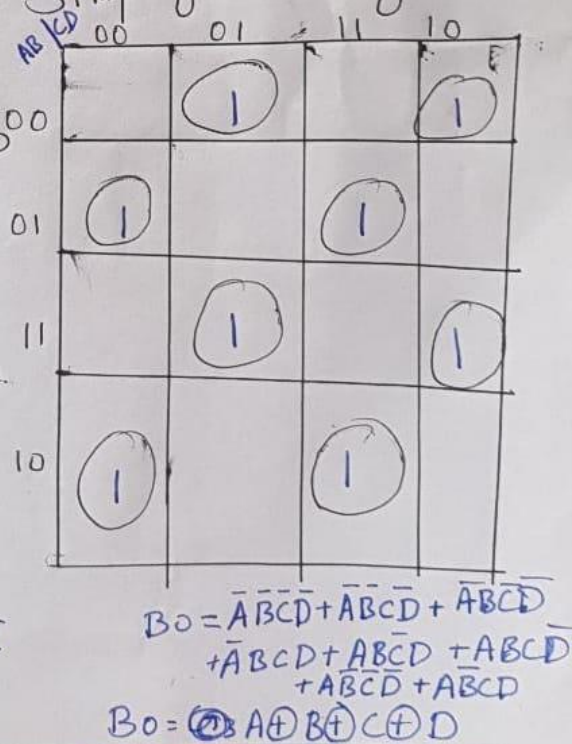

Boolean Expression:-

$$B_3 = A$$

$$B_2 = A \oplus B$$

$$B_1 = A \oplus B \oplus C$$

$$B_0 = A \oplus B \oplus C$$

1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

$$B = \bar{A}B + A\bar{B}$$

$$= A \oplus B$$

$$B = \bar{A}$$