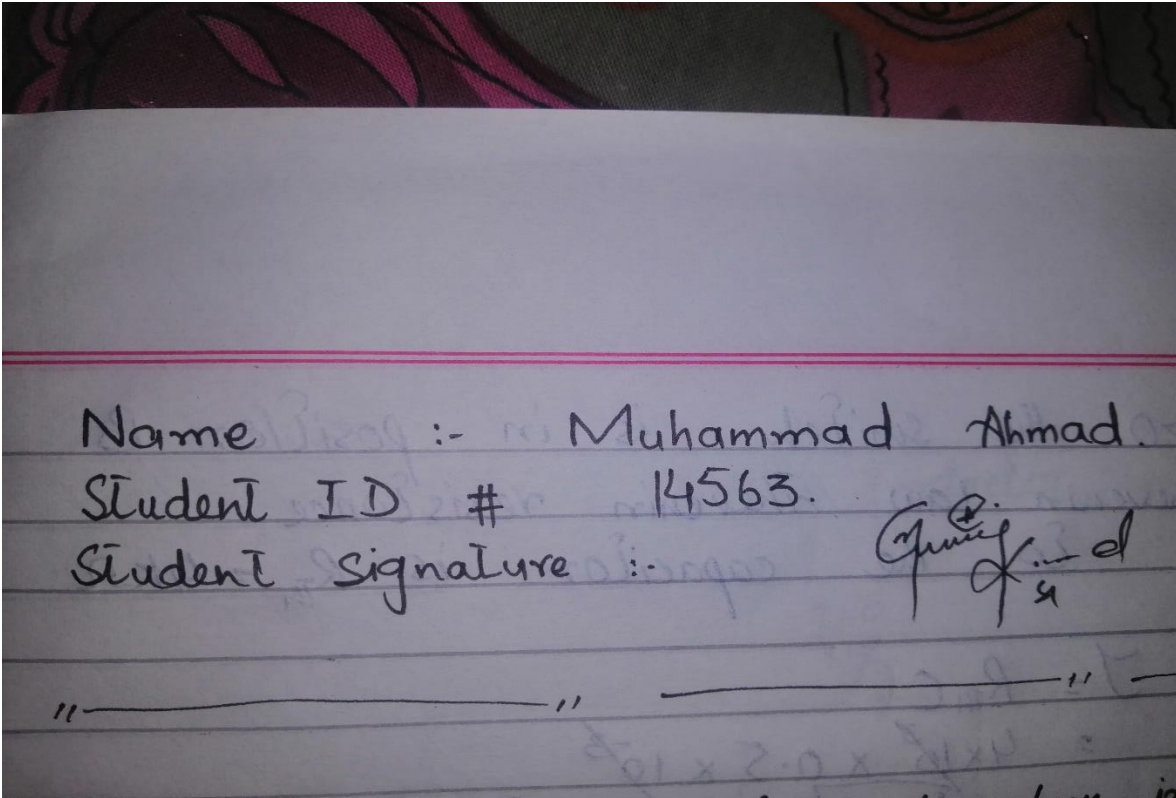


Department of Electrical Engineering

Course Title: Electrical Network Analysis


Module: 4th

Student Detail



Name :- Muhammad Ahmad.

Student ID # 14563.

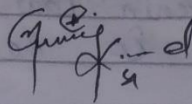Student signature :- 

QNo1:- The switch in fig 1 has been in position A for a long time. At  $t=0$  the switch moves to B. Determine  $v(t)$  for  $t > 0$  & calculate its value at  $t = 25$  & 85.

Solution:-

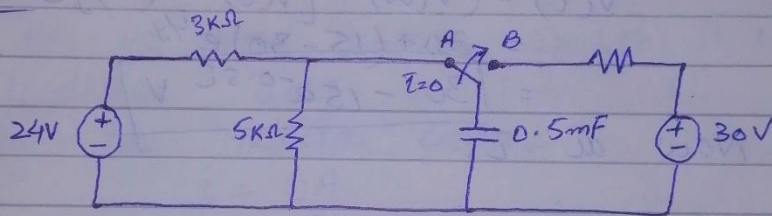


fig 1.

The capacitor acts as open ckt to dc when it is at position A. The voltage across the capacitor just before  $t=0$  is obtained by voltage division.

$$V(0^-) = \frac{5}{(5+3)k\Omega} (24) = 15V$$

Capacitor voltage can't change instantaneously because of storing quality.

$$V(0) = V(0^-)$$

$$V(0) = 15V.$$

(1)



When  $t > 0$  the switch is in position B  
As per Thevenin Law Thevenin resistance  
connected to the capacitor is  $R_{th} = 4k\Omega$

$$\begin{aligned} \tau &= R_{th}C \\ &= 4 \times 10^3 \times 0.5 \times 10^{-6} \\ &= \boxed{2s} \end{aligned}$$

As we discuss capacitor act as  
open ckt to dc

$$V(\infty) = 30V.$$

Now

$$\begin{aligned} V(t) &= (V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}) \\ &= 30 + (15 - 30)e^{-t/2} \\ &= \boxed{30 - 15e^{-0.5t} V} \end{aligned}$$

Now at  $t$ .

When  $t = 2s$

$$\begin{aligned} V(2) &= 30 - 15e^{-2/2} \\ &= 30 - 15e^{-1} \\ &= 30 - 15e^{-1} \\ &= 30 - 15(0.3678) \\ &= 30 - 5.517 \\ &= \boxed{24.483V} \end{aligned}$$

When  $t = 0s$ .

$$\begin{aligned} V(0) &= 30 - 15e^{-0/2} \\ &= 30 - 15e^{-0} \\ &= 30 - 15(1) \\ &= 30 - 15 \\ &= 15 \\ &= \boxed{15V} \end{aligned}$$

(2)

QNO2:- Determine the Inductor current for both  $t > 0$  &  $t < 0$  for the ckt.

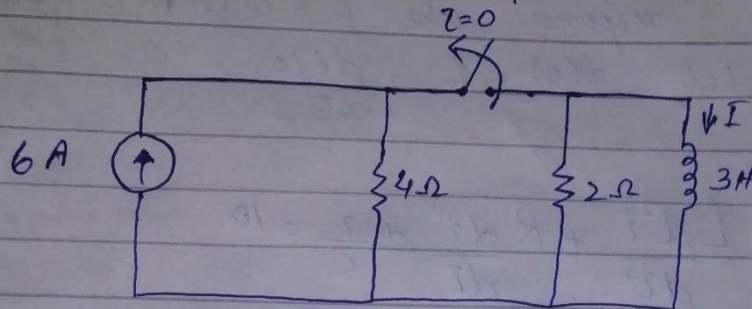


Fig 2

Solu Elong

As we know  $t < 0$  the switch is closed and Inductor acts as short ckt.

Thus the inductor current

$$i = 6A.$$

For  $t > 0$  the switch is open & Time constant  $\tau = \frac{L}{R}$

$$\tau = \frac{3}{2}.$$

Now the inductor current  $i(t) = 6e^{-t/\tau}$

$$i(t) = 6e^{-t/3/2}$$

$$i(t) = 6e^{-\frac{2t}{3}} \text{ A}$$

" " " "

(3)

Answer  $i(t) = 6e^{-\frac{2t}{3}} u(t) \text{ A}$



QNO3:- A series RLC circuit is describe by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10.$$

find the response when  $L = 0.5H, R = 4\Omega$  &  
 $C = 0.2F, \text{Let } i(0) = 1, \frac{di(0)}{dt} = 0.$

Solution:-

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divided by L

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10}{L}$$

Multiply  $\frac{C}{C}$  on R.H.S.

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10C}{LC}$$

And  $C = 0.2F.$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10(0.2)}{LC}$$

Substitute

$$\frac{d^2 i}{dt^2} + B \frac{di}{dt} + 10i = 20 \rightarrow (1)$$

The general eq for source free series RLC circuit is given by

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{1}{LC} \rightarrow (2)$$

Compare ① and ②.

$$\frac{R}{L} = 8 \rightarrow \textcircled{3}$$

$$\frac{1}{LC} = 10 \rightarrow \textcircled{4}$$

$$\frac{I_s}{LC} = 20 \rightarrow \textcircled{5}$$

from ③

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/s} \rightarrow \textcircled{6}$$

The natural frequency  $\omega_0$  is given by

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

from (4)

$$\omega_0 = \sqrt{10} \text{ rad/s} \rightarrow \textcircled{7}$$

from 6 and 7

$$\alpha > \omega_0$$

$\therefore$  the ckt is over damped.

The roots of the characteristic equation are given by.

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 + \sqrt{4^2 - 10}$$

$$= -4 + \sqrt{6} \text{ rad/s}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 - \sqrt{4^2 - 10}$$

$$= -4 - \sqrt{6} \text{ rad/s}$$

From 5, the steady state  $I$  is given

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2$$

$$= 2 \text{ A} \rightarrow \textcircled{8}$$

⑤



The current is over damped case is given

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

Substitute  $t = 0$ ,

$$i(0) = I_s + A_1 + A_2$$

$$1 = 2 + A_1 + A_2$$

Thus  $A_1 + A_2 = -1 \rightarrow (10)$

From (9) Find  $\frac{di(t)}{dt}$ .

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$t = 0$$

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Putting value.

$$(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0 \rightarrow (11)$$


Solve (10) and (11) &

$$A_1 = -1.316$$

$$A_2 = 0.316$$

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t} \text{ A}$$

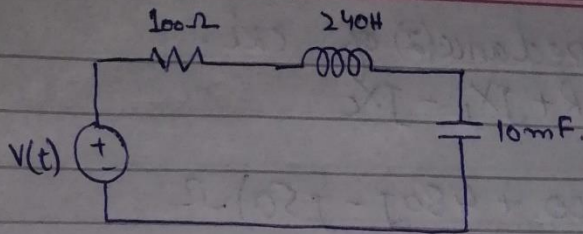Q No 4:- A series RLC ckt has  $R = 100 \Omega$ ,  
 $L = 240 \text{ mH}$  and  $C = 10 \text{ mF}$ . If the input  
voltage is  $v(t) = 10 \cos 2t$ , Find  
the current flowing through the  
ckt.



Solution:-

$$v(t) = 10 \cos 2t \text{ V}$$

Here

The amplitude  $V_m = 10 \text{ V}$ .

The angular frequency  $\omega = 2 \text{ rad/s}$ .

The phase angle  $\phi = 0^\circ$ .

$\therefore$  The phasor is a complex number that represents the amplitude & phase of a sinusoid

$$v(t) = 10 \angle 0^\circ \text{ V}$$

Now Inductive ~~Resistance~~ Reactance of the ckt.

$$X_L = \omega L$$

$$X_L = (2 \text{ rad/s}) (240 \text{ H})$$

$$= 480 \Omega$$

Now the capacitive Reactance of ckt.

$$X_C = \frac{1}{\omega C}$$

$$= \frac{1}{(2 \text{ rad/s})(10 \text{ m} \times 10^{-3})}$$

$$= \frac{1}{20 \times 10^{-3}} \Omega$$

$$= \frac{50}{1000} \Omega$$

⑦

$$50 \Omega$$



Now the impedance ( $Z$ ) of ckt.

$$Z = R + jX_L - jX_C$$

$$Z = (100 + 480j - j50) \Omega$$

$$(100 + j430) \Omega$$

(Z) Impedance in Phasor Form.

$$Z = \sqrt{100^2 + 430^2} \angle \tan^{-1} \left[ \frac{430}{100} \right]$$

$$\sqrt{10000 + 184900} \angle \tan^{-1} 4.3$$

$$\sqrt{194900} \angle (76.9081)$$

$$= 441.47 \angle 76.9081^\circ \Omega$$

$$= 441.47 \angle 76.9081^\circ \Omega$$

Current ( $I$ ) for the ckt.

$$i = \frac{V(t)}{Z}$$

substitute  $10 \angle 0^\circ \text{V}$  for  $V(t)$

$$i = \frac{10 \angle 0^\circ \text{V}}{441.47 \angle 76.9081^\circ \Omega}$$

$$= \frac{10}{441.47} \angle [0 - (76.9081)]^\circ \text{A}$$


$$= 22.65 \angle -76.90^\circ \text{mAmp}$$

$$i = 22.65 \cos(2t - 76.90^\circ) \text{mA}$$

$$i = 22.65 \cos(2t - 76.90^\circ) \text{mA}$$

Q No 5 Find  $V(t)$  and  $i(t)$  in the ckt  
 - Shown in fig 3.

Solution:-

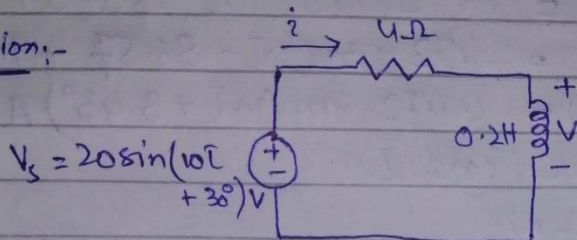

$$V_s = 20 \sin(10t + 30^\circ) \text{ V.}$$

$$V_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V.}$$

$$V_s = 20 \cos(10t - 60^\circ) \text{ V.}$$

$$V_s = 20 \angle -60^\circ \text{ V.}$$


$$\omega = 10 \text{ rad/sec.}$$

$$X_L = j\omega L.$$

$$0.2 \text{ H} = j \times 10 \times 0.2.$$

$$0.2 \text{ H} = j 2 \Omega.$$

Given ckt can be represented as.

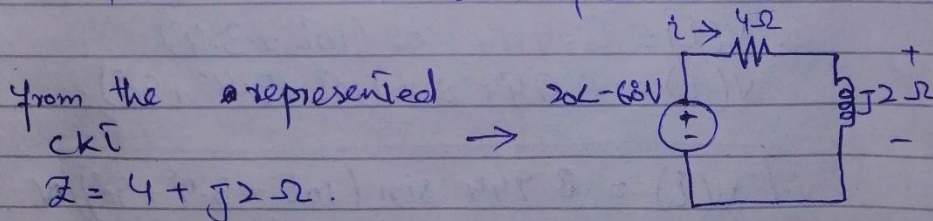

Hence the current is

$$I = \frac{20 \angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1} \left( \frac{2}{4} \right)}$$

$$I = \frac{20 \angle -60^\circ}{4.472 \angle \tan^{-1}(0.5)}.$$

$$I = \frac{20 \angle -60^\circ}{4.472 \angle 26.57^\circ}.$$



$$I = 4.472 \angle -86.57^\circ$$

Now  $i(t) = 4.472 \cos(10t - 86.57^\circ)$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

Voltage across inductor

$$V = j2 \times i$$

$$V = j2 \times (4.472 \angle -86.57^\circ)$$

Converting polar form to Rectangular form.

$$V = j2 \times (0.26756 - j4.464)$$

$$V = 8.928 + j0.53512$$

$$V = \left( \sqrt{(8.928)^2 + (0.53512)^2} \right) \angle \tan^{-1} \left( \frac{0.53512}{8.928} \right)$$

$$V = 8.944 \angle 3.4^\circ$$

$$V(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$V(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$V(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ) \text{ V}$$