

NAME M. Zeeshan

ID 16529

Subject LCA

Dept: BE/Electrical


Semester 2<sup>nd</sup>

Date /24/6/2020/

Assignment Final Term:

Q.1) Find the value of  $i_x$  for the circuit using

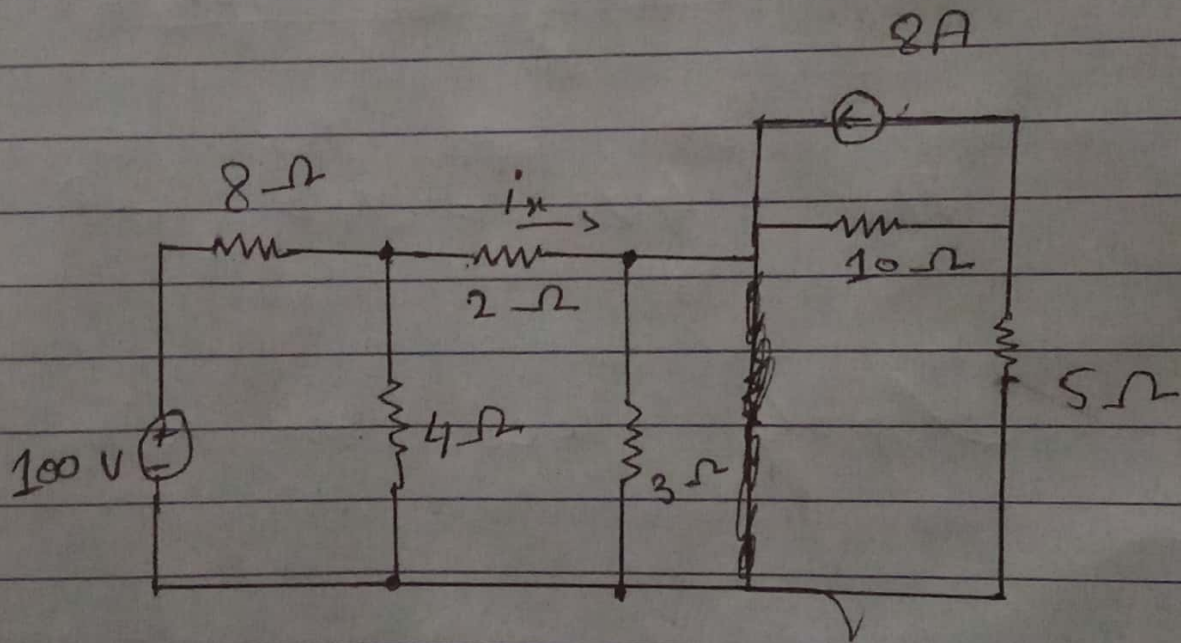- i) Nodal Analysis.
- ii) Mesh Analysis.
- iii) SuperTheorem
- iv) Compare the number of steps and degree easiness of all the three methods with each other.



# Node Analysis!

Apply KCL on node 1:

$$\frac{4-100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{4-100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Apply KCL on Node (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3 = 0$$

$$-30V_1 + 53V_2 - 3V_3 = 240 \quad \text{--- (2)}$$

Apply KCL on Node (3)

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (3)}$$

Taking equation (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7}$$

Taking equation (2) ~~(1)~~ (3)

$$-V_2 + 3V_3 = 100$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting equation (a) and (b)  
in equation (3)

$$-30(0.5702 + 14.28) + 5302 - 3(0.3302 - 26 \cdot 26.67) = \cancel{240} 240$$

$$-17.102 - 428.4 + 5302 - 0.9902 + 80.01 = \cancel{6000} \\ = 240$$

$$34.91 V_2^{T_{00}} = 828.39$$

$$V_2 = 828.39$$

$$\boxed{V_2 = 20.31}$$

putting in equation (a)


$$V_1 = \frac{4(20.31) + 100}{7}$$

$$V_1 = 25.89$$

$$i_x = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$\boxed{i_x = 2.79 A}$$

## Mesh analysis.

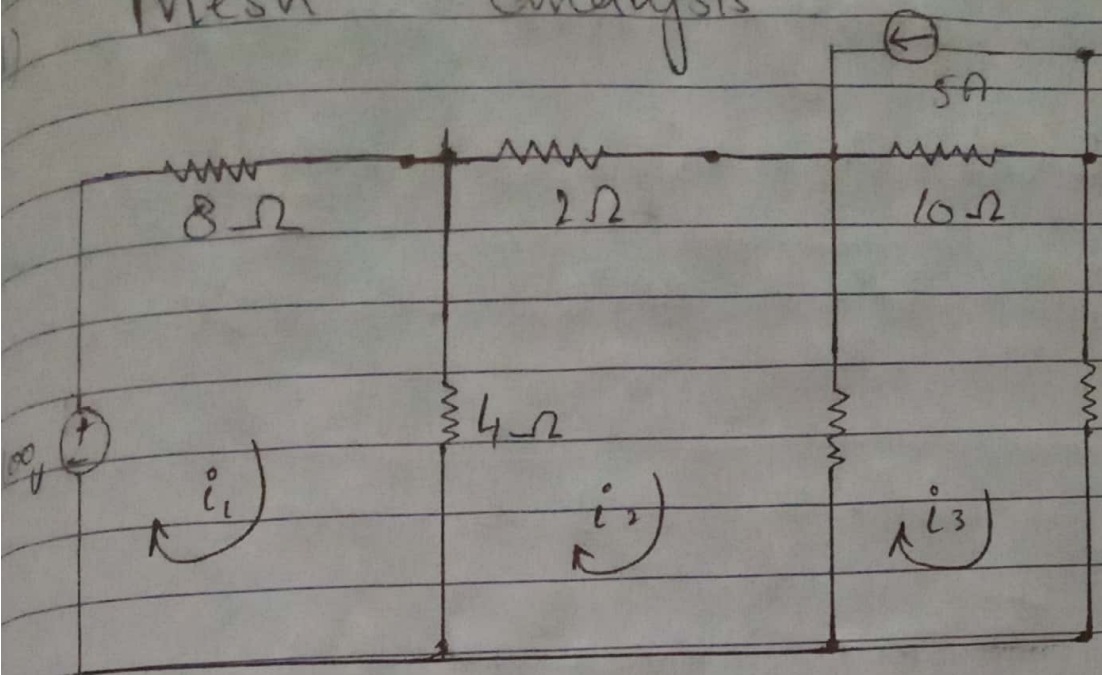

Apply KCL on loop (1)

$$8i_1 + 4(i_1 - i_2) = 100$$

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Apply KCL on loop (2)

$$4i_2 + 4(i_2 - i_1) + 3(i_3 - i_2) = 0$$

$$4i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_1 + 5i_2 + 3i_3 = 0 \quad \text{--- (2)}$$

Apply rule on loop (3)

$$3(i^3 - i^2) + 10(i^3 - i^4) + 5i^3 = 0$$

$$3i^3 - 3i^2 + 10i^3 - 10i^4 + 5i^3 = 0$$

$$\text{As } i^4 = 8$$

$$-3i^2 + 18i^3 = -80$$

Taking equation (1)

$$i^1 = \frac{4i^2 - 100}{12}$$

Taking equation (3)

$$-3i^2 + 18i^3 = -80$$

$$i^3 = \frac{-3i^2 + 80}{18} \quad (b)$$

putting eq (a) and (b) in equation (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

$$7.2i_2 = +20$$


$$i_2 = \frac{20}{7.2} \quad \cdot \quad i_2 = i_x$$

$$i_2 = 2.79 \text{ A} \quad \Rightarrow \quad i_x = 2.79 \text{ A}$$

(iii)

Super position

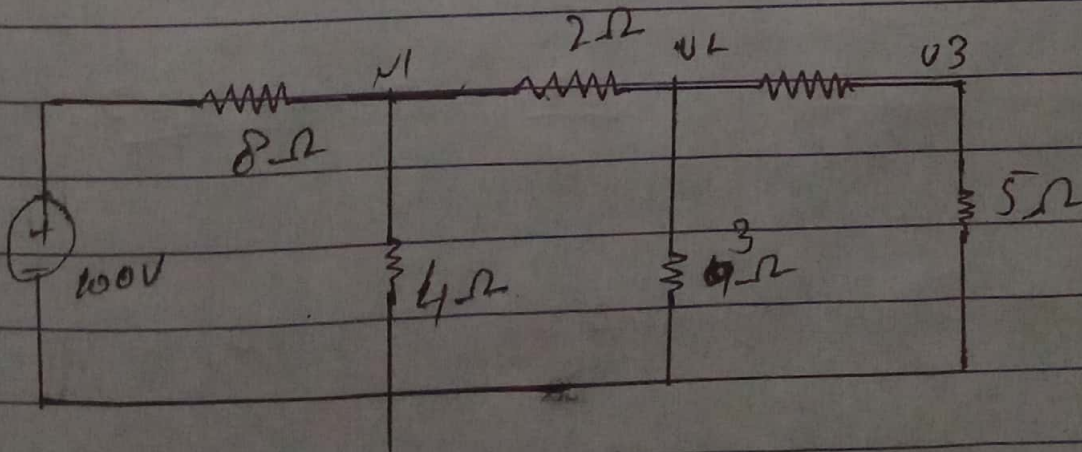First removing the current source and making it an open circuit. Re drawing the circuit.





Apply KCL on Node (1)

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$V_1 - 10 + 4V_1 - 4V_2 + 2V_1 = 0$$

$$7V_1 - 4V_2 = +100$$

Apply KCL on Node (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 - 53V_2 - 3V_3 = 0$$

Apply KCL on Node (3)

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{U_3 - U_2 + U_3}{10} = 0$$

$$-U_2 + 2U_3 = 0$$

Now taking equation ① and ②

$$7U_1 - 4U_2 = 100$$

$$U_1 = \frac{4U_2 + 100}{7} \quad \text{--- (a)}$$

Now  $-U_2 + 3U_3$

$$U_3 = \frac{1}{3} U_2 \quad \text{--- (b)}$$

putting on eq (2)

$$-30(0.57U_2 + 14.28) - 4U_2 + 2(0.33U_2) = 0$$

$$-17.1U_2 - 428.4 - 4U_2 + 0.66U_2 = 0$$

$$20.44U_2 = 428.4$$

$$U_2 = -20.95$$


putting on equation (a)

$$V_2 = 2.31$$

$$i_4 = 2.31 + 20.95$$

$$i_1 = 11.63$$

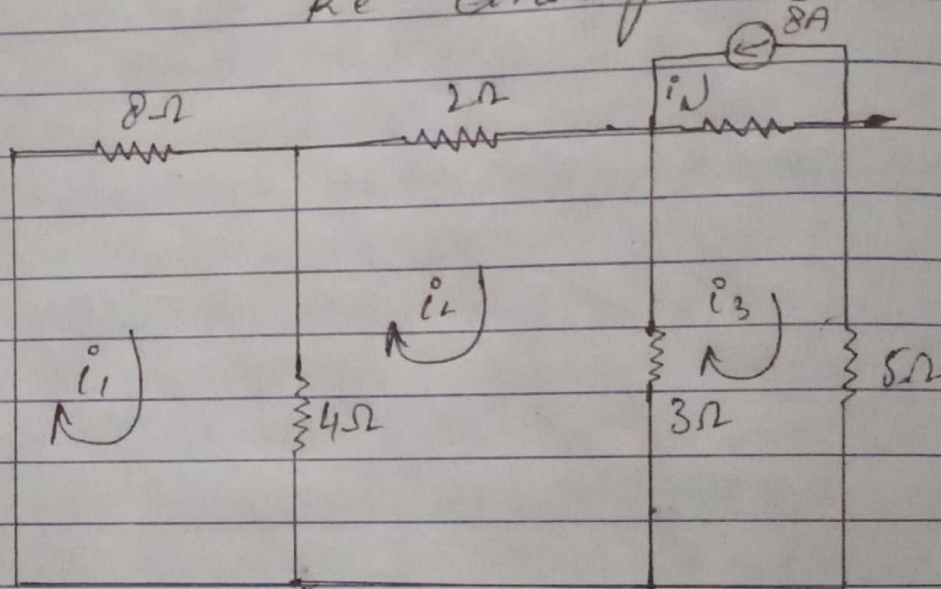Now removing voltage source and making it short circuit  
Re drawing circuit.



$$i_4 = 2A$$

Apply KVL on loop 1

$$2i_1 + 4(i_1 - i_2) = 0$$

$$2i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Apply KVL on loop (2)

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 = 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 - 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop (3)

$$10i_3 - 5i_3 + 3i_3 - 2i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \quad \text{--- (4)}$$

Taking equation (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (5)}$$

$$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$$

$$i_2 = 1.354$$

Now  $i_x = i_1 + i_2$

$$i_x = 1.44 + 1.35$$

$$i_x = 2.79 \text{ A}$$

$$\boxed{i_x = 2.79 \text{ A}}$$

(iv) Compare the number of Step and degree of easiness of all the three method with each other.

Sol:-

The number of Step of nodal and mesh analysis are all most equal but in Superposition the number of Step are almost of mesh and nodal analysis.

Degree of easiness.


According to my opinion mesh analysis is easier than nodal analysis & Superposition Theorem.

Q20250


Consider  $200\ \Omega$  resistor in figure as load resistor and develop

- (i) Thevenin equivalent circuit
- (ii) Norton equivalent circuit

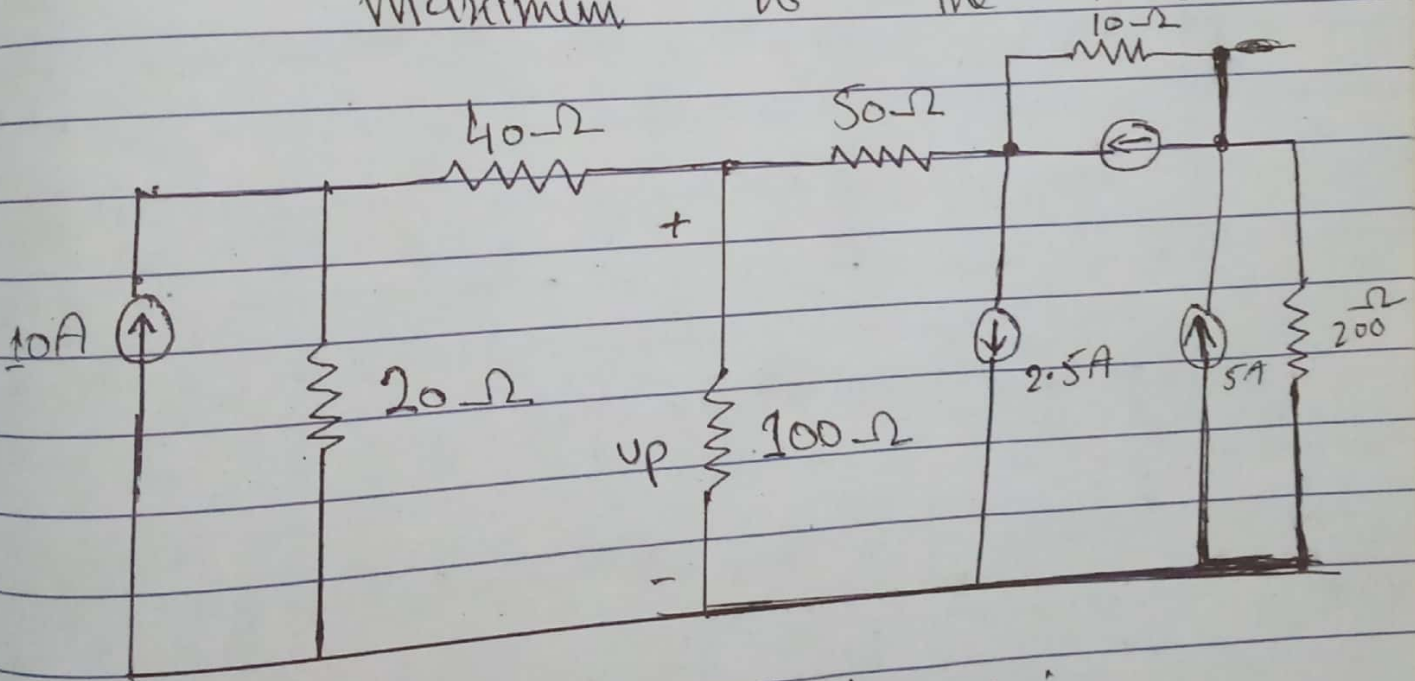(iii) Find out what value of Thevenin resistance should be used to deliver maximum to the load




Solving for thevenin

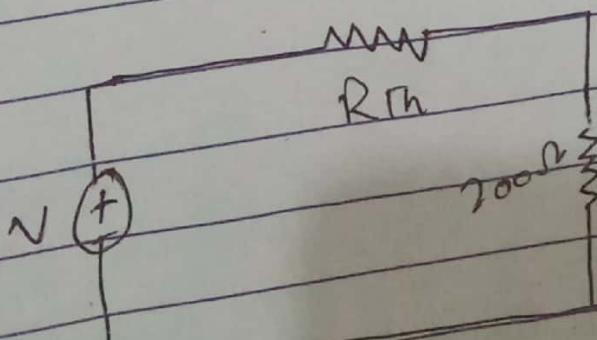

we will find  $R_{th}$  for which  
 we will remove all the  
 current + source & short  
 circuit the load resistor

Redrawing The circuit

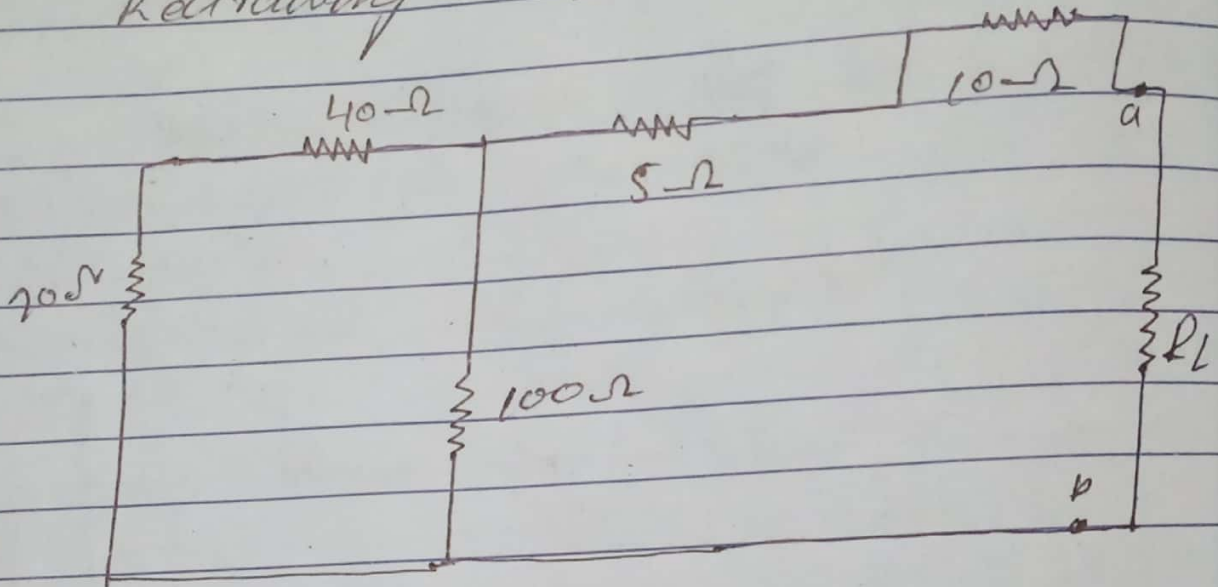

adding the resistance

$$20 + 40 \parallel 100 + 5 + 10$$

$$60 \parallel 100 + 15$$

$$\frac{60 \times 100}{60 + 100} + 15$$


$$60 + 100$$

$$37.5 + 15$$

$$R_{th} = 52.5$$



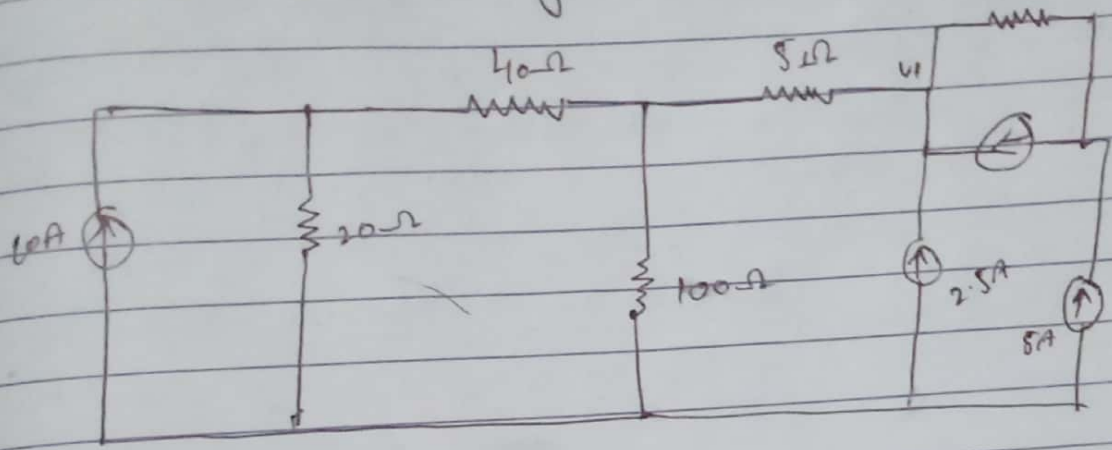For finding  $V_{Th}$  applying nodal analysis



Apply KCL on  $V_1$

$$\frac{V_1 - V_2}{40} + \frac{V_1}{20} = 10$$

$$\frac{V_2 - V_2 + 2V_2}{40} = 10$$

Apply KCL on node (2)

$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{5}$$

$$50V_2 - 50V_1 + 20V_2 + 400V_3 - 400V_3$$

8000

$$-50V_1 + 70V_2 - 400V_3 = 0$$

200

$$-0.05V_1 + 0.035V_2 - 0.2V_3 = 0$$

Apply KCL on node (3)

$$\frac{V_3 - V_2}{5} + \frac{V_3 - V_4}{10} = 2.5 + 2$$

$$\frac{2V_3 - 2V_2 + V_3 - V_4}{10} = 4.5$$

$$-2V_2 + 3V_3 - V_4 = 45 \quad \text{--- (3)}$$

Apply KCL on node 4

$$\frac{V_4 - V_3}{10} = 5 - 2$$

$$V_4 - V_3 = 30 \quad \text{--- (4)}$$

Solving by using Calculator

$$V_1 = 275$$

$$V_2 = -124.9$$


$$V_3 = -87.5$$

$$V_4 = -57.5$$

$$I_{TH} = \frac{5-1}{52.5 + 200}$$

$$I_{TH} = 0.02$$

(ii) For Norton's Theorem

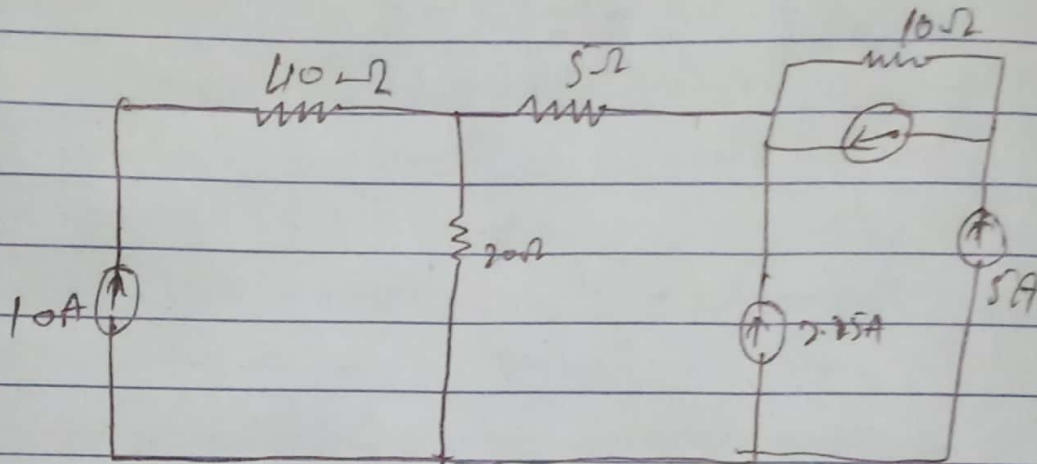

For  $R_N$  will be

$$R_N = R_{TH}$$

$$R_N = 52.5$$

find  $I_n = v_{th}$

$$I_n = 0.09$$

As the circuit one source  
we find it directly

Using Thevenin for finding


we know that

$$P = \left( \frac{R_{th}}{R_{in} + R_L} \right)^2 R_L$$

$$= \left( \frac{5.1}{52.5 + 200} \right)^2 200$$

$$P = 0.08W$$

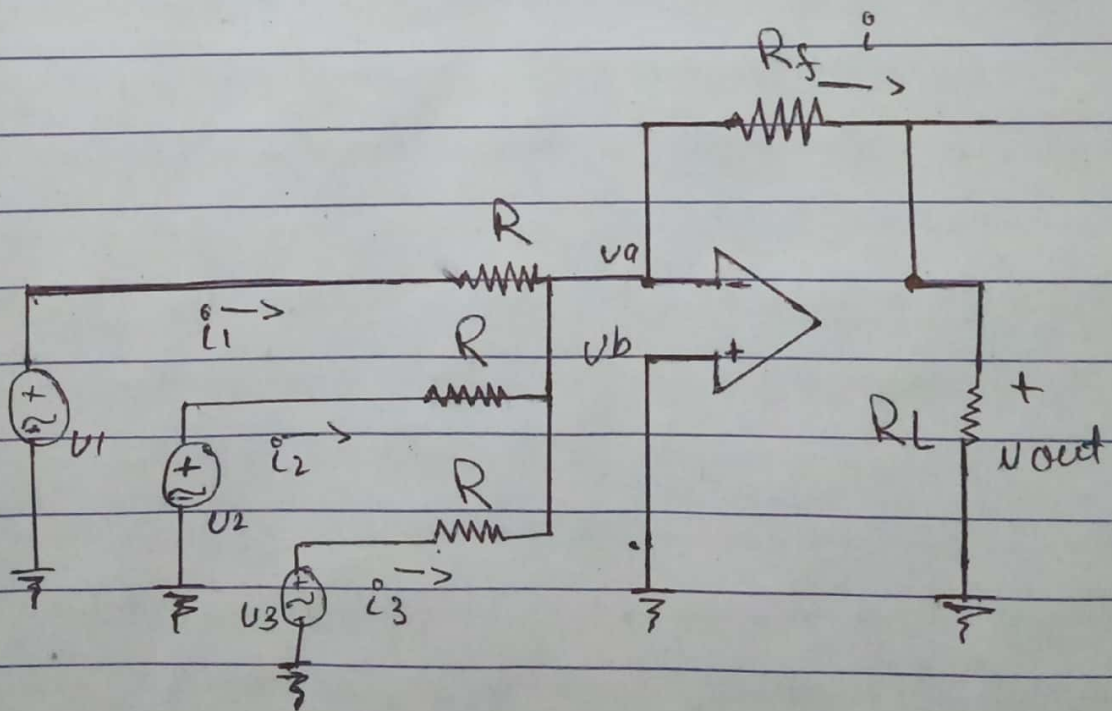Q3 obtain an expression for  $v_{out}$  in terms of  $v_1$ ,  $v_2$  and  $v_3$  for the op amp circuit in figure also known as a summing amplifier.



Solution:

We know that all the current is entering to the inverting terminal or we know that the current enter to inverting or non-inverting are virtually zero

Now 
$$i = i_1 + i_2 + i_3$$

Therefore we are taking node  $v_a$  as maintain on the circuit above

As current  $I$  is flowing from  $v_a$  to  $v_{out}$  as  $v_a$  will be at high potential writing equation.

$$0 = \frac{v_a - v_{out}}{R_f} + \frac{v_a - v_1}{R} + \frac{v_a - v_2}{R} + \frac{v_a - v_3}{R}$$

Now that the potential between inverting and non-inverting terminal is zero.

$$v_a = v_b = 0$$

So the equation will become:

$$0 = \frac{v_{out}}{R_f} + \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R}$$

$$-\frac{v_{out}}{R_f} = \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R}$$

$$-v_{out} = R_f \left( \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R} \right)$$

$$v_{out} = -\frac{R_f}{R} (v_1 + v_2 + v_3)$$

S M T W T F S

Date:.....

In this case where  $u_2 = u_3 = 0$   
we see that our rules  
agress.

(Thank you Sir)