

Sessional Assignment

Course Electric Network Analysis

Module 4th

Instructor Dr. Sharyar


Name Farhan Ali

ID 14873

Signature 

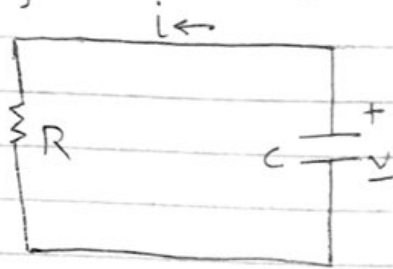Q1: For the circuit in Fig 1.
if $v = 10e^{-4t}$ & $i = 0.2e^{-4t}$ $t > 0$

Find R & C (b)..... (c)..... (d).....
50% of the initial energy.



Step 1

$$(A) \quad \tau = RC = \frac{1}{4}$$

$$\Rightarrow -1 = C \frac{dv}{dt}$$

$$\Rightarrow -0.2e^{-4t} = C(10)(-4)e^{-4t}$$

$$\Rightarrow C = 5 \text{ mF}$$

$$R = \frac{1}{4C} = 50 \Omega$$

Step 2

$$(B) \quad \tau = RC = \frac{1}{4} = 0.250$$

Step 3

$$(C) \quad W_C(0) = \frac{1}{2} CV^2$$

$$\Rightarrow \frac{1}{2} (5 \times 10^{-3})(100)$$

$$\Rightarrow 250 \text{ mJ}$$

Step 4

$$(D) \quad W_R = \frac{1}{2} \times \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{1}{2} C V_0^2 (1 - e^{-2t_0})$$

$$0.5 = 1 - e^{-8t} \Rightarrow e^{-8t_0} = \frac{1}{2}$$

OR


$$e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2)$$

$$= 86.6 \text{ ms.}$$

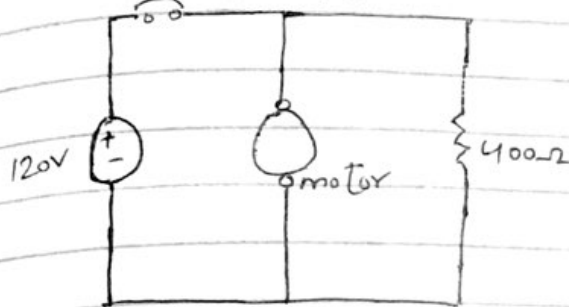Q2:-

120-V dc generator energize a motor whose coil. The breaker is tripped.



Let the inductor current.

For $t < 0$

$$i(0) = \frac{120}{100} = 1.2$$

$$\Rightarrow \frac{6}{5} = 1.2 \text{ A}$$

For $t > 0$ we have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100+400}$$

$$= \frac{50}{500} \Rightarrow \frac{5}{50} \Rightarrow \frac{1}{10} \Rightarrow \boxed{0.1}$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 1.2 e^{-10t}$$

At $t = 100 \text{ ms} = 0.1 \text{ s}$

$$i(0.1) = 1.2 e^{-1} = 0.441 \text{ A}$$

Q39-

the Response of Series RLC circuit the value of R, L, C

Series RLC circuit
 $v(t) = 30 - 10e^{-20t} + 30e^{-10t}$ V

$$v(t) = v_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0]$$

$$40e^{-20t} - 60e^{-30t} \text{ mA}$$

$$\Leftrightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0]$$

Comparing these equation we get

$$V_s = 30 \quad \text{①}$$

$$A_1 = -10 \text{ j} \quad A_2 = 30 \text{ j}$$

$$s_1 = -20 \text{ j} \quad s_2 = -10 \text{ j} \quad \text{--- (a)}$$

$$A'_1 = 40 \text{ j} \quad A'_2 = -60 \text{ j}$$

$$s'_2 = -20 \text{ j} \quad s'_1 = -10 \text{ j} \quad \text{--- (b)}$$

Step 2:-

Now Equ (a) & (b)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{And} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 + s_2 = -2\alpha \quad \text{& } s_1 s_2 = \omega_0^2$$

: Page = 5

$$\left[\text{where } \alpha = \frac{R}{2L} ; \omega_0 = \frac{1}{\sqrt{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$\Rightarrow \alpha = 15$$

$$\Rightarrow \frac{R}{2L} = 15 \rightarrow (c)$$

$$200 = \omega_0^2 \Rightarrow \frac{1}{LC} = 200 \rightarrow (d)$$

step 3:-

$$i(t) = C \frac{dv(t)}{dt} = C [200e^{-20t} - 300e^{-30t}]$$

$$(A_1 e^{s_1 t} + A_2 e^{s_2 t}) \times 10^{-3} \text{ A} = C \left\{ [200e^{-20t} - 300e^{-30t}] v \right\}$$

OR

$$[s_1 = s_1', s_2 = s_2']$$

$$\Rightarrow 200C = A_1 = 40 \times 10^{-3}$$

$$\Rightarrow C = 200 \times 10^{-6} \text{ F} \Rightarrow C = 200 \mu\text{F}$$


Using Eqn (c) & (d)

$$L = \frac{1}{200C} = \frac{1}{200 \times 200 \times 10^{-6}} \Rightarrow L = 2.5 \text{ mH}$$

$$\text{Y } R = 30L = 30 \times 2.5 = 75 \Omega$$

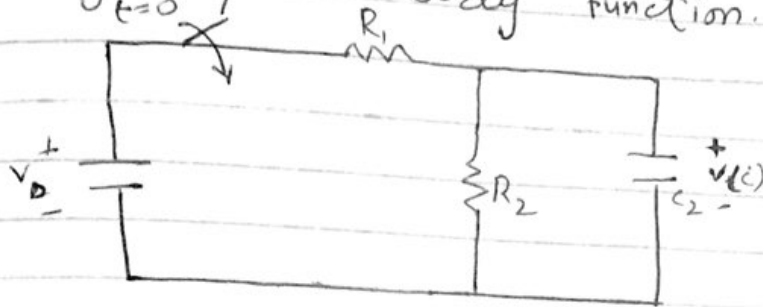
Q48-

The circuit in Fig. 3 is the electrical analog of body function.



For $t = 0$ $v(0) = 0$

For $t > 0$ the circuit is shown below:

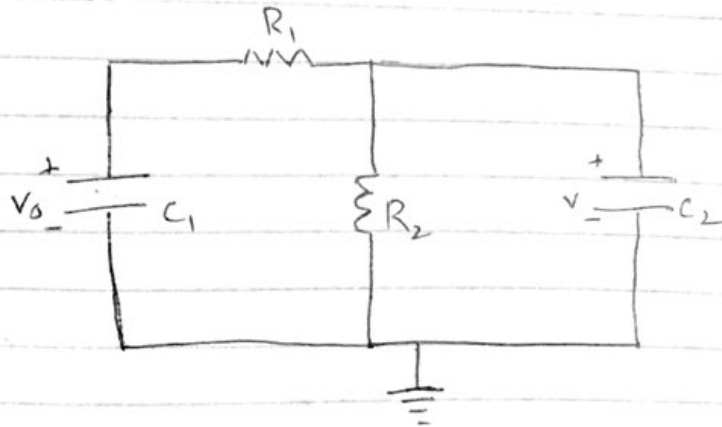

$$V_0 - v/R_1 = (v/R_2) + C_2 dv/dt$$

$$V_0 = v(1 + R_1/R_2) + R_1 C_2 dv/dt$$

$$60 = (1 + 5/2.5) + (5 \times 10^6 \times 5 \times 10^{-6}) dv/dt$$

$$60 = 3v + 25 dv/dt$$

$$v(t) = V_s + [Ae^{-3t/25}]$$

Where

$$3V_s = 60 \text{ yields } V_s = 20$$


Page = 7

$$v(0) = 0 = 20 + A \text{ or } A = -20$$

$$v(t) = 20(1 - e^{-3t/25}) \text{ V.}$$

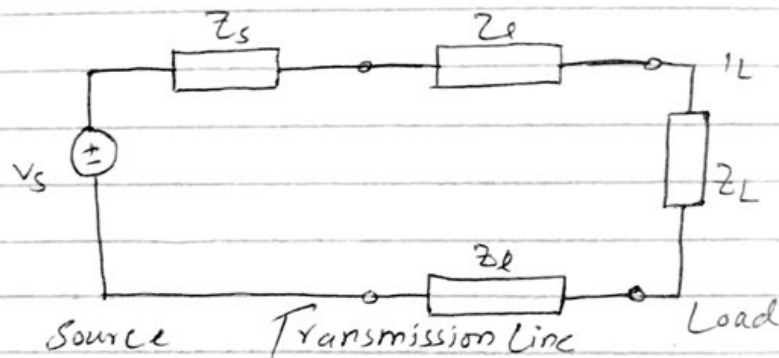Q 58-

A power transmission system is modeled as shown..... Find the load current I_L .



$$Z = Z_s + Z_e + Z_e$$

$$= (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$


$$Z = 25 + j20$$

$$I_L = \frac{V_s}{Z} = \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = 3.592 \angle -38.66^\circ \text{ A.}$$

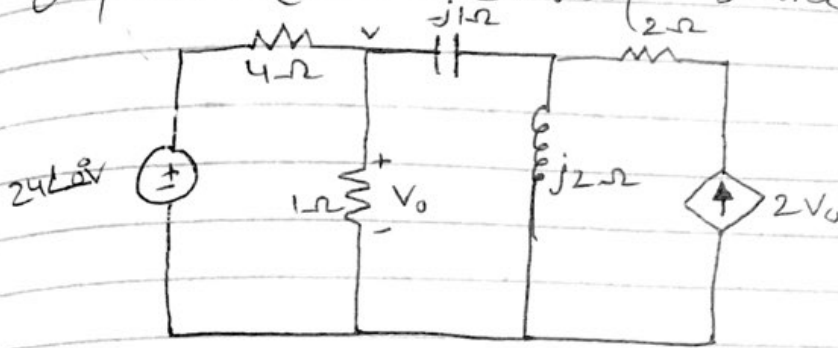Q68-

For the circuit in Fig. 5 find the dependent Current Source.



Consider the ~~circuit~~ circuit as shown

At node 0

$$\frac{24 - V_0}{4} = \frac{V_0}{1} + \frac{V_0 - V_1}{-j}$$

$$24 = (5 + j4)V_0 - j4V_1 \quad \text{--- (1)}$$

At node 1

$$\frac{V_0 - V_1}{-j} + 2V_0 = \frac{V_1}{j2}$$

$$V_1 = (2 - j4)V_0 \quad \text{--- (2)}$$

Subtracting (2) into (1)

$$24 = (5 + j4 - j8 - 16)v_0$$

$$v_0 = \frac{-24}{11 + j4}, \quad v_1 = \frac{(-24)(2 - j4)}{11 + j4}$$

voltage across the dependent source is

$$v_2 = v_1 + (2)(2v_0) = v_1 + 4v_0$$

$$v_2 = \frac{-24}{11 + j4} - (2 - j4 + 4) = \frac{(-24)(6 - j4)}{11 + j4}$$

$$S = v_2 i = v_2 (2v_0)$$

$$S = \frac{(-24)(6 - j4)}{11 + j4} - \frac{-48}{11 - j4} = \left(\frac{1152}{137} \right) (6 - j4)$$

$$S = (50.45 - j33.64) \text{ VA}$$

Q78-

A balance $\sqrt{3}$ -Load to a 60Hz
three Phase Phase draw
5 KW.

(a) determine the Load independence

(b) Find I_a I_b & I_c

(a)

$$|V_{ab}| = \sqrt{3}V_p = 240 \rightarrow V_p = \frac{240}{\sqrt{3}} = 138.56$$

$$V = V_p \angle -30^\circ$$

$$PF = 0.5 = \cos \phi$$

$$P = S \cos \phi \rightarrow S = \frac{P}{\cos \phi} = \frac{5}{0.5} = 10 \text{ KVA}$$

$$Q = S \sin \phi = 10 \sin 60 = 8.66$$

$$S_P = 5 + j8.66 \text{ KVA}$$

But

$$S_P = \frac{V_P^2}{Z_P} \rightarrow Z_P = \frac{V_P^2}{S_P} = \frac{138.56^2}{(5 + j8.66) \times 10^2}$$

(B)

$$\bar{I}_a = \frac{V}{Z_r} = \frac{138.56 \angle -30^\circ}{0.96 + j1.6627} = 72.17 \angle 90^\circ \text{ A}$$

$$\bar{I}_b = \bar{I}_a \angle -120^\circ = 72.17 \angle -210^\circ \text{ A}$$

$$\bar{I}_c = \bar{I}_a \angle +120^\circ = 72.17 \angle 30^\circ \text{ A.}$$