

**Department of Electrical Engineering
Assignment**

**Date:
13/04/2020**

Course Details



Course Title: Linear Circuit Analysis
Instructor: Dr.sohail imran






Module: 2
Total Marks: 30


**Student
Details**

Name: Abdullah

Student ID: 16194

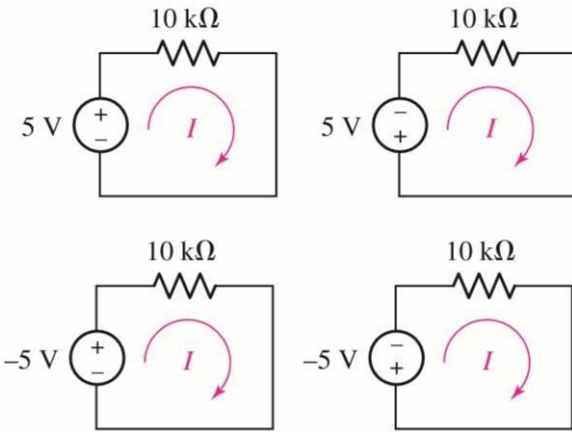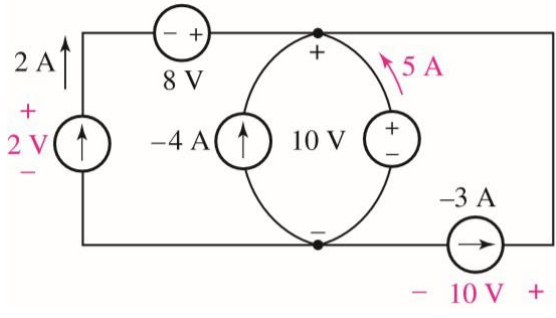Q1	(a)	<p>For each of the circuits in figure, find the current I and compute the power absorbed by the resistor</p> 	<p>Marks 3</p>
			<p>PLO1</p>
	(b)	<p>Determine the power supplied by the leftmost element in the circuit of following figure</p> 	<p>Marks 4</p>
			<p>PLO1</p>
	(c)	<p>Following figure depicts the current-voltage characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.</p>	<p>Marks 3</p>
			<p>PLO1</p>

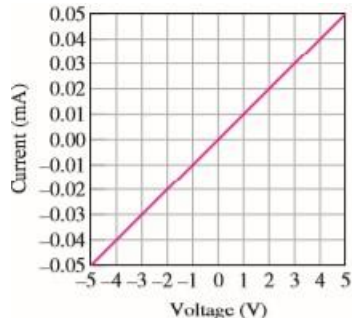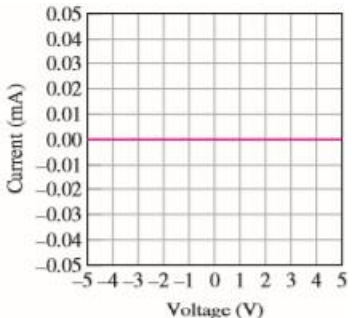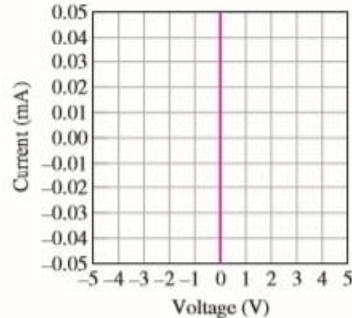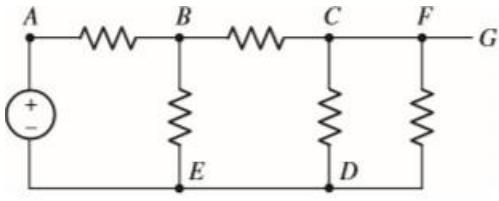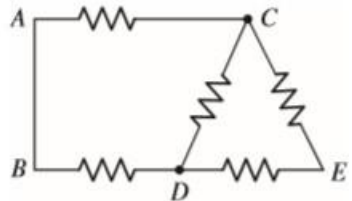	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;">  <p>(a)</p> </div> <div style="text-align: center;">  <p>(b)</p> </div> </div> <div style="text-align: center; margin-top: 20px;">  <p>(c)</p> </div>	
Q2	<p>(a) Refer to the circuits of following figures, and answer the following:</p> <ol style="list-style-type: none"> 1. How many distinct nodes are contained in the circuit? 2. How many elements are contained in the circuit? 3. How many branches does the circuit have? 4. Determine if each of the following represents a path, a loop, both, or neither: <ol style="list-style-type: none"> i. A to B ii. B to D to C to E iii. C to E to D to B to A to C iv. C to D to B to A to C to E <div style="display: flex; justify-content: space-around; margin-top: 20px;">   </div>	<p>Marks 4</p> <p>PLO2</p>
	<p>(b) For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region), I_B is measured to be $100 \mu\text{A}$. Determine I_C and I_E</p>	<p>Marks 6</p> <p>PLO2</p>

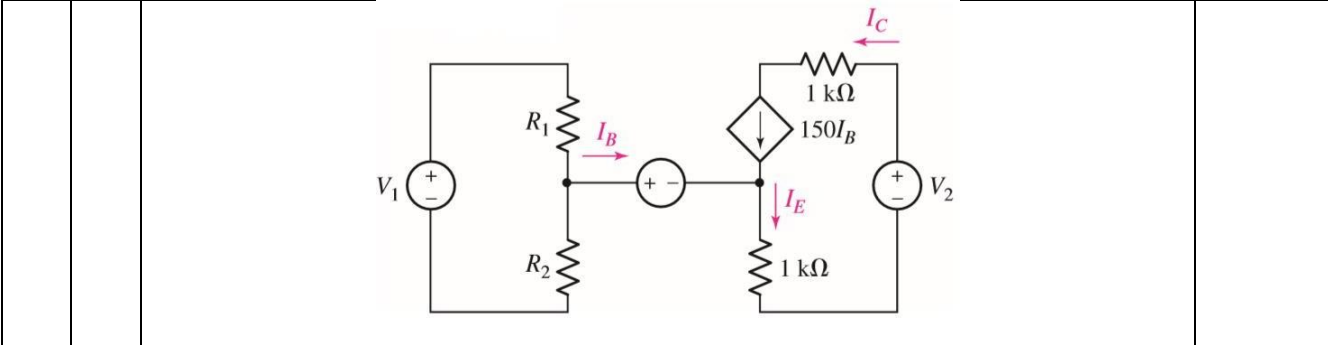


Q3

(a)

Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.

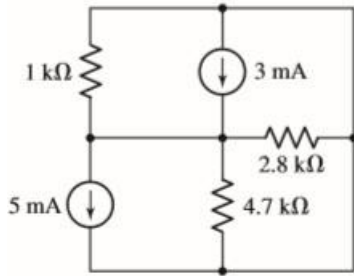- Determine the power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).




Marks
5

PLO1

(b)

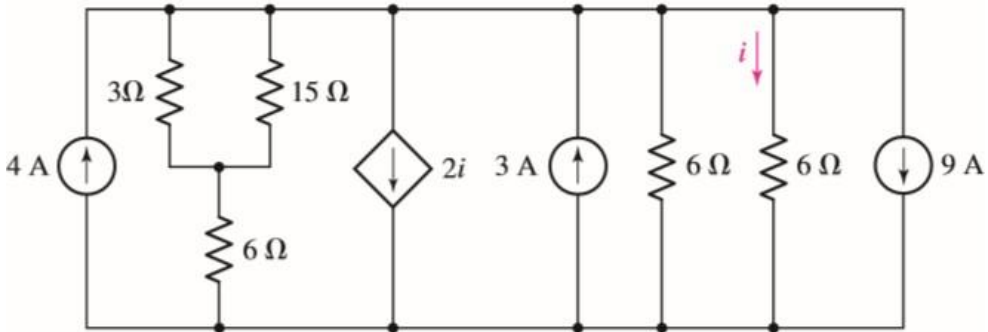Determine the power absorbed by the 15 Ω resistor in the circuit of following figure



Marks
5

PLO1

Solution of LCA PAPER

ANS:- Finding Current and Power:-

=> For find Current and Power (abs) in each circuit we will apply Ohm's law.

$$V = IR$$

$$P = V^2 / R$$

① For Circuit 1:-

$$\text{Voltage} = 5V$$

$$\text{Resistance} = 10K \Omega = 10 \times 10^3 \Omega$$

$$\text{Current} = ?$$

$$\text{Power}_{(abs)} = ?$$

Solutions:-

$$V = IR$$

$$I = V/R = 5 / 10 \times 10^3$$

$$I = 500 \mu A$$

2

$$\text{Power} = \frac{V^2}{R}$$

$$= \frac{(5)^2}{10 \times 10^3}$$

$$P_{abs} = 2.5 \text{ mW}$$

② Figure 2:

$$\text{Current} = ?$$

$$\text{Power} = ?$$

$$\text{Voltage} = -5 \text{ V (because in opposite direction)}$$

$$\text{Resistor} = 10 \times 10^3 \Omega$$

Solution:

$$V = IR$$

$$I = \frac{V}{R} = \frac{-5}{10 \times 10^3}$$

$$I = -500 \mu\text{A}$$

$$\text{Power} = \frac{V^2}{R}$$

$$= \frac{(-5)^2}{10 \times 10^3}$$

$$P_{abs} = 2.5 \text{ mW}$$

③ Figure 3:

$$\text{Voltage} = -5 \text{ V}$$

$$\text{Resistor} = 10 \times 10^3 \Omega$$

$$\text{Current} = ?$$

$$\text{Voltage} = ?$$

3

282

Solution:

$$I = V/R$$

$$I = \frac{-5 \text{ A}}{10 \times 10^3} = -500 \text{ } \mu\text{A}$$

$$P_{\text{abs}} = V^2/R$$

$$= (-5)^2 / (10 \times 10^3)$$

$$= 2.5 \text{ mW}$$

⑧ figure 4 in

voltage = $-(-5) \text{ V}$ (because in opposite direction)Resistance = $10 \times 10^3 \text{ } \Omega$

Current = ?

Power = ?

Solution:

$$V = IR$$

$$I = V/R$$

$$= 5 / (10 \times 10^3) = 500 \text{ } \mu\text{A}$$

$$P_{\text{abs}} = V^2/R$$

$$= (5)^2 / (10 \times 10^3)$$

$$P_{\text{abs}} = 2.5 \text{ mW}$$

4

ANS:-b Find leftmost element

The left most element in the circuit is 2V through which 2A of current is flowing.

We know that

$$\text{Power} = V \times I$$

$$= 2 \times 2$$

$$\text{Power} = 4 \text{ W}$$

ANS NO 2 (Part C)

~~Part (A)~~

(i) To find the P in the figure we have to find any one, all the point will give the same result

We take

$$\text{Voltage} = 1 \text{ V}$$

5 264

$$\text{Current} = 0.01 \text{ mA} = 0.01 \times 10^{-3} \text{ A}$$

According to ohm's law

$$R = V / I$$

$$R = \frac{1}{0.01 \times 10^{-3}} = 100 \times 10^3 \Omega$$

$$\boxed{R = 100 \text{ k}\Omega}$$

(ii) we have to take any point which is

$$\text{Voltage} = 0 \text{ V}$$

$$\text{Current} = 0 \text{ V}$$

According to ohm's law

$$R = \frac{V}{I}$$

$$R = \frac{1}{0} = \infty$$

$$\boxed{R = \infty}$$

(iii) we have to take any point which is

$$V = 0, \quad I = 0.01 \text{ mA}$$

$$R = \frac{V}{I} = \frac{0}{0.01 \text{ mA}} \Rightarrow R = 0$$

QNO: 2 (Part A)

ANS: Figure: 1

- ① Element : 6 elements.
- ② Nodes : 4 nodes
- ③ branches : 6 branches.
- ④ (a) neither (b) neither
(c) neither (d) neither.

Figure: 2

- ① Nodes : 4 nodes
- ② Element : 5 element
- ③ Branches : 5 branches
- ④ (a) neither (b) Path
(c) loop & path (d) neither (c repeated)

Q NO 2 (Part b)

ANS: Given

$$I_B = 100 \mu A = 100 \times 10^{-6} A$$

Required :

$$I_C = ?$$

$$I_E = ?$$

Solution

According to KCL

Total Current Entering = Total Current leaving.

$$I_E = I_C + I_B$$

We also know that

$$\begin{aligned} I_C &= 150 I_B \\ &= (150)(100 \mu A) \end{aligned}$$

$$I_C = 15 \text{ mA}$$

Now

$$I_E = 15 \times 10^{-3} + 100 \times 10^{-6}$$

$$I_E = 15.1 \text{ mA}$$

Result

$$I_C = 15 \text{ mA}$$

$$I_E = 15.1 \text{ mA}$$

8

Q NO 3 Part(A)

Answer

Given data is

$$I_1 = 3 \times 10^{-3} \text{ A}$$

$$I_2 = -5 \times 10^{-3} \text{ A}$$

$$R_1 = 1 \text{ k}\Omega = 1000 \Omega$$

$$R_2 = 2.8 \text{ k}\Omega = 2800 \Omega$$

$$R_3 = 4.7 \text{ k}\Omega = 4700 \Omega$$

Solution is

$$\begin{aligned} I_{\text{Total}} &= I_1 + I_2 \\ &= (3 \times 10^{-3}) + (-5 \times 10^{-3}) \\ &= -2 \times 10^{-3} \end{aligned}$$

For total resistance

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{1000} + \frac{1}{4700} + \frac{1}{2800}$$

$$R_{\text{eq}} = 637$$

9

P68

(a) Finding Power absorbed by resistors:

(i) Power absorbed by resistor 1:

$$P_1 = V^2 / R_1 = (-1.274)^2 / 1000$$

$$= 1623.07$$

$$P = 1.623 \times 10^{-3}$$

$$P = 1.623 \text{ mW}$$

(ii) Power absorbed by resistor 2:

$$P_2 = V^2 / R_2 = (-1.274)^2 / 9800$$

$$= 0.00057967$$

$$P_2 = 579.67 \mu\text{W}$$

(iii) Power absorbed by resistor 3:

$$P_3 = V^2 / R_3 = (-1.274)^2 / 4700$$

$$= 0.00034533$$

$$= 345.3 \mu\text{W}$$

10

(b) Power Supplied by Source :

(i) Power Supplied by Source 1 :

$$P = IV$$

$$= (3 \times 10^{-3})(-1.274)$$

$$= -0.003822 \text{ W}$$

$$= -3.822 \times 10^{-3} \text{ W}$$

$$P_1 = -3.822 \text{ mW}$$

(ii) Power Supplied by Source 2 :

$$P = IV$$

$$= (-5 \times 10^{-3})(-1.274)$$

$$= 0.00637$$

$$P_2 = 6.37 \text{ mW}$$

(c) adding all power absorbed by resistor

$$P_1 = 1.623 \text{ mW}$$

$$P_2 = 579.67 \text{ mW}$$

$$P_3 = 345.3 \text{ mW}$$

$$\Sigma P_{\text{absorbed}} = 0.002548$$

11

1020

$$\sum P_{\text{absorbed}} = 2.548 \text{ mW}$$

(ii) adding all power supplied by source:

$$P_1 = -3.833 \text{ mW}$$

$$P_2 = 6.370 \text{ mW}$$

$$P_{\text{supply}} = 0.000537$$

$$P_{\text{supply}} = 2.54 \text{ mW}$$

Hence

$$\sum P_{\text{absorb}} = \sum P_{\text{supply}}$$

Q NO 3 (part b)

ANS: Given as

$$I_{\text{total}} = 4 - 2i + 3 - 9$$

$$I_{\text{total}} = -2 - 2i$$

Now Req =

$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + R_3 \right) + \frac{1}{R_4} + \frac{1}{R_5}$$

$$= \left(\frac{1}{3} + \frac{1}{15} + 6 \right) + \frac{1}{6} + \frac{1}{6}$$

$$= \left(\frac{1}{0.4} + 6 \right) + \frac{1}{3}$$

$$= (2.5 + 6) + \frac{1}{3} \text{ (still in parallel)}$$

$$\frac{1}{R_{eq}} = \frac{1}{8.5} + \frac{1}{3}$$

$$R_{eq} = 2.2174 \Omega$$

Solution n

$$I_i = -2 - 2i$$

$$R_{eq} = 2.2174 \Omega$$

$$V = I \cdot R$$

$$V = (-2 - 2i)(2.2174) \text{ --- (1)}$$

13

~~13~~

From the figure we know
that $v = 6i$

$$6i = (-2 - 2i)(2.2174)$$

$$6i = -4.4348 - 4.4348i$$

$$4.4348i + 6i = -4.4348$$

$$10.4348i = -4.4348$$

$$i = \frac{-4.4348}{10.4348}$$

$$i = -0.425 \text{ A}$$

Putting i in eq (1)

$$v = (-2 - 2(-0.425))(2.2174)$$

$$= -2$$

We have to find resist power
across $15\ \Omega$ resistor.

$$P = \frac{V^2}{R} \quad \text{--- (a)}$$

We have to find V first

$$V_{15\Omega} = \frac{6}{6+2.5}$$

$$V_{15\Omega} = 1.8\text{V}$$

Putting in eq (a)

$$P = \frac{(1.8)^2}{15}$$

$$P = 0.216\text{W}$$