

# Department of Electrical Engineering

## Assignment

Date: 14/04/2020

### Course Details

Course Title: Electronic Circuit Design  
 Instructor: \_\_\_\_\_

Module: 04  
 Total Marks: 30

### Student Details

Name: syed M zahoor

Student ID: 12595

Q1.	(a)	<p><b>Explain</b> the drain characteristic curve of D-MOSFET given below.</p> <div style="text-align: center;"> </div>	Marks 07
			CLO 1
	(b)	<p><b>Sketch</b> the hybrid model and write equations for the transistor in common emitter configuration.</p>	Marks 06
			CLO 1
Q2.		<p>A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. <b>Evaluate</b> the CMRR &amp; express it in decibels.</p>	Marks 05
			CLO 2
Q3.	(a)	<p><b>Explain</b> the concept behind negative feedback in operational amplifiers.</p>	Marks 06
			CLO 2
	(b)	<p><b>State</b> the following statement as <b>True</b> or <b>False</b> and also give the reason for your answer:                      "The output of a summing amplifier is positive"</p>	Marks 06
			CLO 2


# Electronic Circuit Design

Name: Syed. Muhammad. Zahoor

Student ID:- 12595

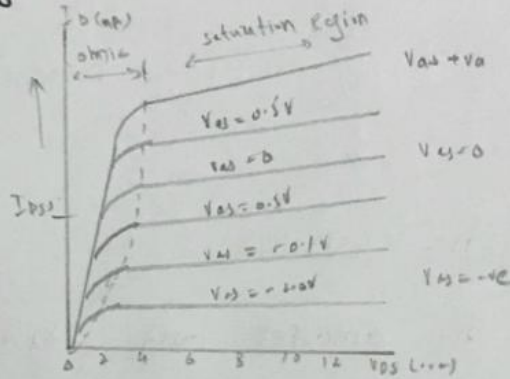Q.1


Q. Explain the drain characteristic curve of D-Mosfet given below.




Ans D-MOSFET:-

A D-Mosfet is a depletion mosfet mean that the threshold voltage is negative instead of positive and its also called a normally on Mosfet because it is on at a gate source of zero voltage.



Schematic Symbols of D-Mosfet:

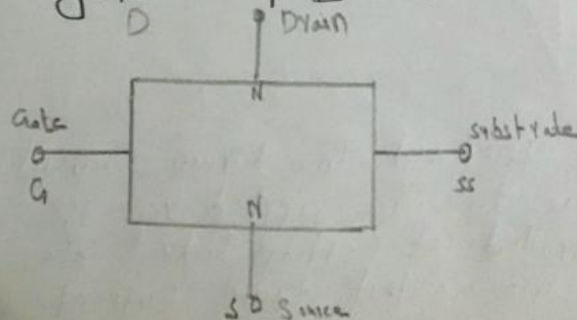

(2)

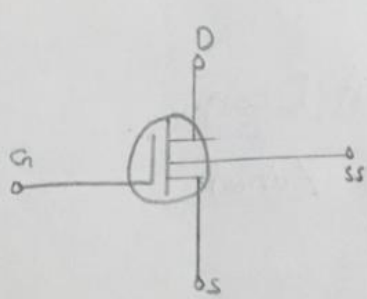

N-channel

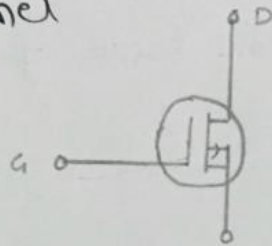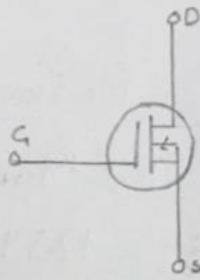


P-channel
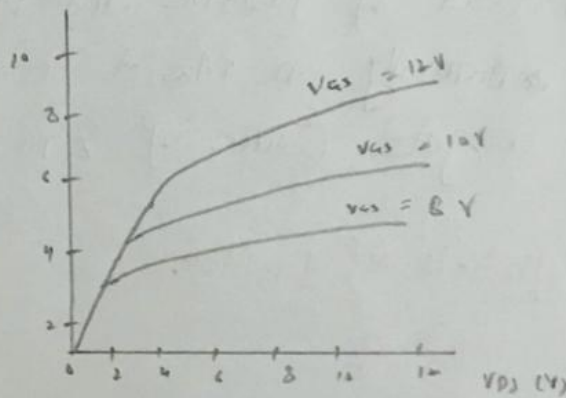
### Drain characteristic curves

The mosfet and drawn below

The Drain to and the ~~low~~ Source voltage  $V_{DS}$ . The characteristic curve shown below for different inputs.



When  $V_{DS}$  is increased, the Drain current  $I_D$  should increase but due to the applied  $V_{GS}$  the drain current is controlled at certain level. Hence the gate current controls the output drain current.



Q2 Sketch the hybrid model and write equations for  
 (b) Ans The transistor in common emitter configuration

In the common emitter of the configuration the input signal is applied between the base and emitter terminals of the ~~trans~~ transistor and the output appears b/w the collector and emitter terminals. The input voltage ( $v_{be}$ ) and the output current ( $i_c$ ) are given by the following eq.

$$v_{be} = h_{ie} \cdot i_b + h_{re} \cdot v_c$$

$$i_c = h_{fe} \cdot i_b + h_{oc} \cdot v_c$$

configuration:-

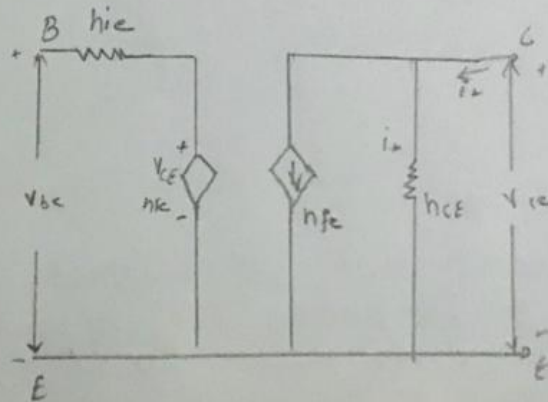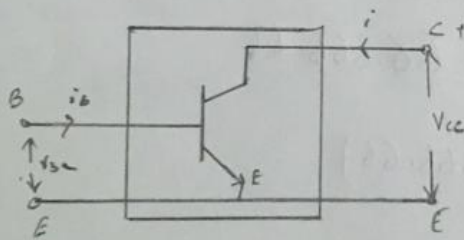

(4)

Q2

Given :-

$A_{ol}$  = open loop differential voltage gain

$$= 400,000$$

common mode gain =  $A_{cm} = 0.6$

Find :-

CMRR = ?

Solution

We know that

$$CMRR = 20 \log \left( \frac{A_{ol}}{A_{cm}} \right)$$

$$= \frac{A_{ol}}{A_{cm}} = \frac{40,000}{0.6}$$

$$= 66,666.66$$

$$= 20 \log (66666.66)$$

$$CMRR = 94.47 \text{ dB Ans}$$

(5)

Q3

(A) Explain the concept behind negative feedback in operational amplifiers.

Ans-


Negative feedback-

It is the process where by a portion of the output voltage of an amplifier is returned to the input with a phase angle that opposes (or subtracts from) the input signal.

Concept behind the negative feedback:-

Negative feedback is the process of feedback a fraction of the output signal back to the input but to make the feedback negative we must feed it back to negative or inverting output terminal of the op-amp using an external feedback connection resistor called  $R_f$ . This feedback connection blows the output and the inverting input terminal force the differential input voltage toward

Zero.

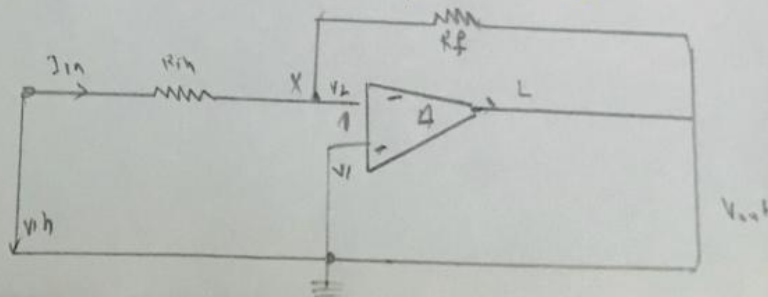

Q3

5

Q3 State the following statement as True or false also given the reason for your answer:  
"The output of a summing amplifier is positive"

Ans:-

The Summing Amplifier is another type of operational amplifier circuit configuration that is used to combine the voltage present on two or more input into a single output voltage.

The statement is false because when the summing point is connected to the inverted input of the op-amp the circuit will produce the negative sum of any number of input voltage likewise when the summing input is connected to the non-inverting input of the op-amp it will produce the positive sum of the input voltages.