

Department of Electrical Engineering

Assignment

Date: 20/04/2020

Course Details

Course Title: Power System Analysis
 Instructor: Eng. Qamir Aman


Module: 6th
 Total Marks: 30

Student Details

Name: Muhammad Hital Khan

Student ID: 6966

Q1.	(a)	A 3 Φ transformer is connected with a residential load of 28.56 KV; the primary side of a transformer is connected with 130 KV feeder while secondary side is stepped down to 10 KV. The transformer is rated with 30 MVA. Find impedance Z_b .	Marks 05 CLO 1
	(b)	Find the Per Unit equivalent impedance of an 11/132 KV transformer having 10 Ω and 1440 Ω , the equivalent impedance. The primary and secondary currents are 909 Amp and 75.75 Amps respectively.	Marks 05 CLO 1
Q2	(a)	Single line diagram of a 3 Φ power system is shown in the below figure. Draw an impedance and reactance diagram in P.U.	Marks 10 CLO 2
Q3	(a)	For the single line diagram shown below, Generators are connected to high tension buses 1 and 2 and supply to load connected at bus 3. Find the reactance diagram, then convert it into equivalent current sources and shunt admittances. Then find the admittance matrix and find the total current.	Marks 10 CLO 2

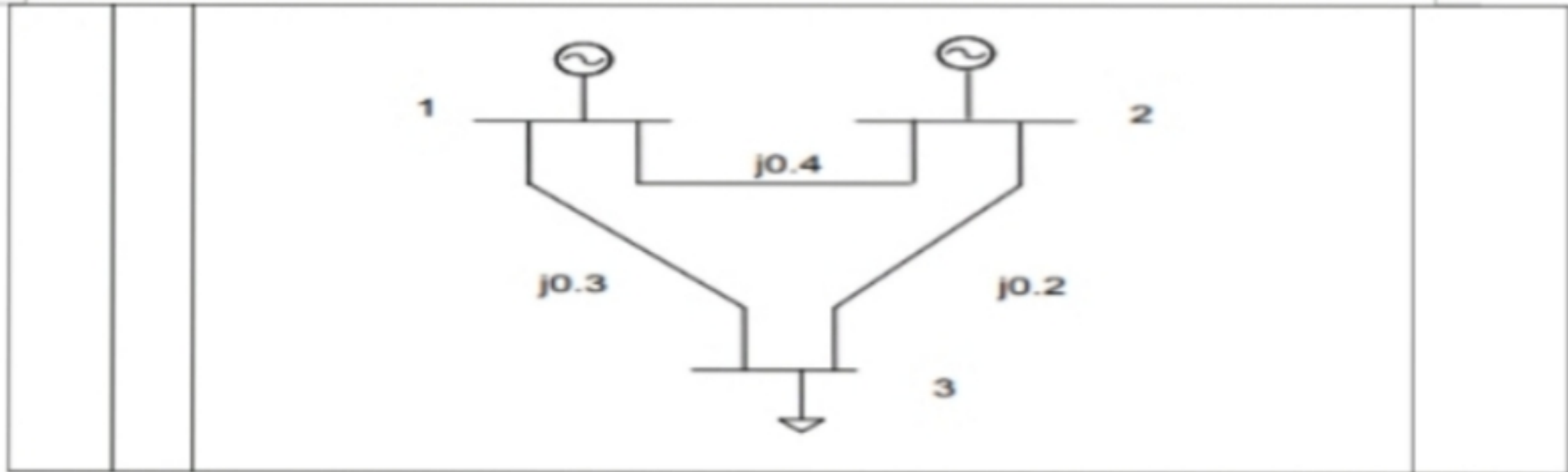

Date: _____

P# 1

NAME :- HILAL KHAN

ROLLNO:- 6966

PAPER Power system

QUESTION :- 1

PART:- A

ANSWER:-

SOLUTION:-

Primary = 130 kV

Secondary = 10 kV

T/F Rated = 30 MVA

Z_b across V_{base} (130 kV)

$$Z_b = \frac{(130 \times 10^3)^2}{30 \text{ MVA}} = \frac{16900000000}{30000000}$$

$$Z_b = 56.33 \text{ Ans}$$

$\Rightarrow Z_b$ across V_{base} (10 kV)

Date: _____

Roll No: 6966

NAME: Hilal Khan

$$Z_b = \frac{(10 \times 10^3)^2}{30 \text{ MVA}}$$

$$= \frac{100000000}{30000000}$$

$$Z_b = 3.33 \text{ Ans}$$

QUESTION : 1

PART : B

ANSWER

SOLUTION:

$$\text{Base impedance (primary)} = \frac{11 \times 10^3}{909} \\ = 12.1 \Omega$$

$$\text{Base impedance (secondary)} = \frac{132 \times 10^3}{75.75} \\ = 1742.57 \Omega$$

$$Z_1 \text{ (P.U)} = \frac{10}{12.1} = 0.826 \text{ P.U}$$


$$Z_2 \text{ (P.U)} = \frac{1440}{1742.57} = 0.826 \text{ P.U}$$

QUESTION: 2

P# 4

ANSWER:

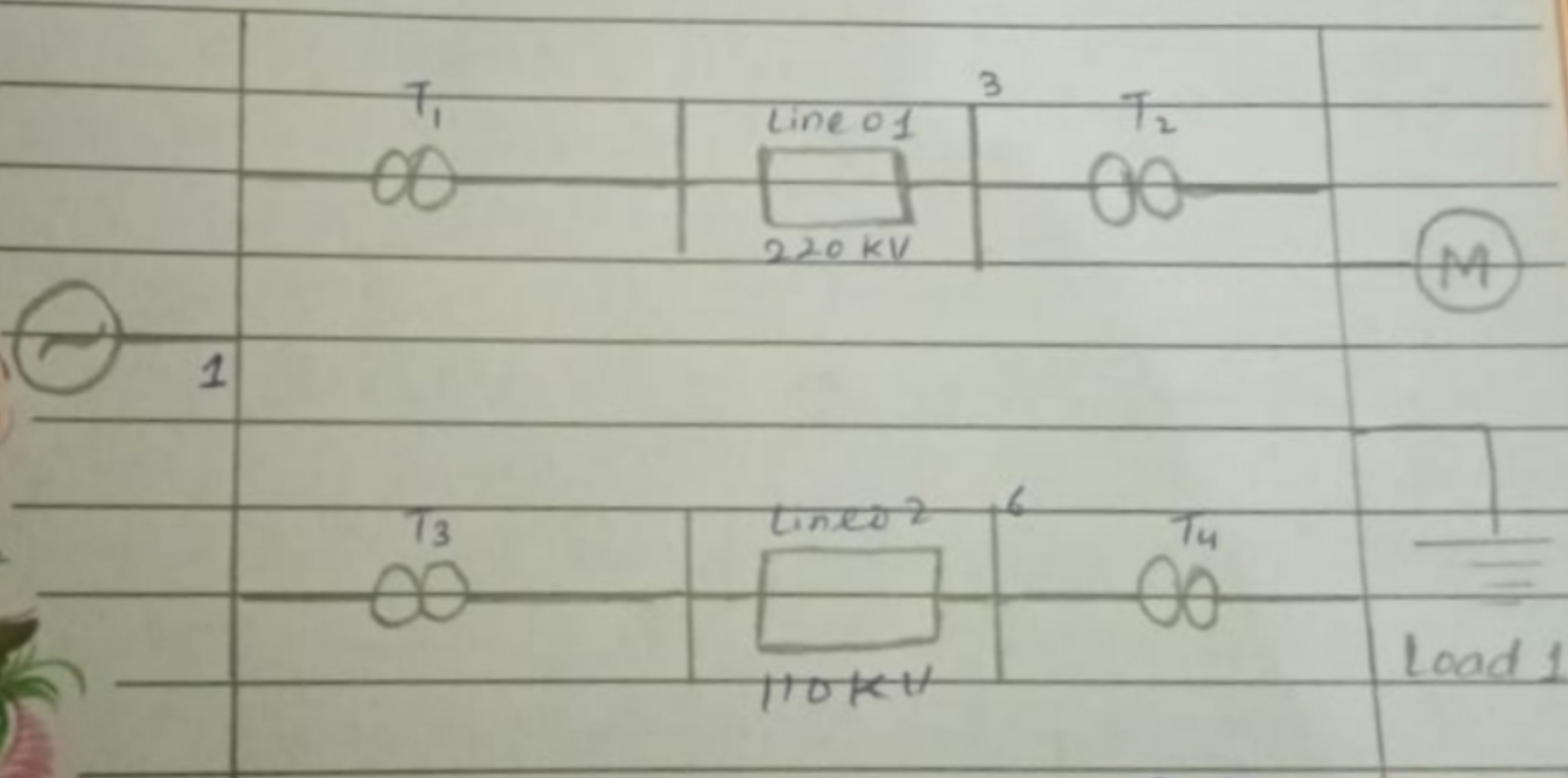a) Single line diagram of a 30 power system in the below figure




Date: _____

Hilal Khan

Roll No: 6966

P # 5

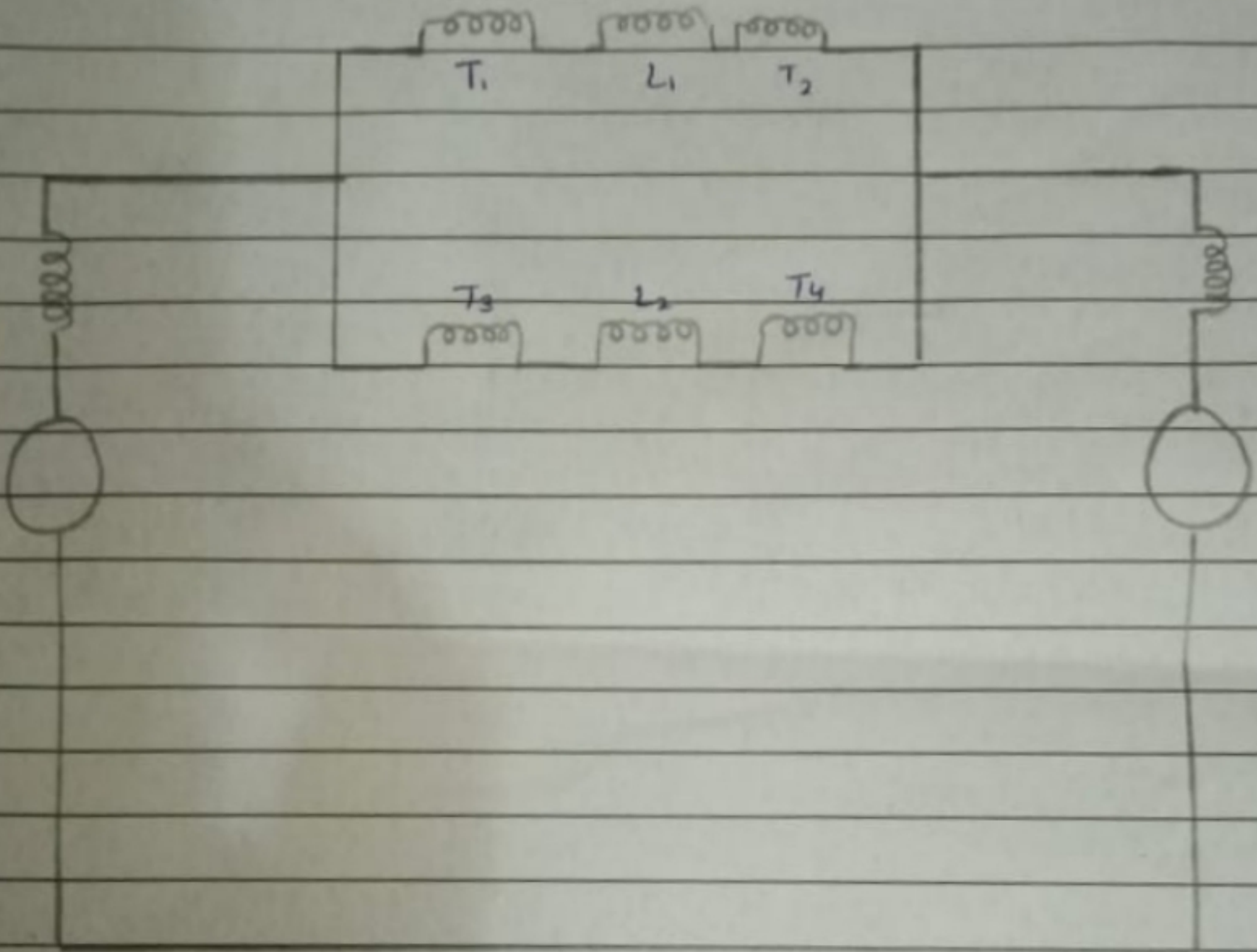

Single Line diagram convert into reactance diagram.

Date: _____

Hilal Khan

Roll No: 6966

P# 6




QUESTION : 3

ANSWER :-

SOLUTION :-

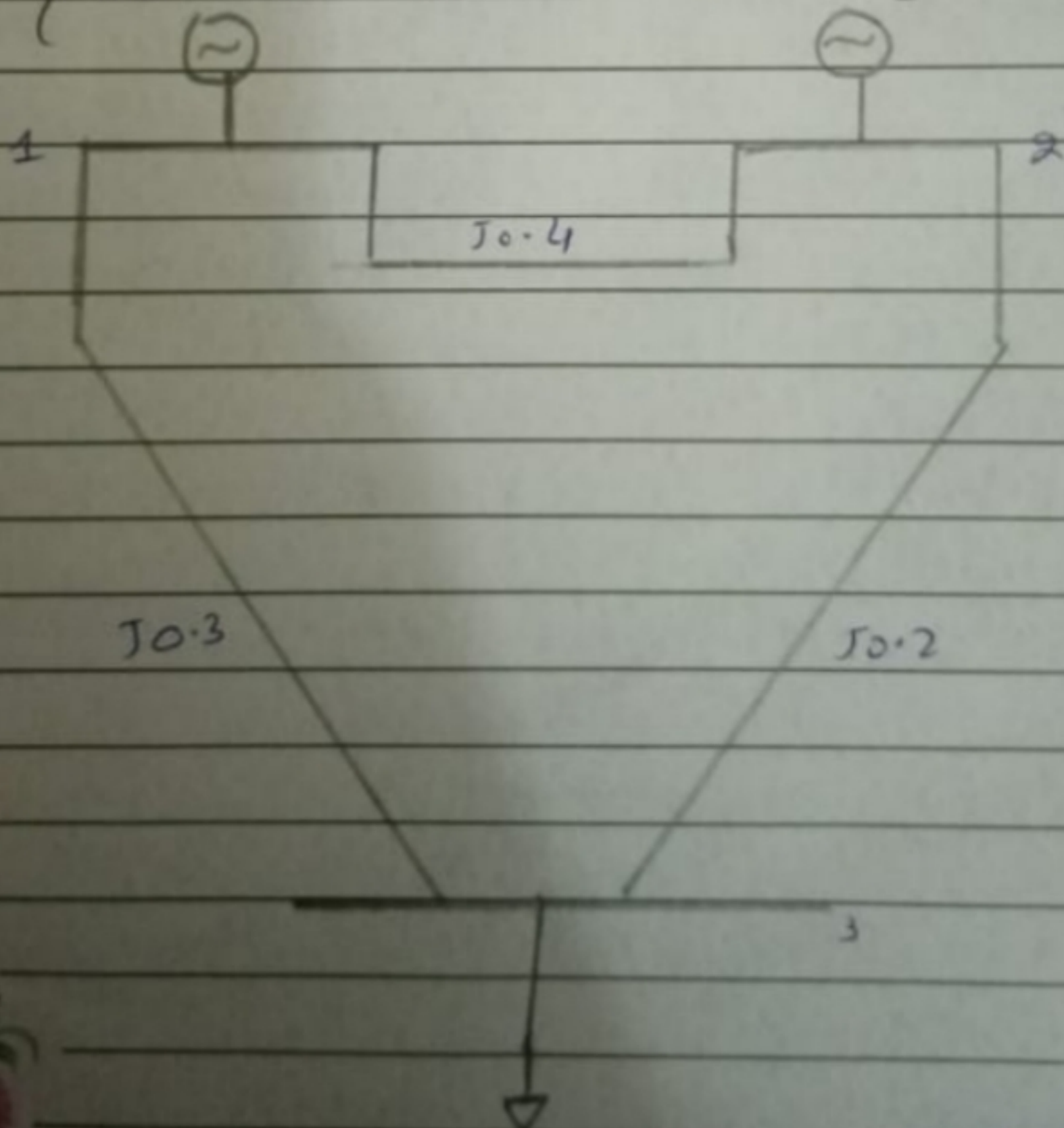Find the reactance diagram, then convert it into equivalent current source circuit admittances. Then find that admittance matrix and find the total current.




Date: _____

Hital khar

Roll No = 6966

P# 8

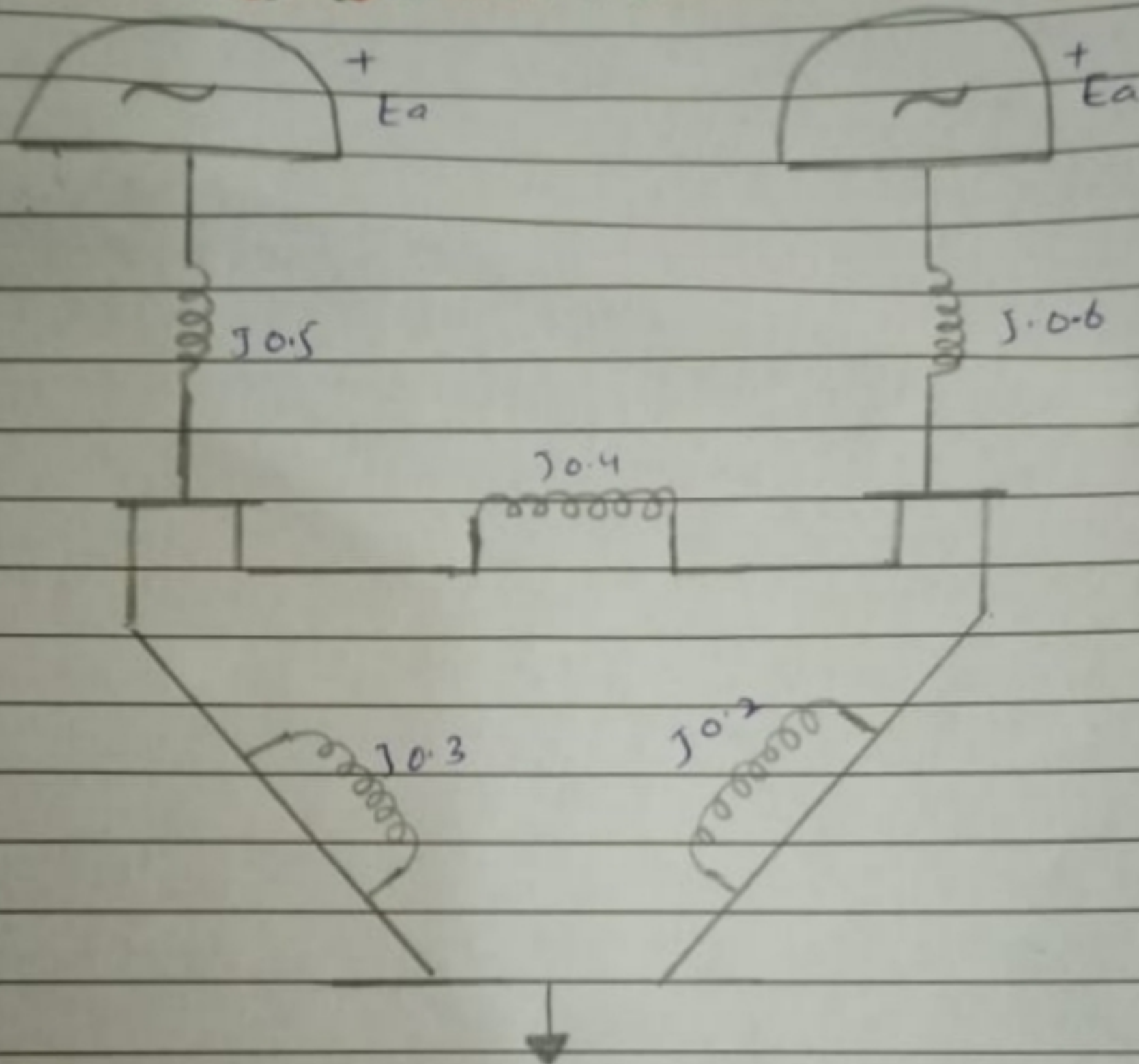

Now calculation \Rightarrow

$$\frac{1}{j0.6} = 160 \quad \frac{1}{j0.5} = 2 \quad \frac{1}{j0.4} = 25 \quad \frac{1}{j0.3} = 333$$

$$\frac{1}{j0.2} = 5$$

\Rightarrow So now we convert the reactance diagram into Admittance.

Date: _____

Hilal Khar

Roll No. 6966

P# 9

