



Industrial Electronics
Assignment

Question No 1. Multiple choice Questions

1. Does the severity of an electric shock increase or decrease with each of the following changes?

a. A decrease in the source voltage **(Increase)**

b. An increase in body current flow

(Increase)

c. An increase in body resistance

(Decrease)

d. A decrease in the length of time of exposure **(Decrease)**

2. State the piece of electrical safety equipment that should be used to perform each of the following tasks:

a. A switching operation where there is a risk of injury to the eyes or face from an electric arc. **(Safety**

Glasses)

b. Using a multimeter to verify the line voltage on a 3-phase 480 volt system

(Safety gloves, safety shoes, safety hat)

c. Opening a manually operated high-voltage disconnect switch. **(Safety**

gloves, safety shoes, safety hat)

3. In which industrial revolution the use of IT and Electronic systems further automated the production of industrial sector

a. First.

b. Second.

✓ **c,Third.**

c. Fourth.

4. Industrial safety is primarily a management activity which is concerned with _____, Controlling, Eliminating hazards from the industries.

✓ **a, Reducing**

b, Increasing

c, suppressing

The _____ is defined as the device which convert the one form of energy into another form of the energy.

a. Sensor

✓ **Transducer**

b. Resistor

c. Capacitor



Industrial Electronics
Assignment

Question No 2

10


- A. Draw digital logic circuit and ladder diagram that is equivalent to the following Boolean function that will initiate a motor “M” to start? (10) **CLO-2**

$$M = B'CD' + B'CE + B'CF$$

Question No 3

10

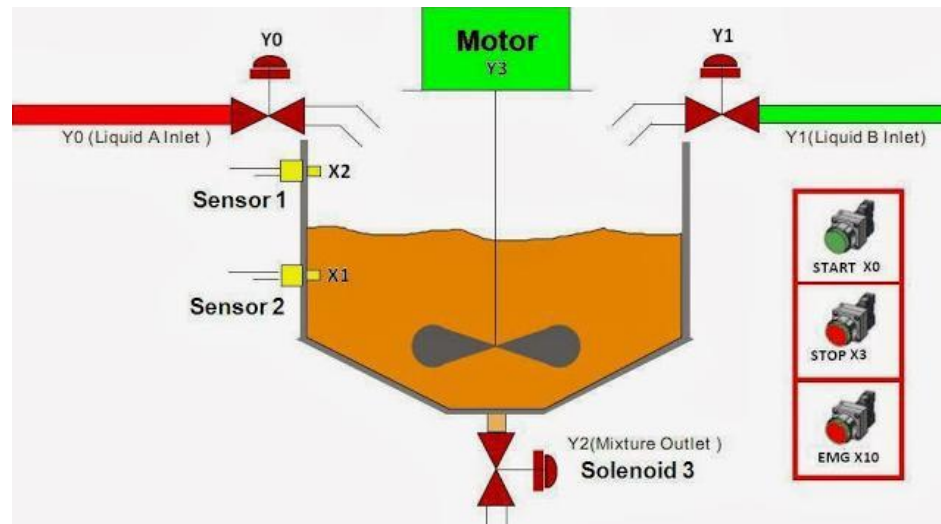- A. Describe and draw ladder diagram for the below given process having a container infused with liquids A and B in order when START is pressed. When it reaches the set level, mix the two liquids evenly then open the valve to let out the mixture? **CLO-2**





.Good Luck

①

Q2:-

$$M = B \cdot C \cdot D + B \cdot C \cdot E + B' \cdot C' \cdot F$$

Sol :-

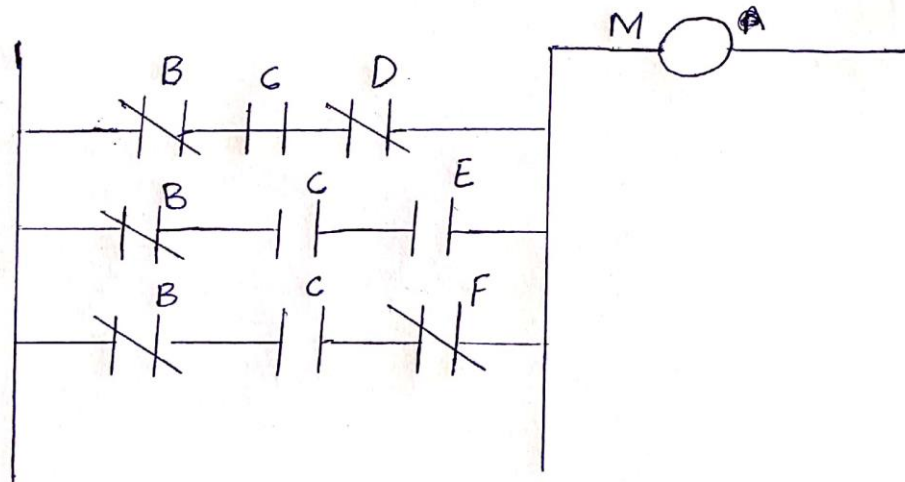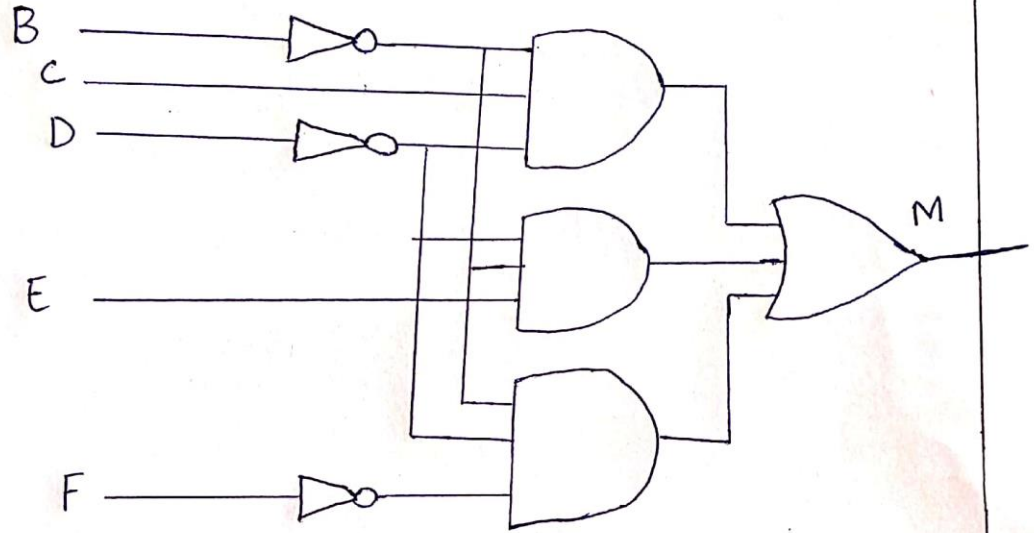

Q 3 A:-

Answer:-

⊛ Number of PLC Input Required:-

X1 - Start Switch

X1 - Low level float sensor. X1 = ON When the liquid level reaches X1.

X2 - High level float sensor. X2 = ON When the liquid level reaches X2.

X10 - Emergency Stop Button. X10 = ON When the Button is pressed.

⊛ Number of PLC output Required:-

Y0 = Liquid A inlet

Y1 = Liquid B Inlet

Y2 = mixture outlet


Y3 = Agitator / Stirrer

⊛ Number of PLC Timer Required:-

→ T0 - 60 second, 100ms Time Base (See K60 Preset Value for Timer)

→ T1 - 120 Second Timer, 100ms Time Base (See K1200 Preset Val, for Timer.

PLC Ladder Diagram:-

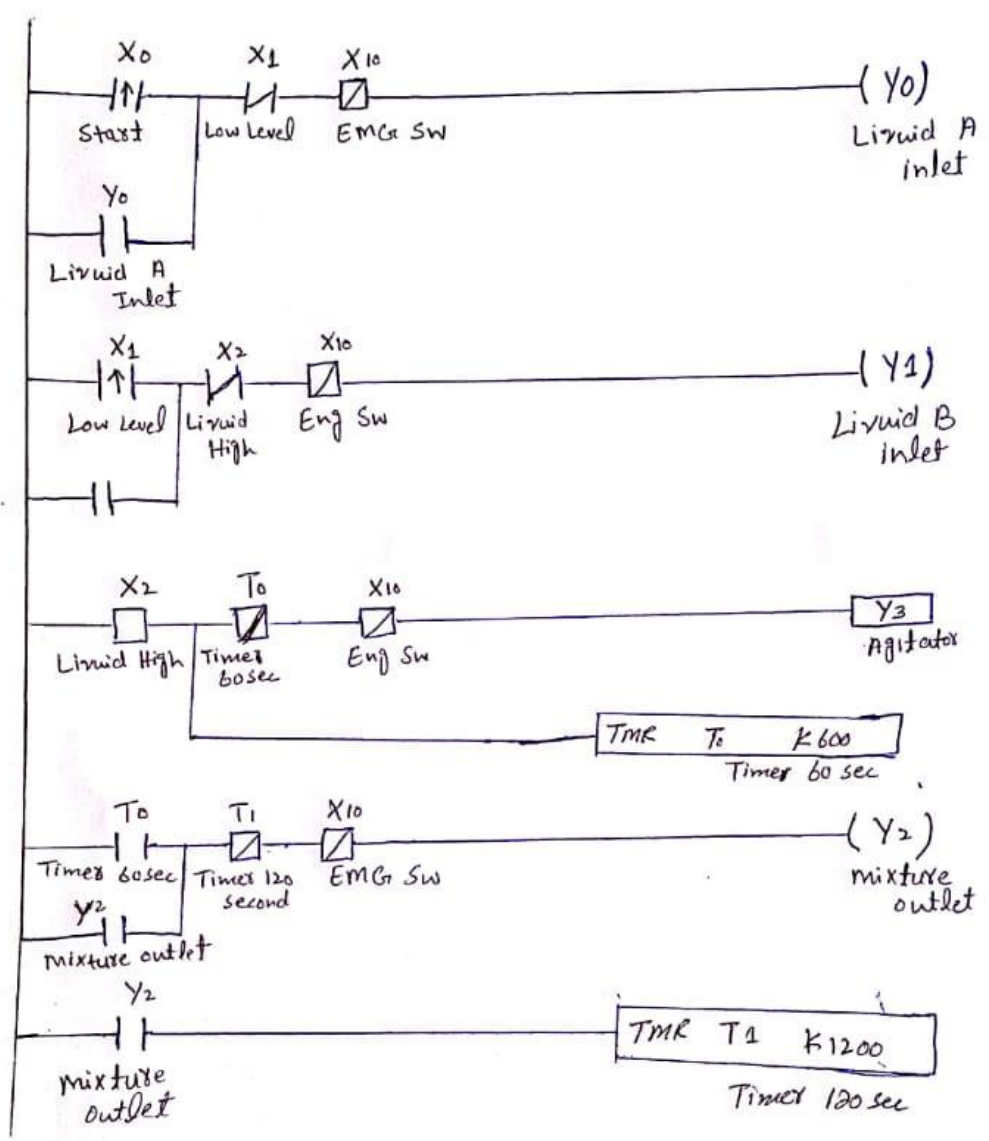

PLC Ladder Diagram Description:-

→ ~~PLC~~ X0 = ON when start is pressed. Y0 will be ON and latched and the valve will be opened for infusing liquid

(4)

A until the level reaches the low-level float sensor

→ $X_1 = ON$ when the level reaches the low level float sensor Y_1 will be ON and latched, and the valve will be opened for infusing liquid B until the level reaches the high level float sensor.

→ $X_2 = ON$ when the level reaches the high level float sensor. Y_3 will be ON and activates the agitator. Also timer T_0 will start to count for 60 sec. After 60 sec T_0 will be ON. and the agitator motor Y_3 will stop working.

→ When $Y_2 = ON$ timer T_1 will start to count for 120 sec. After 120 sec T_1 will be ON and Y_2 will be OFF. The draining process will be stopped.

→ When an error occurs, press Emergency Stop Button X_{10} . The NC contact X_{10} will be ON to disable all the outputs.

The system will ~~be~~ then stop running.