

Name :- Hazrat Bilal


ID :- 14622

Department :- Electrical Engineering

Paper :- Electrical Network Analysis

Instructor :- Dr Shahyar Sir.

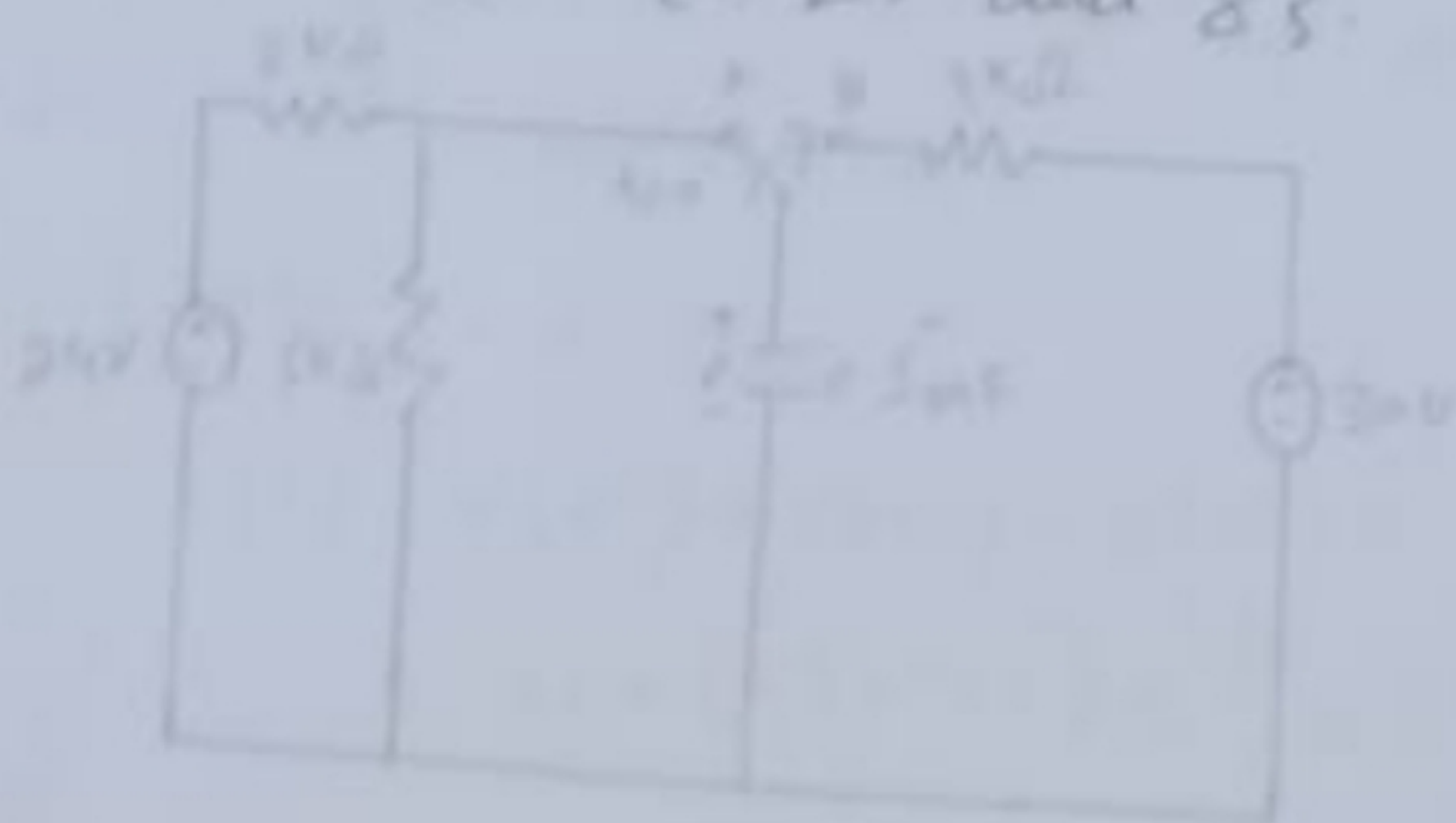Q13- The switch in fig. 1 has been in position A for a long time. At  $t=0$  the switch moves to B. Determine  $V(t)$  for  $t > 0$  and calculate its value at  $t=2s$  and  $8s$ .



Solution:-

For  $t < 0$  the switch is at position A. The capacitor acts like an open circuit to DC, but  $V$  is the same as the voltage across the  $5k\Omega$  resistor. Hence, the voltage across the capacitor just before  $t=0$  is obtained by voltage division as

$$V_C(0^-) = \frac{5}{5+3} (24) = 15V$$

Using the fact that the capacitor voltage cannot change instantaneously,

$$V_C(0) = V_C(0^-) = V_C(0^+) = 15V$$

For  $t > 0$  the switch is in position B. The Thevenin resistance connected to the capacitor is  $R_{Th}$

$R_{th} = 4k\Omega$  and the time constant is

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2s$$

Since the capacitor act like an open circuit to dc at steady state.

$$V(\infty) = 30V \text{ Then}$$

$$\begin{aligned} v(t) &= V(\infty) + (v(0) - V(\infty)) e^{-t/\tau} \\ &= 30 + (15 - 30) e^{-t/2} = (30 - 15e^{-0.5t}) V \end{aligned}$$

At  $t = 2$

$$v(2) = 30 - 15e^{-0.5(2)}$$

$$v(2) = 30 - 15e^{-1}$$

$$v(2) = 30 - 15(0.3678)$$

$$v(2) = 30 - 5.517$$

$$v(2) = 24.483V$$

At  $t = 8$

$$v(8) = 30 - 15e^{-0.5(8)}$$

$$v(8) = 30 - 15e^{-4}$$


$$v(8) = 30 - 15(0.0183)$$

$$v(8) = 30 - 0.2745$$

$$v(8) = 29.7255V$$

P.No 4

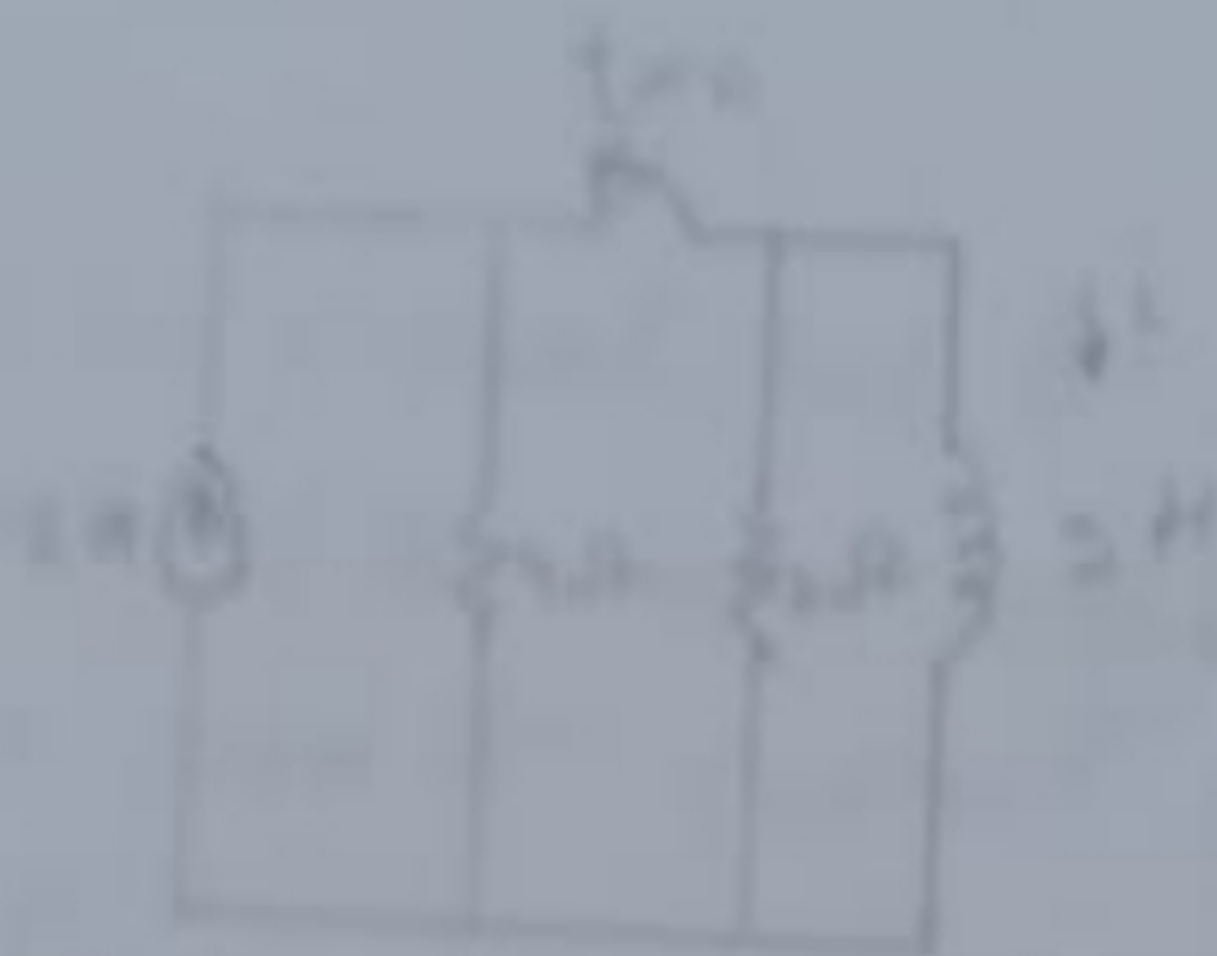2:- Determine the inductor current for both  $t > 0$  and  $t < 0$  for the circuit in Fig 2.



Solution :-

For  $t < 0$

The switch is closed and inductor acts as short circuit therefore inductor current is

$$i = 6A$$

For  $t > 0$

The switch is open and time constant

$$\tau = L/R$$

$$\tau = 3/2$$

Now the inductor current

$$i(t) = 6e^{-t/\tau}$$


$$i(t) = 6e^{-t/3/2}$$

P. No 5<sup>-</sup>

$$i(t) = 6e^{-\frac{2t}{3}} \text{ u(t) A}$$

Q4:- A series RLC circuit has  $R = 100 \Omega$ ,  $L = 240 \text{ mH}$  and  $C = 10 \mu\text{F}$ . If the input voltage is  $v(t) = 10 \cos 2t$  Find the current flowing through the circuit.

Solution:-

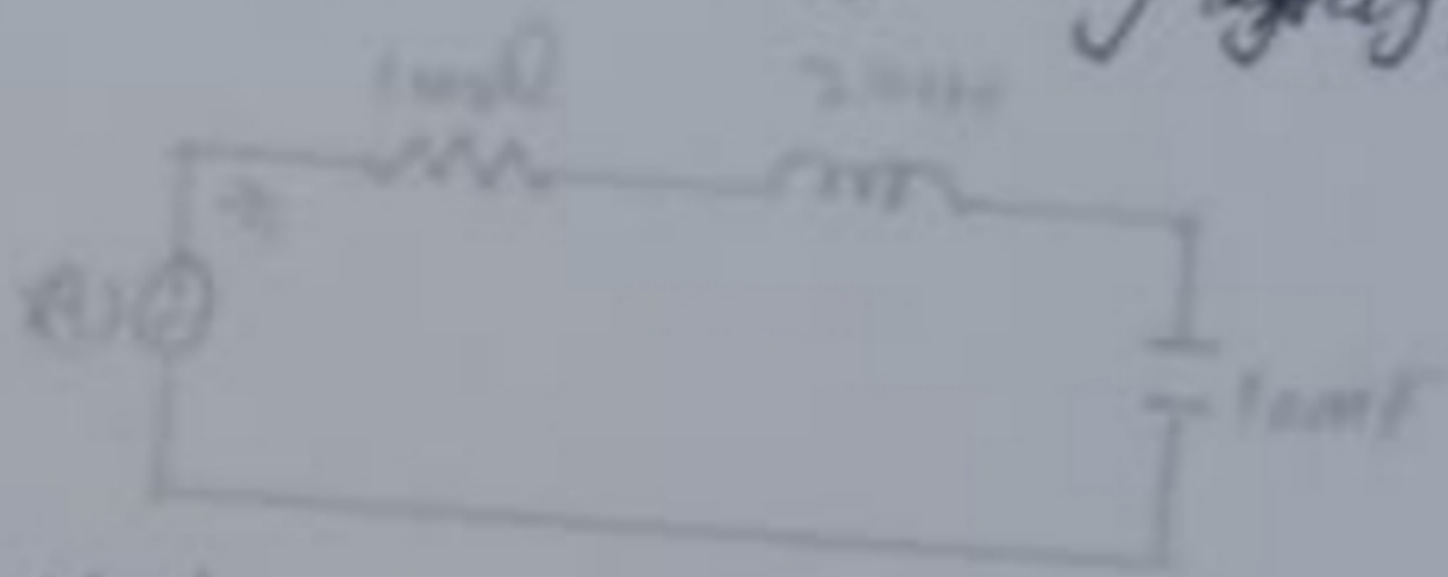

input voltage is  $v(t) = 10 \cos 2t \text{ V}$

Here Amplitude =  $V_m = 10 \text{ V}$

Angular frequency,  $\omega = 2 \text{ rad/s}$

Phase angle,  $\phi = 0$

So phasor for the voltage

$$v(t) = 10 \angle 0^\circ \text{ V}$$

Now for inductive reactance

$$X_L = \omega L$$

So  $\omega = 2 \text{ rad/s}$ ,  $L = 240 \text{ mH}$

$$X_L = 2 (240)$$

$$= 480 \Omega$$

P.No 6

Now for capacitive reactance

$$X_C = \frac{1}{\omega C}, \quad \omega = 2 \text{ rad/s}$$

$$C = 1 \mu\text{F}$$

$$X_C = \frac{1}{2(10 \times 10^{-3})}$$

$$X_C = \frac{1}{2 \times 10^{-2}}$$

$$X_C = \frac{10^2}{2}$$

$$X_C = \frac{100}{2}$$

$$X_C = 50 \Omega$$

Now for impedance

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, \quad X_L = 430 \Omega, \quad X_C = 50 \Omega$$

$$Z = (100 + 430 - 50) \Omega$$

$$Z = (100 + j430) \Omega$$

n . . .  
P. No 7

Represent  $Z$  in phasor form

$$Z = (100 + j430) \Omega$$

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left( \frac{430}{100} \right)$$

$$Z = \sqrt{10000 + 184900} \angle \tan^{-1}(4.3)$$

$$Z = \sqrt{194900} \angle 76.9^\circ \Omega$$

$$Z = 441.47 \angle 76.9^\circ \Omega$$

Now for current flowing;

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ, \quad Z = 441.47 \angle 76.9^\circ$$

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.9^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.9^\circ] \text{ A}$$

n . . .

P. No 8

$$i = 22.6 \times 10^3 \angle -76.90^\circ \text{ A}$$

$$= 22.6 \angle -76.90^\circ \text{ mA}$$

So the general expression for  $i$

$$i = 22.6 \cos(2t - 76.90^\circ) \text{ mA.}$$

Q3:- A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Find the response when  $L = 0.5 \text{ H}$ ,  $R = 4 \Omega$   
and  $C = 0.2 \text{ F}$ . Let  $i(0) = 0$  and  $\frac{di}{dt} = 0$

Solution:-

Given data

$$L = 0.5 \text{ H}$$

$$R = 4 \Omega$$

$$C = 0.2 \text{ F}$$

$$i(0) = 0$$

$$\frac{di(0)}{dt} = 0$$

Voltage of the given RLC  
circuit is described by



Q. No 9

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divided by L

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{10}{L}$$

For R.H.S of the equation multiply  
by  $\frac{C}{L}$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10C}{LC}$$

$C = 0.2 \text{ F}$  thus

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = \frac{2}{LC}$$

Substitute.

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \rightarrow (1)$$

general equation of RLC circuit  
is given by

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10}{LC} \rightarrow (2)$$

compare (1) and (2)

$$\frac{R}{L} = 8 \rightarrow (3)$$

P. No 10

$$\frac{1}{LC} = 10 \text{ --- (4)}$$

$$\frac{2\beta}{LC} = 20 \text{ --- (5)}$$

From equation (3)  $\alpha$  is given by

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/s} \text{ --- (6)}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

From equation (4)

$$\omega_0 = \sqrt{10} \text{ rad/s} \text{ --- (7)}$$

~~Therefore~~ The circuit is over damped

$$\begin{aligned} S_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 + \sqrt{4^2 - 10^2} \\ &= -4 + \sqrt{6} \text{ rad/s} \end{aligned}$$

and

$$\begin{aligned} S_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 - \sqrt{4^2 - 10^2} \\ &= -4 - \sqrt{6} \text{ rad/s} \end{aligned}$$

P. No 11

From eq (5) the steady state current is given by

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2 = 2A \text{ --- (6)}$$

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \text{ --- (7)}$$

$t=0$

$$i(0) = 15 + A_1 + A_2$$

$$1 = 2 + A_1 + A_2$$

$$\text{Thus } A_1 + A_2 = -1 \text{ --- (10)}$$

From eq (9) Find  $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$t=0,$

$$\frac{di(0)}{dt}$$

$$= A_1 s_1 + A_2 s_2$$

substitute the values

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0$$

solve (10) & (11) simultaneously

$$A_1 = -1.336$$

$$A_2 = 0.316$$

Substitute in (9)

$$i(t) = 2 - 1.336 e^{(-4+\sqrt{6})t} + 0.316 e^{(-4-\sqrt{6})t} \text{ A}$$

P. No 12


$$i(t) = 2 - 1.316e^{(-4+\sqrt{5})t} + 0.316e^{(-4-\sqrt{5})t} \text{ A.}$$

Q. 25:-

Find  $v(t)$  and  $i(t)$  in the circuit shown in figure 3

$$v_s = 20 \sin(10t + 30^\circ) \text{ V}$$

Solution:-

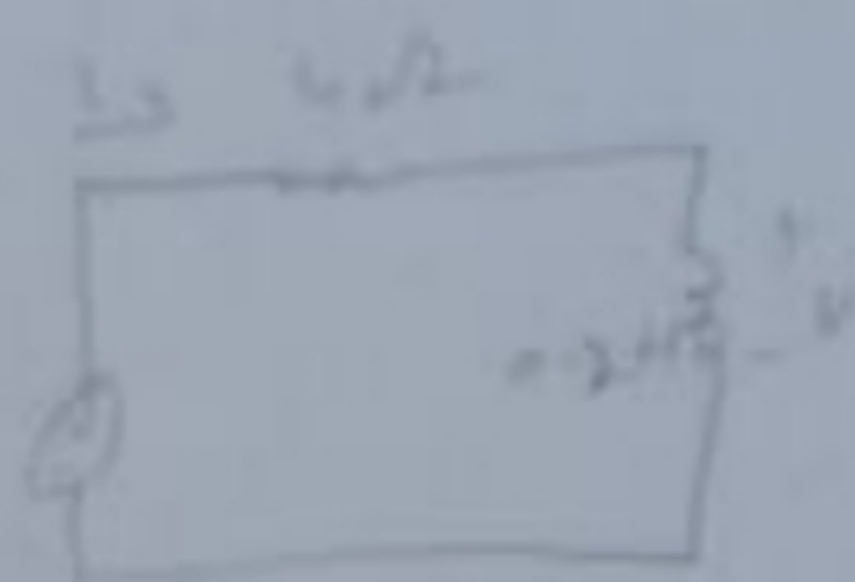

From the voltage source

$$v_s(t) = 20 \sin(10t + 30^\circ) \text{ V}$$

$$v_s = 20 \sin(10t - 60^\circ) \text{ V}$$

$$v_s = 20 \angle -60^\circ \text{ V}$$

$$\omega = 10 \text{ rad/s}$$


$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 10 \times 0.2$$

$$0.2 \text{ H} = j2 \Omega$$

The given circuit can be represented

$$20 \angle -60^\circ \text{ V}$$

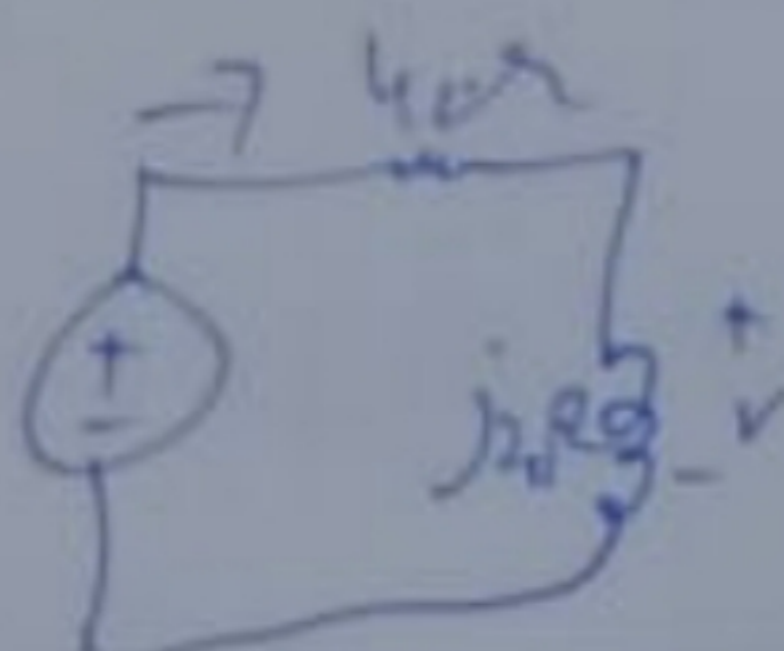

P. No 13

From the circuit diagram.

$$z = 4 + j2 \Omega$$

Hence the current is

$$I = \frac{20 \angle -60^\circ}{4 + j2}$$

$$I = \frac{20 \angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1} \left( \frac{2}{4} \right)}$$

$$I = \frac{20 \angle -60^\circ}{2.472 \angle 26.57^\circ}$$

$$I = 4.472 \angle -86.57^\circ$$

convert into time domain

$$i(t) = 4.472 \cos(\omega t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(\omega t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(\omega t + 3.43^\circ) \text{ A}$$

From the circuit voltage across the inductor is

$$V = j2 \times i$$

$$V = j2 + (4.472 \angle -86.57^\circ)$$

P. No 14

convert Polar form to rectangular form we get

$$V = j2 \times (0.26756 - j4.464)$$

$$V = 8.928 + j0.53512$$

From rectangular to Polar

$$\Rightarrow V = \sqrt{(8.926)^2 + (0.53512)^2} \angle \tan^{-1} \frac{0.53512}{8.926}$$

Now into time domain

$$v(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$