

Course title

E-N-A

module

4th

Instructor

Dr. shahrayaz

Student Detail

Name

Faham Ali

Student ID


14873

Student Signature



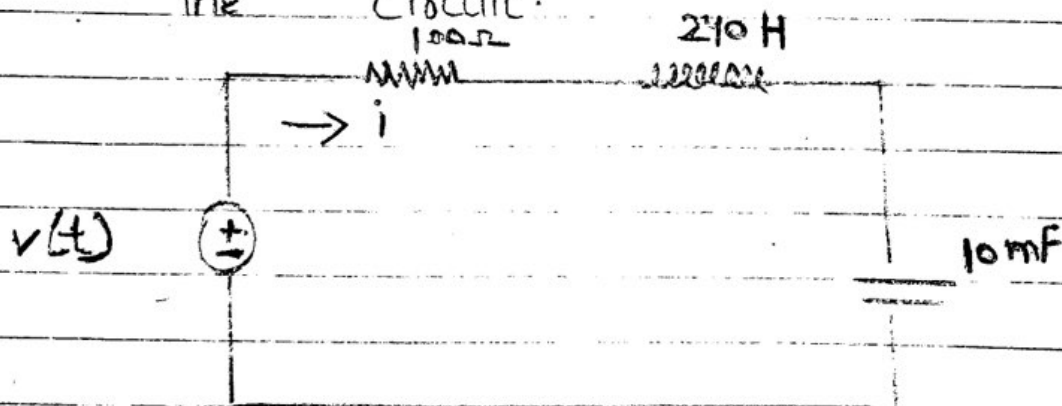Q4 A series RLC circuit has
 $R = 100\Omega$ $L = 240\text{ H}$ and $C = 10\text{mf}$
 if the input voltage is $v(t) = 10 \cos 2t$,
 find the current flowing through
 the circuit?

Ans:4: A series RLC circuit has
 $R = 100\Omega$, $L = 240\text{ H}$ and $C = 10\text{mf}$ If
 the input voltage is $v(t) = 10 \cos 2t$
 Find the current flowing through
 the circuit.



input voltage is $v(t) = 10 \cos 2t\text{v}$

Here

$$\text{Amplitude} = V_m = 10\text{v}$$

$$\text{Angular frequency } \omega = 2 \text{ rad/s}$$

$$\text{phase angle } \phi = 0^\circ$$

So phase for the voltage $v(t)$

$$v(t) = 10 \angle 0^\circ\text{v}$$

Now for inductive reactance $X_L = \omega L$

So $\omega = 2$ radians/s, $L = 240$ H

$$X = (2)(240)$$

$$480 \Omega$$

Now for Capacitive reactance

$$X_C = \frac{1}{\omega C}$$

$\omega = 2$ radians/s, $C = 10$ mf

$$\frac{1}{2(10 \times 10^{-3})}$$

$$\frac{1}{2 \times 10^{-2}}$$

$$\frac{1 \times 10^2}{2}$$

$$\frac{100}{2}$$

$$X_C = 50 \Omega$$

Now for impedance:

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, X_L = 480 \Omega, X_C = 50 \Omega$$

Putting in equation

$$Z = (100 + j430) \Omega$$

$$Z = (100 + j430) \Omega$$

Represent "Z" in polar form

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left(\frac{430}{100} \right)$$

$$= \sqrt{10,000 + 184,900} \angle \tan^{-1}(4.3)$$

$$= \sqrt{194,900} \angle \tan^{-1}(4.3)$$

$$= \sqrt{10,000 + 184,900} \angle \tan^{-1}(4.3)$$

$$= \sqrt{194,900} \angle \tan^{-1}(4.3)$$

$$Z = 441.47 \angle 76.90^\circ \Omega$$

Now for current flowing in the circuit

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ \quad Z = 441.47 \angle 76.90^\circ \Omega$$

Putting in equation

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.90^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.90^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.90^\circ \text{ A}$$

$$= 22.6 \angle -76.90^\circ \text{ mA}$$

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.90^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.90^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.90^\circ \text{ A}$$


$$= 22.6 \angle -76.90^\circ \text{ mA}$$

So

The general expression for "i"

$$i = 22.6 \cos(\omega t - 76.90^\circ) \text{ mA}$$

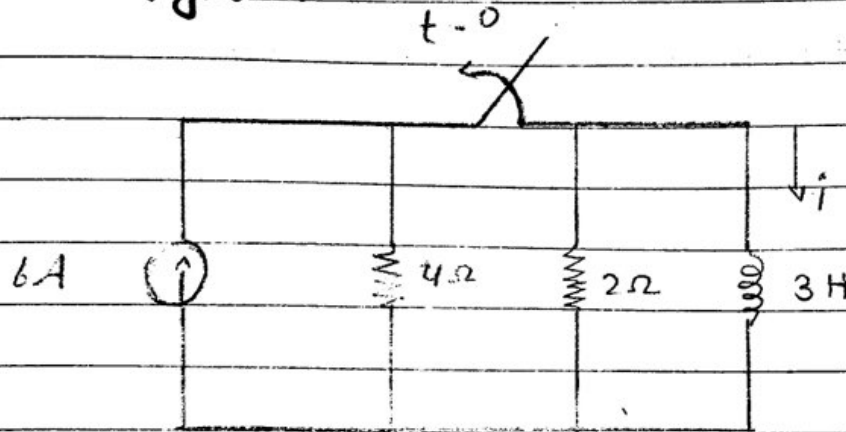Q2: Determine the inductor current for both $t < 0$ and $t > 0$ for the circuit in figure 2.



Solution :

For $t < 0$:

The switch is closed and inductor acts as short circuit. Therefore inductor current

$$i = 6A$$

For $t > 0$:

The switch is opened and time constant $\tau = \frac{L}{R}$


$$\tau = \frac{3}{2}$$

Now the inductor current $i(t) = \frac{-t}{\tau}$

$$i(t) = 6e^{-\frac{t}{3/2}}$$

$$i(t) = 6e^{-2t/3} \text{ A}$$

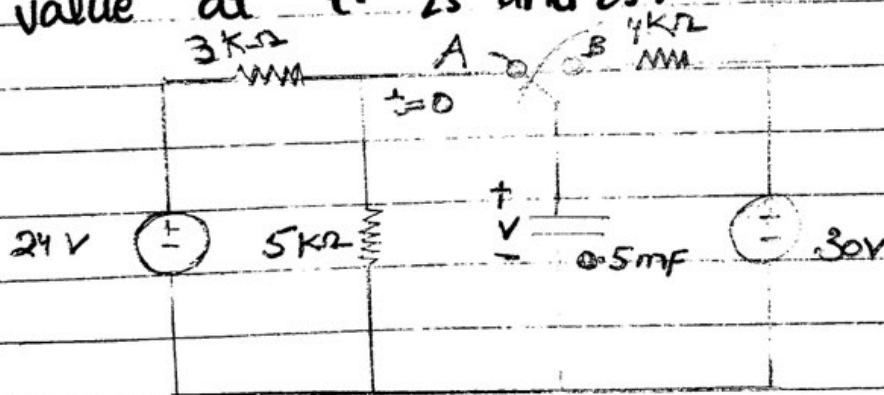Q1: The switch in fig 1 has been in position A for a long time. At $t=0$ the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t=2\text{s}$ and 8s .



Solution:

For $t < 0$

The switch is at position A. The capacitor acts like an open circuit to dc, but v is the same as the voltage across $5\text{k}\Omega$ resistor. Hence the voltage across the capacitor just before $t=0$ is obtained by

by voltage division as;

$$v(0^-) = \frac{5}{5+3} (24) = 15 \text{ v}$$

As the capacitor can't change instantaneously.

$$v(0) = v(0^+) = 15 \text{ v}$$

For $t > 0$:

The switch is in position B. The $R_{th} = 4 \text{ k}\Omega$

Time constant is ;

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\tau = 2 \text{ s}$$

Since the capacitor acts like an open circuit to dc at steady state

$$v(\infty) = 30 \text{ v}$$

Thus

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}}$$

$$= 30 + (15 - 30) e^{-t/2}$$

$$= (30 - 15e^{-0.5t}) \text{ v}$$

At $t = 2$

$$v(2) = 30 - 15e^{-\frac{2}{2}}$$
$$= 30 - 15e^{-1}$$


$$v(2) = 24.48 \text{ V}$$

At $t = 8$:

$$v(8) = 30 - 15e^{-\frac{8}{2}}$$
$$= 30 - 15e^{-4}$$

$$v(8) = 29.72$$

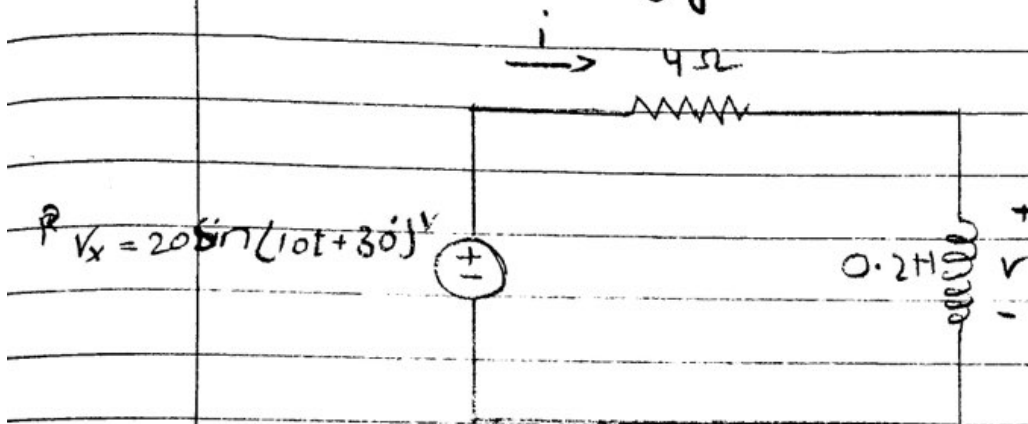Q5: Find $v(t)$ and $i(t)$ in the circuit shown in figure 3.



Solution:

For $i(t)$

From the voltage source

$$v_s = 20 \sin(10t + 30^\circ) \text{ V}$$

$$v_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V}$$

$$v_s = 20 \cos(10t - 60^\circ) \text{ V}$$

$$v_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 10 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 10 \times 0.2$$

$$0.2 \text{ H} = j 2 \Omega$$

Given circuit can be represented As ;

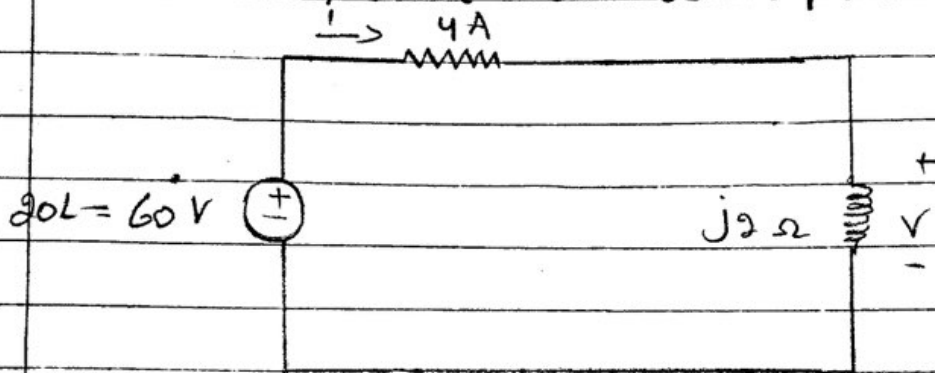

From the above circuit

$$Z = 4 + j2\Omega$$

Hence the current is ;

$$i = \frac{20\angle -60^\circ}{4 + j2}$$

$$i = \frac{20\angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1} \frac{2}{4}}$$

$$i = \frac{20\angle -60^\circ}{4.472\angle 26.57^\circ}$$

$$i = 4.472\angle -86.57^\circ$$

Converting this into time domain

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

For $v(t)$ from the circuit voltage across the inductor is

$$v = j\omega xi$$

$$v = j\omega x(4.472 \angle 86.57^\circ)$$

Converting polar form to rectangular form we get;

$$v = j\omega x(0.26756 - j4.464)$$

$$v = 8.928 + j0.53512$$

Converting rectangular form to polar form

$$V = \sqrt{(8.926)^2 + (0.5312)^2} \angle \tan^{-1} \left(\frac{0.5312}{8.928} \right)$$

$$V = 8.944 \angle 3.4^\circ$$

Converting this into time domain

$$v(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$

Q3 A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Find the response when $L = 0.5 \text{ H}$, $R = 4 \Omega$

and $C = 0.2 \text{ F}$. Let $i(0) = 1$, $\left. \frac{di}{dt} \right|_{t=0} = 0$

Solution:

The step response of the branch voltage of the given RLC circuit is described by:

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by L

$$\frac{d^2 i}{dt^2} + R \frac{di}{L dt} + \frac{i}{LC} = \frac{10}{L}$$

King by $\frac{C}{L}$

$$\frac{d^2 i}{dt^2} + R \frac{di}{L dt} + i = \frac{100}{LC}$$

As $C = 0 \cdot \omega$ thus :

$$\frac{d^2i}{dt^2} + \frac{Rdi}{Ldt} + \frac{i}{L} = \frac{2}{L}$$

Substitute

$$\frac{d^2i}{dt^2} + 8\frac{di}{dt} + 10i = 20 \dots (i)$$

The general form for source-free RLC given by

$$\frac{d^2i}{dt^2} + \frac{Rdi}{Ldt} + \frac{i}{L} = \frac{I_s}{L}$$

Comparing 1 & 2 we get

$$RL = 8 \rightarrow (3)$$

$$\frac{1}{L} = 10 \rightarrow (4)$$

$$\frac{I_s}{L} = 20 \rightarrow (5)$$

From (3), α is given by :

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/sec} \rightarrow (6)$$

The natural frequency ω_0 is given by:

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

From (4)

$$\omega_0 = \sqrt{10} \text{ rad/sec} \rightarrow (7)$$

From (6) & (7)

$$\therefore \alpha > \omega_0$$

\therefore The circuit is over damped

The roots of characteristic equation are given by:

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 + \sqrt{4^2 - 10^2} \\ &= -4 + \sqrt{6} \text{ rad/sec} \end{aligned}$$

And,

$$\begin{aligned} s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 - \sqrt{4^2 - 10^2} \\ &= -4 - \sqrt{6} \text{ rad/sec} \end{aligned}$$

From (5) the steady current is given by

$$I_s = \mathcal{E} / R = 20 \times 0.5 / 2 = 2.5 \text{ A} \rightarrow (8)$$

The current for over damped is given by;

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

$$i(0) = I_s + A_1 + A_2$$

$$1 = 2 + A_1 + A_2$$

$$A_1 + A_2 = -1 \rightarrow (10)$$

From 9, find $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute too;

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute the value

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0 \rightarrow (11)$$

Solving (10) & (11) Simultaneously

$$A_1 = -1.316$$

$$A_2 = 0.316$$

Substitute in (9)

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t} \quad A$$