

Department of electrical
Engineering, -

Name :- Muhammad Faizan

ID :- 16046

Sub :- LCA





Module :- 2nd

Total marks :- 30

Instruction Ch: Sohail Imran

Q No 1: (a)

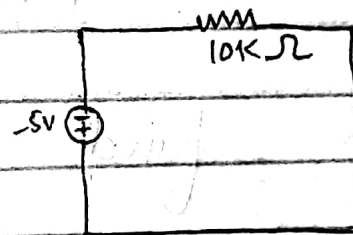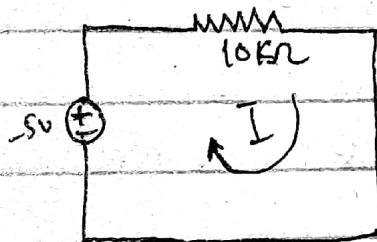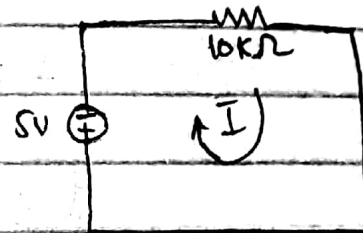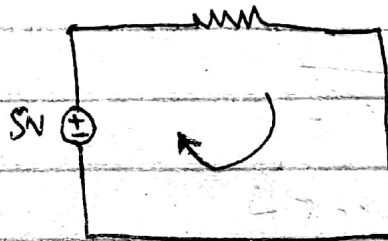For each of the following circuits in figure. Find the current I and by computer the power absorbed by the resistor.



Ans:

Applying ohm law for finding circuit.

$$V = IR$$
$$I = \frac{V}{R}$$

For find power in the circuit we use

$$P = VI, \quad P = I^2R$$

Page # 2

To obtain a result so we need
to Perment a given Value for
each Circuit So if Current

$$V = IR$$

$$I = VR$$

$$I = \frac{5V}{10000\Omega}$$

$$I = 0.0005A$$

$$I = 0.5mA$$

For find Power we use $P = I^2(R)$

$$P = I^2R$$

$$P = (0.5mA)^2 \times (10000)$$

$$P = 0.0025$$

$$(P = 0.25 \times 10^{-3})$$

Page # 3

For Finding and Second Circuit
Current and Power

We apply ohm law for
finding Current

$$V = IR$$

$$I = V/R$$

$$I = V/R$$

$$I = -5V / 10000\Omega$$

$$(I = -0.0005A)$$

For Find Power we use $P = I^2 R$

$$P = I^2 R$$

$$P = -(0.0005)^2 (10000)$$

$$P = -0.0025W$$

$$P = -0.25mW$$

Page # 4

For Finding Current and Power
in 4th Circuit

We apply ohm law = $V = IR$

$$I = V/R$$

$$I = 5V / 10000 \Omega$$

$$I = 0.0005 A$$

$$I = 0.5 mA$$

For Finding Power in a
Circuit we apply $P = I^2 R$

$$P = (0.0005 A)^2 (10000) \Omega$$

$$P = 0.0025$$

$$P = 0.25 mW$$

Page # 5

Q No 18-(c)

Following figure depicts the characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.

Sol:

Ohm law $V = IR$, $R = V/I$
So we calculate R from the slope on the graph. we can take any point on the line to get the value of "I" and "V".

Page # 6

Solution: (a)

$$I = 0.01 \text{ mA}$$

$$V = 1 \text{ V}$$

$$R = ?$$

Applying ohm law

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{0.5 \text{ A}}{5 \text{ V}} \Rightarrow 10 \mu\text{S}$$

$$R = \frac{1 \text{ V}}{0.01} \times 10^{-3}$$

$$R = 100 \text{ k}\Omega$$

Page # 7

Solution:- (B)

through current is zero as zero difficulty to see the as slope

$$V = IR \Rightarrow R = V/I$$

$$R = \frac{1V}{0}$$

$$R = \infty$$

Page # 8

Solution :- (c)

through the is current ∞ (s) difficulty infinite to see as slope

$$R = \frac{1}{\infty}$$

OR


$$R = 0$$

We have this is zero resistance

$$(R = 0)$$

Q No (1) = (B)

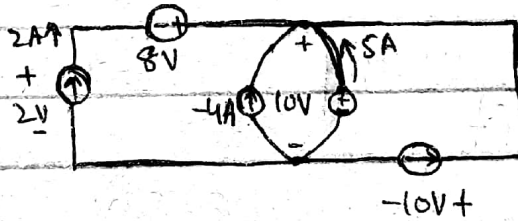Determine the Power Supplied by the leftmost element in the circuit of the following figure.



Solution:-

We apply $P = VI$ for finding Power:-

$$P = VI$$

$$P = 2V \times 2A$$

$$P = 4W \text{ Supplied}$$

4w is Supplied Power in the current + direction with Positive Sign.

QNO 2 (a)

Refer to the Circuits of the following figures and answer.

(1) How many distinct nodes are contained in the circuit?

(2) How many elements are contained in the circuit?

(3) How many branches does the circuit have?


(4) Determine if each of the following represents a path, a loop, both or neither.

(i) A to B

(ii) B to D to C to E

(iii) C to E to D to B to A to C

(iv) C to D to B to A to C to E

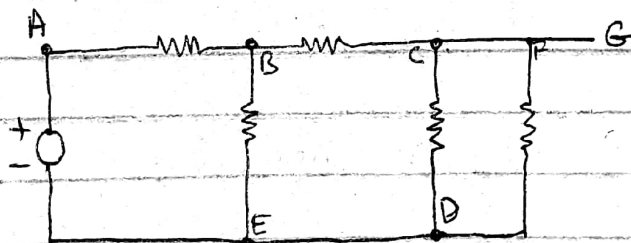

Ans 2(a)

(1) Nodes = 4

(2) Element = 5

(3) Branch = 5

(4)

(i) Neither

(ii) only path

(iii) Path and loop

(iv) Neither

Q2 (b)

For the circuit of following figure (which is a model for the de operation of a bipolar Junction transistor biased in forward active region) I_B is measure to be $100 \mu A$. Determine I_C and I_E .

Ans: 2 (b)

Kcl total current entering a node = total current leaving a node

$$I_C = 150 \times I_B = 150 \times 100 = 15 \text{ mA}$$

$$I_E = 15 + 0.1 = 15.1 \text{ mA}$$

Q3 (a)

Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.

- Determine the power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).

we use ohm's law

$$V = IR$$

$$V = 2 \times 10^3 \times 637$$

$$V = 1.274 \text{ V}$$

Find ~~Current~~ Current

$$V = IR$$

$$I = V/R$$

$$\Rightarrow I_1 = \frac{V}{R_1} \Rightarrow \frac{1.274}{1000} = 1.274 \text{ mA}$$

$$\Rightarrow I_2 = \frac{V}{R_2} = \frac{1.274}{2800} \Rightarrow 0.455 \text{ mA}$$

$$\Rightarrow I_3 = \frac{V}{R_3} = \frac{1.274}{4700} \Rightarrow 0.271 \text{ mA}$$

Find Power

$$\Rightarrow P(1K) = (1.274)(1.274) = (1.623 \text{ mW})$$

$$\Rightarrow P(4.7K) = (1.274)(0.271) = (0.345 \text{ mW})$$

$$\Rightarrow P(2.8K) = (1.274)(0.271) = (0.5797 \text{ mW})$$

$$\Rightarrow P(5 \text{ mA}) = (1.274)(-5) = (-6.37 \text{ mW})$$

$$\Rightarrow P(3 \text{ mA}) = (1.274)(3) = (3.822 \text{ mW})$$

Q3 (b): Determine the power absorbed by the 15Ω resistor on the circuit of the following figure.

Ans 3(b)

First simplify the circuit by calculating resistance ~~and~~ and by equalance

$$I_{eq} = 4 - 2i + 3A = 2 - 2i$$

$$R_{eq} = (6 + 3 // 15) // 6 // 8$$

$$R_{eq} = 8.5 // 3 = 2.2174 \Omega$$

Now we can calculate voltage

$$V = I_{eq} \times R_{eq}$$

$$V = (2 - 2i) \times (2.2174 \Omega)$$

and from the diagram we can see that

$$V = 6i$$

$$= 6i = (-2 - 2i) + 2.2174$$

$$= 10.4348 \times i = -4.4348$$

$$I = 0.42A$$

$$V = -2.55V$$

Page # 14

Power Consumed by the 15Ω resistor well need the Voltage on that resistor that

$$P = V^2/R$$

$$P_{15\Omega} = \frac{V^2 \cdot 15\Omega}{15\Omega}$$

$$V_{15\Omega} = \frac{6}{6+2.5} \cdot V$$

$$V_{15\Omega} = 1.8V$$

and Power is

$$P_{15\Omega} = \frac{1.8^2}{15\Omega}$$

$$P_{15\Omega} = 0.216W$$