

Name

M. Bilal Khan

I.D.

16434

Dept.

BECE)

Semester :-


2nd.

Assignment -

Open Ended  
Lab

Subject

LCA (Lab)

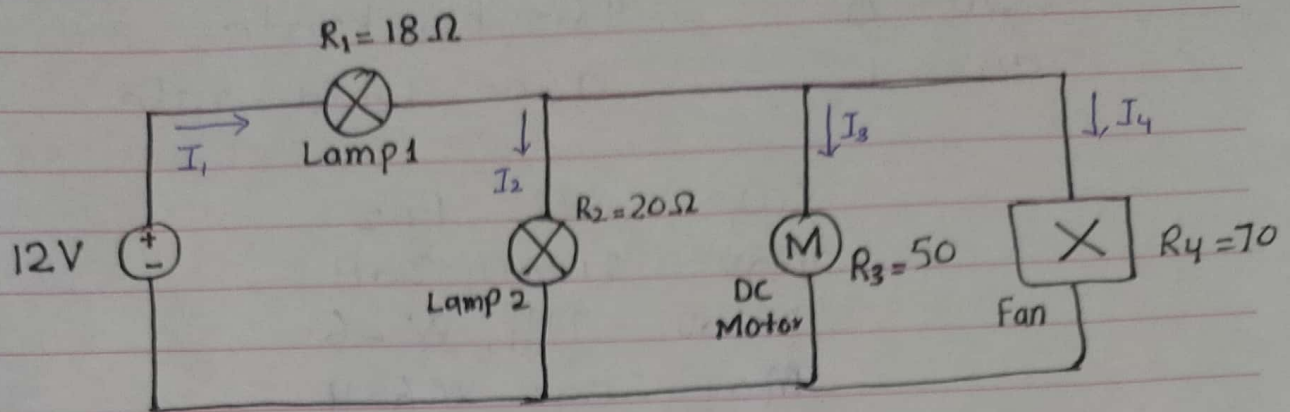

Here  $R_2$ ,  $R_3$  and  $R_4$  are in parallel, therefore

$$R_T = R_2 \parallel R_3 \parallel R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$= \frac{1}{\frac{1}{20} + \frac{1}{50} + \frac{1}{70}}$$


$$= \frac{1}{0.05 + 0.02 + 0.0142857}$$

$$= 11.86 \, \Omega$$

Now the circuit



2

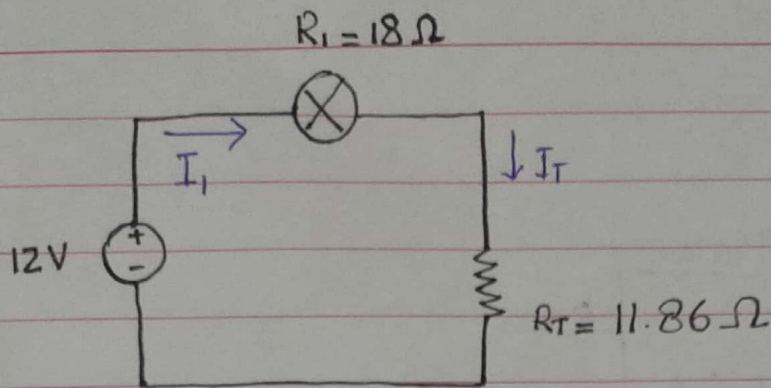

Note

$$R_T = R_2 \parallel R_3 \parallel R_4$$

Since  $R_1$  and  $R_T$  are in series  $I$  through both the resistance are same


$\therefore$  Current through lamp 1 is

$$I_1 = \frac{V}{R_1 + R_T} = \frac{12}{18 + 11.86} = 0.40 \text{ A}$$

Now the circuit modifies to

voltage across lamp  $V_1$
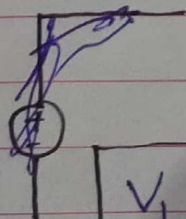
$$V_1 = \left( \frac{R_1}{R_T + R_1} \right) V = \left( \frac{18}{11.86 + 18} \right) 12$$



$$V_1 = 7.2 \text{ V}$$


Now Voltage across  $R_T$

$$= V - V_1$$

$$= 12 - 7.2$$

$$V_T = 4.8V$$

Now the circuit is

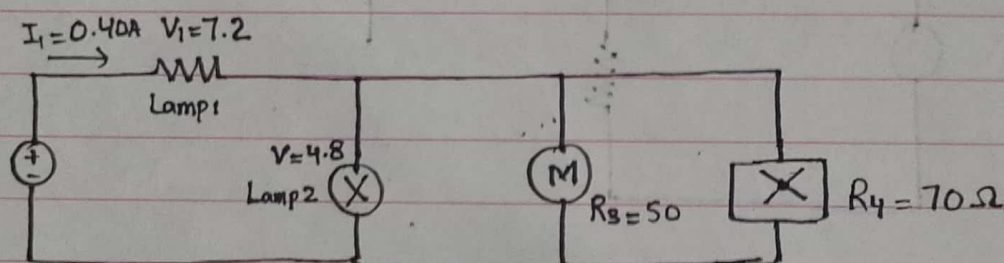

Since the voltage across Lamp 2 is  $V_T = 4.8V$  and  $R_2, R_3$  and  $R_4$  are in parallel So the voltage across  $R_2, R_3$  and  $R_4$  is same hence

$$V_2 (\text{Lamp 2}) = 4.8V$$

$$V_3 (\text{MOTOR}) = 4.8V$$

$$V_4 (\text{Fan}) = 4.8V$$



Now the current through  
 $R_3$  and  $R_4$  are

$$I_2 (\text{lamp 2}) = \frac{4.8}{20} = 0.24 \text{ A}$$

$$I_3 (\text{Motor}) = \frac{4.8}{50} = 0.096 \text{ A}$$

$$I_4 (\text{Fan}) = \frac{4.8}{70} = 0.068 \text{ A}$$

c) Now For Power losses

$$\text{Power loss in Lamp 1} = P_1 = V_1 I_1$$

$$= 7.2 \times 0.40$$

$$= 2.88 \text{ W}$$

$$\text{Power loss in Lamp 2} = P_2 = V_T I_2$$

$$= 4.8 \times 0.24$$

$$= 1.152$$

$$\text{Power Loss in Motor} = P_3 = V_T \times I_3$$

$$= 4.8 \times 0.096$$

$$= 0.4608 \text{ W}$$

(5)

Power Loss in DC Fan =  $P_4 = V_T \times I_4$

$$= 4.8 \times 0.068$$

$$= 0.3264 \text{ W}$$

The final circuit is

