

Name :

M. Idrees Khan

I.D :

16431

Subject :

LCA (Lab)

Instructor :


Sir Waleed Jan

Date :

27-06-2020

Assignment:

Open Ended Lab

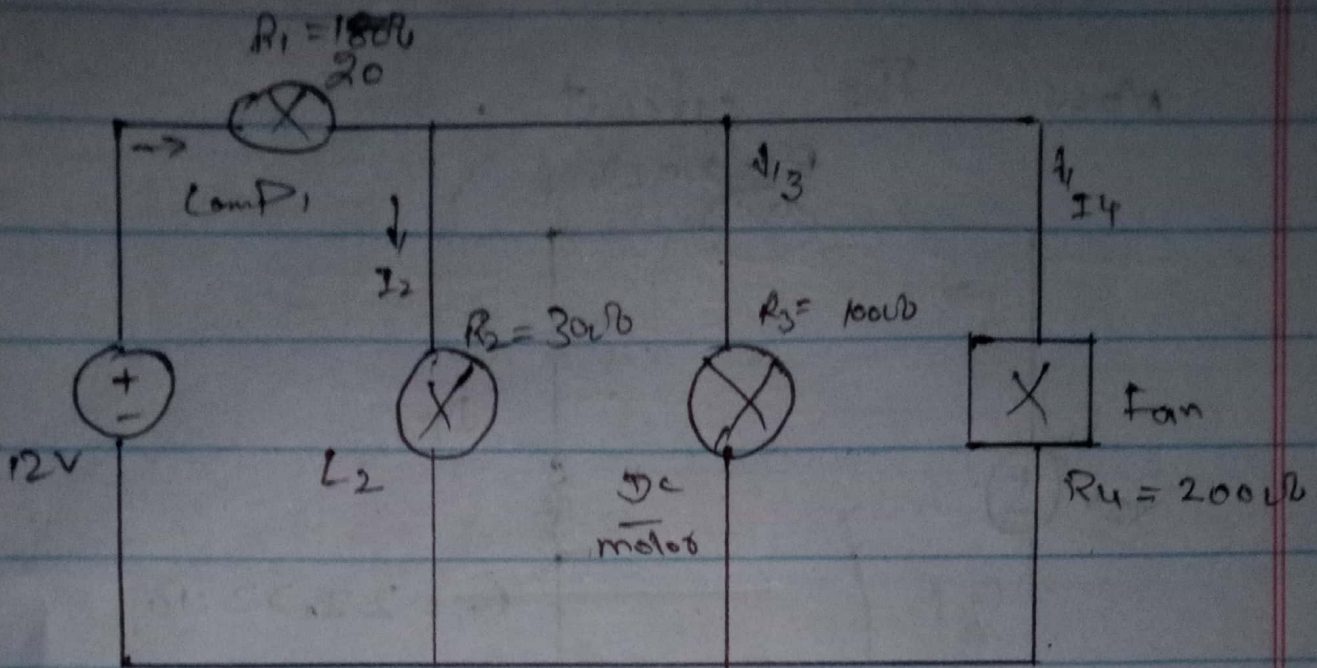

Here R_2 , R_3 and R_4 are in parallel, therefore

$$R_T = R_2 \parallel R_3 \parallel R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$


$$= \frac{1}{\frac{1}{30} + \frac{1}{100} + \frac{1}{200}}$$

$$= \frac{1}{0.03 + 0.01 + 0.005}$$

$$= \frac{1}{0.045}$$

$$R_T = 22.22 \Omega$$

Note: The circuit

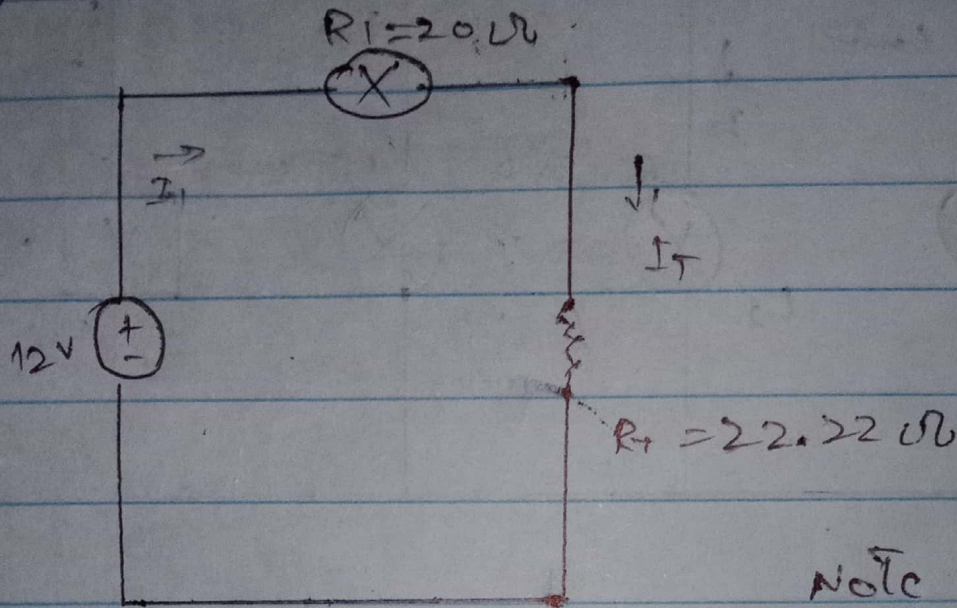

Note

$$R_T = R_2 \parallel R_3 \parallel R_4$$

Since R_1 and R_T are in series I through both resistance are same.

Current through Lamp 1 is

$$I_1 = \frac{V}{R_1 + R_T} = \frac{12}{20 + 22.22}$$

$$I_1 = \frac{12}{42.22} = \boxed{0.2842 \text{ A}}$$

Now The circuit modifies to

voltage across Lamp V_1

$$V_1 = \left(\frac{R_1}{R_T + R_1} \right) V$$

$$V_1 = \left(\frac{20}{22.22 + 20} \right) 12$$

$$V_1 = \frac{(20)(12)}{42.22}$$

$$= \frac{240}{42.22}$$

$$V_1 = 5.6845 \text{ V}$$


Now voltage across R_T

$$V_T = V - V_1$$

$$V_T = 12 - 5.6845$$

$$V_T = 6.31V$$

Now The circuit is

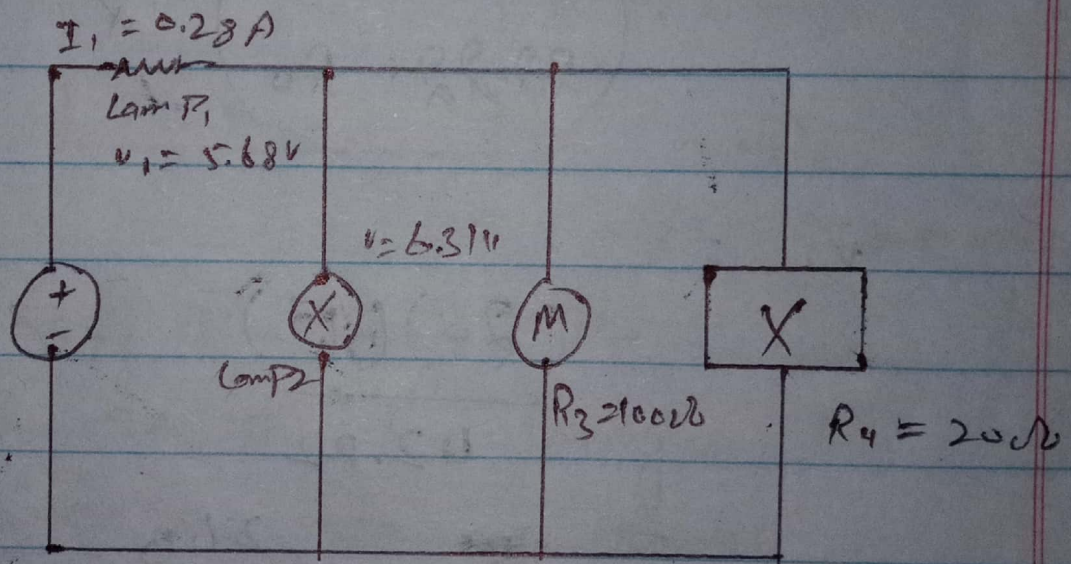

Since The voltage across
Lamp 2 is $V_T = 6.31 V$
and R_2 , R_3 and R_4 are
in parallel, so The voltage
across R_2 , R_3 and R_4
is same,

hence

$$V_2 \text{ (Lamp 2)} = 6.31 \text{ V}$$

$$V_3 \text{ (Motor)} = 6.31 \text{ V}$$

$$V_4 \text{ (Fan)} = 6.31 \text{ V}$$

Now The current through
 R_3 and R_4 are

$$I_2 \text{ (Lamp 2)} = \frac{6.31}{30} = 0.2103 \text{ A}$$

$$I_3 \text{ (Motor)} = \frac{6.31}{100} = 0.0631 \text{ A}$$

$$I_4 \text{ (Fan)} = \frac{6.31}{200} = 0.03155 \text{ A}$$

(c)

Now for Power Losses.

Power losses in Lamp 1 = $P_1 = V_1 I_1$

$$P_1 = (5.68)(0.28)$$

$$P_1 = 1.5916 \text{ W}$$

Power losses in Lamp 2 = $P_2 = V_2 I_2$

$$= (6.31)(0.21)$$

$$P_2 = 1.3251 \text{ W}$$

Power losses in Motor = $P_3 = V_T \times I_3$

$$= (6.31)(0.06)$$


$$P_3 = 0.3786 \text{ W}$$

Power losses in DC Fan = $P_4 = V_T \times I_4$

$$P_4 = (6.31)(0.03)$$

$$P_4 = 0.1893 \text{ W}$$

The Total circuit is

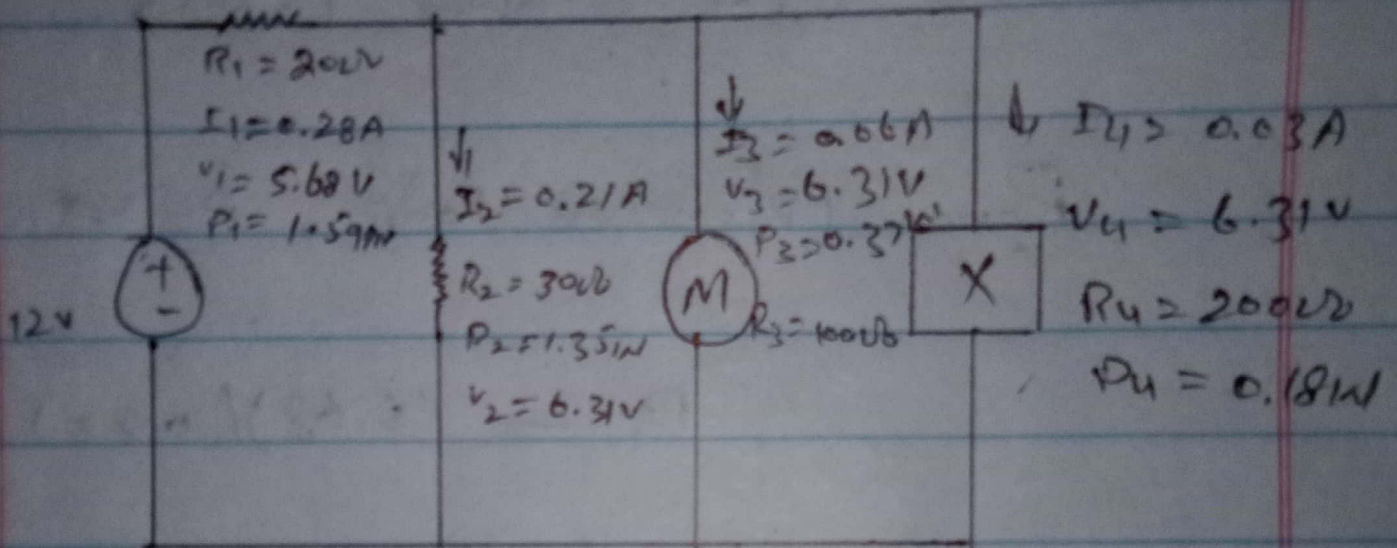

The Total circuit is

