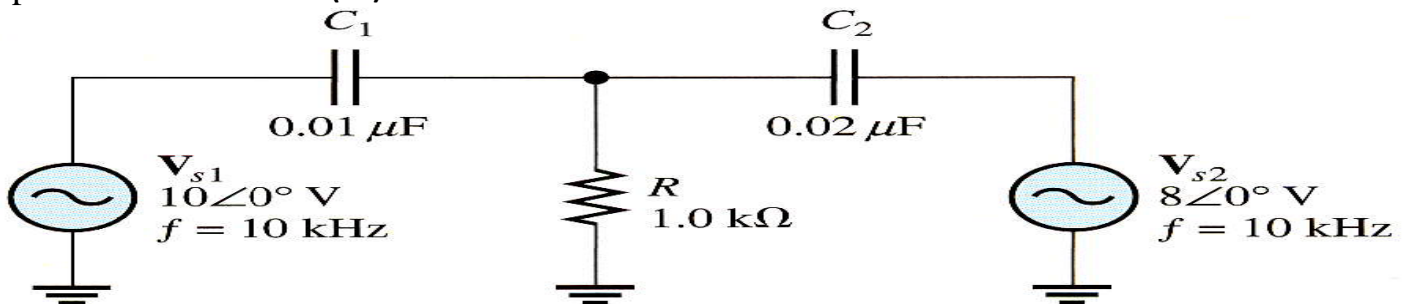


Instructor: Rashid Aleem  
 Paper: Ac Circuit Analysis  
 Time : 4 Hours

Note:


- 1) Attempt all questions.
- 2) Assume missing details if required.
- 3) Draw neat diagrams where required.

Q1: Find the current in R in following fig .using the superposition theorem. Assume the internal impedance source zero. (10)




Q2: Determine  $V_{th}$  for the circuit external to  $R_L$  in Figure . The beige area identifies the portion of the circuit to be thevenized..(10)


5

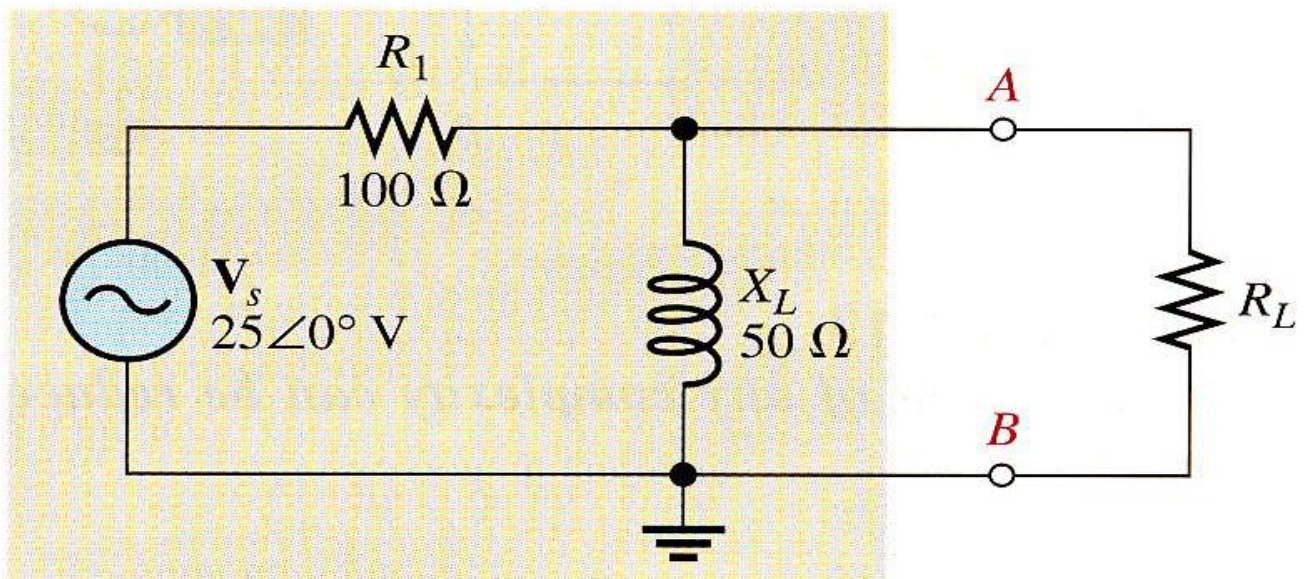

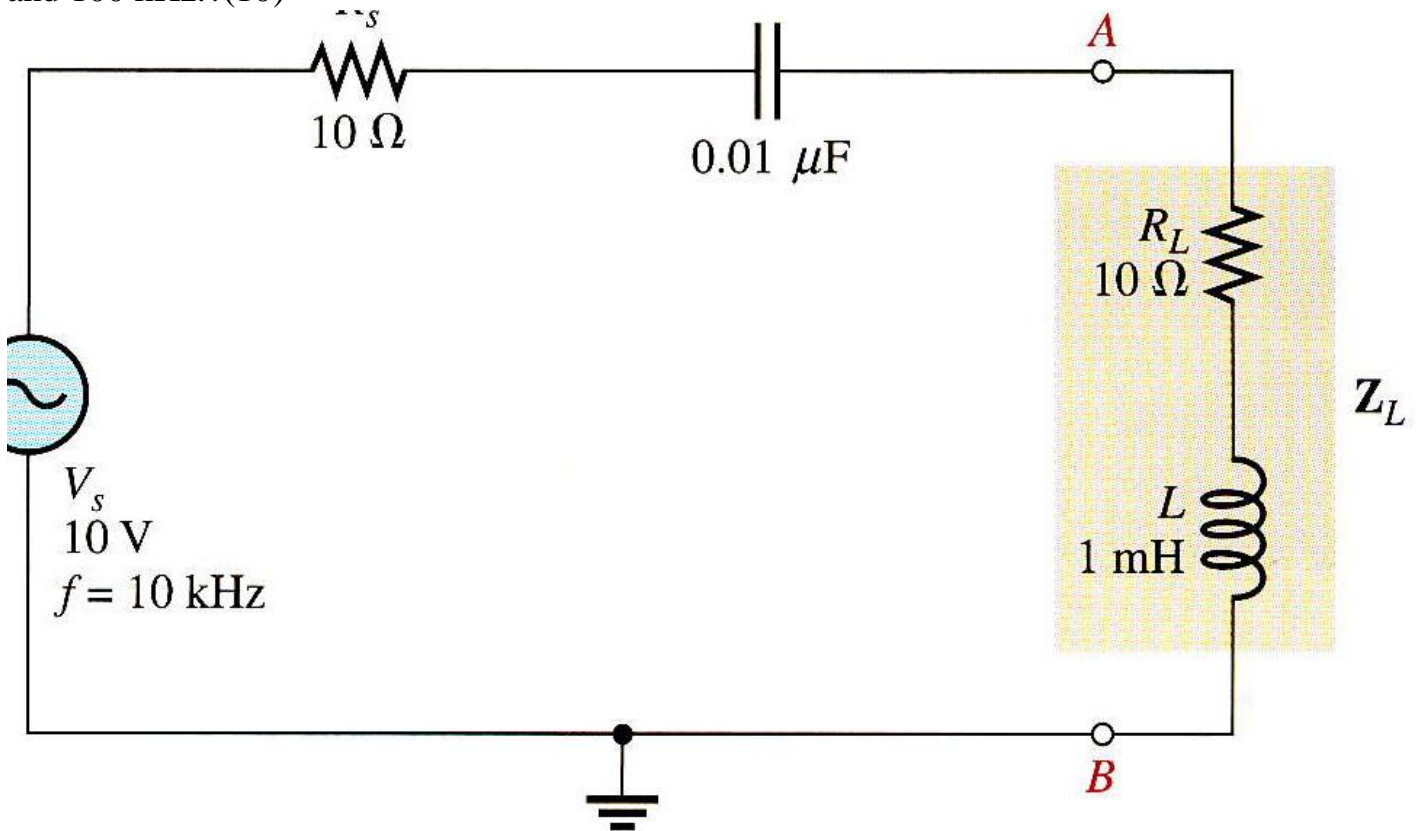
**Q3: (10)** The circuit to the left of terminals A and B in Figure provides power to the load  $Z_L$ . This can be viewed as simulating a power amplifier delivering power to a complex load. It is the Thevenin equivalent of a more complex circuit. Calculate and plot a graph of the power delivered to the load for each of the following frequencies: 10 kHz, 30 kHz, 50 kHz, 80 kHz, and 100 kHz. (10)



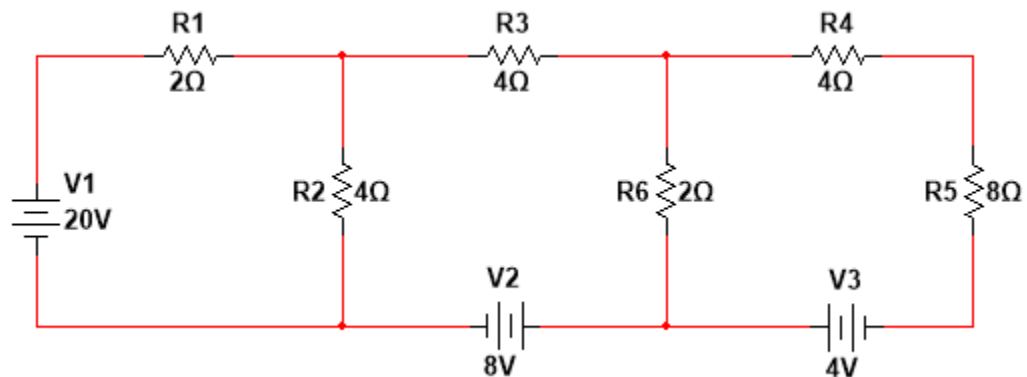**Q4:** Using Thevenin's and Norton's theorem, find the currents in  $8\Omega$  resistor in the figure shown below. (10)



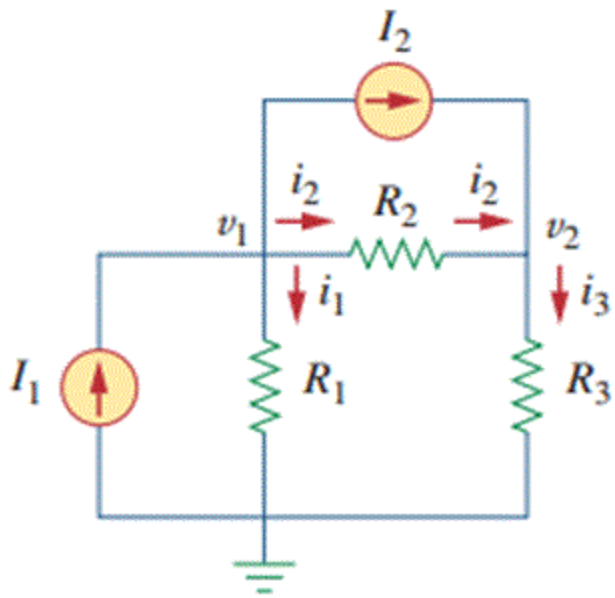
**Q5)** Solve the following example by nodal analysis. Write all the general steps? (10)



## PAPER AC CIRCUIT ANALYSIS

ANS:1

Solution;

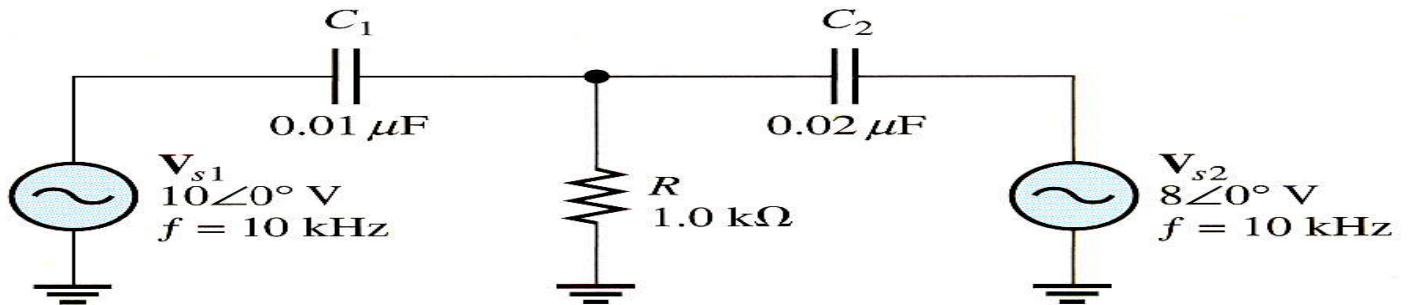Replace  $V_{s2}$  with its internal impedance (zero), and find the current in R due to  $V_{s1}$ 

$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi(10\text{kHz})(0.02\mu\text{f})} = 796\Omega$$

Looking from  $v_{s1}$  the impedance is

$$Z = X_{C1} + \frac{R X_{C2}}{R + X_{C2}} = 15.9 \angle -90^\circ \text{ k}\Omega + \frac{(1.0 \angle 0^\circ \text{ k}\Omega)(796 \angle -90^\circ \Omega)}{1.0 \text{ k}\Omega - j796\Omega}$$

$$= 1.59 \angle -90^\circ \text{ k}\Omega + 622 \angle -51.5^\circ$$

$$= -j1.59 \text{ k}\Omega + 387\Omega - j481\Omega = 387\Omega - j2.08 \text{ k}\Omega$$

Converting to polar form yields

$$Z = 2.12 \angle -79.5^\circ \text{ k}\Omega$$

The total current from source 1 is


$$I_{S1} = \frac{V_{S1}}{Z} = \frac{10 \angle 0^\circ \text{ V}}{2.12 \angle -79.5^\circ \text{ k}\Omega} = 4.72 \angle 79.5^\circ \text{ mA}$$

$$I_{R1} = \left( \frac{X_{C2} \angle -90^\circ}{R - jX_{C2}} \right) I_{S1} = \left( \frac{796 \angle 90^\circ \Omega}{1.0 \text{ k}\Omega - j796\Omega} \right) 4.72 \angle 79.5^\circ \text{ mA}$$

$$= (0.623 \angle -51.5^\circ \Omega)(4.72 \angle 79.5^\circ \text{ mA}) = 2.94 \angle 28.0^\circ \text{ mA}$$

Q2; q2: Determine  $V_{th}$  for the circuit external to  $R_L$  in Figure . The beige area identifies the portion of the circuit to be thevenized..(10)

5

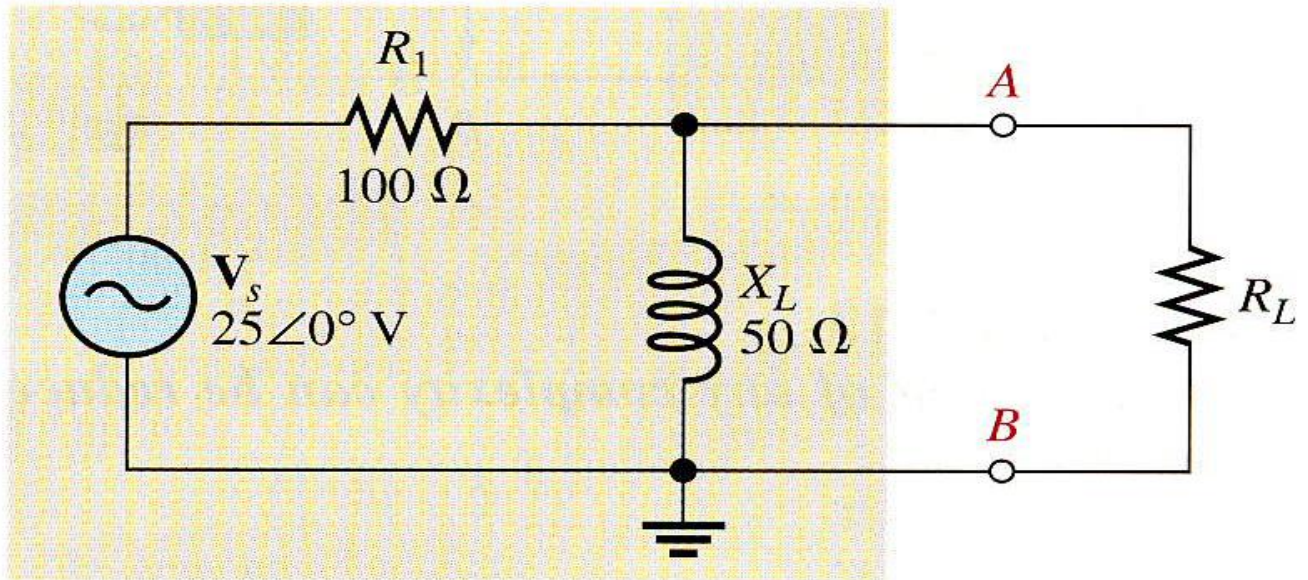

**Solution :**

Remove  $R_L$ , and determine the voltage from A to B ( $V_{th}$ ). In this case, the voltage from A to B is the same as the voltage across  $X_L$ . This is determined using the voltage-divider method

$$V_L = \left( \frac{X_L \angle 90^\circ}{R_1 + jX_L} \right) V_s = \left( \frac{50 \angle 90^\circ \Omega}{112 \angle 26.6^\circ \Omega} \right) 25 \angle 0^\circ V = 11.2 \angle 63.4^\circ V$$

$$V_{th} = V_{AB} = V_L = 11.2 \angle 63.4^\circ V$$

**ANS:3**

**SOLUTION:**

For  $f = 10 \text{ kHz}$

$$X_C = \frac{1}{2\pi fc} = \frac{1}{2\pi(10\text{kHz})(0.01\mu\text{F})} = 1.59\text{k}\Omega$$

$$X_L = 2\pi fL = 2\pi(10\text{kHz})(1\text{mH}) = 62.8\Omega$$

The magnitude of the total impedance is

$$\begin{aligned} Z_{\text{tot}} &= \sqrt{(R_S + R_L)^2 + (X_L + X_C)^2} \\ &= \sqrt{(20\Omega)^2 + (1.53\text{k}\Omega)^2} = 1.53\text{k}\Omega \end{aligned}$$

The current is

$$I = \frac{V_S}{Z_{\text{tot}}} = \frac{10\text{V}}{1.53\text{k}\Omega} = 6.54\text{mA}$$

The load power is

$$P_L = I^2 R_L = (6.54\text{mA})^2 (10\Omega) = 428\mu\text{W}$$

For  $f = 30\text{kHz}$

$$X_C = \frac{1}{2\pi(30\text{kHz})(0.01\mu\text{F})} = 531\Omega$$

$$X_L = 2\pi(30\text{kHz})(1\text{mH}) = 189\Omega$$

$$\sqrt{(20\Omega)^2 + (342\Omega)^2} = 343\Omega$$

$$I = \frac{V_s}{Z_{\text{tot}}} = \frac{10\text{v}}{343\Omega} = 29.2\text{mA}$$

$$P_L = I^2 R_L = (29.2\text{mA})^2 (10\ \Omega) = 8.53\ \text{mW}$$

For  $f = 50\ \text{kHz}$ ,

$$X_C = \frac{1}{2\pi(50\text{kHz})(0.01\mu\text{F})} = 318\Omega$$

$$X_L = 2\pi(50\ \text{kHz})(1\ \text{mH}) = 314\Omega$$

Note that  $X_C$  and  $X_L$  are very close to being equal which makes the impedances approximately complex conjugates. The exact frequency at which  $X_L = X_C$  is 50.3 kHz.

$$Z_{\text{tot}} = \sqrt{(20\Omega)^2 + (4\text{k}\Omega)^2} = 20.4\Omega$$

$$I = \frac{V_s}{Z_{\text{tot}}} = \frac{10\text{v}}{20.4\Omega} = 490\text{mA}$$

$$P_L = I^2 R_L = (490\text{mA})^2 (10\ \Omega) = 2.40\ \text{W}$$

For  $f = 80\ \text{kHz}$ ,

$$X_C = \frac{1}{2\pi(80\text{kHz})(0.01\mu\text{F})} = 199\Omega$$

$$X_L = 2\pi(80\ \text{kHz})(1\ \text{mH}) = 503\Omega$$

$$Z_{\text{tot}} = \sqrt{(20\Omega)^2 + (304\text{k}\Omega)^2} = 305\Omega$$

$$I = \frac{V_s}{Z_{\text{tot}}} = \frac{10\text{v}}{305\Omega} = 490\text{mA}$$

$$P_L = I^2 R_L = (32.8 \text{ mA})^2 (10 \Omega) = 10.8 \text{ mW}$$

For  $f = 100 \text{ kHz}$ ,

$$X_C = \frac{1}{2\pi(100 \text{ kHz})(0.01 \mu\text{F})} = 159 \Omega$$

$$X_L = 2\pi(100 \text{ kHz})(1 \text{ mH}) = 628 \Omega$$


$$Z_{\text{tot}} = \sqrt{(20 \Omega)^2 + (469 \Omega)^2} = 469 \Omega$$

$$I = \frac{V_s}{Z_{\text{tot}}} = \frac{10 \text{ V}}{469 \Omega} = 21.3 \text{ mA}$$

$$P_L = I^2 R_L = (21.3 \text{ mA})^2 (10 \Omega) = 4.54 \text{ mW}$$

ANS:5

SOLUTION:

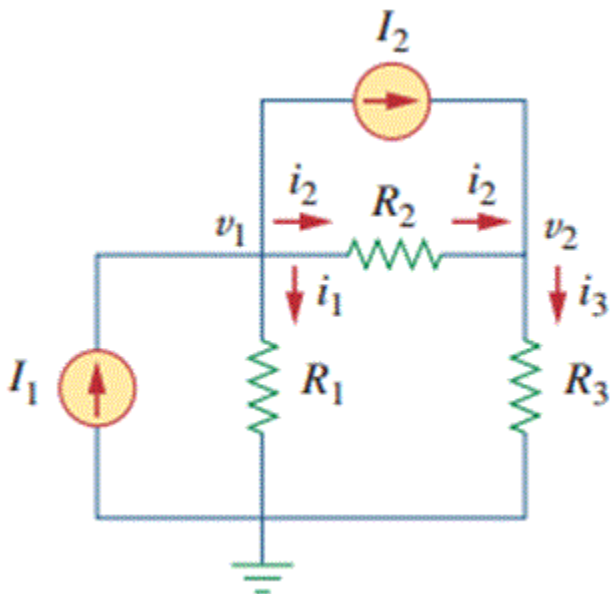



1. Select a node as the reference node. Assign voltages  $V_1, V_2 \dots V_{n-1}$  to the remaining nodes. The voltages are referenced with respect to the reference node.
2. Apply KCL to each of the non reference nodes.
3. Use Ohm's law to express the branch currents in terms of node voltages.

Node Always assumes that current flows from a higher potential to a lower potential in resistor. Hence, current is expressed as follows

$$I = \frac{V_{\text{high}} - V_{\text{low}}}{R}$$

After the application of Ohm's Law get the 'n-1' node equations in terms of node voltages and resistances.

Solve 'n-1' node equations for the values of node voltages and get the required node Voltages as result.

**Q4:** Using Thevenin's and Norton's theorem, find the currents in  $8\Omega$  resistor in the figure Shown below. **(10)**

ANS:4

Solution

The  $8\Omega$  resistor is short circuited as shown in diagram

(a).2.From diagram

(a),  $3010III21=-=-= 5 A$  3. With the voltage sources removed, the resistance 'looking in' at a break in the short circuit is given by  $2\Omega$  in parallel with  $1\Omega$ , i.e.r

$= 212213 \times = \Omega + 4$ . The Norton equivalent circuit is shown in diagram

(b), where the current in the

$8\Omega$  resistor,  $I = \left( \frac{235283}{\dots} \right) \parallel \parallel \parallel \cup = 0.385 \text{ A}$