

Q = 1

Part # (A)

selection:

$$\text{Primary} = 130 \text{ kV}$$

$$\text{Secondary} = 10 \text{ kV}$$

$$\text{T/F Rated} = 30 \text{ MVA}$$

 Z_b across V_{base1} (130 kV)

$$Z_b = \frac{(130 \times 10^3)^2}{30 \text{ MVA}} = \frac{16900000000}{300000000}$$

$$\boxed{Z_b = 56.33} \text{ Ans}$$

 $\Rightarrow Z_b$ across V_{base2} (10 kV)

$$Z_b = \frac{(10 \times 10^3)^2}{30 \text{ MVA}}$$

$$= \frac{100000000}{300000000}$$

$$\boxed{Z_b = 3.33} \text{ Ans}$$

Q = "1" Part # "B"

Solution :-

primary
11/132 KV_{sec}

We know that for S_{base1}

$$I_{base1} = \frac{S_{base1}}{V_{base1}}$$

$$S_{base1} = V_{base1} \times I_{base1}$$

$$= 11 \times 10^3 \times 909 \text{ Amp}$$

$$S_{base1} = 9999000$$

Now S_{base2} :-

$$S_{base2} = V_{base2} \times I_{base2}$$

$$= 132 \times 10^3 \times 75.75 \text{ Amp}$$

$$S_{base2} = 9999000$$

Now Z_{base1} :-

$$Z_{base1} = \frac{(V_{base1})^2}{S_{base1}} = \frac{(11 \times 10^3)^2}{9999000} = 12.101$$

$$Z_{base1} = 12.101$$

Now Z_{base2} :-

$$Z_{base2} = \frac{(V_{base2})^2}{S_{base2}} = \frac{(132 \times 10)^2}{9999000} = 1742.6$$

$$Z_{base} = 1742.574$$

⇒ Now per unit equivalent impedance for Z_{base1}

$$\Rightarrow Z_{base1} \text{ eq. P.U.} = \frac{Z_{eq1}}{Z_{base1}} = \frac{10 \Omega}{12.101}$$

$$Z_{base1} \text{ eq. P.U.} = 0.826$$

⇒ For Z_{base2}


$$Z_{base} \text{ eq. P.U.} = \frac{Z_{eq2}}{Z_{base2}} = \frac{1440 \Omega}{1742.574} = 0.826$$

$$Z_{base1} \text{ eq. P.U.} = 0.826$$


$Q=2$

Single line diagram of a 3 ϕ Power system is shown in the below figure

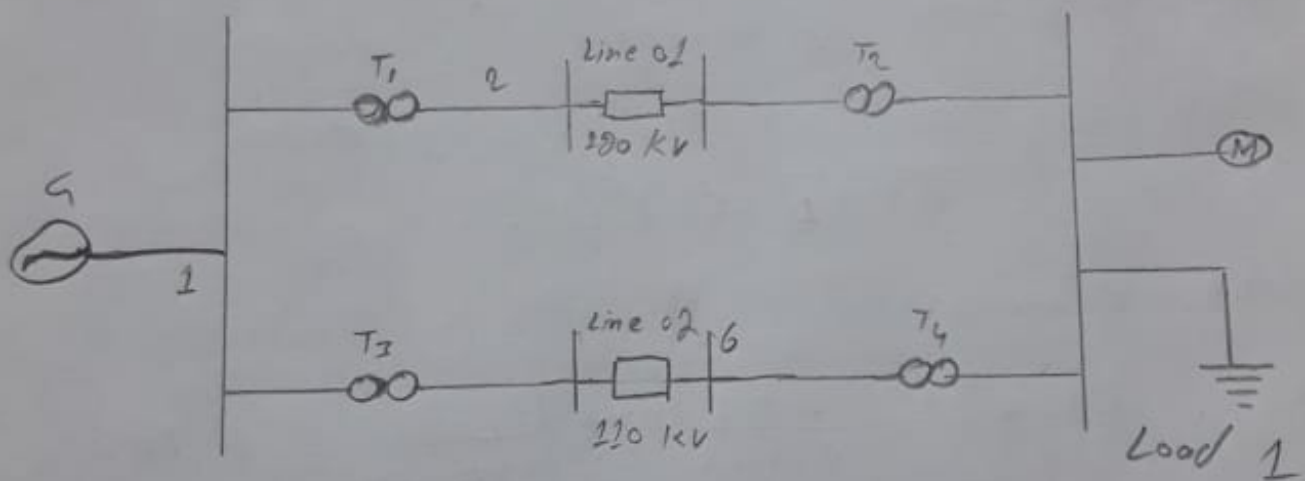
Draw an impedance and reactance diagram in P.U.



P-T-O

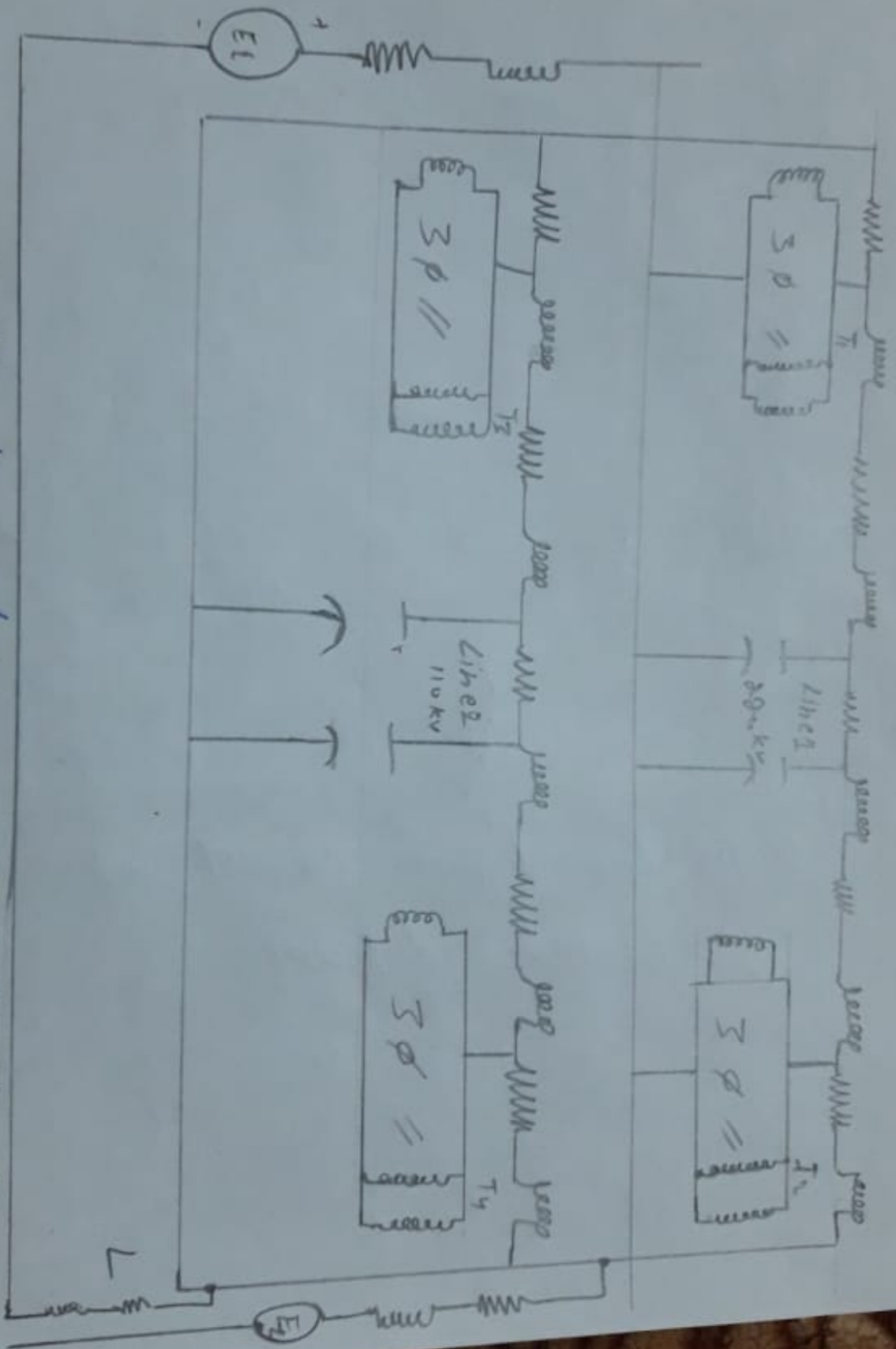

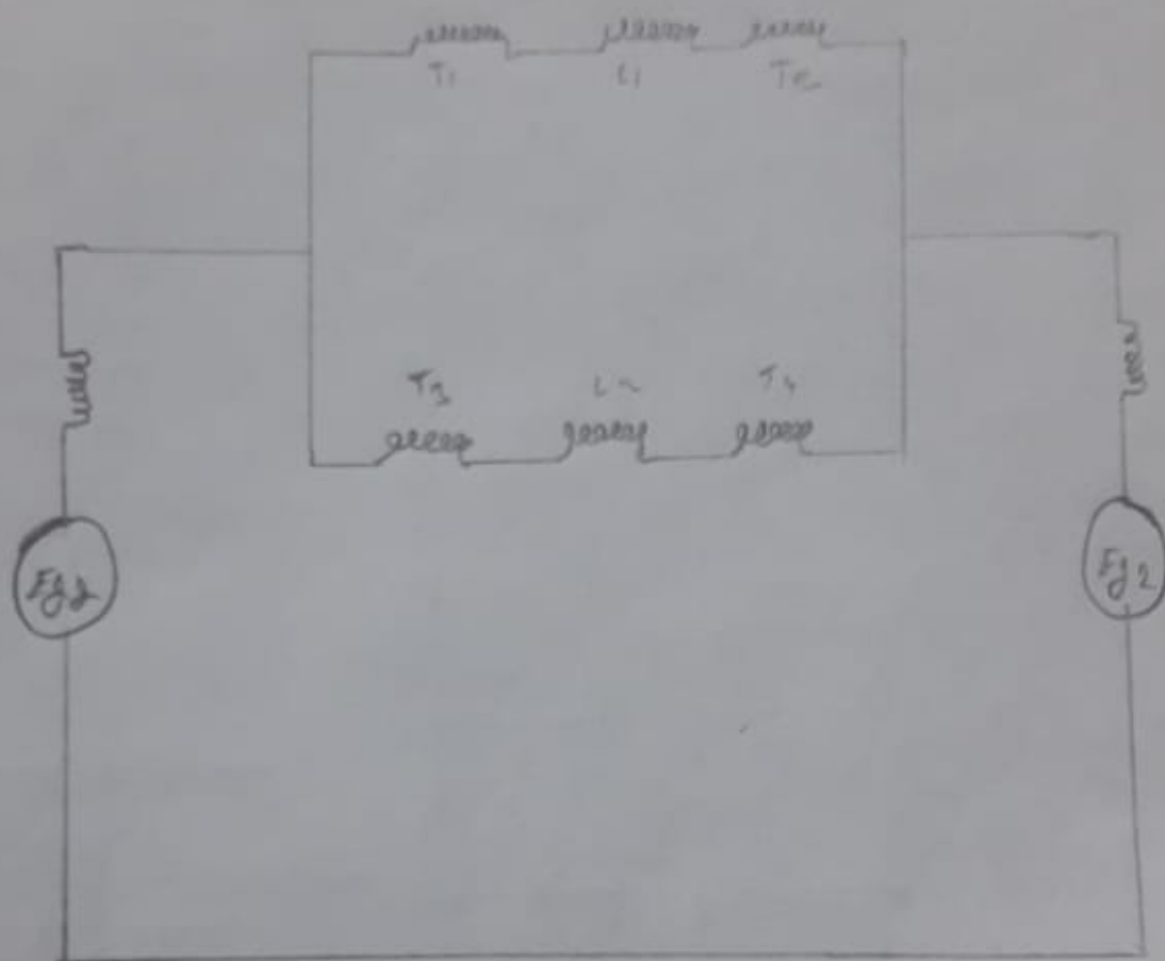Single line diagram convert To Impedance
Program





Single line diagram convert into
Reactance diagram.

M. Usama

(7)

ID # 14150

$Q = 3$ (a)

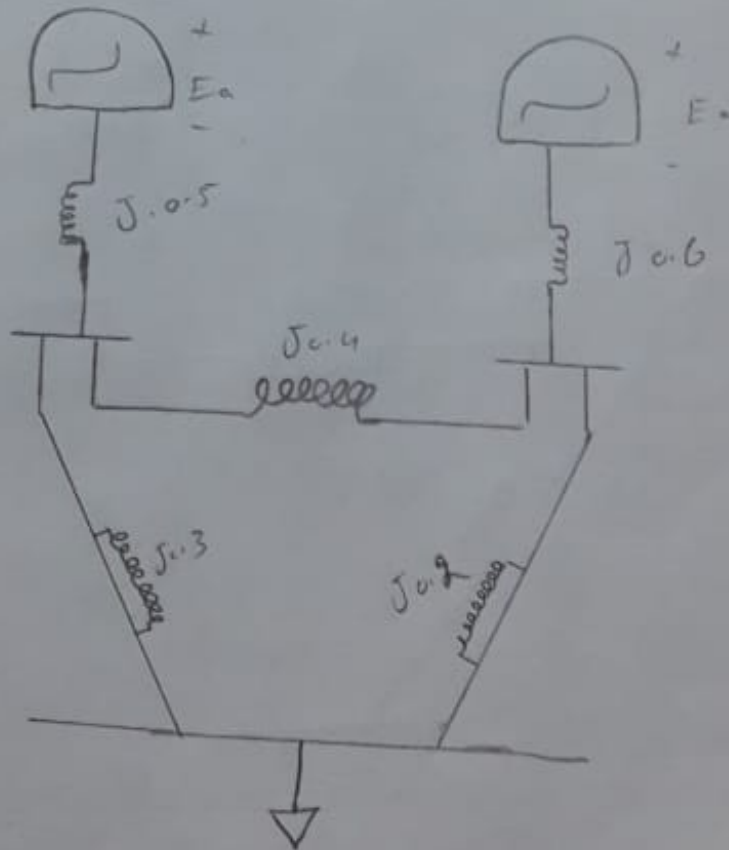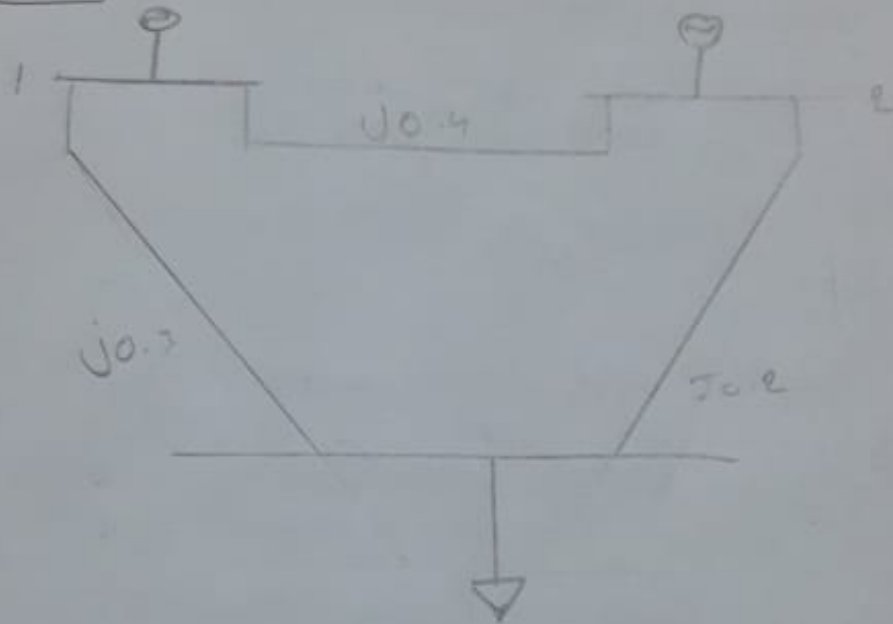


Now calculation :-

$$\frac{1}{j0.6} = 160 \quad \frac{1}{j0.5} = 2 \quad \frac{1}{j0.4} = 2.5 \quad \frac{1}{j0.3} = 3.33$$

$$\frac{1}{j0.2} = 5$$

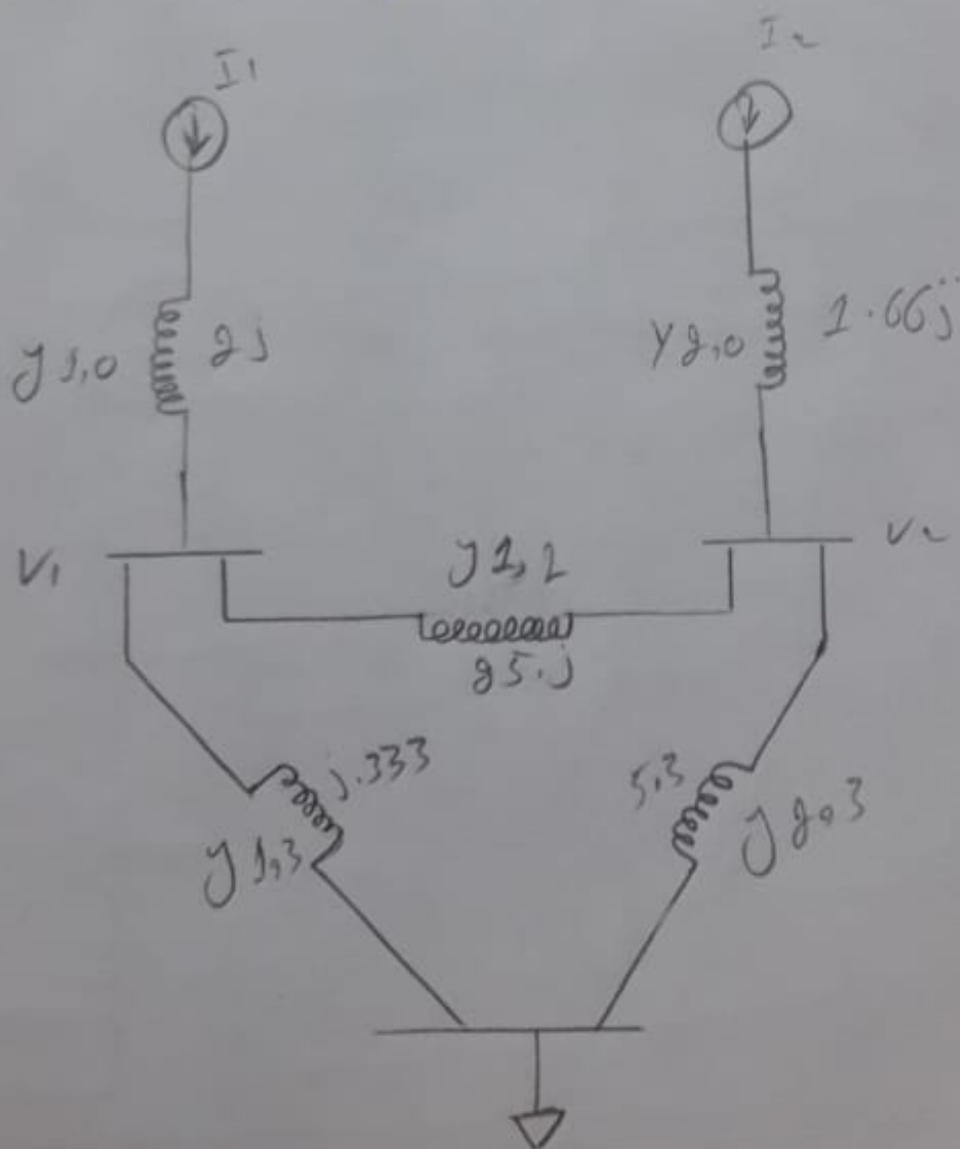⇒ So now we convert the reactance diagram into Admittance.



M. Usama

(9)

ID # 14156

Now we apply KCL equation:

Node (1)

So

$$I_1 = Y_{1,0} V_1 + Y_{1,2} (V_1 - V_2) + Y_{1,3} (V_1 - V_3)$$

$$\left[Y_{1,0} V_1 + Y_{1,2} V_1 - Y_{1,2} V_2 + Y_{1,3} V_1 - Y_{1,3} V_3 \right]$$

Now V_1 common

$$I_1 = V_1 (Y_{1,0} + Y_{1,2} + Y_{1,3}) - Y_{1,2} V_2 - Y_{1,3} V_3$$

$$I_1 = V_1 \left[Y_{1,0} + Y_{1,2} + Y_{1,3} \right] - Y_{1,2} V_2 - Y_{1,3} V_3$$

Now Node 2

eq (1) ←

$$I_2 = Y_{2,0} V_2 + Y_{1,2} (V_2 - V_1) + Y_{2,3} (V_2 - V_3)$$

$$\text{common} \leftarrow \left[-Y_{1,2} V_1 \right]$$

$$= -Y_{1,2} V_1 (Y_{2,0} + Y_{1,2} + Y_{2,3})$$

$$\left[V_2 - V_{2,3} - V_3 \right]$$