


Instructor: Rashid Aleem
 Paper: Electrical Network Analysis
 Time : 4 Hours

Rafaqatullah
 ID 14107

Note:


- 1) Attempt all questions.
- 2) Assume missing details if required.
- 3) Draw neat diagrams where required.

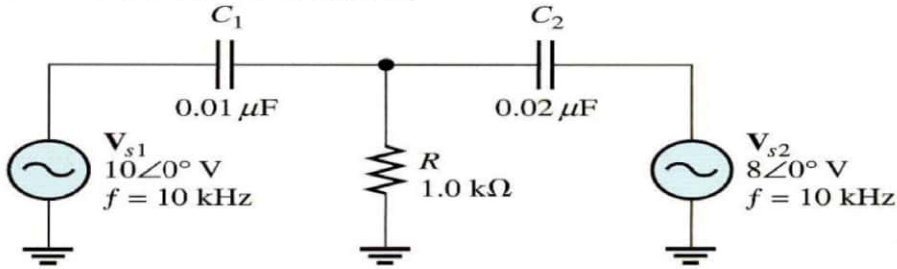Q1: Find the current in R in following fig .using the superposition theorem. Assume the internal impedance source zero. (10)



Q2: Determine Vth for the circuit external to RL in Figure . The beige area identifies the portion of the circuit to be thevenized.. (10)


5

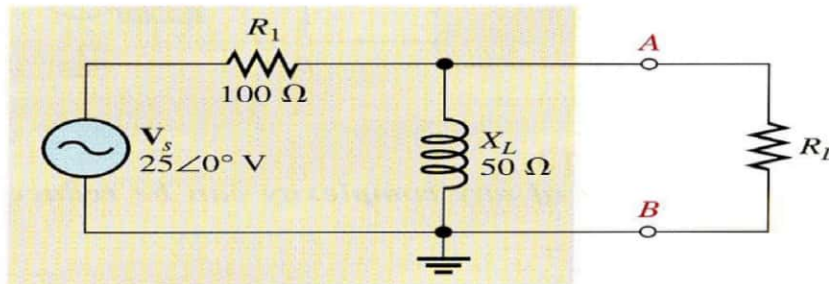

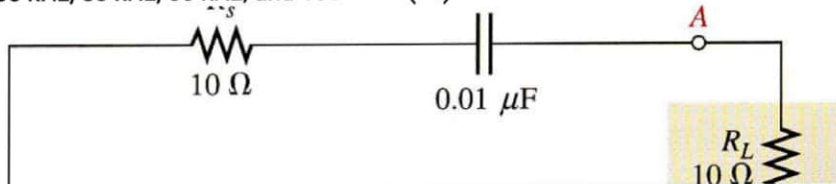Q3: The circuit to the left of terminals A and B in Figure provides power to the load ZL.

Page 1 of 2

This can be viewed as simulating a power amplifier delivering power to a complex load. It is the Thevenin equivalent of a more complex circuit. Calculate and plot a graph of the power delivered to the load for each of the following frequencies: 10 kHz, 30 kHz, 50 kHz, 80 kHz, and 100 kHz.?(10)



Word count

Display directory


Mobile view

Edit

1


Name Rafiqatullah Khan
ID 14107
Date 24/Sep/2020

Question # 01

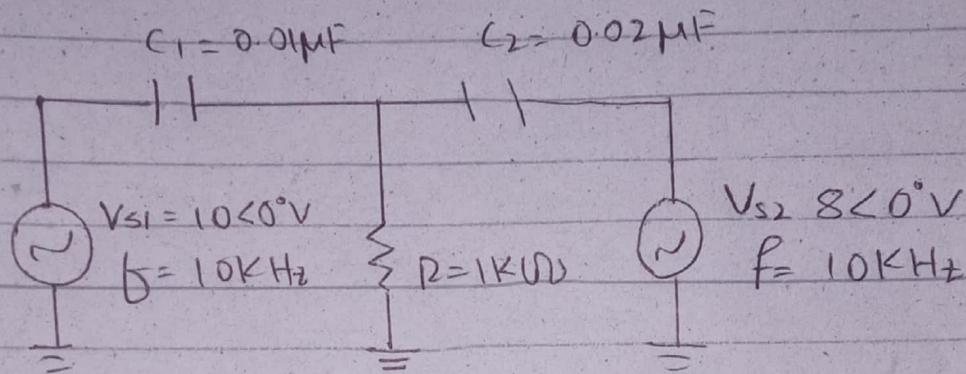

Answer:

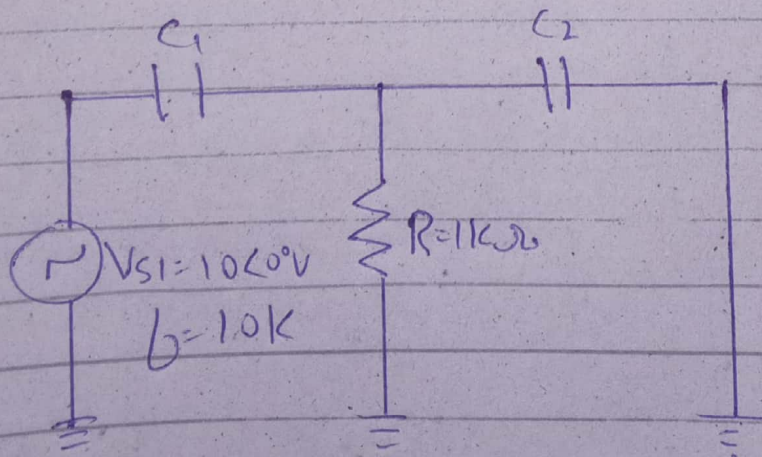Replace V_{s2} with its internal impedance (zero) and find the current in R due to V_{s1} .



(2)

$$X_{C_1} = \frac{1}{2\pi f C_1}$$

$$= \frac{1}{2\pi (10 \times 10^3 \text{ Hz}) (0.01 \times 10^{-6} \text{ F})}$$

$$X_{C_1} = \frac{1}{(6.28) (0.1) (10^{-3-6})}$$

$$X_{C_1} = \frac{1}{0.628 \times 10^{-3}}$$

$$X_{C_1} = 1.592 \text{ k}\Omega$$

$$X_{C_2} = \frac{1}{2\pi f C_2}$$

$$= \frac{1}{(2) (3.14) (10 \times 10^3) (0.02 \times 10^{-6})}$$

$$= \frac{1}{1.256 \times 10^{-3}}$$

$$X_{C_2} = 796 \Omega$$

(3)

Looking from V_{s1} the impedance is

$$Z = X_{C1} + \frac{R X_{C2}}{R + X_{C2}}$$

$$= 1.59 \angle -90^\circ \text{ k}\Omega + \frac{(1.0 \text{ k}\Omega)(796 \angle -90^\circ)}{1.0 \Omega - j796}$$

$$= 1.59 \angle -90^\circ \text{ k}\Omega + 622 \angle -51.5^\circ \Omega$$

$$= -j1.59 \text{ k}\Omega + 387 \Omega - j487 \Omega$$

$$= 387 \Omega - j2.08 \text{ k}\Omega$$

Converting to polar form yields.

$$Z = 2.12 \angle -79.5^\circ \text{ k}\Omega$$

The total current from source 1 is

$$I_{s1} = \frac{V_{s1}}{Z} = \frac{10 \angle 0^\circ \text{ V}}{2.12 \angle -79.5^\circ \text{ k}\Omega}$$

$$I_{s1} = 4.72 \angle 79.5^\circ \text{ mA}$$

(4)

Using the Current divider formula the current through R due to V_{S1} is:


$$I_{R1} = \left(\frac{X_{C2} \angle -90^\circ}{R - jX_{C2}} \right) I_{S1}$$

$$= \left(\frac{796 \angle -90^\circ \Omega}{1.0 \text{ k}\Omega - j796 \Omega} \right) \times 4.72 \angle 79.5^\circ \text{ mA}$$

$$= (0.623 \angle -51.5^\circ) (4.72 \angle 79.5^\circ)$$

$$I_{R1} = 2.94 \angle 28^\circ \text{ mA}$$

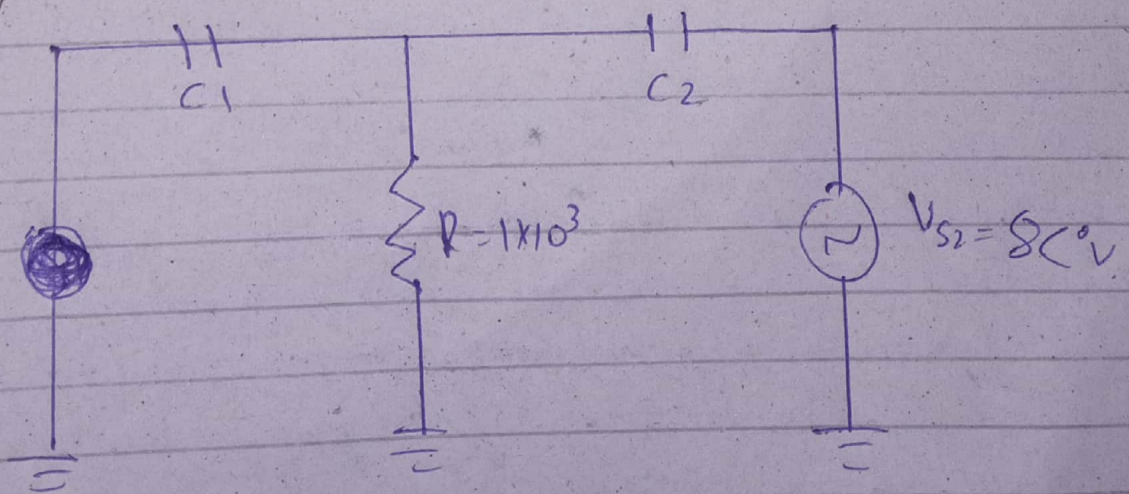Finding the current in R to source V_{S2} by replacing V_{S1} with internal impedance which is zero.



(5)

From V_{s2} the impedance is

$$\begin{aligned} Z &= X_{C2} + \frac{R X_{C1}}{R + X_{C1}} \\ &= 796 \angle -90^\circ + \frac{(1.0 \angle 0^\circ \times 10^3)(1.59 \angle -90^\circ \times 10^3)}{1.0 \times 10^3 \Omega - j1.59 \times 10^3} \\ &= 796 \angle -90^\circ \Omega + 847 \angle -32.2^\circ \Omega \\ &= -j796 \Omega + 717 - j451 \Omega \\ &= 717 \Omega - j1247 \Omega \end{aligned}$$

Converting to polar form yield:

$$Z = 1438 \angle -60.1^\circ \Omega$$

The total current from source 2 is

$$I_{s2} = \frac{V_{s2}}{Z}$$

$$= \frac{8 \angle 0^\circ \text{ V}}{1438 \angle -60.1^\circ \Omega}$$

$$I_{s2} = 557 \angle 60.1^\circ \text{ mA}$$

(b)

Using Current-divider Rule the Current through R due to V_{s2} is

$$\begin{aligned} I_{R2} &= \left(\frac{X_{C1} \angle -90^\circ}{R - jX_{C1}} \right) I_{s2} \\ &= \left(\frac{1.59 \angle -90^\circ \text{ k}\Omega}{1.0 \text{ k}\Omega - j1.59 \text{ k}\Omega} \right) 5.56 \angle 60.1^\circ \text{ mA} \\ &= 4.70 \angle 27.9^\circ \text{ mA} \end{aligned}$$

The total Current through R is:


$$\begin{aligned} I_{R1} &= 294 \angle 28^\circ \text{ mA} \\ &= 2.60 \text{ mA} + j1.38 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_{R2} &= 4.70 \angle 27.9^\circ \text{ mA} \\ &= 4.15 \text{ mA} + j2.20 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_R &= I_{R1} + I_{R2} \\ &= 6.75 \text{ mA} + j3.58 \text{ mA} \\ &= 7.64 \angle 27.9^\circ \text{ mA} \end{aligned}$$


7

Question # 02:

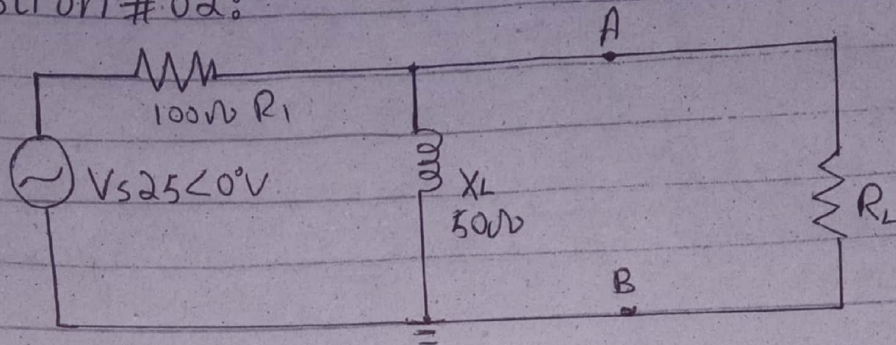

Answer:

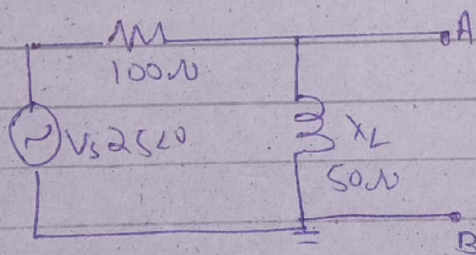First we will remove R_L and then determine the voltage from A to B (V_{th}). In this case the voltage from A to B is the same as the voltage across X_L . This determine using the voltage divider Rule:




$$V_L = \left(\frac{X_L \angle 90^\circ}{R_1 + jX_L} \right) V_s$$

$$= \left(\frac{50 \angle 90^\circ}{112 \angle 26.6^\circ} \right) 25 \angle 0^\circ V$$

$$V_L = 11.2 \angle 63.4^\circ V \Rightarrow V_{th} = V_L = V_{AB}$$

8

Question # 03

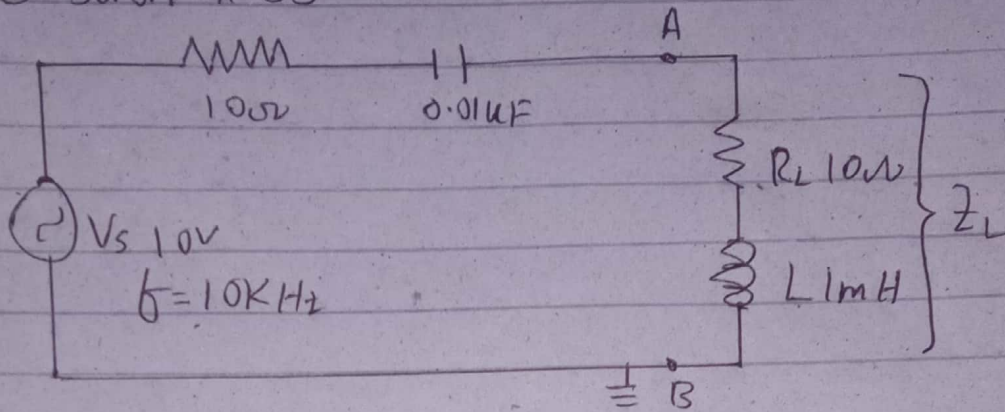

Solution:

$$\text{frequency} = 10 \times 10^3 \text{ Hz}$$

$$X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2(3.14)(10 \times 10^3)(0.01 \times 10^{-6})}$$

$$= 1.59 \times 10^3 \Omega$$

$$X_L = 2\pi fL$$

$$= 2(3.14)(10 \times 10^3)(1 \times 10^{-3})$$

$$X_L = 62.8 \Omega$$

9

Magnitude of total impedance is:

$$Z_T = \sqrt{(R_S + R_L)^2 + (X_L - X_C)^2}$$
$$= \sqrt{(20)^2 + (1.53)^2}$$

$$Z_T = 1.53 \text{ k}\Omega$$

Current is:

$$I = \frac{V_S}{Z_T}$$

$$= \frac{10}{1.53}$$

$$I = 6.54 \text{ mA}$$

Load power is:

$$P_L = I^2 R_L$$
$$= (6.54 \text{ mA})^2 (10)$$

$$P_L = 428 \mu \text{ W}$$

10

For $30 \times 10^3 \text{ Hz}$

$$X_C = \frac{1}{2\pi(30 \times 10^3)(0.01 \times 10^{-6})}$$

$$X_C = 531 \Omega$$

$$X_L = 2\pi(30 \times 10^3)(1 \times 10^{-3})$$

$$X_L = 189 \Omega$$

$$I = \frac{V_s}{Z_t}$$

$$= \frac{10 \text{ V}}{343}$$

$$I = 29.2 \text{ mA}$$

$$P_L = I^2 R_L$$
$$= (29.2)^2 (10)$$

$$P_L = 8.53 \text{ mW}$$

11

For $f = 50 \text{ kHz}$

$$X_c = \frac{1}{2\pi(50 \times 10^3)(0.01 \times 10^{-6})}$$

$$X_c = 318 \Omega$$

$$X_L = 2(3.14)(50 \times 10^3)(1 \times 10^{-3})$$

$$X_L = 314 \Omega$$

X_c and X_L are very close to being equal which makes the impedance approximately complex conjugate. The exact frequency at which $X_L = X_c$ is 50.3 kHz .

$$Z_t = \sqrt{(20)^2 + (4)^2}$$

$$= 20.4 \Omega$$

$$I = \frac{V_s}{Z_t}$$

$$= \frac{10}{20.4 \Omega}$$

$$I = 490 \text{ mA}$$

(12)

$$P_L = I^2 R_L$$
$$= (490 \text{ mA})^2 (10)$$
$$= 2.40 \text{ W}$$

For frequency = 80 kHz

$$X_C = \frac{1}{2(3.14)(80 \times 10^3)(0.01 \times 10^{-6})}$$

$$X_C = 199 \Omega$$

$$X_L = 2(3.14)(80 \times 10^3)(1 \times 10^{-3})$$
$$= 503 \Omega$$

$$Z_T = \sqrt{(20)^2 + (304)^2}$$
$$Z_T = 305 \Omega$$

$$I = \frac{V_s}{Z_T}$$
$$= \frac{10}{305}$$

$$= 32.8 \text{ mA}$$
$$P_L = I^2 R_L$$
$$= (32.8 \text{ mA})^2 (10)$$
$$P_L = 10.8 \text{ mW}$$

(13)

$$\text{frequency} = 100 \text{ KHz}$$

$$X_c = \frac{1}{2(3.14)(100 \times 10^3)(0.01 \times 10^{-6})}$$

$$X_c = 159 \Omega$$

$$X_L = 2(3.14)(100 \times 10^3)(1 \times 10^{-3})$$

$$X_L = 628 \Omega$$

$$I = \frac{V_s}{Z_T}$$

$$= \frac{10}{469}$$

$$I = 21.3 \text{ mA}$$

$$P_L = I^2 R$$


$$= (21.3 \times 10^{-3})^2 (10)$$

$$P_L = 4.54 \text{ mW}$$


From all result power to load peak the frequency 50 KHz for which the load impedance is the complex conjugate of the out-put impedance. A graph of load power versus frequency is shown below. Since the maximum power is so much larger than the other values an accurate plot is difficult to achieve without intermediate values.

(14)

Question #04:

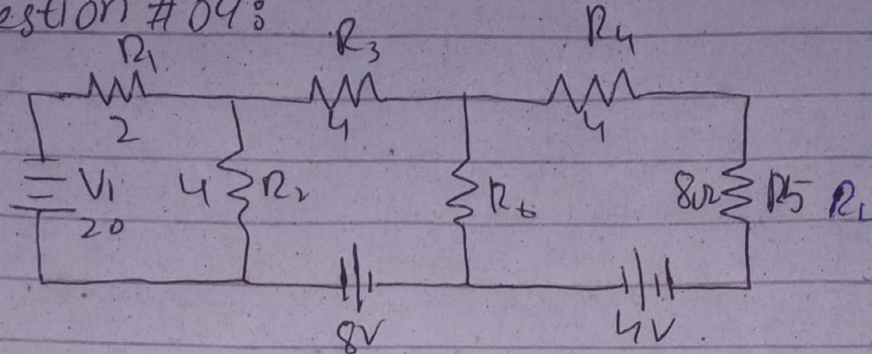

Answer:

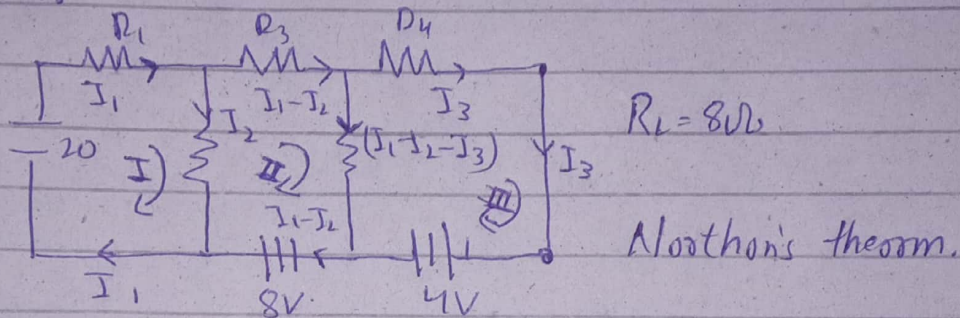

For Loop I:

$$-2I_1 - 4I_2 + 20 = 0$$

$$I_1 + 2I_2 = 10 \quad \text{--- (1)}$$

For Loop II:

$$-4(I_1 - I_2) - 2(I_1 - I_2 - I_3) - 8 + 4I_2 = 0$$

$$-6I_1 + 10I_2 + 2I_3 = 8$$

$$-3I_1 + 5I_2 + I_3 = 4 \quad \text{--- (2)}$$

15

For Loop III:

$$-4I_3 + 4 + 2(I_1 - I_2 - I_3) = 0$$

$$2I_1 - 2I_2 - 6I_3 = -4$$

$$I_1 - I_2 - 3I_3 = -2 \quad \text{--- (3)}$$

We have to solve these three equations simultaneously. Now we are not interested in all the values of I_1 , I_2 ,

We know that current through shotedly A to B.

So we will find only I_3 thus

$$\cancel{I_1} + 2I_2 = 10 \quad \text{--- (i)}$$

$$-3I_1 + 5I_2 + I_3 = 4 \quad \text{--- (ii)}$$

$$I_1 - I_2 - 3I_3 = -2 \quad \text{--- (iii)}$$



So eq (3) become

$$(I_2 + 3I_3 - 2) - (-I_1 + 5I_3 - 2) - 3I_3 = -2$$


$$I_3 = 1 \text{ A (from A to B)}$$

(16)

Remove R_1 Circuit.

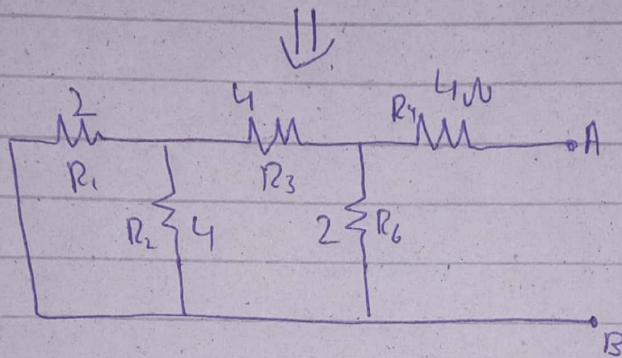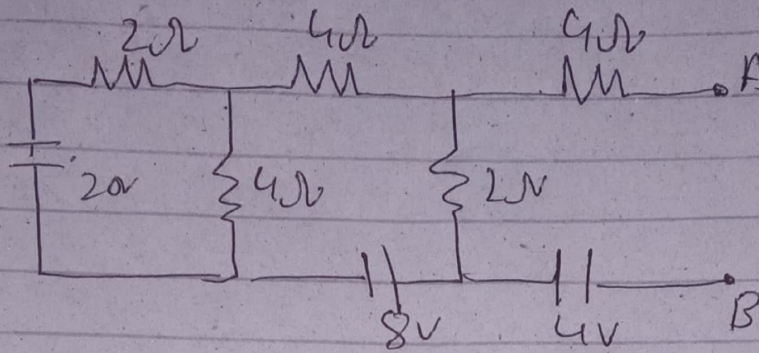


$$R_1 || R_2 = \frac{2 \times 4}{2 + 4} = \frac{8}{6} = \frac{4}{3}$$

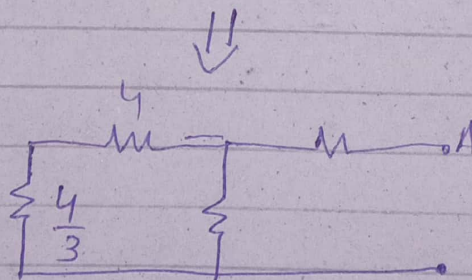

$$\begin{aligned} R_3 + R_4 &= \frac{4}{3} + 4 \\ &= \frac{16}{3} \end{aligned}$$


17

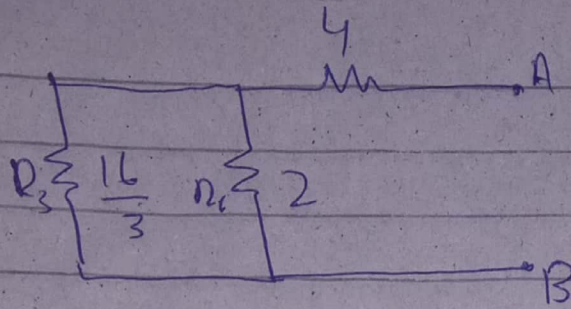

$$R_3 + R_6 = \frac{\frac{16}{3} \times 2}{\frac{16}{3} + 2}$$

$$= \frac{32/3}{22/3}$$


$$= \frac{16}{11}$$

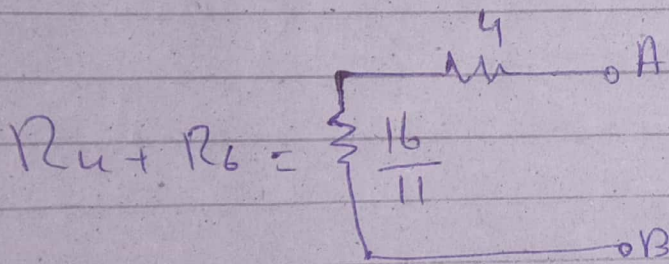


$$R_{in} + R_0 = 4 + \frac{16}{11}$$

$$= \frac{60}{11} \Omega$$

18

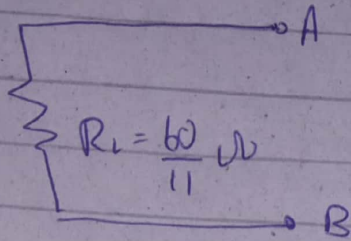

$$R_n = \frac{60}{11} \Omega$$

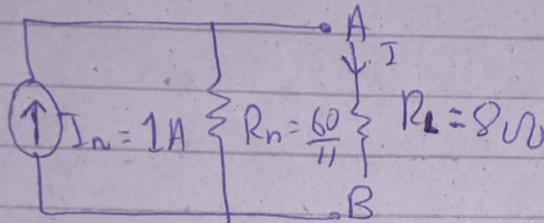

$$I = I_n \left[\frac{R_n}{R_n + R_L} \right]$$

$$= 1 \left[\frac{60/11}{60/11 + 8} \right]$$

$$= \frac{60}{11} \frac{1}{148/11}$$


$$= \frac{60}{148}$$

$$I = \frac{15}{37}$$

$$I = 0.4A$$

19

Question #05:

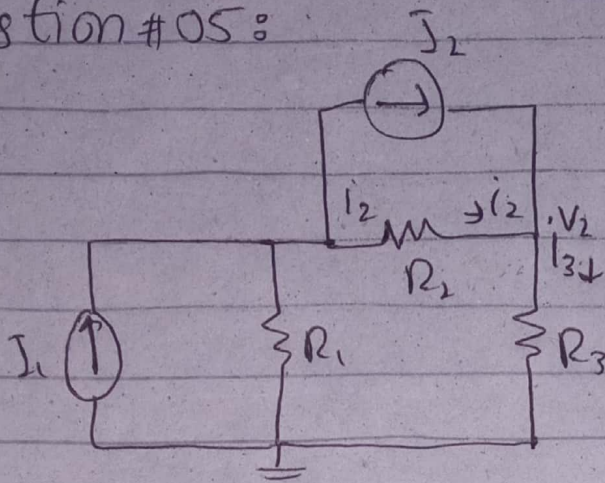

Sol:

In the upper circuit we have 3 nodes from which one is reference node and other is two are non-reference nodes - Node 1 & Node 2.

Step 1:

Assign the nodes voltage as V_1 & V_2 also mark the direction of branch current with respect to the reference.

Step 2:

Apply KCL Nodes 1 & 2

(20)

KCL at node 1

$$i_1 = i_2 + i_3 \quad \text{--- (1)}$$

KCL at node 2

$$i_2 + i_4 = i_1 + i_5 \quad \text{--- (2)}$$

Step III:

Apply ohm's law to KCL eqn:

ohm's law to KCL eqn at node 1

$$i_1 = i_2 + i_3 \Rightarrow \frac{V_1 - V_2}{4}$$

Now ohm's law to KCL eqn at node 2

$$i_2 + i_4 = i_1 + i_5 = \frac{V_1 - V_2}{4}$$

Step 4:

Now sol the eqn to get the values of V_1 , V_2